


Nuts & Volts

Exploring Electronics And Technology For The Hobbyist And Professional

www.nutsvolts.com

November 1999 Vol. 20 No. 11

STAMP ON STEROIDS

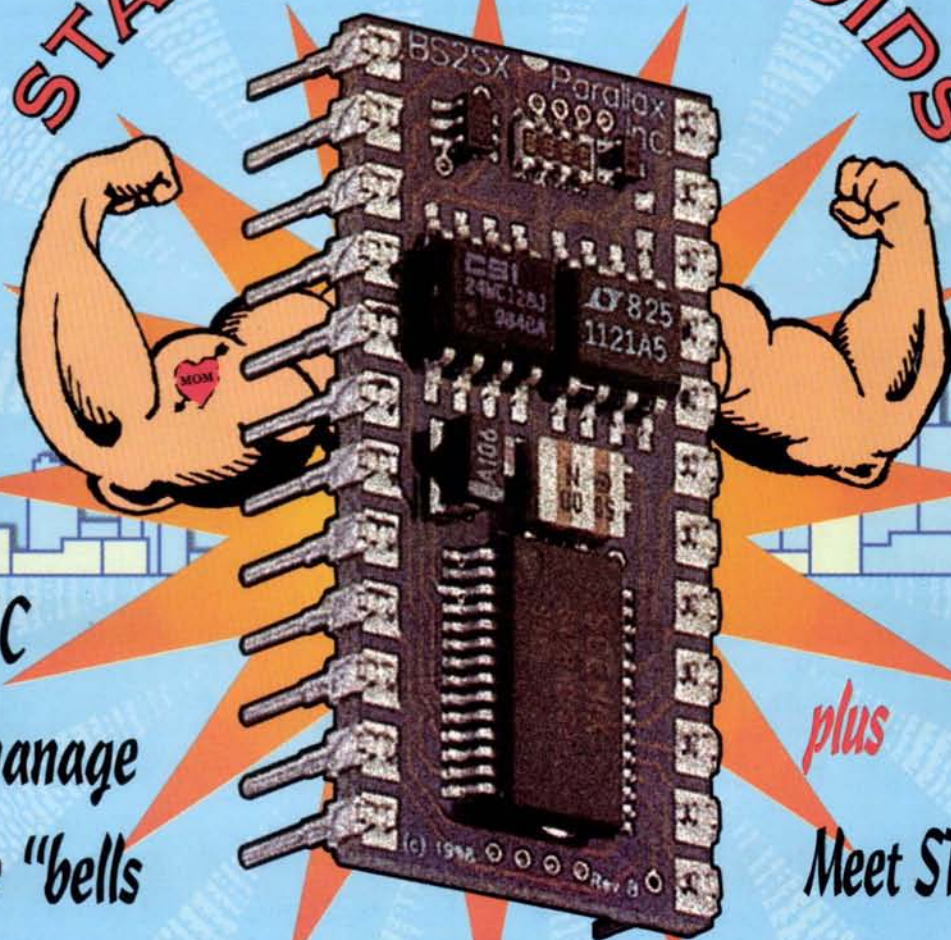

Utilizing the BASIC Stamp II SX to manage a GUI with all the "bells and whistles"

plus
Meet STAMP Net: A multi-drop Stamp-based network


Also this month ...

- **Radio Control Servos – A Primer!**
- **Build a Tunable Noise Generator**
- **Reviving NiCad-Powered Devices**
- **Mass Merchandising the Ham Radio Service**
- **Build a Violin/Guitar Tuner**
- **Much More!**

U.S. \$3.50 CANADA \$5.00



MONSTER 47GB SCSI DRIVE

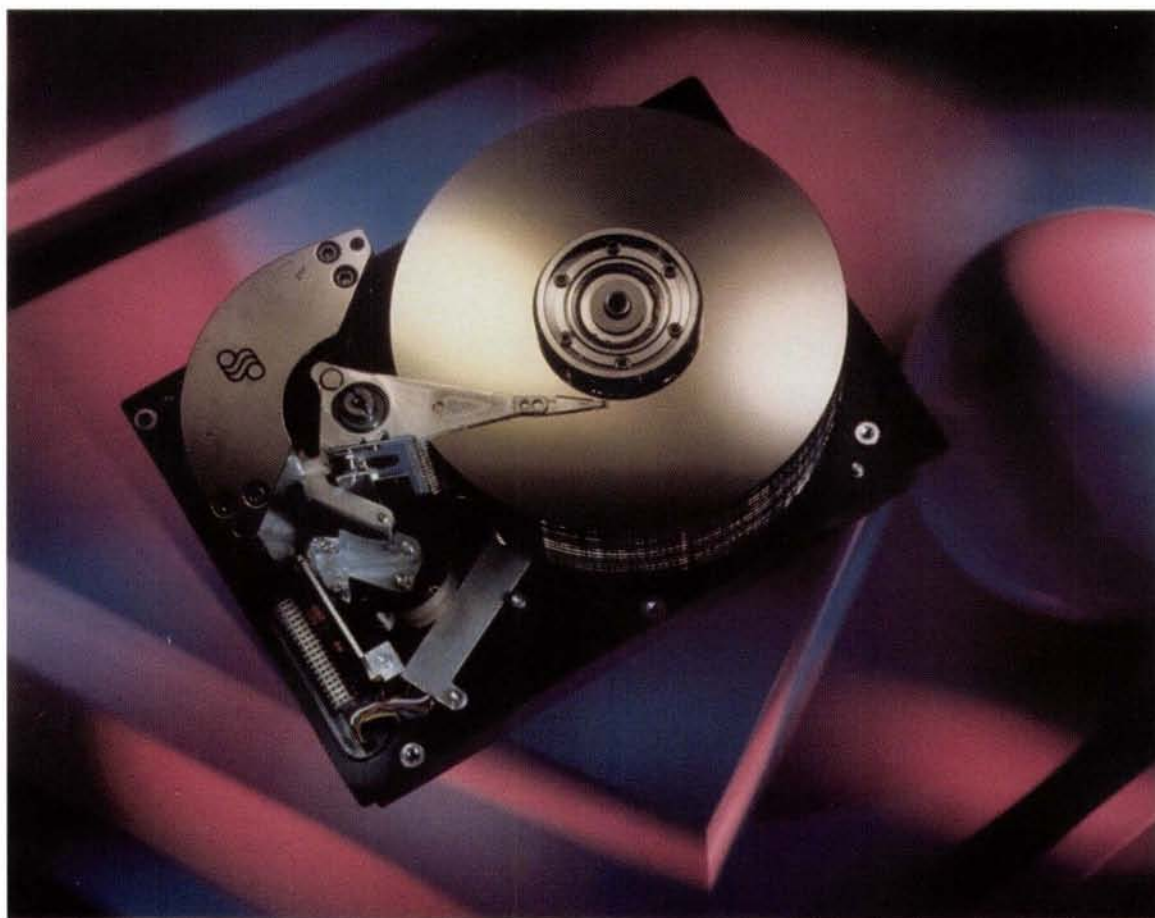

\$695

FREE SCSI ENCLOSURE
408 330-5523

Open Windows instantly. Process huge graphic and database files with ease. Make your file server scream with speed.

The 47GB Seagate Elite is the drive you need for serious performance. It features 14 disks and 28 heads for blazing performance 3.5" drives can't touch. The Ultra Wide interface makes installation a snap. A 4MB cache buffer accelerates data transfers.

A special volume purchase brings you brand new drives at low, low PC prices. Shop around. Compare price. No one else can match this deal.

Buy just one drive and build the ultimate workstation. Or add several to take advantage of NT RAID performance. Let us custom-build your multi-drive disk array at no extra charge. Redundant rack-mount trays stack to build arrays bigger than 1,000GB per rack!

Get the speed you need and the reliability you deserve. Get rock solid Seagate quality backed by a warranty of up to six years! Call now! Try your 47GB monster drive risk-free.



CORPORATE SYSTEMS CENTER
3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.SCSIDRIVES.COM

Seagate ST446452W drives are PC, Mac, SGI, and Sun compatible. 5 1/4" Elite drives are sold only in OEM enclosures and disk array trays. CSC carries low-cost, top-quality PCI controllers and SCSI accessories. If you haven't already upgraded to SCSI, call us for help. No-risk guarantee refunds your entire purchase price (less shipping) if you're not completely satisfied within 15 days. Call for your free catalog of hard drives, duplication equipment, and accessories.

...brings you a potpourri of high-tech goodies for the techno-tinkerer! For thirty years we have been your source for Silicon Valley exotica!

Attention Hams! HSC has QRP!

Announcing the newest development in the hottest field of interest in ham radio...QRP! Low power rigs are the latest rage, and we now have the giant-killer entry on the market...

The MN9 9-Band QRP Transceiver Kit!

by Sierra Radio Enterprises

Available EXCLUSIVELY at HSC Electronics!

For the Ham Radio buff who likes to build his own rig, we offer this technically advanced transceiver that is fun to build and a dream to operate. Containing many features found only in upper-end transceivers, this is not an entry-level kit, although you will need no exotic test equipment to align and test. This will provide several evenings of enjoyable kit-building, and many more operating at the low-power end of the spectrum! Note: you should be fairly confident in your kit-building abilities before attempting this!

- ◆ 50 mW to 12 Watts - CW / SSB
- ◆ USB, LSB, CWHI, CWLO (selectable CW sideband)
- ◆ 160 meters thru 10 meters, including WARC Bands
- ◆ Digital Frequency / Clock Display
- ◆ Vackar VFO with ZERO DRIFT! *
- ◆ Built-in Electronic Keyer -- Built-in SWR Bridge
- ◆ Front-firing speaker, handsome front panel
- ◆ Full QSK CW Break-in, two jacks for paddle & key
- ◆ Narrow-band CW filter option
- ◆ Dual, Half-Lattice 9 MHz Xtal filter for SSB
- ◆ Variable RIT/XIT, Selectable IF Scan with Scan Adjust for filter rejection of unwanted signals.
- ◆ NO RELAYS! -- No external test equipment needed for alignment!
- ◆ Tuning Versatility!...Adjustable bandspread, both in width and in Ham-Band Position!
- ◆ Once a given bandspread is chosen...set the limits and USE!
- ◆ Estimated ship date for preliminary release December 1 -- Advance orders get special price!
- ◆ Price after December 1 will be higher!!

by adjusting two rear-panel mounted pots

HSC#80503 Introductory Price for Advance Orders -- good through Nov. 30! **\$469.00**



Rechargeable Battery Buy!

Three types of rechargeable battery for a variety of uses!

Amazing power in a small package! Nickel-Metal Hydride (Ni-MH) batteries have the capacity of Nicads without the "memory" effect. These are factory-new, not pulls!



- ◆ Toshiba 8TH-F5-F1-AIR, 9.6VDC at 600 mA, measures 4.5" x 1.875" x .25" thick (8 cells in series)
- ◆ Appears to have a thermal fuse for over-current protection

HSC#17871 Now, lower price! **\$9.95**

...Or you can choose a NiCad battery pack in a similar form-factor. These are a flat array of cells, like the battery above, with handy solder tabs for connection.

- ◆ Thin NiCad pack, 8.4VDC at 450 mA, measures 4.5 x 1.875 x .25" thick (7 cells in series)

HSC#17872 Now, lower price! **\$7.50**

...Or you may need the power of a lead-acid battery. These are all new batteries with tab terminals. Perfect for hobbies, security systems, battery back-up, garden equipment, etc.

- ◆ TR1.2-12, 12VDC at 1.2 AH, measures 3.75 x 1.875 x 2"

HSC#17197 **\$4.95**

- ◆ TR4-6, 6VDC at 4 AH, measures 2.75 x 1.75 x 4"

HSC#17588 **\$4.95**

- ◆ BAT-0063 (x2), 12VDC at 10AH, 4" x 6" x 4", this is two 6-volt batteries packaged in series by Best Power

HSC#17810 **\$17.50**

Video-hack is back!

- ◆ Logitech Videoman Video-conference camera & interface
- ◆ These units were sold with Hewlett Packard S-700 workstations for videoconference capability
- ◆ We have collected some data, check on our website at <http://www.halted.com/online/index.htm>
- ◆ All we have is cameras with stand, and SCSI-II interface
- ◆ The camera is on a weighted stand that extends from 13" tall to over 20" tall, and has a electret microphone
- ◆ Color camera is digital output, but some delicate SMT surgery will provide NTSC signals (not for amateurs!)
- ◆ Interface box has two SCSI-II ports on back, and a DC power input (we do not have the adapter), and on the front it has a mic. out jack, composite video input (BNC), and the connector for the camera cable.



HSC#17503 Now -- Lower Price! **\$29.95**

Laptop Carrying Cases

- ◆ Measures 12.5" x 10" x 2" (inside dimensions)
- ◆ Velcro-sealed outer pouch, padded shoulder strap with heavy-duty swivel hooks, zipper closure.
- ◆ Handsome black vinyl "leather-grain" exterior
- ◆ Cushiony plush interior protects your laptop's case
- ◆ Quantity discounts available



HSC#17662 **\$17.50**

Price Breakthrough on Variable Transformers!

You say you've wanted one of these in the past, but the price kept you away? Now you can afford a brand-new variable AC supply for your workbench! All have enclosed cases, knob and dial.

- ◆ Model AICVR-500W, 120 VAC input
- ◆ 0 - 120 VAC output, 500 watts
- ◆ Measures 5" dia., 6" tall
- ◆ Features meter, binding post terminals for input, output
- ◆ New in box, made in China



HSC#80474 **\$50.00**

- ◆ Model AEEC-1090VR, 120 VAC 60 Hz input
- ◆ 0 - 120 VAC output, 1 KVA
- ◆ Measures 6.5" dia., 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China



HSC#80481 **\$85.00**

- ◆ Model AEEC-2090VR, 120 VAC 60 Hz input
- ◆ 0 - 120 VAC output, 2 KVA
- ◆ Measures 8" x 10" x 8" tall
- ◆ Features meter, illuminated switch, line cord, fuse
- ◆ New in box, made in China



HSC#80461 **\$125.00**

ISA to SCSI Adapter

- ◆ Adaptech model AVA-1505AI -- Brand Name Quality!
- ◆ Single, complete PC connection
- ◆ For single non-bootable SCSI2 peripheral
- ◆ New, OEM pack, with install diskette & manual

HSC#17995 **\$17.50**

Special! ...w/DB25 adapter & cable **\$19.95**



Sidewinder Slashed!

- ◆ Microsoft "Sidewinder" game controller ... Wow!
- ◆ New OEM package, high quality for fast action!
- ◆ Download drivers from Microsoft.com
- ◆ Eight programmable action buttons, two fire buttons



HSC#80486 **\$17.50**

ATX-Style Mid-Tower!

- ◆ Need a case for your motherboard?
- ◆ ATX-style mid-tower cabinet
- ◆ ATX power supply included
- ◆ Three 5.25" and two 3.5" front bays
- ◆ 16.5" H x 8.25" W x 16.5" D
- ◆ Brand new in box, 90-day warranty



HSC# 80459 **\$47.50**

External SCSI Drive Cases

- ◆ Small vertical-format case for 3.5" drives, brand new!
- ◆ 3.75" x 5.5" x 9.75" overall size
- ◆ 50-pin SCSI connectors
- ◆ SCSI ID switch, termination switch
- ◆ Universal input 40W Power supply
- ◆ Fan-cooled, uses standard IEC Power cord (not included)



HSC# 18075 **\$24.95**

- ◆ High-power case for 5.25" drives, brand new!
- ◆ 7" x 4.5" x 10.5" overall size
- ◆ 50-pin SCSI connectors
- ◆ SCSI ID switch
- ◆ 65W Power supply (lots of power for hard drives, etc.)
- ◆ Fan-cooled, uses standard IEC Power cord (not included)



HSC# 17130 **\$39.95**

- ◆ High quality low profile case for 5.25" drives, brand new!
- ◆ 7" x 2.25" x 11" overall size
- ◆ 50-pin SCSI connectors, RCA Audio connectors
- ◆ SCSI ID switch, termination switch
- ◆ Tiny 12W Power Supply (5VDC @ 1.4A, 12VDC @ .4A, probably only good for CD-ROM's)
- ◆ Fan-cooled, uses standard IEC Power cord (not included)



HSC# 17357 **\$29.95**

ATX Power Supply Special!

- ◆ "Sparkle Power" 235W fan-cooled ATX supply
- ◆ Perfect for ATX Tower & Mid-Tower Cases
- ◆ Input: 100-120VAC -- 7A/200-240V -- 4A, 50-60Hz
- ◆ Output: 3.3VDC/14A, +5Vsb/0.8A, +5VDC/22A, -5VDC/0.3A, +12VDC/8A, -12VDC/0.8A
- ◆ Power-Good signal line, Noise suppression
- ◆ Standard ATX-motherboard, disk drive power connectors
- ◆ Measures 3.375" x 5.5" x 6" (Standard ATX Form-Factor)
- ◆ New, 90-day warranty



HSC#18108 **\$19.95**

PCMCIA 28.8 Modem!

- ◆ Texas Instruments "WinMax 34SP" 28.8 KBPS modem
- ◆ Driver software available from our website: <http://www.halted.com/online>
- ◆ Telco jack connector/adaptor included
- ◆ New...in OEM pack -- 90 day warranty



HSC#18066 **\$19.95**

Ergonomic Keyboard!

- ◆ Mouse Systems "Contour 107" comfort keyboard!
- ◆ New in box with AT/PS2 adapter
- ◆ 107 keys, (101 plus 1 mouse key, 5 special function)



HSC#18046 **\$19.95**

PCI-Bus 56K Modem!

- ◆ Genica PCI-Bus 56K Modem at unheard-of price!
- ◆ Data, FAX, voice, full V.90 compatibility
- ◆ Voice from handset
- ◆ Windows 95/98 or NT only (Not Win 3.1 compatible)
- ◆ Uses latest Lucent chipset, comes with Lucent drivers
- ◆ New retail box, with expanded application software on CD
- ◆ 90-Day Warranty

HSC#17532 New! Lower Price! **\$29.95**

Visit HSC's Website!

- ◆ Pay us a virtual visit on the World Wide Web!
- ◆ Simply point your browser to <http://www.halted.com>
- ◆ Site is constantly being revised, please visit often!
- ◆ Or, you can email your order to hscmail@halted.com

HSC Catalog online!

- ◆ That's right, get HSC's catalog on the World-Wide Web!
- ◆ Simply go to www.halted.com and follow the big red link.
- ◆ Adobe .PDF files are available for download and viewing.
- ◆ Or drop on by and pick one up...we'd love to see you!

CATCH IT. HOLD IT. TUNE IT.

NEW

Tuning your receiver will never be easier. Introducing the all new Mini Scout Reaction Tuner. With a .001 second measurement time, the Mini Scout will not miss even the briefest of transmissions. While locking onto a frequency from up to 200 feet away (5w UHF), the Mini Scout automatically tunes the receiver* to the action

using its patented Reaction Tune capability. No manual tuning necessary.


*Compatible Receivers:

ICOM
7000, 7100, 8500, 9000, R10
AOR
8000, 8000B, 8200
Optoelectronics
Optocom, R11
Radio Shack
Pro2005/6 with OS456/Lite
Pro 2035/42 with OS535

No modifications necessary. Interface cables required.

Specifications Scout Mini Scout

Specifications	Scout	Mini Scout
10MHz - 1.4GHz	•	•
Reaction Tune	•	•
LCD Display	•	•
<3mV Sensitivity	•	•
Signal Strength Bargraph	•	•
Filter Mode	•	•
Capture Mode	•	•
Backlight	•	•
Beeper	•	•
Vibrator	•	•
400 Memories	•	•
255 Hits Counter	•	•

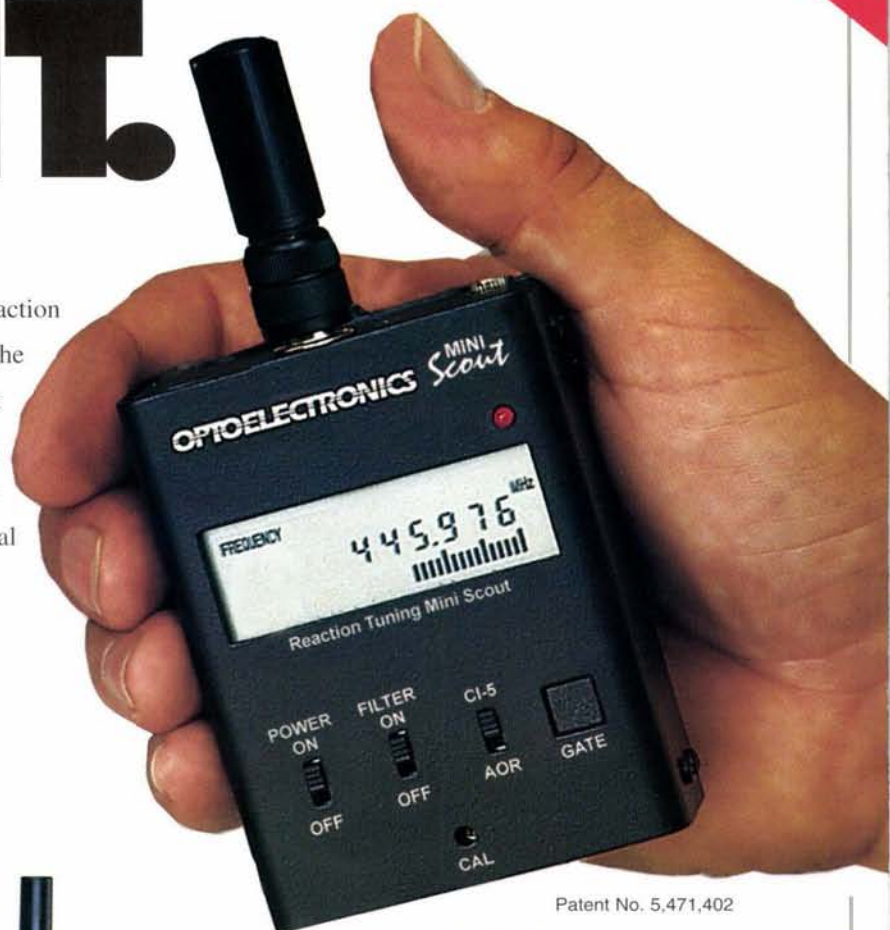

Patent No. 5,471,402

**Mini Scout
Reaction Tuner**
\$249



Patent No. 5,471,402

AR8200 Not Included

Scout Frequency Recorder Reaction Tuner

\$349



SPECIAL
DB32 & CC30 \$29

Place your
Order anytime
at the
Optoelectronics
Cyber Store
www.
optoelectronics.
com



Are FM Broadcast signals a Problem?

Knock them out with the N100 Notch Filter. Blocks 88 - 108MHz, Connect between antenna and Scout or Mini Scout.....\$99

OPTODIRECT • 800-327-5912
OPTOELECTRONICS®

5821 NE 14th Avenue • Ft. Lauderdale, FL 33334
Phone: (954)-771-2050 Fax: (954)-771-2052 E Mail: sales@optoelectronics.com

Prices and Specifications are subject to change without notice or obligation.
DB32 Antenna shown on Scout and Mini Scout sold separately. AOR, ICOM, Radio Shack are all registered trademarks

Contents

VOLUME 20 • NO. 11
NOVEMBER 1999

NUTS & VOLTS MAGAZINE (ISSN 1065-2035) IS PUBLISHED MONTHLY FOR \$19.00 PER YEAR BY T&L PUBLICATIONS, INC., 430 PRINCELAND COURT, CORONA, CA 92879. APPLICATION TO MAIL AT PERIODICALS POSTAGE RATES IS PENDING AT CORONA, CA AND AT ADDITIONAL MAILING OFFICES. POSTMASTER: SEND ADDRESS CHANGES TO NUTS & VOLTS MAGAZINE, 430 PRINCELAND COURT, CORONA, CA 92879-1300.



ANY CONTROVERSY ON MASS MERCHANDISING THE HAM RADIO SERVICE?

6

Electronic superstores such as RadioShack, Tech America (now RadioShack.com), and Fry's provide a nice balance along with local specialized ham businesses in offering service and products for amateur radio operators. *Gordon West*

RADIO CONTROL SERVOS — A PRIMER!

10

Get the skinny on radio control servos and what will work for you. *Eloy Marez*

BUILD A TUNABLE NOISE GENERATOR

25

Electrical noise is often considered an enemy. But, in fact, noise can be useful in a great number of applications. *Thomas Henry*

REVIVING NICAD-POWERED DEVICES

46

Take a look at some ways to salvage dead nicads from the scrap heap and recycle them back into active duty. *Kenton Chun*

POWERPOINTING YOUR PROJECTS — PART 3

48

This month, we put the template from last month to use by doing a board layout for the schematic created in Part 1. *Steve Daniels*

ROBBI'S VIOLIN/GUITAR TUNER

87

Stay in tune with this practical instrument. *Evert Fruitman*

Columns

AMATEUR ROBOTICS NOTEBOOK

68

Bit-level routines for an I2C slave, mini reviews on two robot kits, and a few words about the loneliness of the long-distance robot builder. *Robert Nansel*

COMPUTER-CONTROLLED WORLD

43

Utilizing the BASIC Stamp II SX to manage a graphical user interface with all the "bells and whistles." *Ryan Sheldon*

ELECTRONICS Q & A

TJ Byers

76

OPEN CHANNEL

18

Dealing with AC power line and electrical device EMI. *Joe Carr*

STAMP APPLICATIONS

64

Meet STAMP Net: a multi-drop Stamp-based network. *Lon Glazner*

Classified Ad Index

10. Ham Gear for Sale	36	120. Components	56
20. Ham Gear Wanted	36	125. Microcontrollers	57
30. CB/Scanners	36	130. Antique Electronics	57
40. Music & Accessories	0	135. Aviation Electronics	57
50. Computer Hardware	37	140. Publications	57
60. Computer Software	38	145. Robotics	58
70. Computer Equip. Wanted	38	150. Plans/Kits/Schematics	58
80. Test Equipment	38	155. Manuals/Schematics Wanted	59
85. Security	40	160. Misc. Electronics For Sale	59
90. Satellite Equipment	41	170. Misc. Electronics Wanted	60
95. Military Surplus Electronics	0	175. BBS & Online Services	0
100. Audio/Video/Laser	42	180. Education	0
110. Cable TV	42	190. Business Opportunities	61
115. Telephone/Fax	56	200. Repairs/Services	61

Departments

Advertiser's Index	82
Classified Ad Info	82
Dealer Directory	81
Events Calendar	30
New Product News	93
News Bytes	22
NV AdMart	73-75
NV Bookstore	92
Prize Drawing	7
Reader Feedback	22
Tech Forum	84



Published Monthly By
T & L Publications, Inc.
430 Princeland Court
Corona, CA 92879-1300
(909) 371-8497
FAX (909) 371-3052

E-Mail — editor@nutsvolts.com
URL — <http://www.nutsvolts.com>

Subscription
Order ONLY Line
1-800-783-4624

PUBLISHER
Jack Lemieux N6ZTD

EDITOR
Larry Lemieux KD6UWV

MANAGING EDITOR
Robin Lemieux KD6UWS

**ON-THE-ROAD EXHIBIT
COORDINATOR**
Audrey Lemieux N6VXW

SUBSCRIPTIONS
Abby Madain

CLASSIFIED ADS
Natalie Sigalus

DISPLAY ADS
Mary Gamar
Copyright 1999
by

T & L Publications, Inc.
All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. Nuts & Volts Magazine assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in Nuts & Volts. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in Nuts & Volts. Please send all subscription orders, correspondence, UPS, overnight mail, and artwork to: 430 Princeland Court, Corona, CA 92879.

ANY CONTROVERSY ON MASS MERCHANDISING THE HAM RADIO SERVICE?

by Gordon West WB6NOA

About 15 years ago, I received a telephone call from a Mr. Robert Miller, (present) ham call sign K2RM. Miller was doing some fact-finding about various radio services, and the type of equipment that might be appropriate for a first-time buyer. I explained that amateur radio equipment has traditionally been sold by specialized ham radio dealers, and I would anticipate some raised eyebrows by ham operators who might see the equipment selling through non-traditional ham avenues.

"Has the exposure of ham radio in over 7,000 RadioShack stores helped expose ham radio to radio-hobby beginners, including training materials to obtain the amateur radio license?" asked Miller. I about fell off my chair — how many stores are we talking about???

The stores were RadioShack, and Miller wanted to insure a smooth transition into the entry-level ham radio VHF handheld market, along with training books to underscore the federal requirements to pass the amateur radio examination before transmitting over the two-meter airwaves. The books were written from Novice through Extra, Morse Code tapes were produced specifically for learning the code and then increasing code speed to General class 13 wpm, and RadioShack's HTX-202 two-meter handheld came in, manufactured overseas by Maxon only for RadioShack. While the HTX-202

could take an old ICOM 2-AT battery pack, the equipment was *not* made by ICOM, nor was there any way to alter it to receive out-of-band signals. But it was quite a handheld, and featured band-pass tuning which made it virtually intermod free.

When the radio and training materials hit town across the country, both ham radio manufacturers and ham radio dealers cried FOUL! These inexpensive ham sets might actually get sold to non-hams! Yet many of these dealers were selling mail order on the word that the buyer had just passed a ham test, or selling into marine fishing markets, or selling to buyers who expressed an interest to begin monitoring the airwaves and promised not to transmit until the license arrived.

The inrush of non-licensed radio operators on the two-meter band, talking illegally over the airwaves, *never occurred*. Thanks go to Miller and his staff for the training of RadioShack sales personnel to fully explain the ham radio license requirements to potential buyers, and steer those buyers to 49 MHz no-license equipment if they had no interest in studying for the test.

And guess what happened — ham dealers across the country began to see the ham radio service *grow* with this increased public exposure of equipment, and the availability of my ham radio books and tapes at their local RadioShack store. The RadioShack exposure of the ham radio service was such a big success that the prestigious American Radio Relay League (ARRL) began selling *their* entry-level book, along with a store database of volunteer examiners, volunteer elmers, and a listing of local amateur radio testing dates. Miller

reports that many store managers were actively giving out local ham radio referrals, and local elmers and clubs were quite pleased with this additional exposure.

And the little HTX-202 was a solid performing entry-level handheld, and it was an inexpensive way to get on the air and learn more about the more elaborate beginner equipment available at the local specialty radio store, just down the street or across town. Needless to say, ham specialty dealers began to see that the RadioShack exposure of the ham radio service and beginner ham equipment was actually



Justin Buker
KD7BOQ operates the
Tech America ham
station.



Janet Margelli KL7MF,
manager of Ham Radio
Outlet, Anaheim, CA,
talks about the over
150 years of collective
employee ham
experience at her store.

good for their overall walk-in and call-in sales.

In recent informal surveys that have been conducted, about "How did you get into ham radio?", over 40 percent of the respondents indicated they learned about ham radio from RadioShack, or were referred to RadioShack for their ham radio training materials from this author, as well as the training materials from the ARRL. And for learning the code, over 60 percent indicated they started with RadioShack code tapes to begin learning the dits and dahs. RadioShack has recently expanded their

exposure of ham radio equipment and training materials into their burgeoning chain of technical equipment stores called Tech America.

The popularity of these electronic parts-and-equipment super stores has been so great that they have expanded the chain as "RadioShack.com." If you regularly work in electronics and electronic parts, you will discover these stores, as well as their huge catalog as the ultimate resource for that teeny little coil, that specialized kit, or for high-tech test gear like Fluke.

And ham radio! Big names like Alinco, Cushcraft, Alpha Delta, Rohn Towers, Rainbow and Vectronics radio kits, Valor, Standard Radio, and their own line of single-band and dual-band base and mobile antennas.

"We get a lot of technical personnel who will stop in and look over our shoulder as we

operate our in-store ham station," comments Justin Buker KD7BOQ. "And this gives us an opportunity to tell our customers about all the local ham radio clubs that can help them break into the ham radio hobby," adds Earl Cantie KD7EMK, of Tech America. Both Justin and Earl are active on the air, operating the stations both at home, mobile, as well as at Tech

America in the Mesa, AZ, Tech America store.

"We find many of our technical customers interested in building ham radio kits, too," adds Jed Peretz, General Manager of the Tech America, Mesa, AZ, store.

Is a non-ham-specialized general electronics superstore a good spot for ham radio recruitment? We say an absolute YES!



Gordon West doing a teleconference ham demo for Fry's Electronics sales personnel and customers.



You Win with Nuts & Volts

September Prize Winners:
Richard Saxon
of Baskingridge, NJ
D.W. Blakey
of Conway, MO

Subscribe today and be
automatically entered in
our new MONTHLY PRIZE
DRAWING!!!

NOVEMBER DRAWING HOSTED BY

Velleman

(see page 67)

4HS5 Personal Handheld Scope

If you do not wish to order a subscription, but would like to be entered in our drawing, simply **send or E-Mail** your name, address, and telephone number, to NUTS & VOLTS, 430 Princeland Court, Corona, CA 92879, drawing@nutsvolts.com. *No phone entries accepted.* All orders/entries must be received by the last day of the month to be included in that particular month's drawing.

As a current, paid subscriber, you will be auto-
matically entered each month in our drawing.
To Subscribe — Just fill in and mail the enclosed
subscription card or call our toll free order line
at (800) 783-4624 with a Visa or MasterCard.

Contributors ... Parallax (back cover) • Corporate
Systems Center (pages 2, 95) • HSC (page 3) •
Resources Unlimited (pages 28-29) • Timeline, Inc.
(page 55) • Alltronics (page 24) • Electro Mavin (page 64)
• All Electronics (page 38) • Roger's Systems
Specialist (page 32) • Electronic Goldmine (Oct. issue,
page 87) • MCM Electronics (Oct. issue, page 27) •
Velleman (page 67) • Seabird Technical (page 75)
Providing Prizes Monthly: Netcom (page 23)



Ham Day at Tech America Mesa, AZ store.


During field day a year ago, we set up our amateur radio recruitment communications van in front of Fry's Electronics corporate head-quarter store in San Jose, CA. "The van was mobbed all day, and we saw many of our cus-

tomers purchasing ham radio training materials to become a licensed operator," comments David Randolph KF6JPE, the merchandising and operations supervisor of Fry's Electronics corporate. "And many of our customers went into local ham radio clubs to obtain training; and when they graduated by passing their ham radio tests, many came to us and some also went over to local ham specialty stores to load up on equipment," adds another Fry's representative.

Fry's personnel also attended some of these licensing classes in order to learn more about ham radio themselves, as well as obtain the amateur radio license as a hobby. Fry's carries a full complement of amateur radio equipment and accessories, and was one of the first to bring on Kenwood and Alinco amateur radio equipment.

And I can tell you first-hand, Kenwood and Alinco product managers took some severe

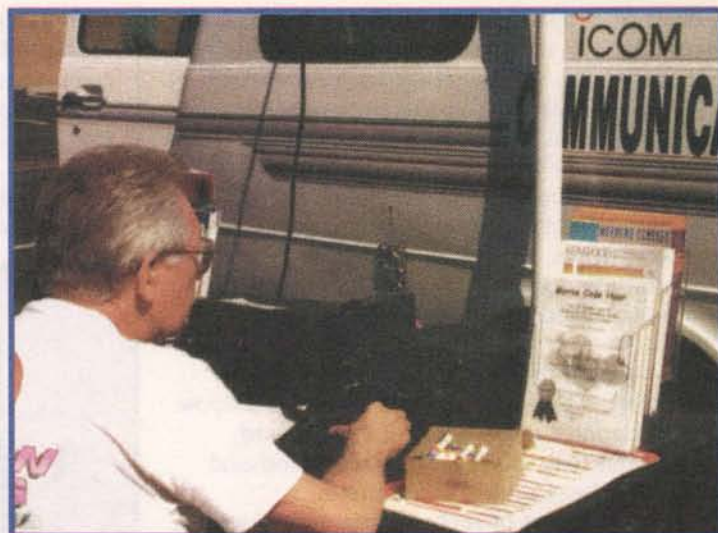Author West (left) and AES Las Vegas store manager Squeak AD7K present a parking lot demo of ham radio at a local APCO convention.



heat from the specialized ham stores because they were one of the first companies, along with West products and ARRL materials, to sell mass merchandisers.


And guess what — after the smoke cleared, most local specialty stores just down the street from Fry's Electronics also enjoyed a pick-up in amateur radio sales from those hams who needed more specialized equipment and technical advice on how to grow further in the amateur radio hobby and public service.

Kenwood went so far as to develop a ham radio primer booklet specifically for the technical and non-technical non-hams to learn more about the ham radio hobby. And this is not just a little three-pager — this is a 24-page, color-cover, illustrated manual that not only "sells" the ham radio service, but also gives out key toll-free telephone numbers about how to learn more about the service, including ARRL, W5YI, AMSAT, and ARES/ RACES contact informa-



UNI-MICRO™ Super-Small-Low Power

The NEW UNI-MICRO series of modules provides a complete ready to use single board computer on a 1.75" X 1.5" module with large amount of non-volatile flash based memory. Expanded capabilities, multiple serial busses, In-circuit programming, including first time programming and a very low power consumption of 58 mA, makes this series of modules perfect for instrumentation, monitoring and control applications.

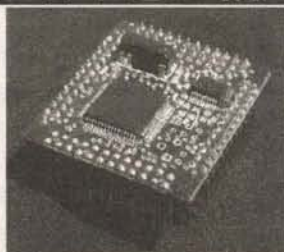

Microcontroller Design Made Simple

Small • 80C51 code compatible • 256 x 8 ram • 2K x 8 Battery backed sram with automatic power switching • 128K x 8 Flash memory • Parallel or serially programmable • 32K x 8 Flash memory • 3 16 bit timers • One 8 channel 10 bit A/D converter • Two 8 bit PWM outputs • One full duplex UART • 16 Mhz speed • 3000 gates flash CPLD • IIC serial bus • JTAG bus • 54 configurable I/O pins • RS232 driver on board • Voltage regulator on board • Power-on reset • Program security • Very low development costs • Assembly, C, Basic programmable.

\$59

OS Systems

908-979-1885 <http://www.ossystems.net>
1464 Route 57th, Port Murray, NJ 07865

Model PTS-10
\$55



LIFETIME WIRE STRIPPER, a breakthrough in wire stripping technology. Extremely fast tool will strip PVC insulation #14 to #30 AWG from solid, stranded or shielded wires. High quality strip is achieved by patented stripping element (.008" thick) which thermally cuts the insulation all the way to the conductor without nicks. Five year test, with over 2 million stripped wires, using the same element, speaks for itself. The stripper has won a —

"FIVE STAR PRODUCT OF THE MONTH"

award in DESIGNFAX magazine. Strippers for TFE, KAPTON, KYNAR, SILICONE RUBBER, etc. and rechargeable, battery powered strippers also available.

PATCO Service, Inc., 2515 Glencoe Rd., Baltimore, MD 21234
(410) 444-4010 Fax (410) 254-9566

tion. The ARRL also supplies both Fry's, as well as RadioShack and Tech America with promotional free ham radio handouts, too.

And all of these stores are eager for local ham radio clubs to work with the store manager for a spot to put up ham radio club announcements, ham radio exercises, and local ham radio elmer and testing contact phone numbers.

These stores also encourage ham radio demos in connection with their store.

Our most recent Tech America Mesa, AZ, communications van display drew both licensed, as well as soon-to-be-licensed radio operators to the facility and parking lot to see what's new in ham radio equipment, what's happening with the new regulations soon to be announced by the Federal Communications Commission, and a one-on-one discussion with local and visiting radio experts.

And how are the specialized ham radio dealers taking the expansion of equipment into mass merchandisers? At first they were outraged. Some dealers said they would either pull the lines or boycott them. And then when things cooled down, guess what happened ... a steady stream of new candidates coming into the specialized store, seeking more personal attention from long-time ham radio experts on the planning of their future station, and more than likely the ultimate purchasing of that step-up ham equipment from the specialized dealer.

"Having one of these big super stores down the street selling a limited selection of ham equipment may actually do us more good than harm," comments a local Southern California ham radio specialized dealer. "Our store alone has more than 130 collective years of ham radio experience, and this is something that only we can offer when the new ham may wish to get real serious about our great hobby," adds the specialized ham store sales person.

It appears the controversy of the big chain stores offering selected pieces of ham radio equipment is no longer a dispute, but rather is turning into an opportunity for further exposure of the ham radio hobby to electronic enthusiasts who may know little about what it takes to get a license and get on the air. And with Tech America offering such a complete line of hard-to-find technical parts and gadgets for the electronic technician, we could very easily see for technical types getting back into a hobby which has recently been going more to family interest, rather than high tech.

But most important to the amateur service is the Tech America, RadioShack, and Fry's willingness to support amateur radio exposure to non-hams through in-store displays, parking lot demos, ham club donations,

and an up-to-date computer listing of local test sites, local elmers, and local clubs through the efforts of the ARRL.

And best of all, if the radio hobbyist is not really that interested in working hard for the ham ticket, the RadioShack's, Fry's, and Tech America's have plenty of Family Radio Service, GMRS, and 49/900 MHz no-license equipment to sell the radio hobbyist if they don't think they can make the ham radio grade.

So the times, they are a changin'. The specialized ham radio dealers will *always* be the very best source of the ultimate complete line of makes, models, and varieties of amateur

radio and shortwave equipment. But for scanning, CB radio, kits, and parts and projects, and individual coils and caps, the electronic superstores are finding a nice balance with their customers who may have come in for an electronic part, but leave with not only the part, but with an exposure to amateur radio equipment and licensing materials, as well as a computer readout of their local ham radio club.

Who's selling ham radio equipment in your area? Spend some time with them and see all that they are doing for the amateur radio service. **NV**

JAMECO®
Since 1974
ELECTRONIC COMPONENTS
COMPUTER PRODUCTS
1-800-831-4242

Catalog 994
www.jameco.com
1999/2000
November - January

FLUKE
123 DIGITAL MULTIMETER
1163.5V 432.6Ω
F1 F2 F3 F4
V_A V_B V_C
JE25
BOTTOM VIEW
9827

Rubycon
4.7µF 50V

JE25

CD-ROM

Your Component Path jameco.com To the New Millennium
Call for Your Free Catalog Today! Just Mention VIP# NV9

RADIO CONTROL SERVOS — A PRIMER!



**The radio control hobby
is alive and well —
unbelievably so!**

by Eloy Marez



To show the relative size of modern radio control model airplanes, shown is Michele Green (Santa Ana, CA) along with the "Tsunami," an airplane built and flown by Tom Easterday of Brea, CA. It is a giant scale racer, intended for Reno-style racing, and capable of speeds in excess of 200 mph.

The technology involved is as advanced as related disciplines allow; to include not only reciprocating but also turbine engines and control systems, using every transmission, control, and display techniques available.

Competition is at Olympic levels, with events in which qualified contestants vie for over \$100K in aerobatics, while others race \$10K airplanes over a Reno-style course at speeds (actual, not scale!) of over 200 MPH.

The subject of radio control servos is not new here in the pages of *Nuts & Volts*, as they have been found to have many uses in robotics and other electro-mechanical applications.

They are truly amazing little devices, generally well-built both mechanically and electrically, precise in their operations, and inexpensive — at least in some cases — though they can also be somewhat expensive.

Most mentions of R/C servos here in the past have dealt only with the low end of the line, those generally marketed in the radio control (R/C) world as "standard" servos; basic units favored for entry level and sport activity. Such servo — all very similar regardless of the maker — generally develop some 50 ounce/inches of torque at a speed of .20 seconds for 60 degrees of rotation of the output wheel. In size, they measure an average of .75(W)" x 1.6(L)" x 1.4(H)" and weigh around 1.5 ounces.

There are many other types of R/C servos, smaller and larger — much, much larger, which I would like to acquaint you with. But first, a short refresher as to what makes these useful devices tick — pun

intended!

Radio control servos are controlled by a Pulse Width Modulation (PWM) signal, the standard being 1.0 to 2.0 milliseconds long, with centering at 1.5 mS. So commanded, most R/C servos travel about 60° stop to stop; that is, $\pm 30^\circ$ each side of center, though a few will go as much as 90° total.

The radio systems themselves use either Pulse Code Modulation (PCM) or Pulse Width Modulation (PWM) for encoding at the transmitter; the latter being completely erroneously referred to in most R/C material as PPM (Pulse Position Modulation). Regardless, the output of the receiver decoder — both PWM and PPM receivers — is PWM, with the above timing, at an amplitude of at least 3.5 volts.

In the R/C system, a multi-channel (read: multi-servo!) system, the encoding starts off with a long sync pulse, followed by a string of 1.0 to 2.0 mS pulses, one for each control channel. The total time of the sync pulse plus all of the control pulses — generally on the order of 20 mS — is referred to as the "frame rate." We can then see that each servo in the string receives a control pulse every 20 mS, or 50 times per second.


At this frame rate, the servo will travel smoothly from one end of its travel to the other. Slowing the rate will cause it to visibly skip from one position to the next as each control pulse is received.

While a faster rate can actually be applied, its benefits are limited by the mechanical design. That is, since the motor has a terminal speed, commanding it to go faster will have no effect.

In a non-R/C, single servo application, the sync pulse is not necessary — the pulse generator needs



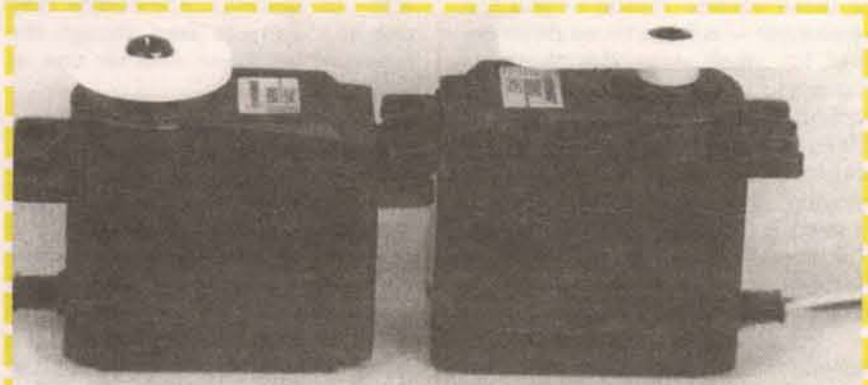
The so-called "Standard" servo generally featured in previous *Nuts & Volts* articles, measures approximately 1.5 x .75 x 1.5", weighs about 1.5-1.6 ounces, and produces about 50 oz.in. of torque.



Only slightly larger than its standard (l) sibling, the Airtronics 94257 and 94258 servos are rated at an unexpected 110 oz.in./0.06 sec. and 145 oz.in./0.09 sec., respectively.

only to provide the 1.0 to 2.0 mS pulses at a minimum of 60 Hz rate.

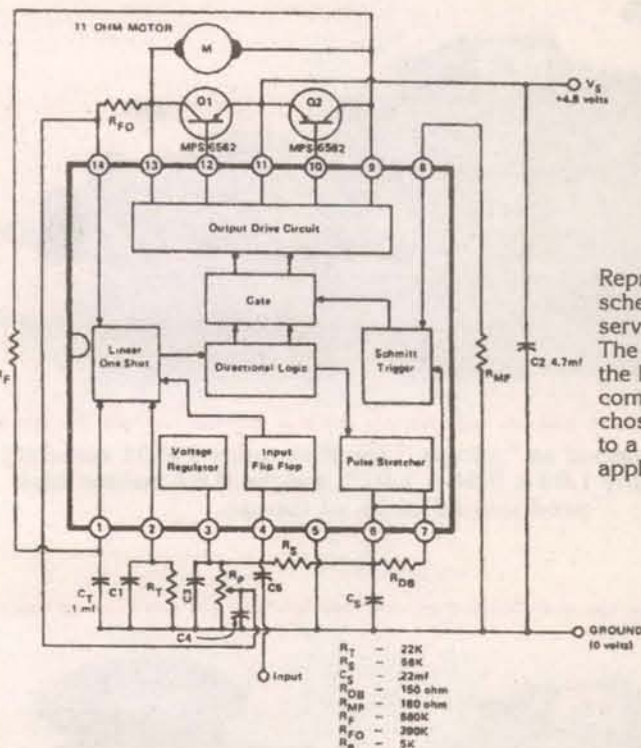What is happening inside? First, there is a reference pulse generator



Representative schematic of a servo's electronics. The heavy border is the IC, the external components are chosen to tailor it to a specific application.

set at 1.5 mS. Its output, and that of the incoming pulse, are fed to a comparator, where the difference, if any, is detected. This difference ultimately results in a DC voltage being applied to the motor, its polarity determined by whether the difference in the length of the incoming pulse is plus or minus.

A feedback pot, mechanically coupled to the motor via the gear train, then adjusts the output of the

reference generator; when it matches the incoming pulse, the difference is canceled, the DC to the motor is removed, and the action stops — until an incoming pulse of a different length is detected. Clever, huh! And all designed and produced primarily for hobby use!

With the exception of filtering and a few components needed to tailor the electronics to a specific use, everything is included in an IC

Panasonic Color Camera

Ask for the **Quick-Start KIT** Accessory

MB-45cB - \$99.95

Size: 1.25" x 1.25" sq. w/ Footprint

Micro Color MB-45cB: \$99.95

- Wide Voltage Range, 5-12 Volts!
- Horizontal Res. More than 380 lines.
- Small Footprint!
- Self contained ultra small package design for various applications.
- MCM PCB design for minimizing the size and improve durability.

Flat Screen TFT-LCD Monitors

TFT-4 \$179.95

Color 4" Screen.

(Size: 6"(W) x 4.5"(H) x 2"(D))

An excellent 4" monitor for one

camera monitoring

or for setting up

cameras during

installation

or maintenance.



Color TFT Monitors

Cameras with Built-In Infrared Illuminators.

LP-850w
Operates on 0.0 LUX in Total Darkness.
Weatherproof Video Camera!

NEW MB-810B - High Powered IR-LED's.
10 X's the power!



MB-810B
• New BLC
• Multi-Mount option
• High Resolution
MB-810B \$119.95

The Door Video Camera Is Designed to replace a Standard Front Door Peep Hole!

- For Home or Office.
- Shipping/Receiving.
- Employee Entrance.
- Viewing without Moving.

INCLUDES 60 Feet of Cable!



DV-810 \$199.95

Micro Video Specialist



MB-650PA - \$Call
2.8mm Pinhole Lens.

MB-650UA - \$Call
4.3mm Micro. Lens.

MB-750P - \$Call
2.8mm Pinhole Lens.

MB-750U - \$Call
4.3mm Micro. Lens.

MB-650a Series
• Built-In Audio
• 1.18" sq.
• 380 TV Line

MB-750 Series
• 1.25" sq.
• 420 TV Line

Call and Compare! We Match or Beat All Prices!

WIRELESS TRANSMITTER MODULES

Makes any Camera Wireless.

When wires are impossible to run, our wireless transmitters & receivers are lightweight and excellent for Hobbyist or Remote Control-Airplanes, Boats & Helicopters enthusiast. Small enough to place anywhere. Can operate off of 12VDC or Battery power supply.

MPX-900HP

900 Mhz High Power \$Call

MPX-900

900 Mhz \$119.95

MPX-2400

2.4 GHz \$119.95

All complete with FM Module 4 Channel Transmitter with Audio/Video cables, Power Switch/LED and Antenna.

Antenna's Included!

GW-2400S - \$449.95

Includes: 2.4 Ghz Color Wireless Camera. Receiver with Built-In Monitor.

"Portable" Color Wireless System



GC-2400 \$229.95
(Camera)

GM-2400 \$269.95
(Monitor/Receiver)

Polaris Industries
<http://www.polarisusa.com>

1-800-752-3571

470 Armour Drive NE • Atlanta GA 30342-3943 • Tech Info 404.872.0722 • FAX 4-4.872.1038




FREE
Polaris Products Catalog


100's of Video Products



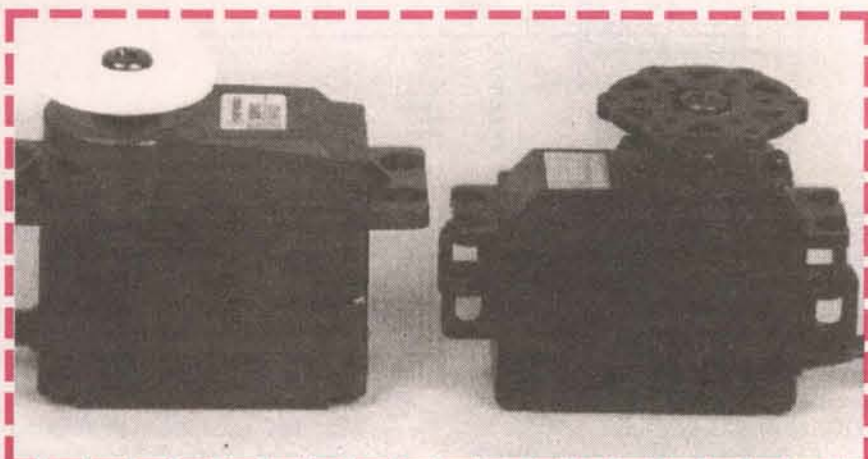
In the class named as "micros," the Airtronics 94501 servo (r) measures only 1.07 x 0.50 x 1.07", weighs 0.57 ounces and produces 29 oz.in. of torque.



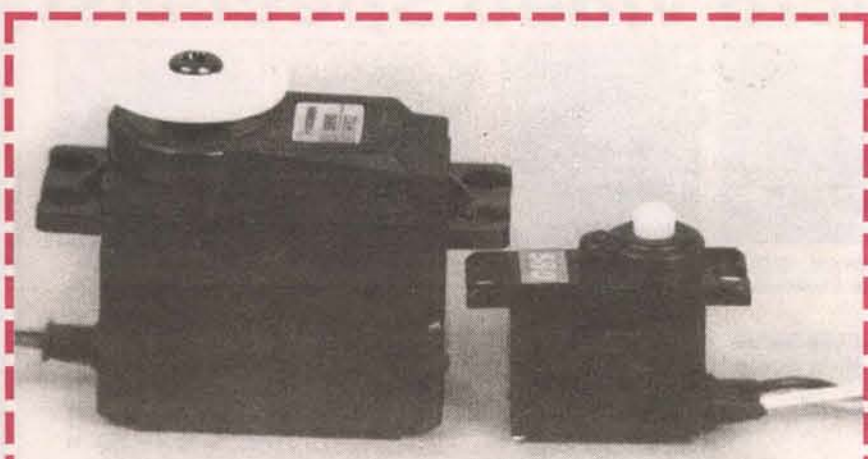Unique for having mounting ears on the case sides, the Airtronics 94141 and 94145 servos measure 1.42 x 0.60 x 1.29", weigh 1.11 ounces, torque being 45 and 33 oz.in., respectively.



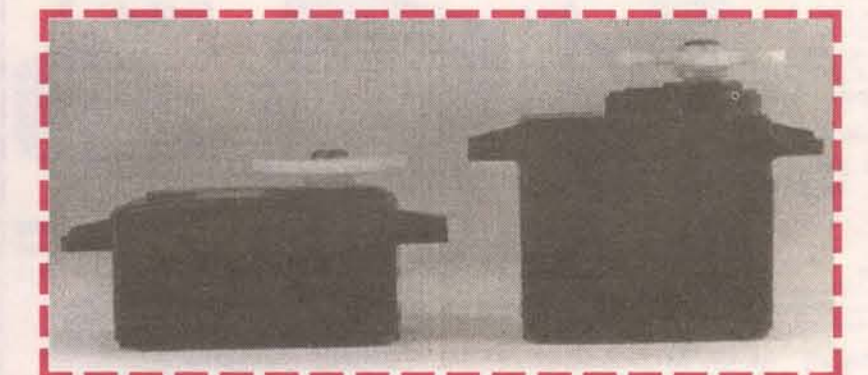Representative of a mini available in a number of different brands, the imported servo shown here (r) is a tiny 0.78 x 0.43 x 0.86", capable of torques from 10 to 20 oz.in.



The squat servo on the left is intended for retract gear operation, close in size to the standards except for height. It is available as positionable and non-positionable versions.

designed specifically for servos. However, the more sophisticated ones to be described — capable of developing much higher power than the "standard" servo — require the addition of external (to the chip) drive transistors capable of carrying the higher current used by the motor. These range from common TO92, to SMD MOSFETS, and in the *really* large servos pictured, TO220 transistors are used. Let us discuss some of the terminology you will run into when you get away from the standard type of servos.

TORQUE AND SPEED

All R/C servos are rated for both of these values. Torque — you will remember — is force times distance, and for small units like these, is expressed in ounce-inches. Standard servos, on the average, are rated at 50 oz.in., that is, when fitted with a one-inch arm, they are capable of moving 50 ounces. If a two-inch arm is used, it can only move 25 ounces. The speed is given in fractions of a second, and is normally stated for either 60 or 90 degrees.

Traditionally, the torque and speed values were given with 4.8 volts (four Ni-Cd cells) for power but, in recent years, because of an increased interest in larger model aircraft, many users are powering the system with five Ni-Cds, or six volts, and now some of the servo manufacturers are rating their products at both voltages. Most servos will safely stand six volts, and some 20 percent increase in performance can be expected. All torque values stated in the captions are manufacturers ratings at 4.8 volts.

GEARS

Within the standard servo, you will find some precisely molded plastic gears. However, those servos rated for higher output torque generally incorporate metal gears. Such servos are generally a little noisier, and actually wear faster, but they can also withstand much higher reverse loads without gear damage. In their intended hobby use, time has not proven one type to be more

durable than the other, and probably as many prefer one as do the other. One of the claimed benefits for plastic gears is that being lighter, they allow the servo to reach full speed faster, and to coast less.

One of the definite advantages of plastic over metal is their replacement cost; \$5.00 or less compared to \$25.00 or more.

BALL BEARINGS

In a few of the standard servos, the load bearing output gear rotates within an Oilite or brass bushing, but more commonly, they are running in the plastic top case. The better class of servos support the output gear with ball bearings. Sometimes only one at the top is used, though the top-rated units use another one at their base.

INDIRECT DRIVE

Remember that feedback pot mentioned above? Well, in some designs, the output gear is attached directly to the pot shaft and, under loaded conditions, will cause it to move sideways enough to lift the wiper off the pot element, enough to effect some unwanted servo output. An indirect pot servo uses either a different gear to drive the pot, or some sort of a flex coupling to prevent this effect, and is a desirable feature in better servos.


CORELESS MOTORS

Found only in the better, more powerful — read: more expensive! — servos, the coreless motor is one designed without the traditional heavy armature, the winding being potted and self-supporting. The results are less inertia; the motor speeds up and stops faster, increasing the positioning precision of the servo. Coreless motors, being more powerful than their cored brethren, means a higher torque output in the same size servo.

MICRO-PROCESSOR SERVOS

Previously, I mentioned that the

POSITION SET

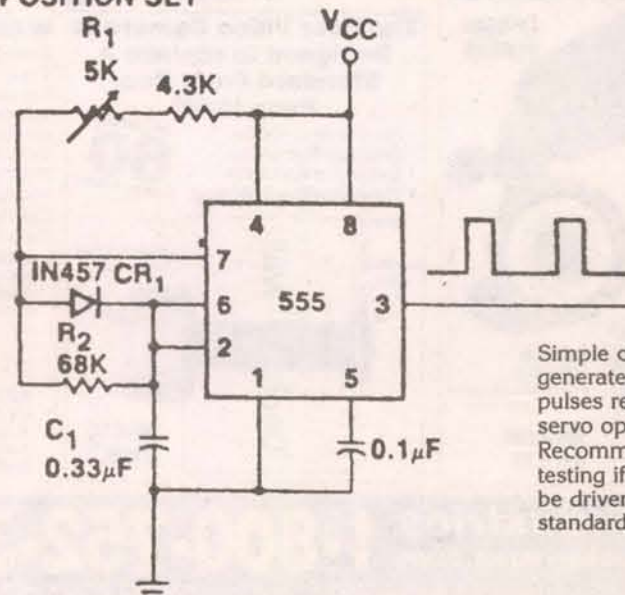

Simple circuit that will generate the control pulses required for servo operation. Recommended for testing if the servo is to be driven by other than standard R/C systems.

control pulse to the motor is applied at some 50 Hz, a value actually determined by the radio transmitter of the R/C system. The latest servo development incorporates a micro processor within the servo amplifier which converts that relatively low frequency to one much higher, resulting in frame rates (see above) from four to eight times shorter.

The results are a faster acting, more precise servo; one capable of producing more holding power. Their standing current — that is the current while they are at rest or not otherwise loaded — is also higher than the common variety. But then, we all know that electronics teaches us much faster than any other discipline that you never get something for nothing.

There are two such servos currently available: one a German design from a company known as "Multiplex," and available in this country from: Multiplex USA, 5399 Harter Lane, La Canada, CA 91011; (800) 375-1312, FAX (818) 790-1346. The Multiplex servos are unique, in that with the use of an external programmer, their output direction, amount of output rotation, and even the speed can be tailored as required.

The other such servos, actually termed "Super Servos" by their manufacturer, are from a Japanese company known as "JR," probably derived from "Japan Radio Control." The US importer is Horizon Hobby Distributors, 4105 Fieldstone, Champaign, IL 61821; (217)355-9511, FAX (217)355-8734. As far as is known, Horizon's JR equipment is available only from retail sources, and the Super Servos, while having the basic advantages derived from using the micro processor, do not include the programming features. In either case, be prepared for much higher than normal servo prices!

RETRACT SERVOS

Named after their primary function, retract servos are intended to operate the landing gear in the R/C airplane. They are available as normal positionable versions, and those with which, when commanded,

rotate only from their extreme CW to CCW positions. When used in a specific application, they offer the advantage of greater torque in a less-tall package.

SAIL WINCH SERVOS

Intended to position the sail in a model sailboat, sail winch servos are much larger than the normal car and/or airplane servos. They are relatively slow, though more powerful, are equipped with a much longer arm, and rotate approximately 180°.

APPLICATION

Like everything else, the proper application and use of a given servo will pay off in reliability and longevity. There are some basic guidelines.

CENTERING

As stated, the servo centers at 1.5 mS. It is important that this value be as accurate as possible, and that the mechanical linkage to whatever the servo is to operate also be adjusted to the center of its travel. There are two reasons for so doing. Most servos include a built-in mechanical stop that limits its total travel to slightly over 200 degrees. More about that later! If the control signal exceeds the indicated values significantly, it can drive the servo to the limits of its mechanical stop and stall. Operating it in that condition will cook something sooner or later.

Similarly, if the external linkage bottoms while the servo still has further movement, the servo will stall and eventually start sending you smoke signals.


SERVO SAVER

To prevent damage in the manner just described, a special output device, called a "Servo Saver" is made available. It incorporates a strong coil spring that does not inhibit normal servo operation, but if its movement is restricted, the spring takes up enough of the back pressure to prevent any damage to the servo. Servo Savers are available


through normal R/C hobby outlets.

DO NOT TURN THE SERVO OUTPUT! Manually, that is — do not grab the servo wheel or arm and turn it back and forth. The gear ratio is extremely high, over 300 to 1 in

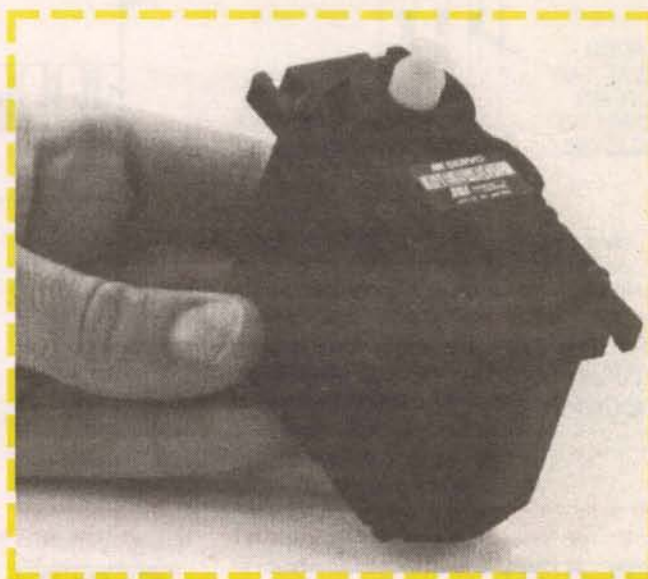
some designs. Forcing it to rotate backwards puts tremendous pressure on the motor pinion and succeeding gear, sometimes distorting the teeth. Think about it, there is absolutely no reason to operate or



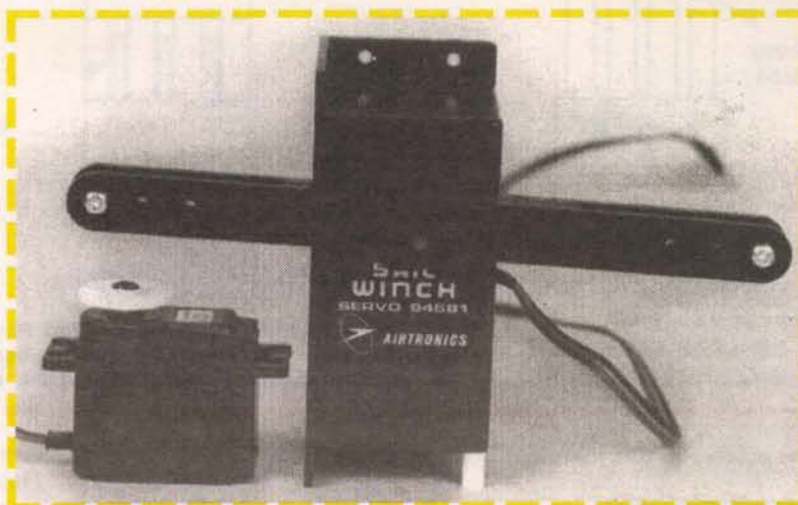
Classified as "Giant or Quarter Scale" servos, the biggie seen here (JR-605) is 2.30 x 1.26 x 2.50" in size, weighs 4.75 ounces and produces 139 oz.in. of torque.



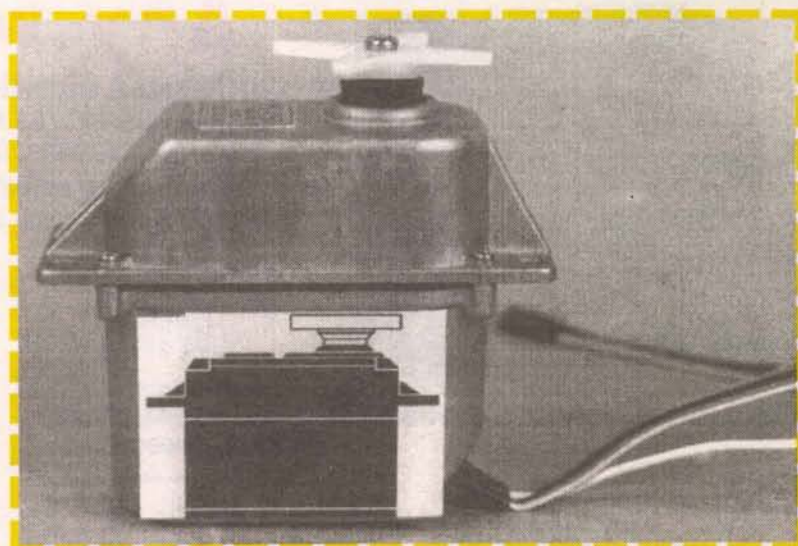Representative of the Sail Winch servos available, the Airtronics 94581 is 3.65 x 1.58 x 1.78" at 4.94 ounces, produces 10 oz.in. of torque at a speed of 5.0 seconds for 170 degrees.



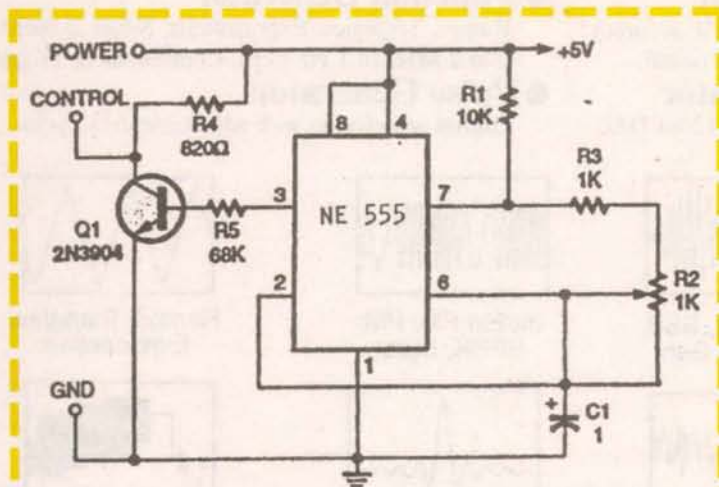With a sketch of a standard servo attached for size comparison, the PS-050 from Condor R/C (see text), though not a hobby servo, but operated by the same command signals, measures 3.94 x 1.73 x 3.66", including mounting and output arm. It weighs 10 ounces, produces 113 to 159 oz.in. depending on input voltage.



Servo control signal generator, used to test and familiarize oneself with their normal operation. The 1.0-2.0 mS pulse timing can be measured with an oscilloscope or for 90° operation of a servo. Battery power is recommended as most AC supplies will cause servo jitter.

maker if any doubt exists. As you might expect, reversing the power connections will harm a servo's electronics same as they will any other electronics device.

REVERSING THE ROTATION

In some applications, it is desirable for the servo to operate in the opposite direction. Obviously, one way to accomplish this is simply to reverse the direction of the control pulse changes. If this is not possible, it can be accomplished at the servo itself.



To do so, it is necessary only to reverse the two wires to the motor, and the outside connections to the pot. The latter's center connection is left untouched. Changing the motor connections is easy in many cases, as they are made with small wires.

However, in other cases, the motor is attached directly to the PC board, with a third connection for ground to the motor case. In that case, it is first necessary to remove the motor.

Many have a case grounding strap that snaps onto the rear end of the case and can be easily removed and installed on the opposite side. Upon replacing the motor back on the board, the power connections will be reversed.

TAILORING THE THROW

Similarly, the throw, that is, the degree of rotation of the servo's output, can be increased by increasing the variation of the pulse length. However, remember the internal stop mentioned earlier! That, and the fact that the feedback pot both also has a mechanical stop limits the total rotation. In some servos, there is a limitation within the amplifier, as they get unstable with travel over 200°, though 180° have been easy to obtain with every one I have ever tried.

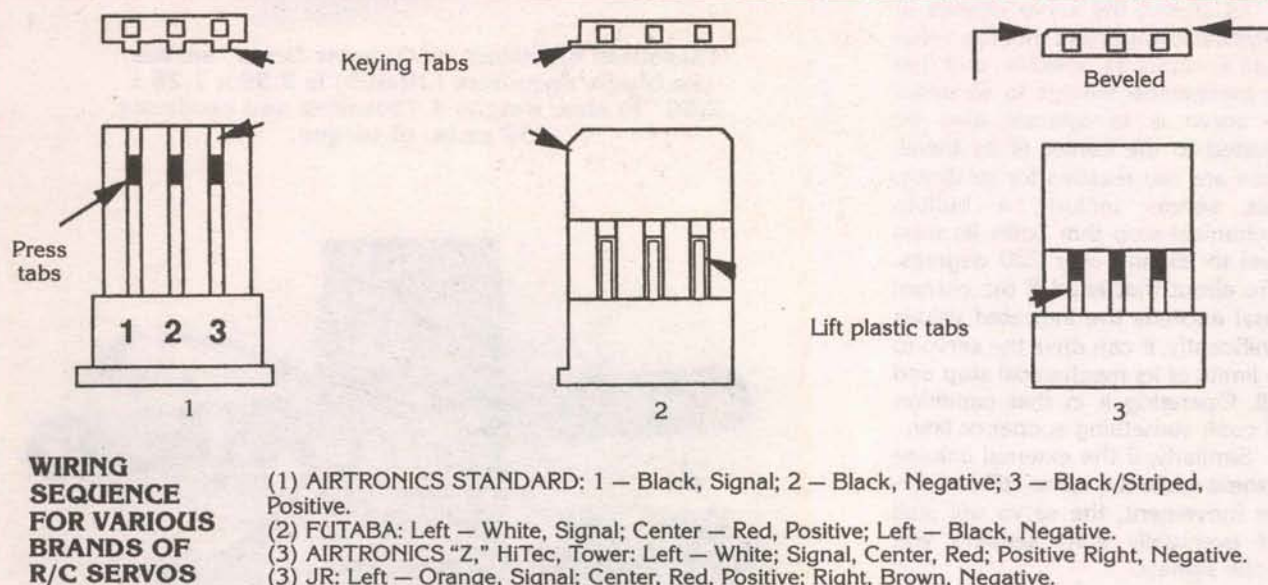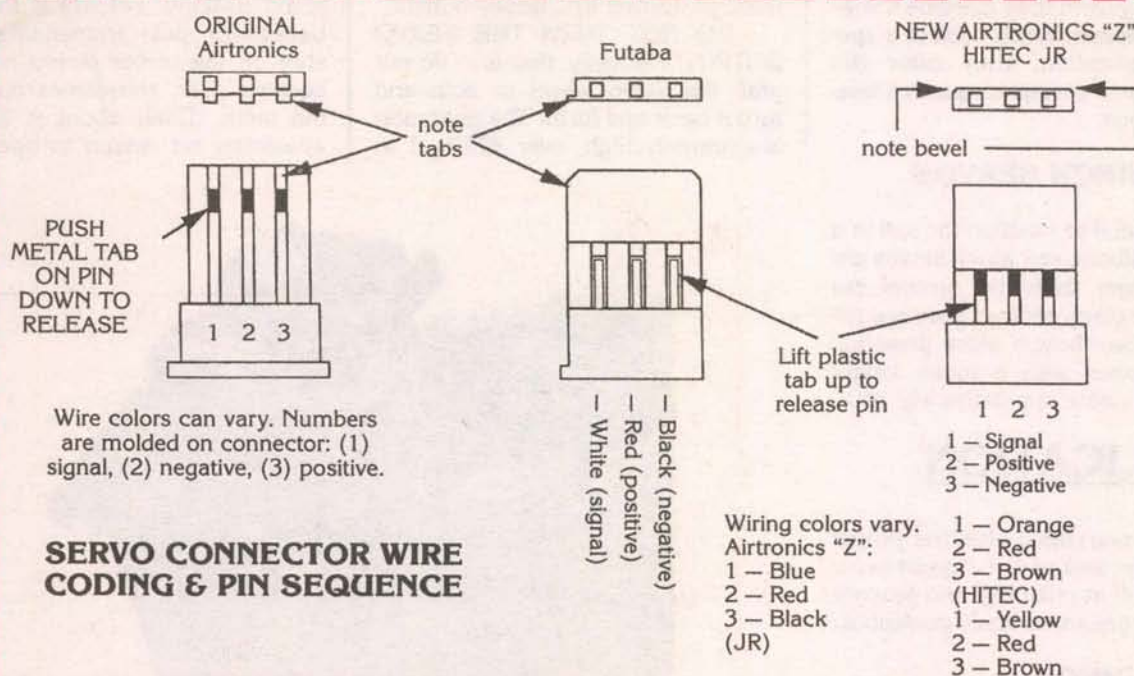

force a servo in this manner.


CONNECTIONS

The radio control servo requires

only three connections: the battery positive, the control pulse, and a common one. There is some variation in the wiring sequence and colors, an example is given in the

accompanying sketch.

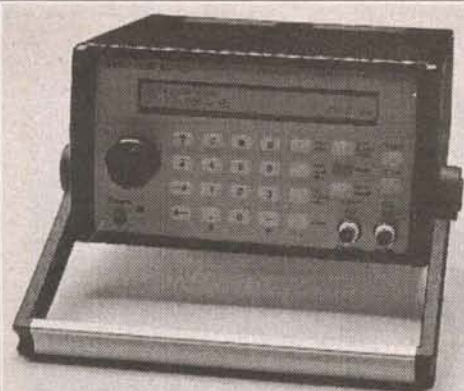Don't rely on wiring information or little else obtained from the young kids who often man the counters at hobby shops. Contact the servos



Telulex Inc. model SG-100A

New Features:

- ✓ 21.5 MHz
- ✓ .01 Hz steps
- ✓ multi-unit phaselock

Telulex Inc.

Any waveform you want!

● Synthesized Signal Generator

Clean sinewaves DC-21.5 MHz with .001% accuracy! .01 Hz steps. DC Offset. RS232 remote control.

● Arbitrary Waveform Generator


40 Megasamples/Second. 32,768 points. 12 bit DAC

● Function Generator


Ramps, Triangles, Exponentials, Noise & more. 0 to 2 MHz in 1 Hz steps. Continuous or Triggered.

● Pulse Generator

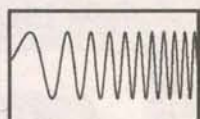
Digital waveforms with adjustable duty cycle




DC to 21.5 MHz linear and log sweeps

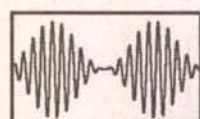


Int/Ext AM, SSB, Dualtone Gen.

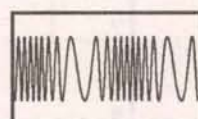


Int/Ext FM, PM, BPSK, Burst

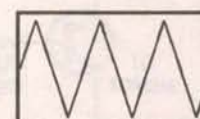


Ramps, Triangles, Exponentials

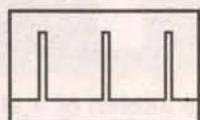


Pulse Generator

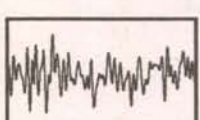

Noise

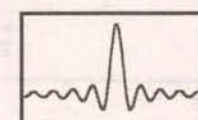

Arbitrary Waveforms

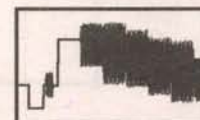

Unlimited Possibilities!

2455 Old Middlefield Way S
Mountain View, CA 94043

Tel (650) 938-0240

Fax (650) 938-0241

<http://www.Telulex.com>

Email: sales@Telulex.com

If your control pulse is fixed at the 1.0 to 2.0 mS rate, it is still possible to extend the servo travel. It is necessary only to pad the pot with fixed resistors, one at each end.

There is no ballpark figure; the value is determined by the exact servo in use and by your requirement. However, the resistor value is easy to obtain: add a 5K pot to each side of the installed pot, starting with it set at zero resistance. Slowly add resistance, equally on both sides, until the required effect is obtained.

Remove and measure the pots, install fixed resistors of the proper value in place.

SERVO DRIVERS

When working with servos, unless you have used and are thoroughly familiar with your power and pulse-generating equipment, it is a good idea to have on hand a drive system you can depend on. They are also available on the R/C market, intended primarily for use during servo installation independent of the radio system. Recommended are units from:


Custom Electronics, RR 1 Box 123B, Higginsville, MO 64037; (816) 584-6284, (816) 584-6285 FAX. Two drivers are available, one with a non-centering knob, though a more useful one for the uninitiated is its "JS" version; joy stick equipped and calibrated for the proper pulse lengths. It is powered by four "N" size alka-

lines (not included), and is priced at \$34.95 less connector, \$37.95 with a connector to match your servo. Also available is a universal plug, fittings, and the proper crimper.


ElectroDynamics, 31185 Schoolcraft Rd., Livonia, MI 48150; (734) 422-5420, (734) 422-5338 FAX. Its unit is called the "Servo-Ciser," is calibrated for proper servo travel, uses push buttons for directional control, and LEDs to indicate the degree of movement from center, in 33% increments. It also incorporates an automatic cycling function which will run the servo back and forth for testing purposes. The Servo-Ciser requires an external normal R/C four-cell battery for power. It is priced at \$44.95. A simple servo tester circuit, based on the ubiquitous LM-555 is included, for the more ambitious among you.

TROUBLE-SHOOTING

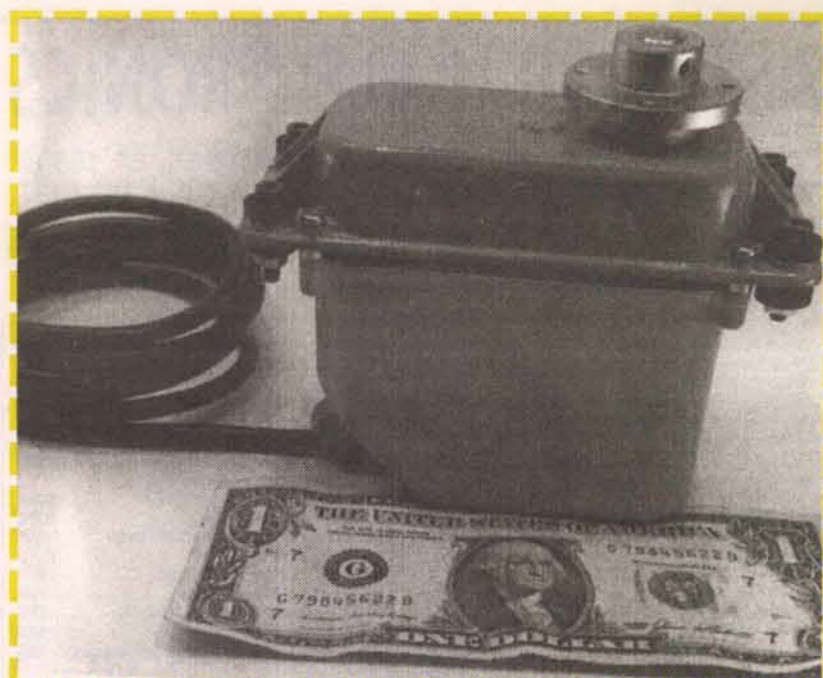Radio control servos are extremely reliable, but like everything else, now and then one acts up. There are only a few things that can be done if one does. Obviously, normal troubleshooting pro-



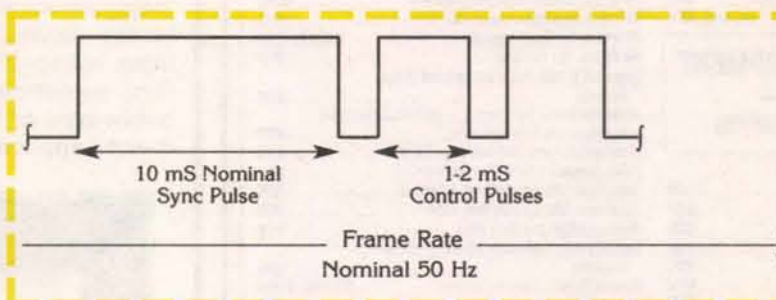Able to move mountains! Well, almost, the PS-105 from Condor R/C has a starting torque of 5278 oz.in., measures 5.12 x 2.17 x 4.37" at 28 ounces. It is available in 12 and 24 volt versions, normal and high speeds, 90 or 180° travel.



Information train as generated by the radio control system for servo operation. The control pulses center at 1.5 mS, drive the servo when varied plus or minus .5 mS. There is a control pulse, designated as 1, 2, etc., for each servo in the system. If only one servo is to be commanded, the sync pulse is not needed.

We accept Visa,
Mastercard, AmEx,
and Discover

Attention: Gearheads

www.shrevesystems.com

To Order Call 1-800-227-3971

Fax: 318-424-9771



PowerMac 7200
75 Mhz PPC 601
4 168 pin DIMM slots
Build your own Mac!
\$79 Brand New!



Peltier Junction
with heat sink
1 3/16" x 1 3/16"
\$10 each or 3 for \$25



Apple Color
Composite Display
Great for Surveillance
Refurbished **\$69**



Apple IIE Logic Board
\$19



LC Power Supply
+5V, -5V, +12V Output
\$5 New

Global Village Bronze CMS Tower SCSI Case \$99
External Modem
2400 Bps/9600 Fax
\$1 Each



Monitor Blowout Sale!
19" Color Monitors
Ridiculously
LARGE!
Ridiculously
CHEAP!
ONLY \$49 "As Is"
No cables



Apple LW
Personal NTR
with Toner
\$399



Claris Works
3.0 For
PC/Mac
EDOCs **\$29**



MacAllly ADB Keyboard
\$19




Apple
Remote
Control
\$1 EACH




PDA Genuine
Leather Carry
Case
Let your palm
pilot lead the life
of luxury!
\$10



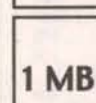RAM
1 MB 30 Pin 4 For \$1
4 MB 72 Pin 2 For \$5



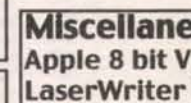Miscellaneous
Apple 8 bit Video Card \$19
LaserWriter IINT \$199
Apple ADB Keyboard \$19
1.44 Super Drive \$49
Clone ADB Mouse \$19
Quicktake 100 Camera \$129
Bernoulli 90 MB EXT \$10



Membrane
Track Pad for
laptop **\$2**



\$25 minimum
order

Shreve Systems
1200 Marshall st
Shreveport, La 71101

Returns subject to a 15% restocking fee.
Prices are subject to change without notice. We accept Visa,
Mastercard, AmEx, Discover

AST GLOBAL ELECTRONICS

24529 STATE HWY. 408, CAMBRIDGE SPRINGS, PA 16403
VOICE 814-398-8080 • 1-888-216-7159 • FAX 814-398-1176

VIEW COMPLETE LISTING AT:
<http://www.astglobal.com>

IF WE DON'T CARRY IT ... WE'LL FIND IT
QUICKLY ... AT REASONABLE PRICES.

EIP 545, Microwave Counter 18GHz.....	\$500
EIP 931, Microwave Source, 0.1-18GHz, Opt. 9320	SPECIAL \$3,200
Fluke 845AB, Null Detector/Micro Voltmeter 1uV-1000VDC.....	\$375
Fluke 5100B, Multifunction Calibrator, Opt. 03/05.....	\$2,800
Fluke 5100B, Multifunction Calibrator.....	\$2,400
Fluke 5200A, Programmable AC Calibrator.....	\$1,000
Fluke 5215A, Precision Power Amp.....	\$800
Fluke 6070A, Synthesized RF Signal Generator	
200KHz-520MHz.....	\$1,400
Fluke 8050A, DMM 4-1/2 Digit w/Battery Pack.....	\$145
Fluke 8050A, DMM 4-1/2 Digit w/o Battery Pack.....	\$145
Fluke 8520A, DMM 5-1/2 Digit.....	\$275
Fluke 9010A, Micro System Troubleshooter.....	\$375
General Radio 1658, Digibridge.....	\$475
Gigatronix 6061A, Synthesized Signal Generator	
10KHz-1050MHz.....	\$2,200
HP 141T, Spectrum Analyzer Mainframe.....	\$475
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,000
HP 141T, Spectrum Analyzer w/8552B/8553B, 1KHz-110MHz.....	\$1,200
HP 141T, Spectrum Analyzer w/8552B/8554B, 1KHz-1.2GHz.....	\$1,100
HP 141T, Spectrum Analyzer w/8552B/8554B, 1KHz-1.2GHz.....	\$1,700
HP 141T, Spectrum Analyzer w/8552B/8555A, 10MHz-18GHz.....	\$1,900
HP 334A, Distortion Analyzer.....	\$275
HP 400EL, AC Voltmeter, 10Hz-10MHz.....	\$150
HP 400FL, RMS Voltmeter, 20Hz-4MHz, 100uV-300V.....	\$175
HP 415E, SWR Meter.....	\$100
HP 432A, Power Meter w/Cable/847B, 0.1-18GHz Sensor.....	\$350
HP 436A, Power Meter w/8481H Sensor/Cable.....	SPECIAL \$975

TURN IDLE TEST EQUIPMENT — INTO CASH — CALL OR FAX FOR QUOTATION

HP 436A, Power Meter, Opt. 002/009/022 w/8481H	
Sensor/Cable.....	\$1,200
HP 651B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 652B, Test Oscillator, 10Hz-10MHz.....	\$125
HP 654A, Oscillator, 10Hz-10MHz, 90dB Attenuator.....	\$195
HP 1630G, Logic Analyzer w/pods.....	\$575
HP 1651A, Logic Analyzer.....	\$875
HP 3312A, Function Generator, 1Hz-13MHz.....	\$425
HP 3314A, Function Generator, Opt. 001.....	SPECIAL \$950
HP 3330B, Automatic Synthesizer, 20Hz-13MHz.....	\$295
HP 3400A, True RMS Voltmeter, 10Hz-10MHz, 1mV-300V.....	\$125
HP 3406A, RF Voltmeter, 50uV-3V, 1.2GHz.....	\$200
HP 3455A, DMM 5-1/2 Digit.....	\$250
HP 3456A, DMM 6-1/2 Digit.....	\$525
HP 3466A, DMM 4-1/2 Digit, AC/Battery, 5 Function.....	\$175
HP 3488A, Switch Control.....	\$450
HP 3551A, Portable Transmission Test Set.....	\$550
HP 3575A, Digital Phase Gain Meter 1Hz-13MHz.....	\$500
HP 3580A, Spectrum Analyzer, 5Hz-50KHz, LED Readout.....	\$650
HP 3580A, Spectrum Analyzer, 5Hz-500KHz, Mechanical.....	\$500
HP 3582A, Spectrum Analyzer, 0.2-25.5KHz.....	\$1,800
HP 3585A, Spectrum Analyzer, 20Hz-40MHz.....	SPECIAL \$2,800
HP 3702B, IF/BF Receiver w/3705 DIF. Phase Detector.....	\$475
HP 3730B, Down Converter Mainframe.....	\$750
HP 3770A, Amplitude/Delay Distortion Analyzer.....	\$300
HP 3779B, Primary MPX Analyzer.....	\$500
HP 3781B, Pattern Generator.....	\$250
HP 4274A/Opt. 001, LCZ Meter.....	SPECIAL \$2,400
HP 4959B, WAN Protocol Analyzer/J2213A.....	\$1,200
HP 4972A, LAN Protocol Analyzer.....	\$750
HP 5314A, Counter, 100MHz, Opt. 002, w/Manual, NICE!.....	\$175
HP 5314A, Counter, 10MHz, Opt. 001 (ICRO), NICE!.....	\$175
HP 5315B, Counter, 100MHz, Opt. 001, w/Manual, NICE!.....	\$275
HP 5315B, Counter, 1GHz, Opt. 001/003, w/Manual.....	\$425
HP 5316A, Counter, 100MHz, HP1B.....	\$350
HP 5328A, Counter, 100MHz w/DVM/Opt. 021.....	\$200
HP 5328A, Counter, 500MHz.....	\$250
HP 5334A, Counter, 100MHz, Opt. 010 Oven.....	\$500
HP 5340A, Counter, 18GHz (mixie).....	\$600
HP 5345A, Counter, 500MHz.....	\$450
HP 5345A, Counter, 500MHz, HP-IB.....	\$650
HP 6101A, Power Supply, 0-20V @ 1A.....	\$125
HP 6104A, Power Supply, 0-20, 20-40V @ 2A, 1A.....	\$150
HP 6112A, Power Supply, 40V @ 5A (metered).....	\$150
HP 6116A, Power Supply, 0-100V @ 200mA.....	\$150
HP 6177C, DC Current Source to 100V @ 500mA.....	\$275
HP 6202B, Power Supply, 40V @ .75A (metered).....	\$150
HP 6203B, Power Supply, 7.5V @ 3A (metered).....	\$150
HP 6205B, Power Supply (dual), 0-40V @ 3A, 0-20V @ 8A (metered).....	\$175
HP 6206B, Power Supply, 0-60V @ 1A (metered).....	\$200
HP 6212A, Power Supply, CV/CC, 0-100V @ 100mA.....	\$125
HP 6213A, Power Supply, CV/CL, 0-10V @ 1A.....	\$75
HP 6217A, Power Supply, CV/CL, 0-50V @ 200mA.....	\$100
HP 6218A, Power Supply, CV/CC, 0-50V @ 200mA.....	\$125
HP 6227B, Dual Tracking PS 0-25V @ 2A.....	\$375
HP 6260B, Power Supply, 10V @ 100A (metered).....	\$300
HP 6264B, Power Supply, 0-20V @ 20A.....	\$225
HP 6265B, Power Supply, 40V @ 3A (metered).....	\$200
HP 6266A, Power Supply, 40V @ 6A (metered).....	\$200
HP 6266B, Power Supply, 0-40V @ 5A.....	\$275
HP 6289A, Power Supply, 0-40V @ 1.5A (metered).....	\$175
HP 6294A, Power Supply, 0-60V @ 1A (metered).....	
New in box w/manual.....	\$275
HP 8011A, Pulse Generator, 1Hz-20MHz.....	\$175

HP 8013B, Pulse Generator, 1Hz-50MHz.....	\$275
HP 8015A, Pulse Generator, 1Hz-50MHz 30V.....	\$400
HP 8016A, Word Generator, 50MHz.....	\$600
HP 8018A, Serial Data Generator.....	\$750
HP 8091A, Rate Generator (1GHz) w/8092A Delay Generator	
(1GHz) w/8093A Output Amp w/15401A & 15400A.....	\$1,000
HP 8160A, Programmable Pulse Generator, 50MHz, Opt. 001.....	\$850
HP 8160A, Programmable Pulse Generator, 50MHz,	
Opt. 001/020.....	\$1,000
HP 8161A, Pulse Generator, 100MHz.....	\$1,500
HP 8165A, Programmable Sig Source, 1mHz-50MHz.....	\$950
HP 8175A, Data Generator.....	\$1,750
HP 8443A, Tracking Generator, 1KHz-110MHz.....	\$275
HP 8445B, Auto Preselector, 1.8-18GHz.....	\$275
HP 8445B, Auto Preselector, 1.8-18GHz Opt. 002/003.....	\$375
HP 8601A, Sweeper Generator, 1-110MHz.....	\$400
HP 8614A, Signal Generator, 800-2400MHz, AM/FM Leveled.....	\$300
HP 8616A, Signal Generator UHF, 1.8-4.5GHz, +10-12dB,	
AM/FM.....	\$300
HP 8620C, Frame w/8622B Sweeper .01-2.4GHz.....	\$1,150
HP 8624D, RF Plug-in, 5.9-9.0GHz.....	\$225
HP 8640B, Signal Generator, 5-1050MHz, Opt. 002/001 or 003.....	\$1,800
HP 8640B, Signal Generator, 5-512MHz, Opt. 001 or 003.....	\$700
HP 8658A, Synthesized Signal Generator, 100KHz-990MHz.....	\$1,400
HP 8684D, RF Signal Generator, 5.4-18GHz.....	\$1,700
HP 8743A, Reflection Test Set, 2-12.4GHz.....	\$200
HP 8770A, Arbitrary Waveform Synthesizer.....	\$2,400
HP 8901A, Modulation Analyzer Opt. 010.....	\$675
HP 8901A, Modulation Analyzer.....	SPECIAL \$650
HP 59303A, D/A Converter.....	\$125
Kepco ATE15-50M, Power Supply, 0-15V @ 50A	
(metered).....	\$500
Krohn-Hite 3202R, Dual Channel Tunable Filter, 20Hz-2MHz,	
High Pass, Low Pass Band Reject.....	\$200
National Instruments GPIB-100A, Bus Extender.....	\$175
Power Designs 2K-10 HV PS 1-2000V @ 10mA.....	\$375
Racal Dana 1991, Counter/Timer, 2 Channel.....	\$275
Racal Dana 1992, Counter/Timer, 1GHz.....	\$375
Rockland 1022F, Dual HiLo Filter.....	\$125
Rockland 5100, Synthesizer, DC-2MHz, .001 Hz	
Resolution.....	\$325
Sencore CM2000, Computer Analyzer.....	SPECIAL \$1,400
Sencore LC102, Capacitor/Inductor Analyzer.....	\$950
Sencore SC61, Scope (100MHz) w/New Probes, Dual Trace.....	\$750
Sencore SC61, Scope (100MHz) w/o Probes, Dual Trace.....	\$400
Sencore TVA92, TV Video Analyzer.....	\$1,100
Sencore VG91, Universal Video Generator.....	\$1,200
Sorenson DCR-80-5A, Power Supply, 80V @ 5A	
(metered).....	\$375
Tek 7514, Plug-in Sampling Plug-in, DC-1GHz.....	\$425
Tek AM501, Plug-in Op Amp.....	\$175
Tek AM502, Plug-in Differential Amp.....	\$225
Tek DC503, Plug-in Counter Universal, 100MHz.....	\$150
Tek DC509, Plug-in Counter, 135MHz, UNUSED.....	\$375
Tek DM502, Plug-in DMM.....	\$125
Tek DM502A, Plug-in DMM.....	\$125
Tek DM502, Plug-in DMM, 4-1/2 Digit.....	\$150
Tek FG504, Plug-in Function Generator, .001-40MHz.....	\$375
Tek PG501, Plug-in Pulse Generator, 5Hz-50MHz.....	\$175
Tek PS501-1, Plug-in Power Supply.....	\$150
Tek PS503A, Plug-in Power Supply Triple.....	\$175
Tek OIG-502, Plug-in Optical Impulse Generator (unused).....	\$500
Tek TR22, Scope (15MHz), Dual Trace, NICE!.....	\$175
Tek TM503, Power Module, 3 Slot.....	\$125
Tek TM504, Power Module, 4 Slot.....	\$150
Tek TM506, Power Module, 6 Slot.....	\$200
Tek TR503, Plug-in Tracking Generator, 100KHz-1.8GHz.....	\$575
Tek 2213, Scope (60MHz), Dual Trace.....	\$375
Tek 2215, Scope (60MHz), Dual Trace.....	\$450
Tek 2235, Scope (100MHz), Dual Trace.....	\$650
Tek 2236, Scope (100MHz) w/Counter/Timer/DMM.....	\$850
Tek 2248, Scope (100MHz) 4-Channel Cursor RO.....	SPECIAL \$1,200
Tek 2247A, Scope (100MHz) Dual Trace w/	
Counter/Timer/Volmeter.....	SPECIAL \$1,400
Tek 2336, Scope (100MHz) Dual Trace.....	SPECIAL \$525
Tek 2445, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,100
Tek 2445A, Scope (150MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 2465, Scope (300MHz), 4-Channel Cursor Readout.....	\$1,400
Tek 453, Scope (60MHz), Dual Trace.....	\$175
Tek 465, Scope (100MHz), Dual Trace.....	\$425
Tek 465B, Scope (100MHz), Dual Trace.....	\$475
Tek 466, Scope (100MHz storage), Dual Trace.....	\$575
Tek 475, Scope (200MHz), Dual Trace.....	\$475
Tek 475A, Scope (250MHz), Dual Trace.....	\$625
Tek 485, Scope (350MHz), Dual Trace.....	\$700
Tek 520A, NTSC Vectorscope.....	\$400
Tek 576, Curve Tracer.....	SPECIAL \$1,400
Tek 7104, Scope (1GHz), Dual Trace.....	\$1,200
Tek 7104, Scope (1GHz) w/7A29, 7A29, 7B10 & 7B15.....	\$2,200
Tek 7844, Scope (dual beam) w/7A24, 7A26, 7B80 & 7B87.....	\$750
Tek 7904, Scope w/7A24, 7A26, 7B80 & 7B85.....	\$750
Tek 7904A, Scope w/7A24, 7A26, 7B80 & 7B85.....	\$825
Tek 7904A, Scope (500MHz) Frame.....	\$425
Wavetek 145, Pulse/Function Generator, .0001-20MHz.....	\$300
Wavetek 157, Programmable Waveform Synthesizer.....	\$425
Wavetek 1855, CATV Sweep/Transmitter.....	\$750
Wavetek 288, Synthesized Function Generator, 20Hz-20MHz	
(unused).....	\$800
Wavetek 442, Dual HiLo Filter, 1Hz-10KHz.....	\$400

cedures are called for: Is it getting power and a control signal? Then look for loose or broken connections.

Erratic, non-smooth operation is due to either defective gears or a worn or dirty feedback pot. In either case, replacement is called for.

A completely dead servo can be traced to one of two things: the motor or the amplifier. The former can be tested by disconnecting one side of it and applying five volts; the results are obvious. If the motor runs, about the only thing left is a visual check of the amplifier.

Most of its circuitry is in a proprietary IC, though, in most cases, you will find external drive transistors. Other than checking them, there is little else to do. It is time for a trip back to its parent company.

THE BIG ONES!

Though not actually intended for or used in the radio control hobby, there are a couple of interesting servos available that operate in the same manner, except for input voltage. They can and are, in fact, sometimes operated with a hobby-type of R/C system, finding many applications in robotics,

UAVs (Unmanned Aerial Vehicles), etc.


They are the PS-050, and PS-105; see the photos for size information. The 050 is rated at 907 oz.in., at a speed of 0.29 for 60° with six volts input, increasing to 1271 oz.in., speed being 0.21 seconds with 8.4 volt power.

The 105 — the Godzilla of servos — is rated at 5278 oz.in. of torque at a speed of 0.9 seconds for 60°. It is available in both 12 and 24, normal and high speed, and even 180° versions. Except for the input voltages, both servos are controlled by the same control signal as their smaller siblings.

These Big Ones are available in the US only from **Condor R/C Specialties**, 1733-G Monrovia Ave., Costa Mesa, CA 92627; (714) 642-8020, (714) 642-8021 FAX. Check with them for current pricing, availability, and complete specs.

AVAILABILITY

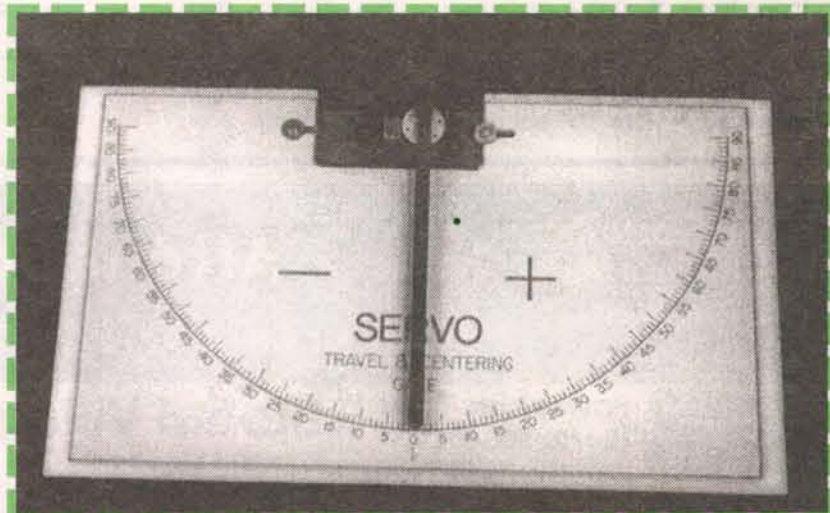Like so much of our country's electronics, most R/C equipment comes from somewhere in Asia, Japan, Korea, Singapore, Taiwan, etc. It is imported by literally dozens of companies, some of which sup-



The RCM Magazine (see text!) Servo Travel and Centering Gauge is useful when evaluating, adjusting, or matching servos. Available from them (P.O. Box 487, Sierra Madre, CA 91025), Plan No. 702, \$6.00. Shipping is \$4.00, folded in an envelope, \$7.00 rolled in a tube.




Though looking pretty much like all other servos, JR's "Super Servos" and Multiplex's MC series use a micro-processor to increase the control pulse rate, increasing power and speed.



• 60-DAY WARRANTY
• 10-DAY RIGHT OF RETURN
• SATISFACTION GUARANTEED



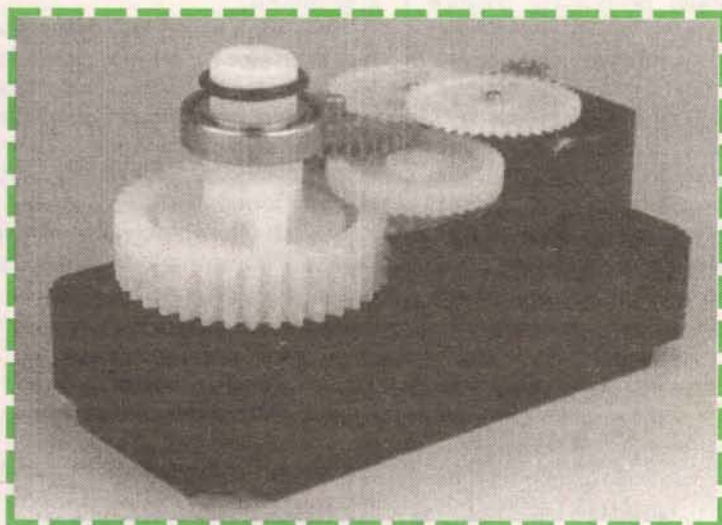There are difference one from another, but all servos contain a gear train, motor, and amplifier. The gear-driven feed-back pot mentioned in the text is hidden under the amp.



The gear train in even the standard R/C servo is extremely precise, molded in reinforced nylon in most cases but also available in hardened metal in some cases.

ply complete R/C systems, others only aftermarket add-ons such as servos. The major systems suppliers are:

Airtronics, Inc., 1185 Stanford Ct., Anaheim, CA 92805; (714) 978-1895, (714) 978-1540 FAX.

Futaba Corp. of America, 4 Studebaker, Irvine, CA 92618; (949) 455-9888, (949) 455-9899 FAX.

Hitec RCD, Inc., 107 Wheatlands Ave. Ste. C, Santee, CA 92071; (619) 258-4940, (619) 449-1002 FAX.

Horizon Hobby Distributors (JR Systems), 4105 Fieldstone Rd., Champaign, IL 61821; (217) 352-1958, (217) 352-2010 FAX.

The following offer proprietary equipment of their own, as well as retailing that of some of the others above:

Hobby Shack, 18480 Bandilier Circle, Fountain Valley, CA 92728-8610; (714) 963-9881, (714) 962-6452 FAX.

Tower Hobbies, 1608 Interstate Dr., Champaign, IL 61820; (800) 637-6050, (800)

637-7303 FAX.

Considerably more information is as near as your Yellow Pages — and the nearest hobby store. Obtain for yourself a copy of *Radio Control Modeler Magazine* in which you will find listings for all major and minor servo and related equipment suppliers.

TECHNICAL INFORMATION?

Bear in mind that this — like most consumer electronics equipment — is intended to be installed and used in a specific manner, and support information for the tinkerer is not always available. Unfortunately also, while you can talk to a salesperson all day long, you can not always reach someone with technical knowledge.

From personal experience, I know that Airtronics, listed above, is the exception. They will provide technical support and even schematics if required. I really do not know about the others, my comments are general in nature.

I am available for help that you may not be able to obtain otherwise at: 2626 Northwood, Santa Ana, CA 92794; (714) 540-4935 Phone & FAX.


Wanna go flying? NV

SAME DAY PROTOS

Modem Gerber files before 9 AM EST.
We ship the boards same day.
Multilayers NEXT DAY.

Service:

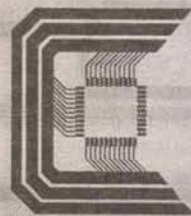- Instant Quotes
- Single / Double / Multi-Layers
- SMOBC and LPI
- Thru Hole or SMT
- Nickel and Gold Plating
- Routing / Scored Panels
- Blind and Buried Vias
- Electrical Testing
- Carbon Ink / Peelable Mask
- UL Approved



CHICAGO CIRCUITS CORPORATION

Manufacturer of Printed Circuit Boards

2685 UNITED LANE

ELK GROVE VILLAGE, IL 60007


E-MAIL: sales@chicagocircuits.com

TEL: (847) 238-1623 • FAX: (847) 238-9160

MODEM: (847) 238-1728

Write in 96 on Reader Service Card.

RF Data Modules

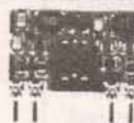

AM TRANSMITTER

- Small size: 17.78 x 11.43mm
- CMOS/TTL input
- No adjustable components
- Low Current. 4mA typical.
- 418MHz or 433.92MHz OOK
- Simple to integrate - simply add antenna, data and power
- Range up to 250ft.
- Wide supply range, 2-14Vdc
- SAW controlled - stability
- Also available in DIL package

AM-RT5 \$12.10



AM RECEIVER

- Compact size: 38.1 x 13.7mm
- On-board data recovery. CMOS
- Low current. 2.4mA typical
- 2kHz data rate. CMOS/TTL output
- 5Vdc operation
- On 418MHz or 433.92MHz (4xx)
- No adjustable components
- Patented Laser Trimmed component
- High stability
- Sensitivity: -105dBm
- Available also in 0.8mA version

AM-HRR3-4xx \$10.95



FM TRANSCIVER

- Only 23 x 33 x 11mm
- Up to 40k bps data rate
- 19200 baud with ASCII
- Up to 500ft. range
- 5v operation
- 0.25mW into 50
- 418 or 433MHz FM
- Fast 1ms enable
- Direct interface to 5V CMOS
- Auto TX/RX changeover

BIM-4xx-F \$87.36

RS232 TRANSCIVER MODULES



- 4,800 to 38,400 bps half duplex
- 3-wire RS232 interface
- μ Controller with user EEPROM
- RS232 interface protected to $\pm 15kV$
- Data packetizing performed by user
- Auto TX/RX changeover
- 418 MHz and 433MHz versions
- Range up to 500ft. (0.25mW ver.)
- 0.25mW & 10mW versions
- Reset switch and status LED's
- 7.5-15V dc via DB9 connector, 20mA

BIM-4xx-RS232 \$139.30



Transceiver.....
Transmitter.....
Receiver.....

- Up to 19,200 bps half duplex
- 3 wire RS232 interface
- Range up to 500ft
- Transparent data packetizing
- Supports 8 or 9 bit protocols
- Self test function
- Reset Switch & Status LED's
- 1/4 wave wire antenna on board
- Available in a Simplex Tx/Rx pair (RTcomTX & RTcomRx)
- 7.5V-15Vdc operation
- RTcom-4xx..... \$247.90
- RTcomTx-4xx..... \$ 87.15
- RTcomRx-4xx..... \$105.52



ABACOM
TECHNOLOGIES



Tel: (416) 236-3858
Fax: (416) 236-8866
www.abacom-tech.com
abacomtech@compuserve.com

by Joseph J. Carr

Open Channel

AC Power Line and Electrical Device EMI

Power lines are regulated as incidental radiators under Part-15 of the Federal Communications Commission (FCC) Rules and Regulations. This means that they will incidentally generate EMI, rather than produce it as a normal part of their operation.

Power lines are supposed to be clean and trim ... right? Wrong, not by a long shot! Power lines are as "dirty" as you please ... perhaps dirtier.

A number of different conducted sources interfere with equipment through the power lines. There are brown outs (when voltage sags to 95 volts in the USA and Canada), and surges (when the voltage increases to 135 volts). Lightning causes its share of havoc, as do ordinary switching transients.

In a medical center, we once flunked the entire freshman class of medical students on their standardized physiology exam. Also failed were all of the basic sciences (i.e., PhD) students and allied health students (e.g., nurse anesthesia, nurse practitioner, physicians assistant). Those people are about "up-to-here" with stress their first year in medical school so the professors hoped that the results would not get out until we solved the problem. It turned out to be power line noise.

In those days, computing was mainframe computing. The examination was taken on "mark sense" optical scanner paper. You know the stuff ... "use a No. 2 pencil and completely blacken the desired box." In our case, the optical scanner was connected to a keypunch machine. To younger readers: A keypunch was a noisy, clunky machine that looked like a typewriter on steroids that punched the

holes in old-fashioned computer cards. The cards were then taken to the computer center for processing overnight. When the computer print-out paper was returned, the grades were recorded (manually!) and the paper posted for all to see. The problem was solved when one of the engineers I worked with noticed that one column on the computer card had all digits punched out. There is no EBCDIC code that has all digits punched out in a single column! The problem was traced to high voltage power

line transients arising from load shifting switching gear in the basement. It seems that the local power company gave the university a two-percent break on the electric bill if they installed equipment that would periodically balance the load between the three phases (which makes for more efficient operation). Unfortunately, the TRIAC switches tossed huge (>2KV) transients that averaged 50 to 100 microseconds.

The solution to the problem (we couldn't rewire the building or turn off the load switchers) was to place a Topaz isolation transformer between the power line and the optical scanner and

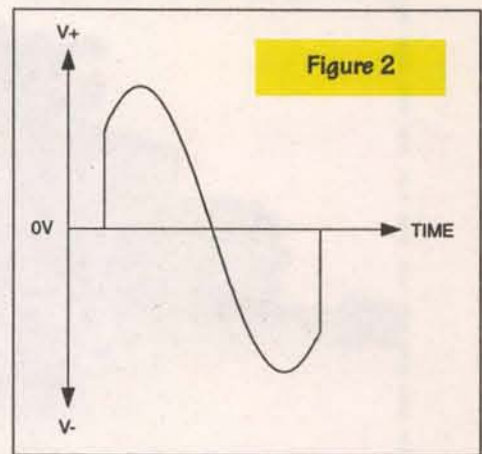


Figure 2

keypunch machine. These transformers are specially designed to snuff power line noise (today, we might use a computer surge suppressor for many such applications).

We then found that the noise was the basis for a lot of problems. For example, the electron microscope guy had been attempting to find a "vibration problem" in his equipment (it didn't help that the subway ran right beneath our building foundation ... so he was tuned in on "vibration problems"). Adding an isolation transformer to his equipment cured the little glitches that were


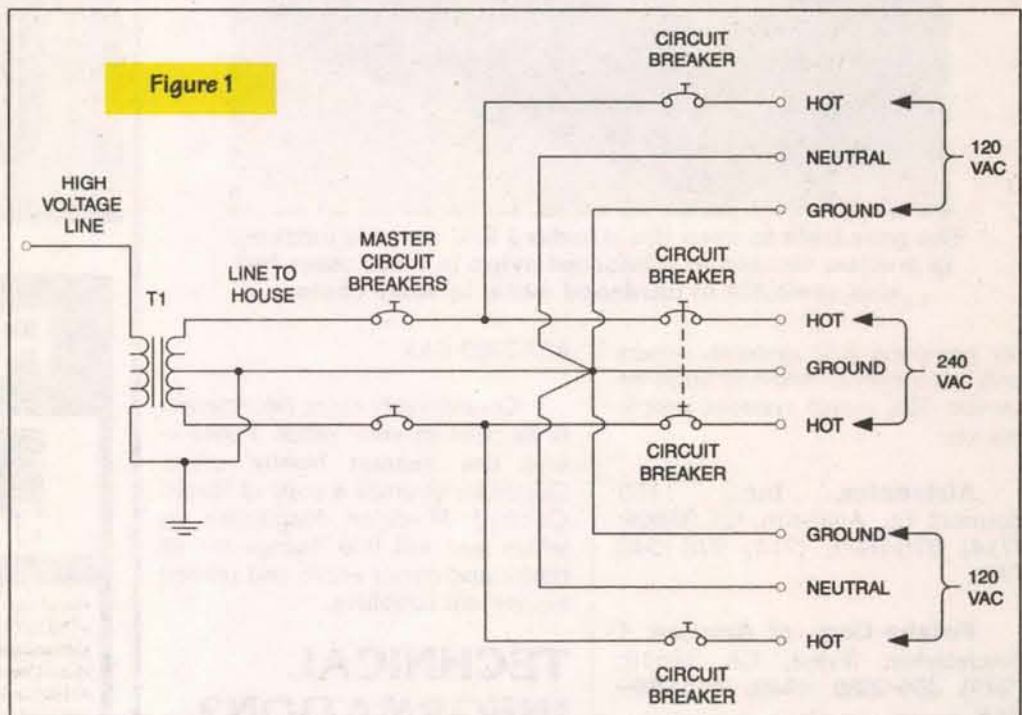


Figure 1

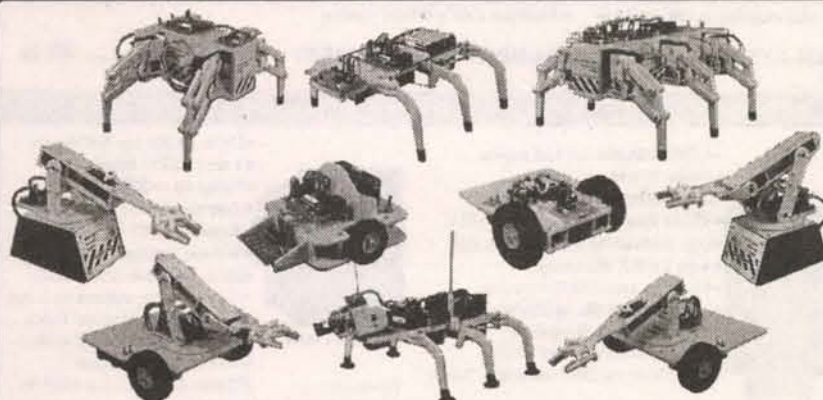Build Your Own Intelligent Robot, We Make It Easy!



At Lynxmotion we cater to the beginner. All of our kits are easy to assemble, requiring only common hand tools in the construction process. The detailed assembly manuals include 2D and 3D exploded view diagrams. The kits can be controlled or programmed in an easy to follow BASIC programming language. The technology is here, the costs are affordable, the support is available, join in and become a robot builder!

Lynxmotion, Inc.
104 Partridge Road
Pekin, IL 61554-1403
www.lynxmotion.com

Lynxmotion

Tel: 309-382-1816
Fax: 309-382-1254
sales@lynxmotion.com
tech@lynxmotion.com

Visit our website or ask for our free catalog!

EPROM+

A device programming system for design, repair and field service

- ◆ EXCEPTIONAL POWER FOR THE PRO
- ◆ EASY-TO-USE FOR THE NOVICE

Here's what you get: A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters*. Comprehensive, easy-to-use software which is specifically designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

Broad device support: Including FIRST GENERATION EPROMS (2708, TMS2716*, 25XX etc.) SECOND GENERATION EPROMS (2716-27C080)(8 MEG), 40 and 42 PIN EPROMS* (27C1024-27C160)(16 MEG) EEPROMS (2816-28C010) PLUS ER5901, FLASH EPROMS (28F29C, 29EE, 29F)(32 MEG), NVRAMS (12,20,X2210/12) 8 PIN SERIAL EPROMS* (24, 25, 85, 93, 95, 80011A) PLUS ER1400/M58657* BIPOLAR PROMS* (74S/82S), SERIAL FPGA CONFIGURATORS (17CXXX) MICROS* (874X, 875X, 87C5X, 87C75X, 89C) ATMEL MICROS* (89S, 90S)(AVR) PIC MICROS* 8, 18, 28, 40 PIN (12CXXX, 16C5X, 6X, 7X, 8X PLUS FLASH & 17C) MOTOROLA MICROS* (68705P3/U3/R3, 68HC705C8/C9/J2/P9, 68HC711E9/D3)

□ Includes step-by-step tutorial plus explanation of EPROM fundamentals
□ 1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE
*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF)

\$289

\$5.00 SHIPPING = \$5.00 C.O.D.
VISA • MASTERCARD • AMEX

ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OHIO 45150

(513) 831-9708 FAX (513) 831-7562

website - www.arlabs.com

email - arlabs@worldnet.att.net

MADE IN THE U.S.A.

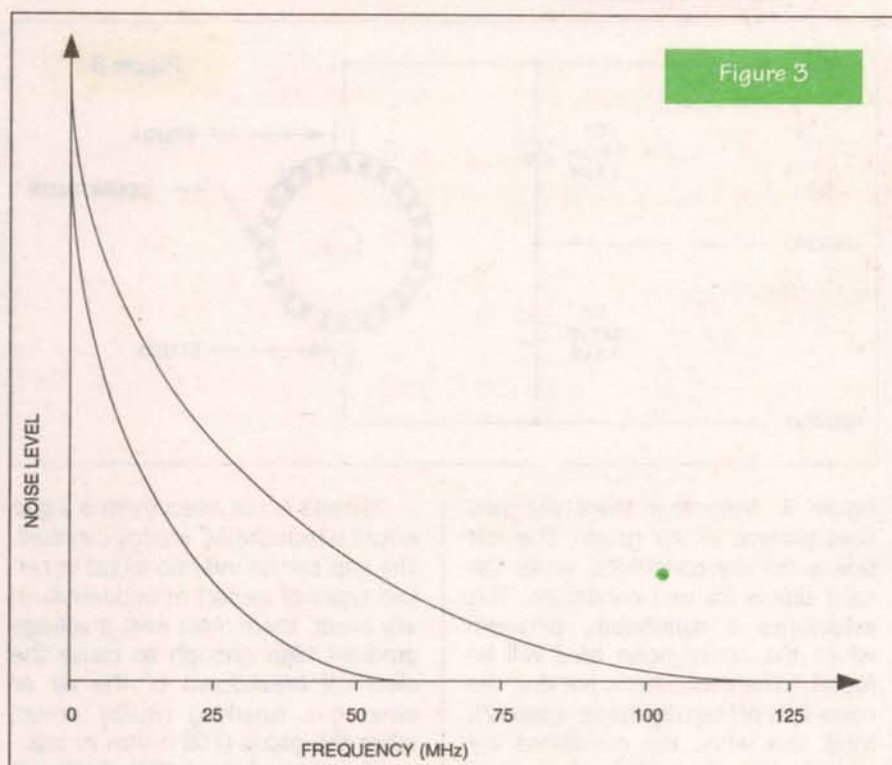


Figure 3

showing up in the pictures he took.

Still another guy was almost comical. He was a hematology researcher, i.e., he knew more about human blood than anyone else. He had a high priced microscope that had a special light source. It was a glass tube that had been evacuated, and then refilled with a special combination of rare gases that each gave off a different color light when ionized. There were about a half dozen electrodes on the tube that each had to see a different voltage. The poor guy had to spend 45 minutes (anytime he wanted to use the microscope) balancing the voltages on these interactive electrodes ... it was a touchy thing, I suspect. Once in awhile, usually (as Murphy's law dictates) when he could ill afford the time, a power line transient would commutate the tube, extinguishing

the light. After cursing and yelling at his Graduate Research Assistant (GRA), he would spend another half hour to 45 minutes re-doing the job. When we gave him an isolation transformer, it solved both his technical problem and the GRA's blood pressure problem.

The standard for digital equipment today is to withstand the ANSI standard pulse of 20 μ S and 2-kV. Beyond that point, we have to provide a little magic of our own.

120/240 Volt Electrical System

The standard 120/240 volt electrical system is shown in Figure 1 (this is for the USA and Canada, other countries will differ). Transformer T1 is the "pole-pig" transformer outside of your house.

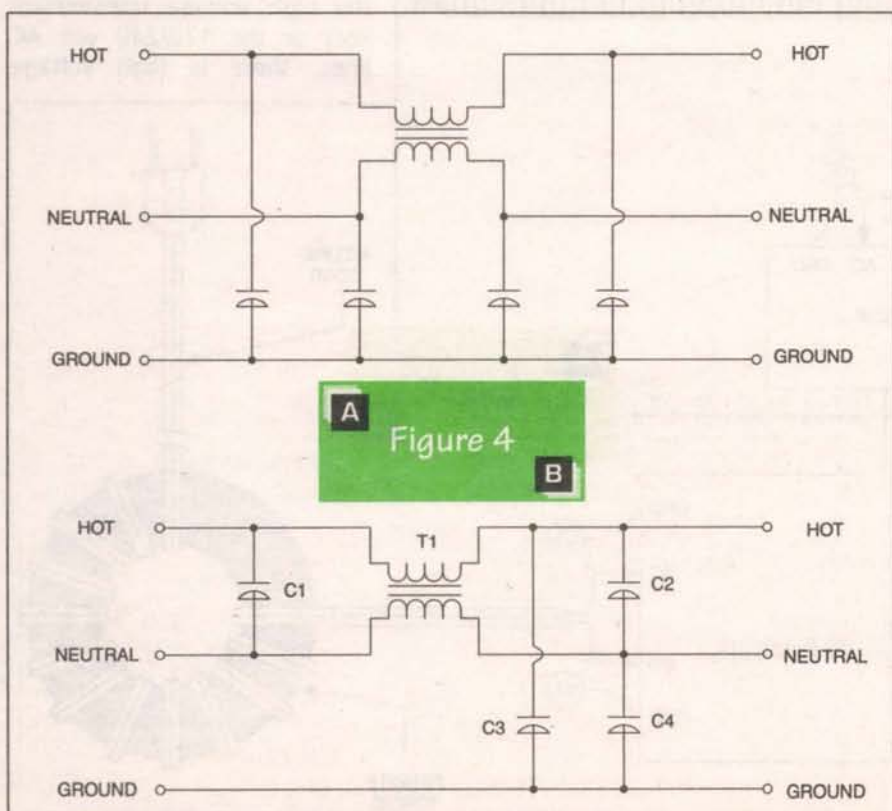


Figure 4

The purpose of that transformer is that it reduces the high voltage that the power is transmitted under to 240-volts AC center-tapped. Three wires are brought into the house where they encounter a pair of Master Circuit Breakers (which may be breakers or fuses). From there, the circuits branch out.

The 240 VAC circuit is used to run heavy appliances (dryers, stoves, air conditioners, etc). It is operated across the two hot lines and has its own set of circuit breakers. A ground wire is provided to keep the circuit safe.

One 120-VAC circuit is provided from each side of the transformer making two independent circuits. Each circuit has its own circuit breaker.

The independent circuits are used separately, but there is some interaction through the neutral line. Normally, one expects to see the lights on a line decrease in brilliance when a large load (e.g., compressor) comes on. But what happens when the neutral is open? In that case, the lights will become more brilliant when the heavy load comes on. This occurs because the 120-VAC lines are not loaded the same, and as a result of the neutral being open. The high drain of the compressor starting up is in series with the low drain of the light bulb, making for a very unbalanced situation.

Noise

Noise can occur on the electrical system whenever there is sparking or any type of truncated waveform in use. Sparking can exist because of loose tie wires or other hardware in the high voltage end of the circuit. We also see sparking on the 120/240-VAC side of the transformer due to electrical motor commutators, switches, and so forth. Sparking also occurs when there is a fault on the system.

The use of truncated waveforms occurs in TRIAC or SCR circuits when not all of AC waveform is used. Figure 2 shows a truncated AC waveform. The harmonics generated by this scheme are tremendous. Recall that the sinewave is pure, all other waveforms have significant harmonics. Therefore, when not all of an AC waveform is used, harmonics are generated. Light dimmers are examples of such devices.

Regulatory/Legal Issues

Power lines are regulated as incidental radiators under Part-15 of the Federal Communications Commission (FCC) Rules and Regulations. This means that they will incidentally generate EMI, rather than produce it as a normal part of their operation. The Rules and Regulations regarding incidental radiators say the device shall:

JFETS

ULTRA LOW NOISE
LS843 - 3nV/Hz typ

TIGHT MATCHING
LS843 - 1 mV max

- ◆ N & P Channel
- ◆ Duals & Singles
- ◆ Custom Screening
- ◆ Die, SMT, Thru-Hole
- ◆ No Order Minimum
- ◆ COD's Accepted

Second Source for Domestic & Foreign JFETs & Bipolars

Full Service U.S. Manufacturer of Specialty Linear Products

LINEAR SYSTEMS

4042 Clipper Court
Fremont, CA 94538
510-490-9160/510-353-0261(Fax)
E-mail: 3623671@MCI.MAIL.COM

Write in 75 on Reader Service Card.

PICmicros & BASIC

PicBasic Compiler - \$99.95

PicBasic Pro Compiler - \$249.95

Now it's even easier to program the fast and powerful Microchip PICmicros. The PicBasic and PicBasic Pro Compilers convert your English-like BASIC programs to files that can be put directly into a PICmicro. True compilers for faster, longer programs. BASIC Stamp™ I/II* libraries. For mid-range PIC12C67x, 14Cxxx, 16C55x, 6xx, 7xx, 8x, 87x, 9xx and high-end 17Cxxx (PicBasic Pro only).

*BASIC Stamp is a registered trademark of Parallax Inc.

New! PIC-X1 Experimenter/ Lab Board

Assembled - \$199.95
Kit with parts - \$139.95
Bare PCB only - \$49.95



EPIC Plus PIC Programmer - \$59.95



Programs PIC12C5xx, 67x, 14Cxxx, 16C505, 55x, 6xx, 7xx, 8x, 87x and 9xx.

Optional ZIF adapters for DIP, SOIC, MQFP, PLCC.

Runs off two 9-volt batts or optional AC adapter. Includes programming software and assembler.

PICProto Prototyping Boards

Get it wired quicker! High-quality blank prototyping boards for PICmicros. Holds PICmicro, 5V reg, caps, oscillator, DB9-25, large proto area. \$8.95 - \$19.95



microEngineering Labs, Inc.

Box 7532 Colorado Springs CO 80933
(719) 520-5323 (719) 520-1867 fax
<http://www.melabs.com>

Write in 74 on Reader Service Card.

D.T.M.F. DECODER

For interconnect and remote control applications

The Model NC401 is a micro-miniature DTMF decoder, designed for selective control of local or remote applications.

Model NC401

\$59.95

Measuring .80"Wx1.37"Lx.23"H, the NC401 combines three distinct, multi-addressing decoders offering multiple user-configurable functions. All programmed features are stored in non-volatile E2PROM memory and are easily programmed by means of a conventional DTMF encoder or the Model NC500 Universal/P.C. programmer. This highly engineered decoder is ideal for portable radio applications having limited space for accessories. The NC401 comes complete with micro-miniature 14 pin header and 12" color coded cable assembly.

Nor-fax Doc. #5545

VOICE SECURITY ENCRYPTION

The Model NC802 is a miniature inversion scrambler designed to provide intermediate level security for two-way radio voice communication systems and is a perfect, cost-effective solution to entry-level voice scrambling as a defense against unauthorized or casual listeners. The NC802 provides eight user selectable carrier codes commonly used by other manufacturers and interfaces easily to most radios with near transparency to the user.

Model NC802

\$59.95

Nor-fax Doc. #5759

For Detailed Specifications or Product Catalog call our 24-Hour NorFax retrieval system at 530-477-8403 or on our Web Site at www.norcommcorp.com



800-874-8663

15385 Carrie Drive
Grass Valley, CA 95949 USA

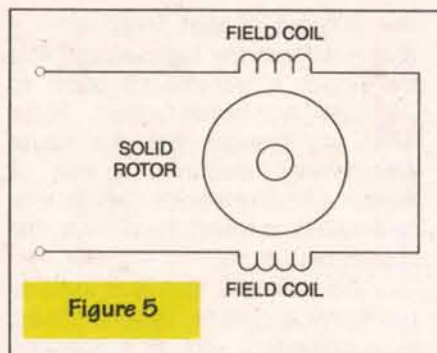


Figure 5

1. use good engineering practices and
2. shall not cause harmful interference

The operator of an incidental device shall cease operating upon notification by the FCC, and shall promptly take steps to ensure that operation of the device does not cause interference. That sounds like strong language, but there is a hidden argument. The argument hinges on the definition of "harmful interference." What is harmful in one case, might not be harmful in another.

As a result, there are no absolute limits that the power company must meet. And electrical power is necessary in modern society, so there is a built-in bias against turning it off. The FCC uses cost, the number of people involved, severity of interference, and a host of other factors to determine whether or not to get involved. In general, it is wise to try troubleshooting the problem yourself before involving the FCC.

Corona and Spark

The interference caused by power lines can be due to corona or sparking. Corona is "... a partial breakdown of the air that surrounds an electrical element such as a conductor, hardware, or insulator." A corona discharge is often visible, and will be a pale blue light around the conductor. A voltage gradient must exist between two different points such as the conductor and ground. As a result, you will see corona discharge around 7.5 kV lines, but they are more common with 230 kV lines.

The frequency components of corona discharge EMI is shown in

Open Channel

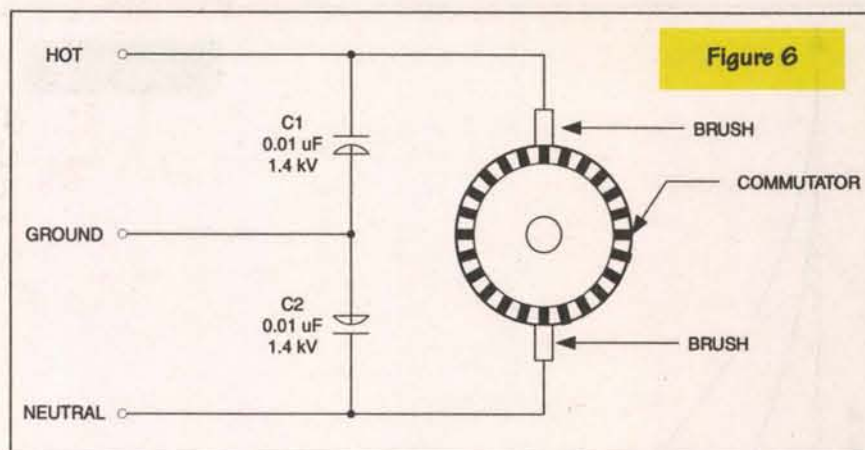


Figure 6

Figure 3. Note that there are two lines present in the graph. The left side is for dry conditions, while the right side is for wet conditions. This establishes a continuum, between which the actual noise level will be found. When conditions are dry, the noise falls off rapidly above about 25 MHz, but when the conditions are wet, the noise level is significant well into the VHF spectrum. It can affect up to the lower VHF TV channels, the FM BCB, and even some of the aviation band. The corona is generally restricted to 1,000 yards from the power line.

Sparks occur when there is a gap across which the AC energy can leap. The gap can be intentional (as in certain types of motor) or accidental. In any event, there must exist a voltage gradient high enough to cause the electrical breakdown of the air or other gas. Sparking usually occurs when the gap is 0.06 inches or less.

Because of the fact that we use 60 Hz in the USA and Canada, there will be 120 voltage peaks per second. This means that there will be 120 instances per second that are capable of causing noise peaks. This causes a characteristic "buzz" that can be heard at broadband frequencies to 1 or 1.5 GHz. Unlike corona noise, spark noise tends to die off when conditions are wet.

Both spark and corona noise is normally louder close to the power lines, which helps in locating it. Unfortunately, the noise will vary as one tracks along the line, peaking at the point where the noise occurs. This can cause you to misidentify points where the noise occurs.

Safety

Whether you are working with the high voltage transmission lines or the 120/240 volt AC lines, there is high voltage


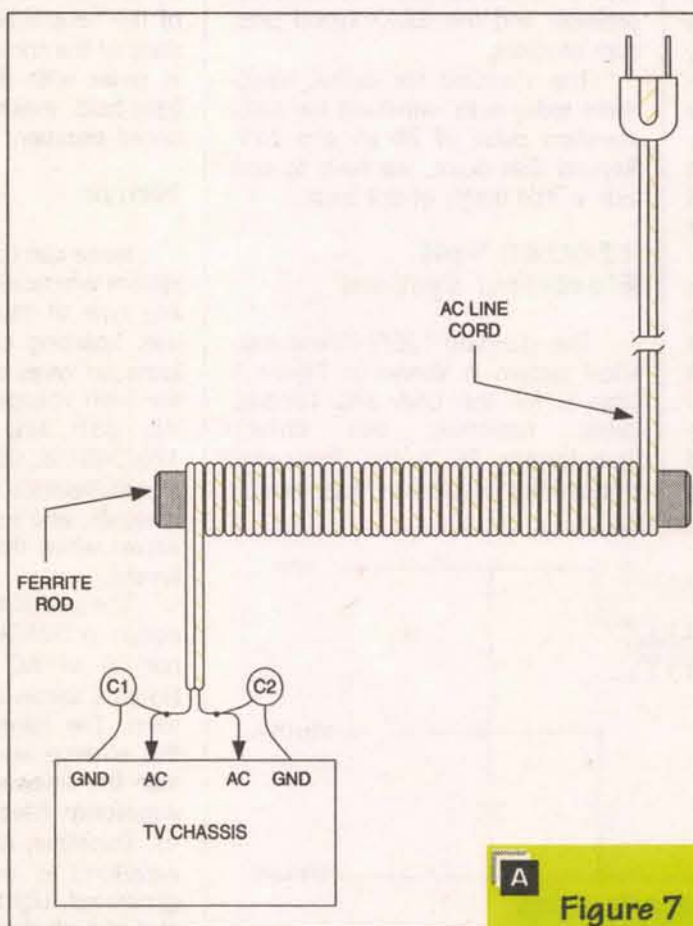


Figure 7

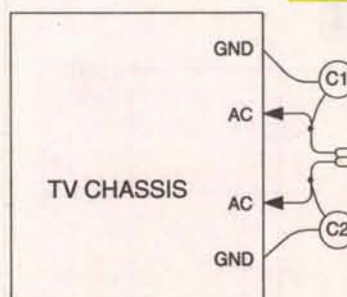

FERRITE TOROID

present on the lines. It is essential that you operate in a manner that is consistent with safety when working on those lines. *These lines can kill you ... so don't take any chances.*

Locating EMI Sources

Before attempting to find an EMI source outside the home or business, it is necessary to eliminate sources inside the building. Every device that has a motor in it is capable of generating EMI, so be careful.

Filter Solution

The filter solution works best when the source is at least partially shielded, but will work at least some most of the time. Figures 4A and 4B shows two circuits that can be used to filter AC noise carried on the AC power line. Interestingly enough, these filters can be used on either generators or victims of EMI.

Notice that each of these filters uses a special type of inductor. The inductor is designed as a common mode coil having a single core for the two coils. This is not strictly necessary, but is a highly recommended form of construction.

The capacitors selected are 0.01 μ F to 0.1 μ F of a type intended for use on the AC line. They will typically have a WVDC rating of 1,400 volts, and will be rated for use in AC circuits. Lesser capacitors (such as 600 WVDC types) will not be able to withstand the peak and transient conditions.

When installing such filters, they should be as close to the offending equipment as possible. This eliminates the wiring to/from the sparking contacts as radiated sources of EMI. Alternatively, when protecting equipment from EMI due to power line conduction, place the filter as close as possible to the point where the power line enters the cabinet of the equipment. There are EMI AC filters available that are built right into the AC plug assembly.

Electric Motors

There are two types of AC motors available: induction (Figure 5) and brush-commutator (Figure 6). Generally speaking, it is the brush-commutator motors that cause the most problems due to the sparking that occurs. Whether vacuum cleaners, electric driers, sewing machines, mixers, or power tools, the brush-commutator motor will cause problems. The fix is to add capacitors such as seen in Figure 6 and filtering. Attempt the capacitors first, and then follow up with filters if that doesn't work.

Common-Mode Filtering

Regardless of whether or not

there is filtering or capacitors in the circuit, there should be a common mode filter in the circuit. In fact, rolling up the power cord is the first thing that ought to be tried because it is non-intrusive. Figure 7 shows two versions of the common mode choke installed on a TV set. It could just as easily be installed on any device that generates or is victimized by power line EMI. In Figure 7A is a version using a linear rod, while Figure 7B is based on a toroidal core.

Transients

Transients are (usually) high amplitude, short duration pulses of energy. They are transmitted along an AC line for many miles, resulting in interruption of equipment (especially digital) at your end. They can also be locally generated, as in the scenario at the beginning of this article. The solution adopted back in 1975 was to use a special transformer. Today, however, I would start by using a MOV (metal oxide varistor) device across the AC power line. The MOV device clips the voltage at something over 185 volts, but a lot less than 2,000 volts.

Trip to Ireland, Scotland, and England

This summer, I decided to let the wind out of my head a bit. My wife and I took a vacation to Ireland, Scotland (where we Carr's come from), and England. We flew through London on British Airways (a first class outfit), on to Shannon Airport in Ireland. We then rented a car and drove north about 80 miles to Galway City. It was a real treat watching the sunset on Galway Bay at 10:30 at night (it's that far north). We then drove across the country to County Louth, where we visited a childhood friend of mine for a day.

After visiting with Doug and Anne, we flew on to Edinburgh, Scotland. Don't do Edinburgh in only three days like we did! We also saw Rosslyn Chapel and Ferniehirst (the castle of the Kerr's ... root of the family Carr). After Scotland, we went to England, and Bonnie flew home while I attended the annual symposium of the International Council on Systems Engineering (INCOSE) at Brighton, England. For a few days after the conference, I wandered around England and saw Salisbury Cathedral, Stonehenge, and Glastonbury Abbey. All in all it was a really great trip! **NV**

Connections ...

I can be reached by snail mail at P.O. Box 1099, Falls Church, VA 22041, or via E-Mail at CARRJJ@AOL.COM.

SURPLUS TEST EQUIPMENT

HEWLETT PACKARD

11666A, Reference Bridge, 0.4-18GHz	\$800
11667A, Power Splitter, DC-18GHz	\$600
11975A, Amplifier, 2-8GHz	\$2000
1650B, 80 Channel Logic Analyzer	\$2000
16500A, Logic Analyzer Mainframe	\$750
214B, 10MHz Pulse Generator	\$1000
3312A, Function Generator, 1Hz-13MHz	\$1000
3325A, Synthesizer/Function Generator	\$1000
3325A/01/02, Synthesizer/Function Generator	\$1500
3335A, Frequency Synthesizer, 200Hz-81MHz w/Opt. 01	\$4500
3456A, Digital Multimeter, 6.5 Digits	\$800
3468A, 5.5 Digit Multimeter	\$300
3468B, 3.5 to 5.5 Digit Multimeter	\$375
3478A, Digital Multimeter	\$700
3488A, Switch Control	\$600
3551A, Transmission Test Set	\$800
3575A, Phase Gain Meter 1Hz-13MHz	\$1000
3581C, Selective Voltmeter	\$800
3582A, Spectrum Analyzer, 0.02Hz-25.5KHz	\$1600
3585A, Spectrum Analyzer, 20Hz-40.1MHz	\$4750
3852A, Data Acquisition/Control Unit	\$1000
4342A, Q-Meter	\$1800
435B, Power Meter	\$400
436A, Power Meter w/Opt. 022	\$1000
438A, Power Meter	\$2750
4935A, Transmission Impairment Test Set w/Opt. 003	\$1100
5316B, Universal Counter	\$800
5328B, Universal Counter	\$1000
5340A, Frequency Counter w/Opt. 01/02/011	\$1000
5342A, Microwave Frequency Counter, 10Hz-18GHz	\$900
54100A, Digitizing Oscilloscope	\$1700
54100D, 1GHz Digital Oscilloscope	\$2700
54110D, 1GHz Color Digitizing Oscilloscope	\$2500
54201D, Digitizing Oscilloscope	\$2650
6011A, Autoranging Power Supply, 20V/120A, 1000 Watt	\$1200
6012A, DC Power Supply, 0-60V/0-50A, 1000 Watt	\$1200
6034A, DC Power Supply, 0-60V/0-10A, 200 Watt	\$1000
6274B, DC Power Supply, 0-60V, 0-15A	\$1250
6475C, DC Power Supply, 0-110V, 0-100A	\$3500
6632A, DC Power Supply, 0-20V, 0-5A, 100 Watt	\$1000
7035B, X-Y Recorder	\$250
778D, Dual Directional Coupler	\$400
8013B, Pulse Generator	\$750
8082A, Dual Pulse Generator, 250MHz	\$1200
8112A, 50MHz Pulse Generator	\$3300
8116A, 50MHz Programmable Pulse/Function Generator	\$3350
8165A/002, Programmable Signal Source w/AM	\$2200
8347A, RF Amplifier, 100KHz-3GHz	\$2500
8349B, Microwave Amplifier, 2-20GHz	\$4000
8350A, Sweep Oscillator Mainframe	\$1000
8350B, Sweep Oscillator Mainframe	\$1250
83522A, Sweeper Plug-In, 01-2.4GHz, w/Opt. 02	\$3500
83545A, Oscillator Plug-In, 5.9-12.4GHz	\$1750
8449A, Pre-amplifier, 2-22GHz	\$3000
8495H, Programmable Attenuator (unused)	\$600
8501A, Storage Normalizer	\$1000
85021B, Directional Bridge	\$1200
8510B, Network Analyzer w/Opt. 010	\$13,000
8511A, Harmonic Frequency Converter, 45MHz-26.5GHz	\$5500
8554B, RF Spectrum Analyzer Plug-In, 500KHz-1250MHz	\$800
8562A, Spectrum Analyzer, 1KHz-22GHz	\$15,000
8569A, Spectrum Analyzer, 01-22GHz	\$5000
86222B, Sweep Oscillator Plug-In, 01-2.4GHz w/Opt. 04, Rear Output and 8620C Mainframe	\$1250
86290A, RF Plug-In, 2.0-18GHz	\$1150
86290B, RF Plug-In, 2.0-18.6GHz	\$1250
86290C, RF Plug-In, 2.0-18.6GHz	\$1550
8640A, Signal Generator, 0.5-512MHz	\$700
8640B, Signal Generator, Opt. 002, 5-1024MHz	\$2100
8640B, Signal Generator, Opt. 1, 2	\$2200
8654A, Signal Generator, 10-520MHz	\$450
8656A, Signal Generator, 100KHz-990MHz	\$1700
8656B, Signal Generator, 0.1-990MHz w/Opt. 02	\$2250
8660C, Synth. Signal Generator w/Opt. 1 & 100	\$1000
86603A, RF Plug-In, 1-2600MHz	\$800
86603A, RF Plug-In, 1-2600MHz w/Opt. 02	\$950
8671B, Synthesized CW Generator	\$5500
8672A, Synth. Signal Gen., 2.0-18.0GHz	\$4000
8672A, Synth. Signal Gen., 2GHz-18GHz, w/Opt. 08	\$5000
8748A, S-Parameter Test Set w/Opt. 026	\$1350
8753A, Network Analyzer, 300KHz-3GHz	\$5500
8753A, Network Analyzer, 300KHz-3GHz w/Opt. 010	\$6500
8756A, Scalar Network Analyzer	\$1500
8757A, Scalar Network Analyzer, 10MHz-60GHz	\$4000
8970A, Noise Figure Meter	\$4500

TEKTRONIX

11A32, Two Channel Amplifier Plug-In, DC-400MHz	\$1250
---	--------

11A34, Four Channel Amplifier Plug-In, DC-300MHz	\$1500
11A52, 600MHz Two Channel Vertical Amplifier	\$700
11A71, Amplifier, DC-1GHz	\$450
11A72, Two Channel Amplifier Plug-In, DC-1GHz	\$850
1503, TDR Cable Tester w/Opt. 04 Recorder	\$1550
2215, 60MHz Oscilloscope	\$500
2236, 100MHz Oscilloscope w/Counter/Timer/DMM	\$1000
2246, 100MHz Oscilloscope	\$1600
2247A, 100MHz Oscilloscope w/Counter/Timer/Voltmeter	\$2500
2337, 100MHz Oscilloscope w/DMM	\$1650
2430A, 150MHz Digital Oscilloscope	\$2850
2430R, 150MHz Digital Storage Oscilloscope	\$1850
2432A, 300MHz Digital Storage Oscilloscope	\$3000
2445, Four Channel 150MHz Oscilloscope	\$1500
2465, Four Channel 300MHz Oscilloscope	\$2500
2465A DV, Four Channel 350MHz Oscilloscope	\$3850
2465CTS, Four Channel 300MHz Oscilloscope w/CCT/WR	\$2500
2467, Four Channel 350MHz Oscilloscope	\$3000
2467B, Four Channel 400MHz Oscilloscope	\$6000
2630, Fourier Analyzer	\$2500
466, 100MHz Storage Oscilloscope w/DMM4	\$800
475, 200MHz Oscilloscope	\$850
475A, 250MHz Oscilloscope	\$800
492P, Programmable Spectrum Analyzer	

VISIT OUR WEBPAGE AT
WWW.RSSURPLUS.COM

50KHz-21GHz w/Opt. 1/2/3	\$8000
577/D2, Curve Tracer, Non-storage w/177 Fixture	\$1750
7D20, Programmable Digitizer	\$400
7L5/L3, Spectrum Analyzer, 20Hz-5MHz, w/Opt. 025 Tracking Generator	\$1850
7L12, Spectrum Analyzer, 100KHz-1.8GHz	\$1500
7L18, Spectrum Analyzer Plug-In, 1.5-18GHz Capable of 60GHz with Mixers	\$2500
7512, TDR/Sampler	\$450
TM5003, Three Slot Power Mainframe	\$450
TM5006, Six Slot Power Mainframe	\$550

MISCELLANEOUS

Acme Elect. PS2L1000, Electronic Load	\$850
Datron 1061A, 6.5 Digit Autocal Multimeter, DC Only	\$700
Datron 1062, 6.5 Digit Autocal Multimeter, DC/AC/Ohms	\$900
EIP 545A, Microwave Frequency Counter	\$800
EIP 548A, Frequency Counter, 10Hz-26.5GHz	\$2000
EIP 548B, Frequency Counter, 10Hz-26.5GHz	\$3250
EIP 578, Source Locking Frequency Counter	\$2500
Electro-Metric NTR-51C, Receiver	\$1250
Fluke 5100B, Voltage Calibrator w/Opt. 03 & 05	\$2500
Fluke 5200A, AC Voltage Calibrator w/5205A Amp	\$1850
Fluke 7261A, Universal Counter/Timer, 0Hz-125MHz	\$350
Fluke 8010A, Digital Multimeter	\$175
Fluke 8012A, Digital Multimeter	\$175
Fluke 8050A, Digital Multimeter	\$250
Fluke 8502A, Digital Multimeter, DC Only	\$225
Fluke 8520A, Digital Multimeter	\$350
Fluke 8600A, Digital Multimeter	\$65
Fluke 8810A, Digital Multimeter	\$250
Fluke 8840A, Digital Voltmeter w/Opt. 059	\$600
Keithley 195A, Digital Multimeter	\$700
LeCroy 7200, Precision 400MHz Digital Oscilloscope w/ (2) 7242B Plug-Ins	\$10,000
LeCroy 9450, 350MHz High Performance Digital Oscilloscope	\$3250
Marconi 2019A, Signal Gen., 80KHz-1040MHz	\$2200
Polarad 1105E-FT, Signal Generator, 0.8-2.4GHz	\$400
PTS 500, Frequency Synthesizer, 1-500MHz	\$450
Syston Donner 1730B, Frequency Synthesizer, 01-26.5GHz	\$6000
Trans. Devices DLR400 15 3500A, Dynamic Load	\$1500
Trans. Devices DLP 50-60-1000A, Electronic Load	\$800
Trans. Devices DLVP 130-110-1000 Electronic Load	\$950
Vaihallia 2703, AC Voltage Standard	\$2350
Vaihallia 4150ATC, Digital Ohmmeter	\$750
Wavetek 171, 2MHz Synth. Function Generator	\$450
Wavetek 178, Automatic Synthesizer	\$1700
Wavetek 852, Dual Hi/Lo Filter	\$1000
Wavetek 2001A, Sweep Generator, 1-1400MHz	\$450
Wavetek 2500A, Signal Generator, 2-11MHz	\$2250
Wavetek 3000-200, Signal Generator	\$900
Wavetek 8003, Precision Scalar Analyzer, 10MHz-40GHz	\$2000
Wavetek 8501, Peak Power Meter	\$2000
Wiltron 560-7550, RF Detector, 10MHz-18.5GHz	\$300
Wiltron 6747B-20, Frequency Synthesizer, 10MHz-20GHz, w/Opt. 01 & 02	\$13,500



R & S Surplus

1050 E. CYPRESS STREET, COVINA, CA 91724

(626) 967-0846 • FAX (626) 967-1999



www.mouser.com

Subscribe,
download, or view
catalog online!



800-992-9943

817-483-6828

Fax: 817-483-6899

catalog@mouser.com

958 N. Main St., Mansfield, TX 76063

MOUSER
ELECTRONICS

Write in 151 on Reader Service Card.



The RF Connection
213 North Frederick Ave.
Suite 11NV
Gaithersburg, MD USA
20877

http://www.therfc.com/

Complete Selection of MIL-Spec Coax, RF
Connectors and Relays

UG-21B/U N Male for RG-213/214.....\$5.00
UG-21D/U N Male for RG-213/214.....\$3.25

N Connectors for 9913/Flexi4XL/9096

UG-21B/9913.....\$6.00 Pins Only.....\$1.50
UG-21D/9913.....\$4.00 Extra Gasket......75

Amphenol 83-1SP-1050 PL-259.....\$0.90
UG-176/U Reducer RG-59/8X .25 or 5/\$1.00
UG-175/U Reducer RG-58/58A .25 or 5/\$1.00
Silver Teflon PL-259/Gold Pin.....\$1.00 or 10/\$9.00

MIL-Spec Coax Available (Teflon, PVC IIA)

New Product: Belden 9913F. 9913 with
High Density PE Foam dielectric, stranded
center cond. and Duobond III Jacket.....
.....80/ft or \$76.00/100ft

Also New: 9092, RG8X with Type II Jacket
Intro Price.....\$23.00/100ft

Call for Specials of the Month

Full Line of Audio Connectors for Icom,
Kenwood, and Yaesu

8 Pin Mike Female.....\$2.50
8 Pin Mike Male Panel.....\$2.50
13 Pin DIN for Kenwood.....\$2.75
8 Pin DIN for Icom.....\$1.00
8 Pin DIN for Kenwood.....\$1.50

Prices Do Not Include Shipping

Orders 800/783-2666
Info 301/840-5477
FAX 301/869-3680



Dear Nuts & Volts:

The circuit diagram for the return loss bridge (Open Channel, Sept. '99 page 76) is incorrect.

As drawn, T1 imposes a short between the junction of R1-R2 and the unknown impedance (J2). The bridge cannot balance because the legs are unequal. The lower left impedance is $R2+Z0 = 2 Z0$; all other corners are just $Z0$.

To fix the circuit, connect the bottom of R2 to ground. Then the bridge can balance: R1 and R2 form the left side; R3 and the unknown form the right side. T1 should be a balun that converts the balanced signal across the bridge to a single-ended output. Disconnect one of T1's bottom terminals from ground and connect it to J3. That completes the fix.

Gerald Roylance, Mountain View, CA

Dear Nuts & Volts:

I have a comment regarding the Tech Forum answer given for #6996. Michael Mruzek's idea for determining frequency of a PTO driven generator using a clock is great. It is simple and uses something that everyone almost certainly has on hand. He should understand, however, that even most electronic clocks can be used rather than just motor-driven clocks.

Electronic clocks almost always derive their time-keeping signal from the line frequency via an AC feed from the secondary of the power transformer. Clocks with battery backup do have an internal oscillator, however, as often as not, it uses a low precision ceramic resonator and is only energized when the power is off. When under AC external power they too use the line frequency as a reference.

David B. Sarraf, via Internet

Dear Nuts & Volts:

Dan North's questions (Sept. '99, Electronics Q & A) about the lightning detector in Joe Carr's column (Feb. '99 Open Channel) were very good, but many of the answers were wrong.

The basic detector is described in Thomas P. Leary's article in QST (June '64, page 23-26). If I were back in Boston, I would build one, but we don't get much lightning in Silicon Valley.

The coil is electrostatically shielded to reduce capacitive coupling. Carr states this at the bottom of page 16. The shield has no effect on magnetic coupling. The shields do not, as TJ Byers claims, magnetically isolate the coils. Byers is also incorrect in his claim that without the shield, "the antenna appears as a single turn of wire that has no value in detecting lightning strikes." Without the shield, the antenna will pick up more noise (and be less useful), but the turns in the loop don't magically merge together. Its sensitivity to lightning strikes is undiminished.

The output voltage of the loop is proportional to the number of turns and is also proportional to the area of the loop, but the issue is more complicated than that. The loop antenna can only intercept a certain amount of power, so the number of turns and the amplifier impedance are important.

Increasing the area increases the amount of power the antenna intercepts. Increasing the number

of turns does not increase the power (but it does affect the impedance match).

For a typical configuration, the amplifier input impedance should be small to match the small impedance of the loop antenna. The 10M input of your

scope is too high; it allows a lot of thermal noise. One saving grace is that lightning has a lot of power, so even an insensitive 10M scope might see a strike. Leary's amplifiers were high impedance, and he got results.

Grounding one end of each coil will not hurt the sensitivity. Several authors have made claims about keeping a loop antenna balanced, but I'm suspicious of these claims because they don't say why. Using a balanced/differential configuration is a good idea because it forces the builder to pay more attention to ground noise, but I don't think it is essential.

Reversing the coils does not "null out the signal altogether." Reversing the coils just mirrors the axis on the scope display. The QST article discusses how to connect the two antennas to align the north-south and east-west directions. The antennas are in quadrature and cannot null each other out. They will only null if they are in the same plane and connected in opposition (so the turns cancel).

The Z-input does not provide directionality "because of the cardioid pattern of the antenna." The crossed loop antenna is omni-directional in the horizontal plane. A signal arriving from an angle theta will generate a $\cos(\theta)$ signal in the NS loop and a $\sin(\theta)$ signal in the EW loop.

The length of signal displayed on the scope is independent of the angle. There is no cardioid antenna pattern. The Z-input detects the electric field. The loop antennas detect the magnetic field. Looking at both the electric and magnetic fields lets us sort out the direction the wave travels.

Electromagnetic waves have a handedness, and the electronic storm finder uses the E field to gate the M field detectors (the two loops antennas). If you look at a drawing of an EM wave you can get an idea of how this works. Unfortunately, the details get in the way. The loop antennas introduce a 90-degree phase shift. Leary compensated for this phase shift by putting a 90-degree phase shift in his Z-axis amplifier (but his circuit has problems).

Carr's column omits the Z-axis amplifier and ignores the phase shift issue. (Some radio direction finding (RDF) antennas use both E and M antennas, and the tuning instructions include adjusting the phase shift to 90 degrees.) Without the phase shift, the Z-axis gating does not work.

Thanks for the intriguing article about detecting lightning. It made me think about many interesting things. Both Carr and Byers have many interesting things to say.

Gerald Roylance, Mountain View, CA

Dear Nuts & Volts:

Thanks for the Tesla Coil article in the Sept. 99 issue. This is a project my 10-year-old son and I have been talking about for the past couple of months. Ever since he garbage-picked fluorescent tubes and as he and his buddies escaped on their bikes, they passed under a high-voltage line. In an instant they "got religion" when the lights started to flicker in their hands in the gathering dusk. My son, who loves to experiment with electronics, figured it out after a few incredulous minutes and started the boys riding in circles under the wire. As darkness fell, I am sure they

Very Affordable GIFT IDEAS

Netcom #1 in Customer Service Since 1983

IBM ROAD WARRIOR
Professional Road Equipment

MAXIMUM ABUSE
strictly for professionals

Blazing Sunlight or Rain Storm

On the **DESERT** or **SNOW**

Instant ON - ZERO boot up time

Drop 3' to Concrete

Rain: (4"/hr Rain w/ 40 MPH Winds)

Silicone Rubberized & Diecast Case!

Ultra Shock Mounted 1GIG EIDE Hard Drive!

ESD / EMF & RF Resistant, Works from -4 to 120 Deg F & Vacuum to 15,000 ft

- > 1- PCMCIA (type 1, 2 or 3), Serial & Parallel Ports in rear
 - > 16m Ram / 1m Video / 32 Bit Local Bus 486-50 Mhz & Math Co-processor, 28.8k Modem (Internet Ready)
 - > Very Long Lasting Hydride Battery (\$150 Value)
 - > Sound & Microphone, External Mini 3.5 Floppy
 - > 8.25" Display-64 Shade Monochrome REFLECTIVE
 - > (Optional) Touch Screen with Handwriting Recognition
 - Rough Service Handle with Loops for optional Shoulder Strap
 - Roxanne's Voice Annotates all Windows 3.X Functions
- OPTIONS**
- > W95 \$89
 - > 12V Car cord \$29
 - > Touch Screen \$250
 - > 33k Baud PCMCIA Fax- Modem Upgrade \$35


This was a unique (one shot) purchasing opportunity
IT'S NOT OPEN STOCK

WHEN THEY'RE GONE, THEY'RE GONE FOR GOOD

Sold till recently by IBM through their Local Area Network Div at \$4,699 & \$6,912 as shown here. (they were never discounted)

Perfect for **GPS**
Satellite Navigation

Actual Selling Price From IBM
\$6,912

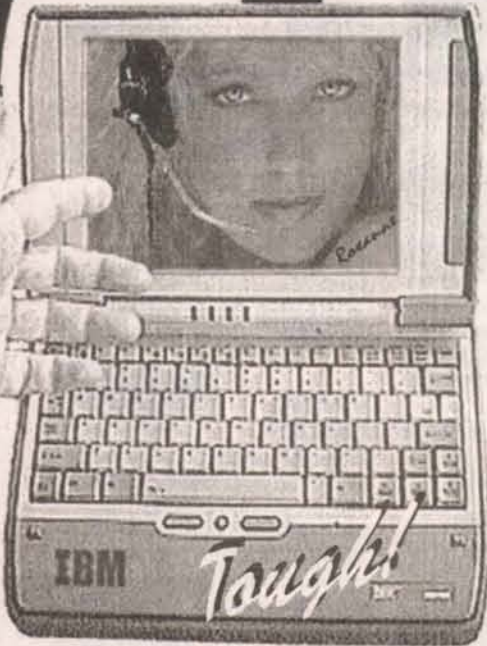

233 MHz

Pentium SubNotebook

3 easy payments of
\$333!
Wow!
0% Financing!
On Credit Cards only



Looks so nice
in person,
it gives you
Goose Bumps

Low Price / High Performance

233 mhz

3.2Gig

32m ram

56k modem

CD 24x

USB (2)

W98

External CD 8" SVGA Color Display Built-in Stereo Speakers & Mic
External Mini Floppy Convenient Touch Pad Mouse (excellent!)
Lithium Ion battery 2 USB ports, IR Port, All standard ports on rear
2 PCMCIA Ports Light-weight 3.3 lb 9.5 x 7 x 1.5 Built-in palm rests
One year Manufacturer Direct Warranty FREE Lifetime NetcomTech support

OPTIONAL CUSTOM Carrying Case \$24 SOYO Embossed LOGO, Tailored fit, Pockets, Handle & includes Shoulder Strap

SOYO is the leading maker of Computer Motherboards for FAMOUS NAME BRAND computers. The "Commuter" from SOYO has all the best features you're looking for without the big price tag. The best part is it's light weight, compact & State-of-the-Art. Sells for \$1200 on QVC! (The Shopping Channel)

IBM Thinkpads

Pentium P-75 -or- 486 DX4-100

Huge 10.5" Active Matrix SVGA Color Display (the Best)
33k FAX MODEM - 2 PCMCIA Expansion Slots
Dual Infrared Ports (Front & Rear)
Track Point Mouse All Standard Ports (1S,1P,1VGA,1Kbd)
Pop out - Hard Drive, Ram, Battery & Floppy.
Ram & Hard Drive Expandable & Upgradable.
Includes Power Supply & Hydride Battery
Free Lifetime Tech Support Web Site Creator Software
Internet Ready, America On Line 4.X Latest Version
Fax Modem Software, Searchable Owners Manual s/w, W95
DX4-100 810Meg Hard Drive Standard -or- (2Gig only \$59!)
16M Ram Standard -or- (optional 24M Ram \$24!)
Pentium P-75 2Gig Hard Drive & 24 Meg Ram Standard

3 easy payments of
DX4-100 \$218!
Wow!
0% Financing on Credit Cards only
Docks \$189 alone

3 easy payments of
Pent-75 \$286!
Wow!
0% Financing on Credit Cards only
Docks \$189 alone



ICM Bible
of the IC Industry
Every Cross-reference
3 Volume Set with Tons of Information

ICMaster Earlier Editions Perfect for Service or Lite Design. Later Editions Perfect for Advanced Design

ICM 95 3Book Set \$29 !!!!!!!
96 3Book Set \$49 !!!!!
97 3Book Set \$69 !! CD Rom \$ 99!!
98 3Book gone CD " \$135!
99 3Book gone CD " \$189!

EEM Contains the Complete Catalogs of Most Electronic Component Manufacturers & Distributors

EEM 97 4 Book Set only on CD \$35
98 4 Book Set only on CD \$55
99 4 Book Set \$75

Over a Quarter Million Devices
2 Easy Payments

\$49!

FREE Upgrade which will include a Huge, Asian Transistor Spec Database: \$69 option in the new version

"REFEREE" CROSS REFERENCE & SPEC
Transistors, ICs & Diodes

A Specialist in "Hard to Cross House Numbers"
Easy, Powerful & Fast.
The Most Comprehensive Software Sold.

Yields Device Specifications & 75 to 250 Potential Replacements!

Replacement Numbers are Totally Global including Domestic, Asian, European, House, Branded, as well as ECG, NTE, SK & GE. Displays Case Drawings, Lead Configuration & Pin-outs for many Devices. Coverage of Replacement Numbers is Very Impressive. 7 Disk Set (17 Meg decompressed) For DOS, W3.1 & 95, 98 & NT. Current Version 7.11

Includes:
4 HUGE Consumer Electronics Industry Directories
1- Consumer Electronics Parts Sources (Service) 2- Consumer Electronics Manufacturers 3- The Entire Computer Industry 4- Semiconductor Manufacturers

#1 Choice of Service Centers



IBM Docking Stations

This is not just a port expander it's a full blown docking station
You can add ANY desktop ISA card and it will work with your IBM laptop
Imagine the possibilities. Add a TV card and watch TV while you compute!
ISA computer card hides in the base of the unit.

FREE Local Area Network (LAN) card (a \$79 value) Notebook Snaps onto the dock.
Expansion Port for optional CD Rom Built-in Speakers Built-in Power Supply & Fan
SCSI Expansion Port / Parallel / Serial / Keyboard / Mouse / Monitor / Stereo In & out
Front panel headphone Jack Hidden Carry handle LED Status Indicators
Color Black (matches notebook) ISA Port cover & Key optional (not required)

From IBM
\$450

1 Year Warranty - Satisfaction Guaranteed - The Friendliest People - The Best Customer Service
PAYMENT PLAN with Credit Card -or- Layaway ONLY 843-650-5700 For Questions-or- email: netcomd@aol.com
COD's SINGLE PAYMENT ONLY ORDERS ONLY 800-733-3733 ORDERS ONLY FAX 843 650 5777 10-8 EST Mon-Fri



LONGWAVE ULTRAVIOLET LAMP

Pocket-sized longwave ultraviolet light may be used for detecting invisible inks, minerals in rocks, etc. It's the size of a pocket pager and even has a belt clip to keep it handy. Runs on two "AA" batteries (not included). 3.25"W x 1.75"H x 1"D.

95L007 \$7.95 each

LASER DIODE

Toshiba TOLD9200. 670nm, 9mm dia. case, 3mW, 2V @ 80mA.

99S004 \$14.95



REMOVABLE HARD DRIVE

Syquest SO555 44MB removable SCSI cartridge hard drive. (Removed during upgrade)

97C024 \$9.95 each

DECODER KIT

Grab a telephone tone from the phone line or from an audio source like a microphone or tape recorder & decode it.

Show the number on a 2x16 LCD supplied. Also call duration. Source code supplied on disk.

KIT 56 \$44.95



CURLY RAZOR POWER CORD

Stretches to six feet. Black.

98W016 \$2.49 each



Powersonic AUTOMATIC CHARGER

For 12V gel cell. Input: 120VAC, 60Hz.

98E025 \$9.95 each



150W MINI TOWER POWER SUPPLY

Pulled from unused equipment.

96C009 \$9.95 each

14-DAY PROGRAMMABLE TIMER

Originally used to control a satellite receiver through its IR port. Time on/off for eight distinct events. Modify it for your needs or dismantle it for its parts. Programmable with a 2732 EPROM in a removable "personality" module, the unit may be modified to control any IR device through its IR port. Contains Z80 CPU, clock display and associated parts. Operates from 9VDC 500 mA wall transformer which is included.

92V014 \$9.95 each

COMPUTER CASE & POWER SUPPLY

Mini tower case with 230W power supply, two 5.25" and two 3.5" external bays, plus one internal bay for hard drive. LEDs for power, turbo and HD. Limited supply at this price!

99C003 Only \$19.95



UNENCODED MATRIX KEYBOARD

80 full-sized keys mounted on 10.5"W x 4.625"H 0.5"D board with I/O cables. Used in laptop computers. New.

99C004 \$6.95 each

MS DOS 5.0

3.5" diskettes, with manual.

97C048 \$4.95 each

VERO VME I/O CHANNEL BACKPLANE

Five positions: male one side, female other side, 3- and 4-pin amp connections for power (+5V, ±12V). With mating plugs. Vero #243-39122C.

98C043 \$9.95 each

PLUG PARADISE!

Molex, Amp, Cannon, Viking, etc. A great assortment of connectors.

92J048 5 Lbs for \$5.00

30-GAUGE WIRE WRAP

100' rolls. Choice of color.

99W013BR - Brown \$3.95

99W013LB - Lite Blue \$3.95

99W013VI - Violet \$3.95

RACK MOUNT CABINETS

High-quality rackmount enclosures come in an attractive charcoal grey epoxy finish. The top, bottom and sides have ventilation holes to assist in cooling. The front and back panels are made of 0.059" thick aluminum for easy custom design. The top, bottom and sides are 0.035" steel. Choose from six sizes. All include handles except RC3120A.

RC3120A-1.5"H x 16.75"W x 9.5"D \$38.00

RC3120B - 3.25"H x 16.75"W x 9.5"D \$46.00

RC3120C - 3.25"H x 16.75"W x 13"D \$53.00

RC3120D - 5"H x 16.75"W x 13"D \$58.00

RC3120E-5"H x 16.75"W x 16.75"D \$63.00

RC3120H - 8.5"H x 16.75"W x 16.75"D \$83.00



SOLAR FURNACE!

Build your very own solar furnace with this giant (approx. 30" x 40") Fresnel lens. The men in the photo are our staff scientists melting metal with the furnace they made. It's capable of generating over 2500°F.

99L003 \$99.95 each

BROW MOUNTED BINOCULAR MAGNIFIER


Wear this handy magnifier with its velcro clasp. One size fits all so it's always comfortable. Magnifier assembly tilts up out of the way when not needed. Fixed lens gives 1.8X magnification for most close-up activity. For a closer look a second binocular lens tilts down from inside visor. For turbo peep mode, swivel the loupe in front of the right eye. Combinations are 1.8X, 2.3X, 3.7X and 4.8X.

MP242 \$23.95 each

RG-58 CABLE

25 feet long, with BNC connector on each end.

97W023 \$8.95 each

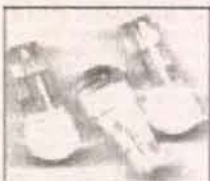

LIGHT AMPLIFIER???

This clear 5/16" diameter plastic lens fits nicely on a T-1 LED or the end of a fiberoptic cable and magnifies the output.

98L004 4 for \$1.00

HPIB/GPIB CABLES

Your choice \$24.95.

1 meter - HPIB-1

2 meters - HPIB-2

4 meters - HPIB-4

6 meters - HPIB-6



RED PROJECTION TV LENS

Used in rear screen projection TV sets. Also useful for photography and laser light shows. Focal length = 7.5mm; diameter 75mm.

99L001 \$24.95 each

NEC AMPLIFIED SPEAKERS

Use to amplify output of tape or portable radio, or as multimedia speakers. Excellent sound quality for their size. Approx. 30 watts, line out for recording, and ear-phone jacks. Simple schematics to build your own power supply included. ±15VDC @ 1A. Approximate size: 11"H x 5"W x 5"D.

98V013 \$9.95/pr.

Swivel Base BABY BENCH VISE

Clamps onto benches up to 1.5" thick. Base swivels 360° and clamps in any position. Jaws are 1.5" wide and will clamp workpiece up to 1.25" thick.

8433MVCS \$12.75

MEMBRANE KEYPAD

5 x 4 matrix, approx. 3" sq., with adhesive backing.

97B014 99¢ each

INFRARED CAMERA

3.6mm CCD camera with 430 lines of resolution. Minimum illumination: 0.03 Lux. Built-in microphone sensitivity: -60dB. Audio out: 1V/600 Ohms. 90mA, 7.5-14VDC, 9V standard. Includes 9V AC adapter.

99V002 \$79.95

NEC NE710 FET

Ku-K Band GaAs. With docs.

92S073 \$9.95 each

LCD DISPLAY

Four lines by 20 characters. Back light attached. Standard 14-pin connection.

94L010 \$14.95 each



AMPLIFIED MULTIMEDIA SPEAKERS WITH SUBWOOFER

Built-in amplifier gives the left and right speakers 20 Watts of audio power while the companion subwoofer puts out 30 Watts. Speakers measure 7" x 5" x 6" and subwoofer is 7" x 14" x 13". These are Advent AV370 speakers so quality is no doubt superb. List price was \$234.95. Refurbished.

99V011 \$69.95/set



PLATFORM JACK

Minimum height: 2-3/16". Maximum height: 11". Will support labware, optical apparatus, mechanical parts, and countless other items with a great deal of stability. Scissor action. New, unused jacks. Compare our low prices for the 6" and 8" models to the list prices of \$185 and \$234 respectively.

99Z005 (6" x 6", 33lbs Max. Load) \$49.95

99Z006 (8" x 8", 44lbs Max. Load) \$64.95



SMALL INSTRUMENT CASE

Plastic enclosure measures 1.5" x 8" w x 4.5" d. Grooves in top and bottom hold front and rear panels (not included).

97Z013 \$3.49 each



LIQUID CRYSTAL SHUTTER/VARIABLE DENSITY FILTER

0.5" x 1.625" active area. 0% to 23% transmission. Switching rate up to 4 KHz. Specs included.

92L012 Only \$9.95 each



EPROM ERASER

Erase up to 20 EPROMs in as little as 15 minutes. Conductive foam pad prevents static buildup. UV lamp rated at 6,000 hours runs on 110 VAC for simple operation. Low profile, durable plastic case for greater portability. Dimensions: 12.5L" x 4.75" x 3"H.

94Z021 \$49.95 each

BIPOLAR STEPPER MOTOR

400 step/rev. (0.9°/step). NEMA 17 size, 2.5 cm deep, ball bearing, 5mm dia. shaft front and rear. Front shaft has a sleeve pinned to it to make it 7mm dia. by 1.5cm long. Bipolar 7 Ohm coils. Menebea (Japan) P/N 16PY-Q203-01.

96M005 \$4.95 each

BIPOLAR STEPPER MOTOR DRIVER IC

600mA output current capability per channel. 1.2A peak output current (non-repetitive) per channel. Enable facility. Temperature protection. Logical "0" input voltage up to 1.5V (high noise immunity). Internal clamp diodes. With documentation.

L293D \$3.00 each




ALLTRONICS

2300-D Zanker Road - San Jose, CA 95131-1114

World Wide Web: <http://www.alltronics.com>

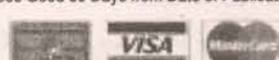(408) 943-9773 - Fax (408) 943-9776

Store Hours: 9-6 M-F & 10-3 Sat. - Pacific
Visa, M/C, AmEx Accepted. All Sales Final.
California Residents Add Sales Tax.
Shipping Additional on All Orders
Prices Subject to Change Without Notice.
Prices Good 60 Days from Date of Publication



Visit our website and download our catalog. 9911

by Thomas Henry

Build a Tunable Noise Generator

Electrical noise is most often considered an enemy.

In audio and radio circuits, for example, it can lead to an annoying background hiss or distorted reception. But, in fact, noise can be useful in a great number of applications. For example:

- A medical researcher might use it to study ways of reducing ringing in the ears, a condition known as tinnitus.
- An audio technician can use white noise to equalize a public address system (set the tonal balance) for a particular room.

similar, but more emphasis is given to the frequencies within the audio band. It's possible to carry this even further and create other types of noise by emphasizing or shunning various frequencies. This is usually done by following a white noise source with an active filter whose cutoff frequency can be adjusted. The filter can quickly become quite complicated and be touchy to adjust.

But here's a new approach to the problem. This article describes a tunable noise generator which, instead of using an active filter, employs FM (frequency modulation) to obtain a broad range of sounds. What comes out of it is noise, of course, but it's possible to emphasize certain bands of frequencies.

When sweeping it over its range, the effect is quite ethereal, a

modulating white noise, then, causes the VCO to vary randomly from this center frequency. In this way, a certain tonality is imparted to the sound thus created; it's still noise, but it seems to be focused around a certain band of frequencies. By twisting the tuning control, it is possible to sweep the sound across the entire audio spectrum.

Incidentally, a VCO with a triangle wave output seems to work best here, giving a fairly smooth sound. Squarewaves, on the other hand, lead to a rather harsh and gritty effect. In any case, the output of the VCO is dropped across the volume control which lets you set the amplitude.

So we have arrived at a unique method for "tuning" the response of a noise generator without requiring the use of active filters. Let's check out a practical circuit which

This article describes a tunable noise generator which, instead of using an active filter, employs FM (frequency modulation) to obtain a broad range of sounds.

R18, while the base connects to the negative side of things. Thus, the transistor is straddling a full 30V (+15V and -15V) which is enough to overcome the base-emitter breakdown voltage. This forces it into avalanche mode and produces a really decent source of white noise at the emitter. R18 limits the current flow through the transistor, so that it doesn't fry in the process.

R18 also acts as a load resistor for the noise thus generated. Unfortunately, the signal is a trifle weak just now and needs to be boosted. So, we send it to a preamplifier configured around IC1a, AC coupling it in the process by means of capacitor C6. Notice that C6 is purposely kept fairly small so that the bass frequencies will be attenuated a tad. This helps prevent rumbles in the sub-sonic region.

R1 and R13 set the gain of op-amp IC1a to a factor of 101. But believe it or not, that's still not enough "oomph" to properly modulate the VCO yet to come. So we move on to yet another preamplifier, this time comprising IC1b, R4, and R14. Operating in inverting mode now, this op-amp will have a gain of 10. Put the two preamps together, and we have boosted the white noise by a factor of over 1,000. Now it's strong enough to do what we require of it!

The hefty noise available at pin 7 of IC1b may have accumulated an unwanted offset, so we AC couple it to the next stage via C8. The full strength signal is applied across potentiometer R9, which lets you manually adjust how deeply the noise will modulate the VCO.

And speaking of which, let's look into the VCO now. It was

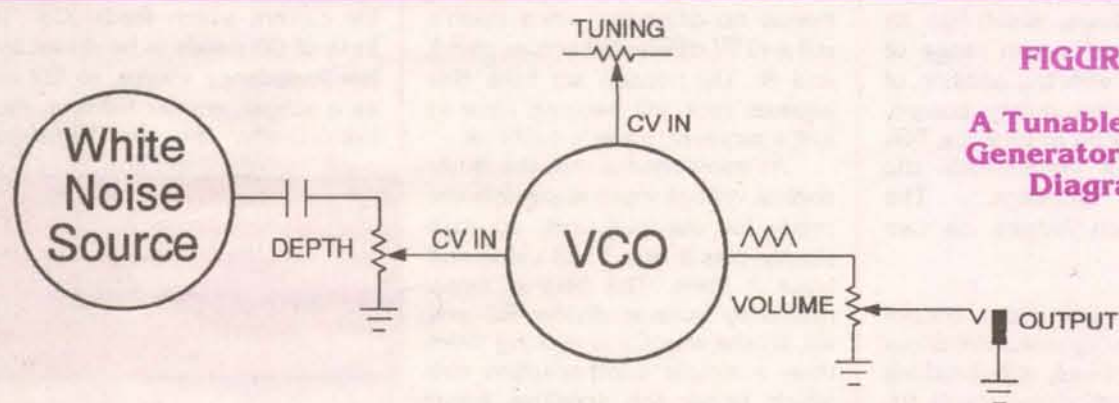


FIGURE 1

A Tunable Noise Generator: Block Diagram

• An electronic musician uses noise when synthesizing percussive instruments like snare drums.

In these and other situations, we need a reliable source of noise. Now by definition white noise — as it is often called — is a completely random mix of all frequencies, just as white light is a blend of all colors. On the other hand, pink noise is

sort of "swooshing" not unlike the sound of wind whistling through forest trees. Let's investigate the general procedure first before turning to the circuit itself.

PRINCIPLE OF OPERATION

Figure 1 shows the block diagram of the tunable noise generator. First, white noise is created using standard techniques which then modulate the frequency of a VCO (voltage-controlled oscillator). The depth control is used to set the amount of modulation desired. A separate tuning control adjusts the center frequency of the VCO. The

implements the block diagram of Figure 1.

HOW IT WORKS

Refer to Figure 2 which shows the schematic for the tunable noise generator. Let's start out by analyzing the white noise source first, leaving the VCO portion for later. Notice the unusual arrangement of transistor Q1. The collector isn't used at all, which suggests that Q1 is being pressed into service as a diode. In fact, it's really behaving as a zener diode since the base-emitter junction has been deliberately reverse-biased. Observe that the emitter has been tied high through

But, in fact, noise can be useful in a great number of applications.

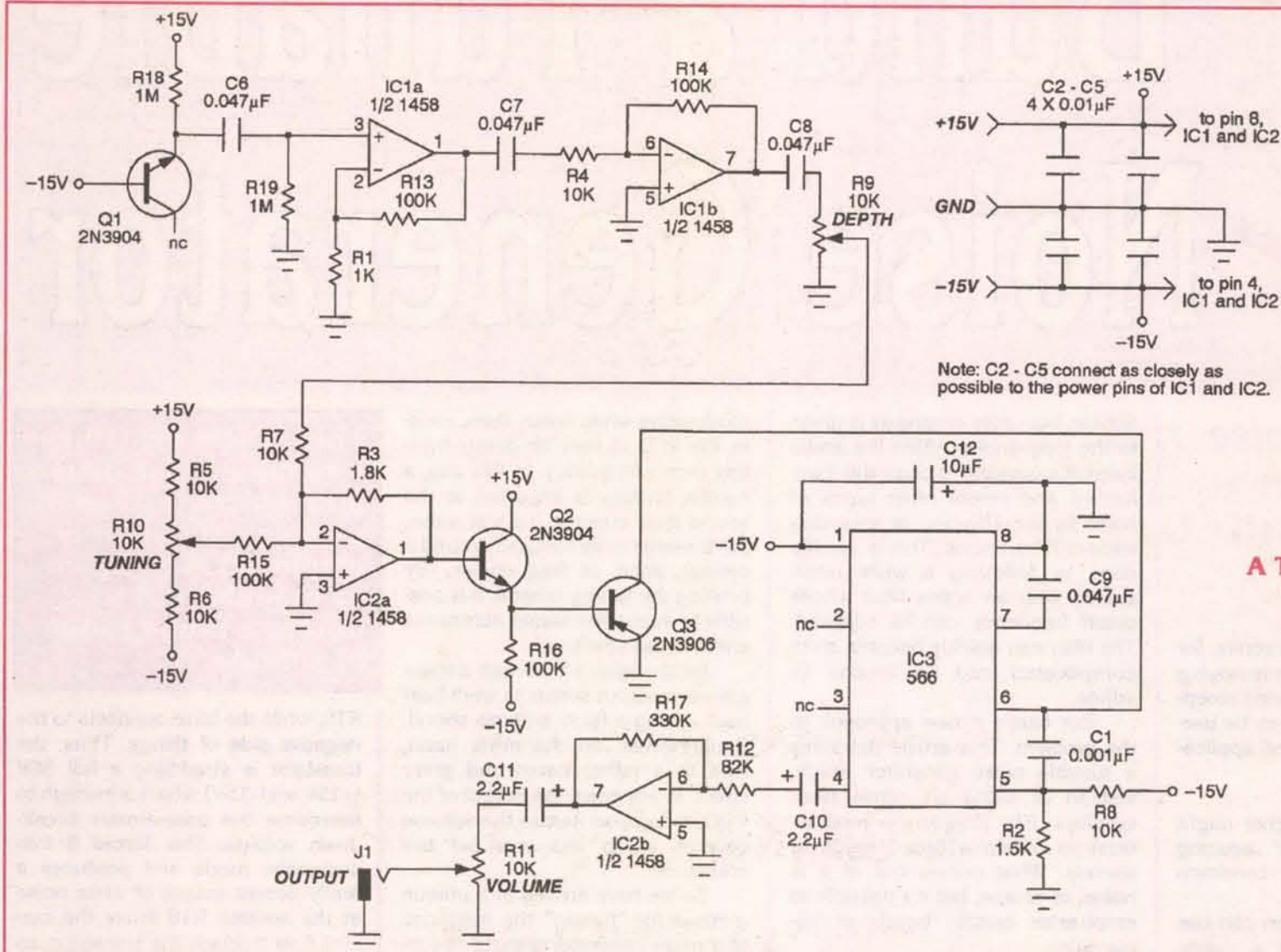


FIGURE 2
A Tunable Noise
Generator:
Schematic

designed with several important factors in mind; let's overview them before getting into the circuit details.

First, after much experimentation, it was determined that, for best results, the frequency sweep range should be at least 1000:1. Next, to make the device more suitable for audio and musical work, a 1V/octave exponential response

By pulling some clever circuit stunts, we can coerce the 566 VCO chip (which is both common and cheap) to do exactly what we require.

seemed appropriate. (Each increment of 1V at the control input should cause the VCO to jump up an octave.)

Finally, the design had to be carried out with easy-to-find and inexpensive parts.

The last criterion may seem to be the hardest to overcome, since exponential VCO chips are a rarity nowadays. But here's the surprise: By pulling some clever circuit stunts, we can coerce the 566 VCO chip (which is both common and cheap) to do exactly what we

require. Now, as it comes from the factory, this chip responds to a linear control voltage, which has an extremely limited sweep range of 10:1. However, with the addition of just a few garden variety components it is possible to trick the 566 into thinking it understands the exponential language. The approach taken hinges on two basic ideas:

- We can get better control over the 566 by ignoring the linear control voltage input, and throttling the current which charges and discharges the timing capacitor instead.
- The collector current of a bipolar transistor is exponentially related to the base-emitter voltage.

So, we'll whip up an exponential converter based upon the transistor characteristic mentioned above, and let that current directly govern the charge/discharge cycle of the timing capacitor.

That's the general idea. Now let's get back to specifics by examining Figure 2 in more detail. The first thing you'll notice is that the power supply connections to IC3 — the 566 — seem a little weird; -15V and ground (instead of the usual ground and +15V) connect to pins

1 and 8, respectively. Of course, from the 566's point of view, this makes no difference since there's still a +15V differential across pins 1 and 8. The reason we take this unusual tack will become clear in just a moment, so let's continue.

As mentioned above, the linear control voltage input at pin 5 is too seedy for our purposes, so we'll simply bias it at a fixed value and leave it there. The bias is determined by voltage divider R2 and R8. By the way, C1 is nothing more than a simple compensation cap which keeps the sensitive linear input from breaking into spurious oscillations.

Capacitor C9 sets the basic operating range of the VCO. On the other hand, the current fed into pin 6 sweeps the VCO's frequency up and down. And now we can see the reason for the somewhat exotic power supply arrangement.

The exponential converter — to be described next — is a current source and pin 6 of IC3 is a current sink. Voila — an exact match! (Had we employed the usual power supply arrangement, both the exponential converter and the 566 would have been current sources.)

Let's see how that magical exponential converter works. Recall that linear changes in the base-

emitter voltage on Q3 will cause exponential changes in the collector current which feeds IC3. The base of Q3 needs to be driven by a low impedance source, so Q2 acts as a simple emitter follower. More importantly, the two transistors

All of the components are commonly available, and there's nothing particularly tricky about the construction.

tend to act in harmony to reduce VCO frequency variation caused by temperature changes. (The theory of this can get pretty complicated in a hurry, but the basic idea is that if the emitter saturation currents of the two transistors are reasonably close to each other, then temperature dependence is reduced.)

There are a couple more details to consider, then we'll have this exponential converter under control.

First, when Q2 and Q3 do their thing, the response from the VCO will be "backwards;" the smaller the input voltage, the higher the frequency. Moreover, the scaling factor of the converter isn't quite right. It can be proven via some rather

tedious calculations that the VCO frequency will double for every 18mV decrease at the base of Q2. (Recall that we want a 1V/octave response, i.e., a doubling for every 1V increase.) Both of these problems are easily dispatched by IC2a.

First of all, notice that this has been set up as an inverting amplifier. That takes care of getting the sense of the control voltage correct; an increasing voltage at the input leads to an increasing frequency of the 566. Also, the ratio of R3 and R15 set the gain of IC2a at about 0.018. So, when the input changes by one volt, the output of the op-amp changes by 18mV, as required.

R15 is driven by the wiper of R10, the tuning potentiometer. The top and bottom ranges of this control have been limited appropriately by R5 and R6, respectively. With this pot you can sweep the VCO's basic frequency from about 20Hz to 20KHz in one fell swoop; there's lots of usable range here!

But here is the key to the whole circuit. Recall that the white noise generator output can be picked off the wiper of R9, the depth control. This signal feeds R7, which then sums into IC2a. Thus, the noise modulates the basic frequency of the VCO, completely at random. Potentiometer R9 lets you adjust how much modulation you want. Naturally, when set to zero, the circuit performs as a normal VCO.

And that brings us up to the output of the entire circuit. There are two waveforms available from the 566 chip, a squarewave (pin 3) and a trianglewave (pin 4). Feel free to use either waveform, but in general, the triangle output sounds quite a bit smoother. But note that pin 4 rides on a rather heavy DC bias which needs to be blocked, and the amplitude of the triangle there is only about 2.4Vp-p. Capacitor C10 AC couples the signal to op-amp IC2b, which then boosts it up to about 10Vp-p. The output is applied to volume control R11, which can tame the signal as

desired before it finally appears at output jack J1.

BUILDING THE TUNABLE NOISE GENERATOR

Checking out the Parts List makes it clear that this would be an easy and inexpensive weekend project. All of the components are commonly available, and there's nothing particularly tricky about the construction. You can build it using just about any method, from breadboards to wire wrap to printed circuit boards. For best temperature stability, though, be sure to mount Q2 and Q3 so that they're touching each other. You might even want to epoxy them together. And be sure that the wiring around the two transistors is neat since some rather low currents are involved.

When using the tunable noise generator, be careful not to blow out either your loudspeakers or your ears! The output of this device is pretty hefty (up to a max of 10Vp-p). This higher value was selected so that the circuit would be compatible with analog synthesis equipment. On the other hand, if using the tunable noise generator with standard hi-fi gear, you'll want to turn volume control R11 down to give an output of around 2Vp-p.

Finally, if you're looking for some other uses for the tunable noise generator, be sure to check the Internet site mentioned in the Parts List. You'll find modifications and hints concerning this circuit there. **NV**

ACKNOWLEDGEMENTS

I wish to thank the following two authors whose writings provided key information used in the design of the VCO portion. First, the 566 power supply trick was suggested by John Simonton, in his article, "Potpourri and the Apple Connection," Polyphony, November 1977, pp. 28-31. Next, Terry Mikulic explained the operation of the exponential converter in his article, "Exponential Converters," Electronotes, Volume 5, Number 37, pp. 2-4.

PARTS LIST

All resistors are 1/4-watt, 5% values.

R1 1K
R2 1.5K
R3 1.8K
R4 - R8 10K
R9, R10 10K linear potentiometer
R11 10K audio potentiometer
R12 82K
R13 - R16 100K
R17 330K
R18, R19 1M

All capacitors are 16V or better.

C1 0.001 mfd. mylar
C2-C5 0.01 mfd. disc
C6-C9 0.047 mfd. mylar

C10, C11 2.2 mfd. electrolytic
C12 10 mfd. electrolytic

Semiconductors

Q1, Q2 2N3904 NPN transistor
Q3 2N3906 PNP transistor
IC1, IC2 1458 dual op-amp
IC3 566 VCO chip

Other components

J1 1/4" phone jack

RESOURCE

Modifications, hints, and tips concerning the Tunable Noise Generator are available free of charge on the Web page of Midwest Analog Products.
<http://mail.lakes.com/~map>
E-Mail: map@prairie.lakes.com

Go Wireless With Our Modules

SILRX/TXM

SILRX — \$26.00 ea.
TXM — \$15.50 ea.

The TXM and SILRX modules are a transmitter and receiver pair which can achieve a one-way radio data link-up to a distance of 200m over open ground.

Both units are supplied in space-saving single-in-line packages and offer SAW controlled, wide band FM transmission/reception.

The modules are particularly suited to battery-powered, portable applications where low power and small size are critical design criteria.



TX2/RX2

TX2 — \$19.50 ea.
RX2 — \$38.50 ea.

The TX2 and RX2 radio transmitter and receiver pair enable the simple implementation of a data link at up to 40kbit/s at distances up to 75m in-building and 300m open ground. Both modules combine full screening with extensive internal filtering to ensure EMC compliance by minimizing spurious radiations and susceptibilities. The TX2 and RX2 modules will suit one-to-one and multinode wireless links in applications including car and building security, EPOS and inventory tracking, remote industrial process monitoring, and computer networking. Because of their small size and low power requirements, both modules are ideal for use in portable, battery-powered applications such as hand-held terminals.



900 MHz
AVAILABLE NOW

RPC

RPC — \$99.00 ea.


The RPC module is an intelligent transceiver which enables a radio network link to be simply implemented between a number of digital devices. The module combines an RF circuit with processor-intensive low-level packet formatting and recovery functionality, requiring only a simple antenna and 5V supply to operate with a microcontroller or a PC.



BiM

BiM — \$69.00 ea.

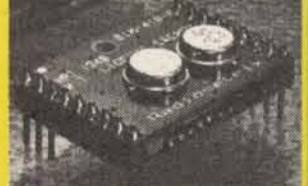The BiM module integrates a low-power UHF FM transmitter and matching superhet receiver together with data recovery and TX/RX change over circuits to provide a low-cost solution to implementing a bi-directional short-range radio data link.



Lemos International Co., Inc.

65 Southbridge Street, Auburn, MA 01501
Phone (508) 798-5004 ♦ Fax (508) 798-4782
www.lemosint.com ♦ sales@lemosint.com

All products available in either 418 or 433 MHz

Write in 121 on Reader Service Card.

ALLTECH ELECTRONICS

WWW.COMPUTERCHOPPER.COM

WE CHOP
PRICE\$!

SCSI CD ROM
Matsushita / Apple OEM
PC or Mac SCSI
4x \$19 24x \$79

486 Mini System
486SX25 • Great for Linux
DX266 Upgradable • 2 ISA
Slots • VGA, LPT,
2COMs • FD \$29

250VA Isolation Transformer
115V Pri - 115V 250VA Sec
Magnetek Triad
6" x 4" x 5" \$29

10" Open Frame SVGA
Metal Enclosed - Displays Up
to 1024 x 768 • 110V AC
Also Available in a
standard case. \$129 \$119

7 SCSI CD's in a Tower
7 CR-504-L
Drives in a SCSI Tower
case - 50 Pin \$179

Open Frame Industrial DC P/S
+5/12 -5/12 +24V \$29

24 Bit Flat Bed Scanner
Win95/98 - ImageWave by Storm
Technology. Parallel Port Interface
Software Included!
5 Minute Installation \$39

LCD Closeout!
Various LCD's - In New
Condition - We have No Docs
or controllers. See
the web. Starting at \$29

9" Mono VGA
Small footprint monitor
Great for servers, test benches,
etc. 640 x 480 only.
Refurbished. \$49

9.75" Mono, 8.6" and 10.4" Color LCDs



\$89 & up.

Great for Servers:
ISA Controller Included!!
All screens are 640x480. The
controller supports 256 Colors.
9.75" Mono Passive.....\$89.00
9.5" Color Passive.....\$199.00
10.4" Color Active.....\$319.00
Touch Screen Option
Available.
See our web site
for more details.

Cheaper Ethernet Stuff
Industrial Surplus
PC Parts • Mac Parts

For more information
on these products and
hundreds of other
products check out:

WWW.ComputerChopper.Com

760/724-2404
Fax 760/724-8808
Computer Circulation Center, Inc.
2618 Temple Heights Drive
Oceanside, CA 92056

Mon-Fri 9AM -5:30PM - Or see us on the internet.
VISA • Mastercard • Discover • American Express
Prices & Availability subject to change without notice • Government
& Educational PO's Accepted. • Not Responsible for Typographical Errors

Write in 120 on Reader Service Card.

Nuts & Volts Magazine/NOVEMBER 1999 27

350MHz, TEKTRONIX 2467, MICRO CHANNEL PLATE CRT!
4 Channels, 500ps per div. in normal room light.

Displays intermittent variations as they happen. Captures the slowest one shot events with 4ns per division a 100 fold increase in the visual writing rate over conventional CRT features. 1ns rise time. 500ps/div line rate. 2mV/div vertical sensitivity at 350MHz. 20ps time interval resolution. 1Mohm / 50-ohm input. 500MHz trigger bandwidth. Four channels. On-screen waveform cursors provide vertical & horizontal scale indicators. Trigger level, voltage, time, freq., phase, ratio values and mode indication. Complete with 2 probes, pouch, and manual. Mint cond. 90 day warranty.

New.....\$12K. Now TEK2467.....\$3250.

MAGNETIC STRIPE READER, with BAR CODE WAND.

New from United Barcode Industries, MAGSCAN model 1P0-155000-M-01 on-line magnetic stripe and BAR CODE reader designed for compactness and flexibility. The Magscan connects to the keyboard port via the standard mini-DIN connector. Perfect for use with a laptop. A good read is indicated by an audible beep and a visual signal from its LED. The unit reads track 1, track 2, or track 1 & 2. No software is required. Simply plug it in and start scanning/reading. Very compact, 5" x 2.5" x 1.5". No external power is required. 60 page manual included with complete user configuration info. Done using the wizard. Give manual per order. A super hacker device. SPECIAL.....\$49ea. or 2 for \$79.

MINIATURE and, PRECISE, PORTSCAR SWISS GEAR MOTOR.

State of the art "ironless" type mini motor type MT-210-54-0 with approx. 40.7 gearbox size. 16mm d. x 43mm l. Operating parameters: 6VDC input 3W, 141RPM No load, 40.12VDC input 12mA, 290RPM No load.

PORTSCAR TYPE B: \$15ea. 2 for \$27, Special.....10 for \$125

ULTRA MINI and WEATHERPROOF "LIPSTICK" CAM

Steel black anodized, alum. housing. O-Ring sealed & RAINPROOF. Adj. lining mount. 1/3" CCD. 380 lines. 0.3 Lux. AGC. Auto Shutter. 9-12VDC @100mA. 4mm. f1.8. 78° FOV. real glass lens. NTSC video. <100mV. 0.1 SENSITIVE. 23mmx45mm. 36" cable with BNC video & DC barrel jack.

GM-200K PIN-HOLE Model: So tiny you can install it directly into a door. Only 0.9" diameter hole! Specs as above. 90° FOV. Pinhole lens. 1/2" once! Size only 23mm d. x 35mm long. Think of the places you could put this little jewel.

GM-200K-STD.....\$99
GM-200K-PH lens.....\$99

STEPPER DRIVERS, SUPERIOR ELECTRIC, SLO-SYN Type, 3180-PT125. These drivers are removed from equipment and in good condition. They are designed for use with an external inductor. We have no documentation for these units. They are a compact 7"x5"x4". We always sell out of these so don't delay. Very limited quantity.

NOW.....\$139ea. or 2 for \$249

PORTABLE MINI PRINTER, 40 COLUMN, with INTERNAL NI-CAD POWER!

The model SD222-1000 is a NEW and very cool, self contained, alphanumeric, impact type printer. It features a standard parallel port and an internal Ni-Cad power supply. Can also be powered via the 9VDC power adapter supplied. Uses standard 2" wide paper rolls available everywhere. Has self test function and diagnostic mode. Can emulate Epson and Citizen 560. It will print from the LPT port of your PC. Very rugged and well made. Perfect for any remote printing or data logging application. Size: 8.1" x 4.1" x 3.5".

OUR PRICE.....\$49ea. or 2 for \$75

"A STRANGE LITTLE DEVICE"

AT&T Universal Digital Echo Canceller, Model ATNE120R2-2. If you have a use for this you know they are quite pricey. We have several available. They are like new. Standard 6pin RJ style jack for connection. Give us a call if you know how to use this and get one for free.

AT&T, UDEC.....\$89ea.

OPTICAL EXPERIMENTERS DELIGHT, Light Source, Fibre Optics, Two Detectors, Four Bandpass Filters, Stepper Motor, A/D Converter..... What more do you want?

We are sure this would make an interesting building block for the circuit savvy among you. A precision mini lamp sends to illuminate a bifurcated F.O. cable. One leg, 2 detector, presumably to compensate for any change in the source intensity. The other leg, 12" terminates at a mini convex projection lens and illuminates an unknown item under scrutiny. Light passing through the subject matter is gathered by another mini lens and directed to a 2" diameter filter wheel with 4 1/2" diam. bandpass filters with pass wavelengths of: 409nm, 450nm, 490nm and 630nm, individually selected with the help of a mini stepper motor and gears. Light passing through the filters is detected via a large area photo diode whose output is presumably passed to the a/d converter (ADI 7533KR) and the rest of the surface mount components. Very nicely made, shielded and supported on an intricate aluminum extrusion. (black anodized.) Overall size of the assembly is 5.6" x 2" x 5.4". Now you know what we know. Must have cost a bundle. Our price, less than the cost of one bandpass filter.

SUPER EXPERIMENTERS SPECIAL.....\$39ea.

FUTABA, 2X20 VACUUM FLUORESCENT DISPLAY MODULE

New or like new, model M202SD series. Can directly replace LCD displays. The module includes the VFD, microcomputer and driver. Connects directly to the system bus. Display up to 40 dot matrix, 5 x 7 characters (222 characters and symbols), 5mm H x 3.5mm W with cursor. Display color is green at 505nm. Brightness is 690 cd/m² with four level dimming function. Weight: 5 oz. Size: 6.7" x 2.6" x 1" thick. Power required is 5VDC @ 350mA. Serial or parallel interface selectable. Perfect for any high visibility display requirement. With data. SPECIAL FUTABA.....\$15ea. 3 for \$39

DAYLIGHT/LOW LIGHT MINI CAM & A/I LENS, For dawn 'till dusk applications. Rugged alum. housing, dual mtg. sockets. 1/3" CCD, 420 lines res., 0.1 Lux sens., AGC, 12VDC @120mA. Take full advantage of camera sensitivity with super, 4mm, f1.4, 78° FOV Auto Iris lens included. BNC video out. 50mm sq. x 65mm l. With pwr. adapt. SPECIAL, GM-510A/L.....\$189 or 2/\$349

NEW! 4 or 8 CHANNEL, SEQUENCER

Model GM34 or GM38. Connect to any four standard video signals and they will be sequentially output to the dual rear panel BNC outputs. Front panel user adjustable, variable dwell 1 to 15 sec per channel. Auto or manual switching with channel bypass. Compact only 8.6" W x 3.7" D x 1.75" H, ac powered. Video loop through. Special, GM-34.....\$69, GM-38.....\$89

WORLD'S SMALLEST * 100mW *** VIDEO TRANSMITTER, ON SALE**

Incredibly only 0.9" x 0.8" x 0.3" Transmits crystal controlled hi-res. images with 100mW output! The transmitter you've been waiting for. Shown actual size, smaller than the TV battery which powers it. Draws only 35mA! Factory lined. Receive on cable channel 59. Will work with color or B&W cameras. UHF Bow tie antenna with balun and 3' F cable for TV included. Perfect with our GM1000A. Both will fit in a cig. pack with battery.

SPECIAL TVX-100-\$159. with GM1000A CAM.....\$209.

TOROIDAL ISOLATION, STEP DOWN TRANSFORMER

Nicely made ULVECO LSA model 22432. Thermally protected. Primary is 0-120VAC. Secondary is 0-12VDC 300VAC and 18V @50VA. Includes heavy duty mounting bracket. Size: 5 1/2" diam. x 2 1/2" thick. Weighs in at 10.5 Pounds.

ULVECO XFMR.....\$20ea.

NEW! 0.008lux, COLOR NIGHT VISION CAMERA! UNBELIEVABLE LOW LIGHT PERFORMANCE.

Our GMV-2K, DOES IT in COLOR TOO!

For covert military & scientific applications that must be color, this is it. Performance is enhanced through low speed electronic shuttling and digital frame memory. With the optional, auto iris lens, 24 hour monitoring is possible. Auto sensitivity mode starts as it becomes dark. Eight Gain/Shutter modes are available. Selectable. Normal. X4, X8, X16, X24, X32, X64, X128. These provide frame rates of 60, 15, 8, 4, 3, 2, 1, and 0.5 per second. Auto/Man white balance. Alum. housing, dual 1/4"x20 mtg. Specs: 1/3" CCD with 291K pixels. 320 lines, 12VDC @200mA. Sid video out on BNC. Size: 54mm x 50mm x 94mm long. With pwr. adaptor. All functions can be externally controlled via an 8 pin mini DIN. Used as a night vision aid.

GMV2K.....\$589ea.
OPT. 4mm, f1.4 A/I lens w/cable \$119

CLOCK RADIO, COVERT CAMERA, New, Magnavox clock radio with covert low light video camera.

Specifications per our GM1000A shown on page one. Connect the output to anything with a "video input" jack via RCA style output.

SPECIAL, CRC-1-STD.....\$119ea.

GRAPHIC LCD DISPLAY, SEIKO Model G191C21R0A0

Like new, G191 series, monochrome with E&L electroluminescent backlight. These gorgeous FSTN type panels are perfect for direct sunlight applications. They won't wash out! The dot format is 192 x 126. The module size is 98 x 86 x 13.4mm. The viewing area is 78 x 54mm. The dot size is 0.33mm x 0.33mm. Power requirements are +5VDC @ 3.1mA and -12VDC @ 2.9mA. The backlight adds 120mA to the +5 current. Weight is 3.6oz. The viewing angle is 40°. Operating temperature range 0°C to 50°C. Now's your chance to design a really high-tech display into your next project. Data included. These are sophisticated devices, please be sure you are capable of integrating them into your device. Please review data at Seiko web page: www.seiko-usa-elec.com/cdr/html/graphic/modules/g191c21r0a0.html. All sales final. Current price \$111 each. Very limited quantity. SPECIAL.....\$29ea. or 2 for \$49 or 5 for \$99

PARKER-COMPUMOTOR, SM231A BRUSHLESS SERVO MOTOR

New, 3A series with optical encoder feedback. (1000PPR). Rated shaft output power is 205 watts. Stall current is 2.1 Amps. Rated speed is 7300RPM. Torque at rated speed: 2.37 lb-in. Shaft diameter: 0.25". Full specs are available on the web at: WWW.compumotor.com/catalog/SMseries59a.pdf. Size: 41 x 3.2" x 2.15". These are sure to sell out. Very limited quantity. SPECIAL.....\$149ea. or 2 for \$269

BIO CHEM VALVE CORP. Type 100P7-550 Solenoid

check valve. This unique valve has no contact with the controlled substance. It operates by squeezing a 1/8" diam. living and thereby "clamping" it closed when activated by 24VDC. The action is normally open. Shown right Size: 1" diam. x 2.8" l. With 1/2" wire leads. Removed from equip. PREDYNE, MINI VALVE, Type A92037-926, 24VDC @1200mA, solenoid operated. 5732" article. 8PS, pass through valve with 1/8" barbed nylon fittings attached. Removable for screw in connection. 1/2" wire leads. Shown left. Removed from equip. Both are like new condition.

BIO CHEM VALVE.....\$5ea., PREDYNE VALVE.....\$6ea.

NEW, GM960 TIME LAPSE VIDEO RECORDER

Finally a brand new, 4 Head, 1/2" recorder with all the features at a price you can afford. Features: • Up to 960 holes on a standard 1-120 VHS tape • 12 different modes for record and playback • Audio recording in the 12H and 24H mode • 30day memory backup • Easy mode setting • On-screen menus • Auto-repeat recording mode • Serial or One-shot recording • Time, Date, speed, and Alarm indicators on screen. These deluxe units are front loading and are 14W x 3.5" x 12.2". 110VAC powered.

SPECIAL.....\$699ea. or 2 for \$1349

HAPPY HOLIDAYS!

RESOURCES UN-LTD.

VISA, MC, AMEX, DISCOVER, COD.
ORDER: 800-810-4070 TECH: 603-668-2499
FAX: 603-644-7825 E-MAIL unltd4u@m20.net
300 BEDFORD STREET, MANCHESTER, NH 03101

NEWPORT TRANSLATION STAGES, also a few other goodies too!

MODEL:	DESCRIPTION:	EACH
270	LAB JACK	\$249
RSA-2T	360 deg. Rotary Stage with Clear Aperture.	\$129
625A-4	Laser Holder	\$149
481A	Rotary Stage	\$189
M36	Translation Stage	\$249
460A-XY	X-Y Translation Stage	\$189
M37	3 Axis Trans. Stage	\$289
415	Vertical Trans. Stage	\$129
M360-90	Rotating Plate 90deg.	\$29
M436	Translation Stage	\$199
M150	Magnetic Mtg. Base	\$129
420	Linear Trans. Stage	\$119
HP10703A	INTERFEROMETER	\$129
HP10702A	INTERFEROMETER	\$129
HP10780A	RECEIVER	\$199
RUCKER & KOLLS 222	X-Y-Z Micro Positioner	\$ 50

10V @ 2.5 AH SEALED, LEAD ACID, PACK. Each pack has 5. 2 Volt cells. 10 size cells are arranged as 1X5 cells. Enclosed in an ABS outer shell. Removed for photo! Perfect for high drain applications. Make custom packs of any rating. Size: 7.5" x 2.8" x 1.5". SALE! 6-five packs for \$20, 40 for \$99

SUPER, MINI C-MOUNT CAMERAS, Super sensitive, GM410 or the general purpose GM412.

The GM-412 specs: 8W, size 1.5" sq. x 2.4" l. 250,000 Pixels, 380 Lines Resolution. Sensitivity 0.3 Lux. The GM410 specs: size only 1.5" sq. x 1.6" l. >270,000 Pixels, 410 Lines Res., Sens. 0.05 LUX. Both cameras are 1/3" CCD with AGC & Electronic shutter. 12V @110mA power. NTSC out. IR SENSITIVE, BNC video out. Both use std. DC pwr. jack. Aluminum housings with dual threaded top and bottom mounting. True performance not hype! These cameras will outperform ANY camera in this magazine. Multi-lens options are available to exploit their superior performance. GM412 shown bottom. GM410 shown top.

GM412, less lens.....\$119, GM410, less lens.....\$169

low cost MICRO CAMERAS, w/audio 1/3" CCD, 410 Lines Res., 0.3 Lux sens., AGC, Auto Shutter.

Pwr. from 9 to 12VDC @100mA, 250K PIXELS, Std. model, 4mm, 78° FOV lens, Pinhole, 90° FOV. A real glass lens. Both focus from 10mm to infinity. Std. NTSC video out. 1/2 ounce! SENSITIVE to IR. Size Std. 1.25" sq. x 1.4" l. PH is 0.6" d. 1.6M long wiring harness with connectors included. WARNING: Don't confuse these models with LOW RESOLUTION, HIGH LUX C-MOS CAMERAS.

**GM-1000A-STD.....\$59 GM-1000A-STD/Aud.....\$64
GM-1000A-PH.....\$59 GM-1000A-PH/Aud.....\$64
GM-1000A-CMNT.....\$59 GM-1000A-CMNT/Aud.....\$64**

Micro Lenses for GM1000 series

2.5mm, 150°.....\$22	8.0mm, f2.0.....\$22
4.3mm, 78° f1.8.....\$22	12.0mm, f2.0.....\$22
6.0mm, f2.0.....\$22	5mm, 70°PH.....\$22

C-MOUNT LENSES

LOW LIGHT	STANDARD
16mm, f1.6, 15° FOV.....\$39	4mm, 80° FOV.....\$24
8mm, f1.3, 40° FOV.....\$49	8mm, 40° FOV.....\$24
4mm, f1.4, 78° FOV.....\$49	12mm, 28° FOV.....\$24

Please fax us your list of unique surplus material.

MOTORIZED ZOOM LENS SPECIAL

6X magnification, 12X on a 1/3" camera! Auto iris too!

New, fabulous hi-res. optics with std. C-Mount. Superior Fujinon and Vicon lenses. Normally cost from \$600 to \$1500. There is no substitute for a good lens! All drive motors will operate from 6-12VDC. Auto iris has a built in amp which works with any camera video output for control.

**Type B-6, 12.5 to 75mm, 6X, f1.2.....\$179 or 2 for \$349
ZOOM LENS CONTROLLER, NEW.....\$169**

MINI ROTARY DRIVE with on board LINEAR SLIDE, Provides 300° rotation between removable stop. Rotates continuously with-out stop. 2 optical position sensors for start & end. Same stepper as above. Each full step = -0.25° of rotation. Made from cast & machined resin & alum. Attached slide provides 3" travel. Construction similar to slide above. Moves 0.008" per step. Dual optical end of travel sensors. Overall: 7.5" x 5.25" x 4.5" MRD-1.....\$39 or 2/\$69

NEW, TRIPLE OUTPUT, 60W, POWER SUPPLY

Astec model: SA40-1313, outputs of +12VDC @ 3Amps, +5V @ 5Amps and -12V @ 350mA. 110VAC input. Very compact size: 3" W x 5" x 1.3" H. Perfect for many hobby applications as well as an external disk drive power supply.

SPECIAL.....\$5ea. or 5 for \$20

DEL TRON LINEAR SLIDE with CLEVER LEVER

An interesting assembly, consisting of a Del Tron mini linear, ball bearing slide (2.5" x 1" W x 0.56" H) with 2" travel. Slide is placed next to a 2" diam. stepper mounted wheel. A 1.5" sq. Four wire stepper, rated at 4V, 0.95A, 1.8°/step. The bottom side of the wheel acts as a cam with roller and moves a spring loaded arm (3.4" x 1" W) up and down 1/2". All components, including an optical end of travel detector are mounted on precision machined, 0.2" thick, black anodized aluminum. Overall size: 8.5" L x 3.3" D x 2.5" H. Ex. Cond. Ltd. Qty.

DelTron-W.....\$39ea.

COMPACT, THK, LINEAR SLIDE with STEPPER DRIVE,

A really slick, super precision, THK LWL-12 series, recirculating ball slide with a 3.6" long toothed rack (14TPI) mounted next to the rail. The rack mates with a 0.6" diam. nylon drive gear mounted to a compact, 1.5" sq. l. Four wire stepper, rated at 4V, 0.95A, 1.8°/step. One full step moves the slide approx. 0.050". All components, including an optical end of travel detector are mounted on precision machined, 0.2" thick, black anodized aluminum. Overall size: 5.5" W x 3.3" D x 3.4" H. The system provides 3.1" of extremely rigid travel. Ex. cond. Ltd. Qty. **LS-LWL-12.....\$49ea.**

Events

CALENDAR

NOVEMBER 1999

NOVEMBER 5-6

LA - MONROE - Hamfest. Twin City Ham Club, Jim Rasch K5JMR, 318-372-8164. E-Mail: tchc@qsl.net Web: <http://www.qsl.net/tchc>

NOVEMBER 6

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

FL - SORRENTO - Hamfest. East Lake Chamber of Commerce Bldg. VE Exams. Talk-in: 147.255. Lake ARA, John Wentz W8HFK, 352-728-2615. E-Mail: capias@gate.com Chuck Crittenden KE4EXM, 352-669-2075. Web: <http://www.qsl.net/kf4c/index.html>

IL - BELLEVILLE - Hamfest. Belleville Area College, Carlyle Rd. (Rt. 161) & Green Mount Rd., Main Campus. 8am-2pm. VE testing. Talk-in: 147.120 K9GXU repeater. Scott Composite ARS, Howard "Skip" Mize KA9VKE, 618-277-9767. E-Mail: fluinc@peaknet.net

IN - FORT WAYNE - Hamfest & State Conv. Allen County War Memorial Coliseum Expo Center. Sat: 9am-4pm, Sun: 9am-3pm. Talk-in: 146.88-. ACARTS, 219-484-1314.

Web: <http://www.pipeline.com/~dagagnon/>
KY - HAZARD - Hamfest. High School, Hwy. 15 S. & Bulldog Rd. 8am-2pm. VEC exams by WCARS. Talk-in: 146.07/67. Kentucky Mountains ARC, John Farler K4AVX, 606-436-5354. E-Mail: jfarler@mis.net Web: <http://www.geocities.com/SiliconValley/2564/kmarc.htm>

NH - MANCHESTER - Hamfest. St. John Church. 305 Kelley St. Talk-in: 146.850 PL 85.4. Paul K1LLX 603-432-1538.

E-Mail: K1LLX@juno.com
OK - ENID - Hamfest. Garfield County Fairgrounds, Hoover Bldg., Oxford & 4th. 8am-5pm. VE testing. Talk-in: 147.150+ or 444.400+. Enid Hamfest Group, Tom Worth N5LWT, 580-233-8473. E-Mail: n5lwt@hotmail.com

SC - MYRTLE BEACH - Beachfest '99. Old Myrtle Beach Air Force Base. 7am-2pm. Talk-in: 147.120 +600. Grand Strand ARC, Jim Wood KF4CJE, 843-238-0800. E-Mail: kf4cje@juno.com Web: <http://www.w4gs.org>

WI - MILWAUKEE - Hamfest. Milwaukee Repeater Club, Mike Borchardt N9NPB, 414-367-3953. Web: <http://execpc.com/~mrc/friendlyfest.htm>

NOVEMBER 6-7

GA - LAWRENCEVILLE - Hamfest. Gwinnett County Fairgrounds. Talk-in: 145.45- (PL 107.2), 444.25+ (PL 131.8), 146.76- (PL 107.2). Alford Memorial RC, Hotline: 770-410-3989.

E-Mail: hamfest@totrbsbbs.radio.org
TX - ODESSA - Hamfest. West Texas ARC, Robert Jordan N5RKN, 915-335-7980. E-Mail: n5rkn@apex2000.net Web: <http://www.w5arc.org> Web: <http://nonprofit.apex2000.net/hamfest/>

NOVEMBER 7

MI - ST. JOSEPH - Hamfest. Blossomland ARA, Duane Durlinger KX8D, 616-982-0404. E-Mail: comdac@comdac.com

Web: <http://www.comdac.com/bara>
NY - POUGHKEEPSIE - Hamfest. ML Beacon ARC, Ken Akasofu KL7JCQ, 914-485-9617. E-Mail: kl7jcq@arrl.net

Web: <http://www.mhv.net/~fritzing>
PA - LINGESTOWN - Hamfest. Linglestown Fire Hall. VE testing. Talk-in: 145.470 & 146.520 simplex. Central PA Repeater Assn., Harold Baer KE3TM, 717-566-8895

WI - KAUKAUNA - Hamfest. Starlight Club. VE testing. Talk-in: 146.52 simplex. Fox Cities ARC, Chad Pennings N9PRC, 920-993-0485. E-Mail: n9prc@kb9byq.ampr.org Web: <http://www.w9zl.ampr.org>

NOVEMBER 13

AL - MONTGOMERY - State Convention. Garrett Coliseum, South LA State Fairgrounds, Federal Dr. 9am-3pm. FCC exams. Talk-in: 146.24/84, W4AP. Montgomery ARC, Phil Salley K4OZN, 334-272-7980 after 5pm CST. E-Mail: wb4ozn@worldnet.att.net

Web: <http://jschool.troyst.edu/~w4ap/>
CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

FL - MIAMI - Hamfest. Physics Parking Lot of University of Miami. Talk-in: 146.865 (-6). Flamingo Net/U of M ARC, Walt W4DWN, 305-895-0398.

FL - PORT ST. LUCIE - Hamfest. Port St. Lucie ARA, Bill Sullivan W4TSM, 561-343-0557. Web: <http://www.qsl.net/pslara>

NM - SOCORRO - Hamfest. Socorro ARA, Al Braun AC5BX, 505-835-3456.

The Events Calendar is a free service for publicizing electronic events such as amateur radio hamfests, flea markets, etc. If your organization is sponsoring an event and would like a free listing, contact us at least 60 days in advance. Include your flyer, estimated attendance, name of the person to contact, and phone number.

Complimentary issues are available upon request for distribution to your attendees. A street address for UPS is required.

While we strive for accuracy in our calendar, we can not be responsible for errors or cancellations. The information contained in this column is for the use of the readers of *Nuts & Volts* and may not be republished in any form without the written permission of T & L Publications, Inc.

All listing information should be sent to:

**Nuts & Volts Magazine
Events Calendar**
430 Princeland Court
Corona, CA 92879
Phone 909-371-8497
Fax 909-371-3052
E-mail events@nutsvolts.com

E-Mail: ac5bx@juno.com Web: <http://www.ees.nmt.edu/sara/homepage.html>

NOVEMBER 13-14

IN - FORT WAYNE - IN State ARRL Convention & Hamfest. Allen County War Memorial Coliseum Expo Center. Sat: 9am-4pm, Sun: 9am-3pm. Talk-in: 146.88-. Allen County AR Technical Society, Doug Jones N9NNT, 219-484-1314; E-Mail: djones2233@aol.com, Jim Boyer KB9IH, 219-484-3317. Web: <http://www.acarts.com>

NOVEMBER 14

IL - LITCHFIELD - Hamfest. Central IL/St. Louis Area ATV Club, Scott Millick K9SM, 217-532-3837. E-Mail: smillick@ciilnet.com

IL - PEORIA - Autonomous Sumo Robot Competition. 1pm. Central IL Robotics Club, Jim Munro. E-Mail: jimmn@xnet.com Web: <http://circ.mtco.com/contest.htm>

NY - FARMINGDALE - Hamfest. Radio Central ARC, Neil Heft KC2KY, 516-737-0019. E-Mail: nheft@ibm.net Web: <http://www.li.net/~n2mdq>

NOVEMBER 19-20

MS - OCEAN SPRINGS - Hamfest. St. Martin Community Center. Fri: 5-9pm, Sat: 8am-2pm. VEC testing Sat: 11am. Talk-in: N5OS 145.11-. West Jackson County ARC, Phil Hunsberger W9NZ, 228-872-1499. Stan Hecker N5SP, 228-875-0222

NOVEMBER 20

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

CO - GOLDEN - Hamfest. Jefferson County Fairgrounds, 15200 W. 6th Ave. 8am-2pm. VE testing. Talk-in: 144.62/145.22. Rocky Mountain Radio League, Inc., Ron Rose N0MQJ, 303-985-8692. E-Mail: n0mqj@arrl.net Web: <http://rmr.hamradios.com>

MA - NEWTONVILLE - Auction. Masonic Hall, second floor, 460 Newtonville Ave. 11am-4pm. WARA/1200 RC, Eliot Mayer W1MJ, 617-484-1089. E-Mail: W1MJ@amsat.org Web: <http://ourworld.compuserve.com/homepages/emayer/auct>

OH - GEORGETOWN - Hamfest. Grant ARC, Dorothy Silman KB8TQI, 937-446-2234. E-Mail: huggee@bright.net Web: <http://www.qsl.net/~n1djs>

NOVEMBER 20-21

FL - TAMPA - Suncoast Hamfest, FL State ARRL Convention. State Fairgrounds, Expo Hall. Florida Gulf Coast Amateur Radio Council, Jean Endicott KC4KZU, 727-525-5178. E-Mail: swaps@fgc.org Web: <http://www.fgc.org>

NOVEMBER 21

NC - BENSON - Hamfest. Johnston ARS, Doug Williams KS4TI. E-Mail: ks4ti@nceye.net Web: <http://www.jars.net>

NOVEMBER 26

NJ - FAIR LAWN - Auction. Fair Lawn ARC, John Garis N2VKY, 201-444-0885. E-Mail: jgaris@worldnet.att.net

NOVEMBER 27

IN - EVANSVILLE - Hamfest. Vanderburgh Co. 4-H Center, Fairgrounds Auditorium. 8am-2pm. EARS, Neil Rapp WB9VPG, 812-479-5741. E-Mail: earsham@aol.com Web: <http://members.aol.com/earsham>

NC - GREENSBORO - Hamfest. Greensboro Coliseum Special Events Center. GGH, 336-851-1676. Web: <http://www.sabwc.com/gsohamfest>

NOVEMBER 28

CA - SANTA ANA - Swapmeet. ACP parking lot.

COMPUTER SHOWS

AGI Shows, 317-299-8827. E-Mail: info@agishows.com <http://www.agishows.com>

Blue Star Productions 612-788-1901. <http://www.supercomputersale.com>

Computers And You, 734-283-1754. www.al-supercomputersales.com

Computer Central Shows 847-412-1900 & 1-888-296-6066. E-Mail: compcent@megsint.net www.computercentralshows.com

Five Star Productions 810-379-3333. E-Mail: jeff@fivestar www.fivestarshows.com

Georgia Mountain Productions 706-838-4827. E-Mail: gamtpro@blrg.tds.net georgiamountain.com

Gibraltar Trade Center, Inc. 734-287-2000. Taylor, MI. E-Mail: taylor@gibraltartrade.com www.gibraltartrade.com

Mary Russo 714-558-8813

IL - WHEATON - Hamfest. DuPage County Fairgrounds. GMRS of IL, Inc., 815-436-7090 or 630-393-3937
NY - PATCHOGUE - Hamfest. Mid-Island ARC, Mike Grant N2OX, 516-736-9126. E-Mail: globalcm@erols.com Web: <http://www.qsl.net/mid-islandarc/hamfest.html>

DECEMBER 1999

DECEMBER 4

AZ - MESA - Hamfest. AR Council of AZ, Mark Kesauer N7KKQ, 602-779-2722. E-Mail: arcathill@aol.com

CA - SANTEE - ARC of El Cajon Ham, Computer & Electronic Swapmeet. Santee Drive-in. 619-561-0052

FL - OKEECHOBEE - Hamfest. Okeechobee ARC, Bill Gastle. E-Mail: wgastle@okeechobee.com

GA - CLAXTON - Hamfest. Claxton ARES, John Perkins W4HYU, 912-739-4589. E-Mail: w4hyu@juno.com

LA - MINDEN - Hamfest. Minden ARA, Lowell A. "Dusty" Collins KB5WFE, 318-371-0636. E-Mail: dusty1@microgear.net Web: <http://www.microgear.net/gwinford/mara.htm>

DECEMBER 5

IN - GREENFIELD - Hamfest. Greenfield Central High School Pavilion, N. Broadway St. Talk-in: 145.330, 444.725. Hancock ARC, Tom Donaldson N9LFU, 317-326-3168. E-Mail: tomd@freewwwweb.com Web: <http://www.iei.net/~n9hgo>

DECEMBER 11

CA - FONTANA - Inland Empire ARC Amateur Radio & Electronics Swapmeet. A B Miller High School. Bill 909-822-4138 eves

DECEMBER 18

CA - SANTEE - ARC of El Cajon Ham, Computer

Gibraltar Trade Center, Inc. 810-465-6440. Mt. Clemens, MI. E-Mail: mtclemens@gibraltartrade.com www.gibraltartrade.com

KGP Productions 1-800-631-0062, 732-297-2526. E-Mail: kgp@mail.com

MarketPro, Inc., 201-825-2229. <http://www.marketpro.com>

MarketPro, Inc., 301-984-0880. E-Mail: md@marketpro.com <http://marketpro.com>

Narisaam Computer Show 770-663-0983. E-Mail: narisaam@aol.com Web: <http://www.showsale.com>

Northern Computer Shows 978-744-8440. E-Mail: inquiries@ncshows.com Web: ncshows.com

Peter Trapp Computer Shows 603-272-5008. Web: www.petertrapp.com

& Electronic Swapmeet. Santee Drive-in. 619-561-0052

JANUARY 2000

JANUARY 7-8

FL - GAINESVILLE - Hamfest. Alachua County Fairgrounds, SR-222 (3400 NE 39th Ave.), 1/2 mi. E. of SR-24 (Waldo Rd.). Talk-in: 146.820 (-). Gainesville ARS, Tom Scott KF4I, 352-378-9711 eves. E-Mail: k4gnv@arrl.net Web: <http://www.gars.net/hamfest/>

JANUARY 8

IN - SOUTH BEND - Hamfest. Michiana Valley Hamfest Assn., Bob Denniston KA9WNR, 219-291-0252
WI - WAUKESHA - Hamfest. Waukesha Co. Expo Center Forum. 8am-2pm. VE exams. West Allis RAC, Phil Gural W9NAW, 414-425-3649.

JANUARY 8-9

FL - FT. MYERS - Hamfest. Ft. Myers ARC, Doug Douglas N8SAQ, 941-542-4741. E-Mail: douglas2@illine.com

JANUARY 15

LA - HAMMOND - Hamfest. South East LA ARC, Nathan Gifford N5BFC, 504-465-7522. E-Mail: n5bfc@arrl.net Web: <http://www.selarc.org/selarcchamfest.html>

MO - ST. JOSEPH - Hamfest. MO Valley & Ray-Clay ARCs, Kevin R. Phillips KC0AWM, 816-320-2129. E-Mail: KevinRPhillips@hotmail.com Web: <http://www.kc.net/~oconnor>

JANUARY 15-16

FL - SARASOTA - Hamfest. Sarasota ARA, William Eddie Martin KI4ZJ, 941-954-1869. E-Mail: ki4zj@msn.com Web: <http://www.saraclub.org>

JANUARY 16

MI - HAZEL PARK - Hamfest. High School,

Events CALENDAR

23400 Hughes St. 8am-2pm. Talk-in: 146.64 (-).
HPARC, Tom Krausnick WC9F, E-Mail:
wc9f@arri.org Web: <http://www.qsl.net/w8hp>
NY - YONKERS - Flea Market. Lincoln High
School, Kneeland Ave. 9am-3pm. VE Exams.
Talk-in: 440.425 PL 156.7, 223.760 PL 67.0,
146.910, 443.350 PL 156.7. Metro 70cm Network,
Otto Supliski WB2SLQ, 914-969-1053.
E-Mail: wb2slq@juno.com
Web: <http://www.metro70cmnetwork.com>

JANUARY 22

FL - BROOKSVILLE - Hamfest. Hernando
County Fairgrounds. 9am-4pm. Hernando County
ARA, John Nedjedlo WB4NOD, 727-856-2568.
E-Mail: wb4nod@gate.net
FL - PENSACOLA - Hamfest. University of West
FL ARC, Ray Killough KE4UNR, 850-968-1048.
E-Mail: ke4unr@spydee.net
Web: <http://qso.arc.uwf.org/~hamfest>

MO - ST. CHARLES - Hamfest. St. Louis
Repeater, Brad Ziegler KC0CDG, 314-569-5775.
E-Mail: kc0cdg@qsl.net
NC - WINSTON-SALEM - Hamfest. Forsyth ARC,
John Kippe N0KTY, 336-723-7388. Web:
<http://members.xoom.com/w4nc/hamfest.htm>

NH - NASHUA - Hamfest. Res Ctr Church. NE
Antique RC 617-923-2665

JANUARY 29

AL - GREENVILLE - Hamfest. Butler County
Fairgrounds. 8am-3pm. Talk-in: 146.67 or 145.19.
Butler County & Pike County RACES, Jerry
McCullough KE4ERO, 334-382-7644.
E-Mail: KE4ERO@alaweb.com

JANUARY 30

MD - ODENTON - Hamfest. MD Mobileers ARC,
William Hampton N3WQM, 410-766-2199.
E-Mail: diamondb@space4less.com
Web: www.space4less.com/usr/mmamc
OH - DOVER - Hamfest. Tusco ARC, Billy Harper
KB8CQG, 330-484-4634.
E-Mail: bharper@neo.rr.com

FEBRUARY 2000

FEBRUARY 5

MI - NEGAUNEE - Hamfest. Hiawatha ARA, Bill
Beitel N8NRG, 906-226-2779.
E-Mail: n8nrg@portup.com
SC - NORTH CHARLESTON - Hamfest.
Charleston ARS, Jenny Myers WA4NGV, 843-747-
2324. E-Mail: brycemyers@aol.com
Web: <http://www.qsl.net/wa4usn/index.html>

FEBRUARY 5-6

FL - MIAMI - Southeastern Division Convention.
Dade Radio Club, Evelyn Gauzens W4WYR, 305-
642-4139. E-Mail: w4wyr@bellsouth.net
Web: <http://www.hamboree.org>

FEBRUARY 11-12-13

FL - ORLANDO - State Convention. Orlando
ARC, Ken Christensen KD4JQR, 407-291-2465.
E-Mail: KD4JQR@Juno.Com
Web: <http://www.oarc.org/hamcat.html>

FEBRUARY 19

AR - RUSSELLVILLE - Hamfest. AR River Valley
AR Foundation, Jonathan Setcer KC5BRY, 501-
968-2938. E-Mail: hamfest@setcer.com

FEBRUARY 26

VT - MILTON - NVT Winter Hamfest. High School,
Rt. 7. Mitch Stern W1SJ, 802-879-6589. E-Mail:
w1sj@arri.net Web: <http://www.ranv.together.com>

FEBRUARY 27

FL - ZEPHYRHILLS - Hamfest. Zephyrhills ARC,
Ernie Vanselow KD4VRV, 813-783-8389
E-Mail: kd4vrv@gte.net
VA - ANNANDALE - Hamfest. Vienna Wireless
Society, Mike Toia K3MT, 703-757-7021.
E-Mail: k3mt@erols.com
Web: <http://www.erols.com/k3mt/vws>

MARCH 2000

MARCH 4-5

FL - NEW PORT RICHEY - Hamfest. Gulf Coast
ARC, Rickie Brown KF4QXS, 727-863-1457. E-
Mail: richar@gte.net. Don KK4VK, 727-848-8000.
Web: <http://homel.gte.net/koerner/gcsrc.htm>

MARCH 5

NY - LINDENHURST - Hamfest. GSBARC &
SCRC, Lenore N2KYP, 516-785-0826. E-Mail:
info@gsbarc.org Web: <http://www.gsbarc.org>

MARCH 11

WA - PUVALUP - Hamfest. Mike & Key ARC,
Michael Dinkelman N7WA, 253-631-3756 or 425-
867-4797. E-Mail: mwdink@eskimo.com

MARCH 11-12

NC - CHARLOTTE - Charlotte Hamfest and
Computerfair. Mecklenburg Amateur Radio

Society.

MARCH 12

PA - YORK - Hamfest. Keystone VHF Club, Dick
Goodman WA3USG, 717-697-2353.
E-Mail: wa3usg@compuserve.com
Web: <http://members.aol.com/yorkfest>
WI - WAUKESHA - Hamfest. County Expo
Center, N.1 W.24848 N. View Rd. 8am-2pm. Talk-
in: 146.820 PL 127.3. SEWFARS ARC, John
Breecher, 414-835-7035

MARCH 17-18

GA - MARIETTA - Hamfest. Kennehochee ARC,
Charles Golsen N4TZM, 404-252-3303.
E-Mail: cgolsen@atlanta.com

MARCH 18

FL - STUART - Hamfest. Martin County ARA,
Romund Madson KS4KM, 561-337-1841
NJ - NORTH HUNTERDON - Hamfest.
Cherryville Repeater Assn., Marty Grozinski
W2CG, 908-788-2644 or 908-730-2771.
E-Mail: w2cg@arri.net
WV - CHARLESTON - Hamfest. Jimmie Hewlett
WD8MKS, 304-768-1142

MARCH 18-19

TX - MIDLAND - West Texas ARRL Section
Convention, Beverley Harwood KC5BNT, 915-686-
1841. E-Mail: shamrock@apex2000.net
Web: <http://www.lxnet/edge/midswap.htm>

MARCH 19

OH - MAUMEE - Hamfest. Lucas County
Recreation Center, 2901 Key St. 8am-2pm. Talk-
in: 147.27+ or 442.85+. Toledo Mobile RA, Paul
Hanslik, 419-385-5056.
Web: www.tmrhamradio.org

MARCH 25-26

MD - TIMONIKUM - Greater Baltimore Hamboree
& Computerfest/MD State ARRL Convention.
Timonium Fairgrounds, York Rd. Sat: 8am-5pm,
Sun: 8am-4pm. VE Exams. Baltimore ARC,
Sharon Dobson N3QQC, 410-HAM-FEST or 800-
HAM-FEST. E-Mail: n3qqc@amsat.org
Web: <http://www.gbhc.org>

APRIL 2000



LEVITRON

"The Amazing Anti-Gravity Top"

This spinning top floats in mid air, supported by opposing magnetic forces. Includes floating top, levitron magnetic base, assortment of adjustment weights, lifter plate, levelling shims, and instructions. It takes some practice and a lot of patience to keep the top afloat, but the results are truly amazing! Levitron Floating Top \$39.95



AMAZING MINI MICRO FM RADIO! \$7.50

Much lighter than a heavy jam box with really good sound! This tiny radio (1.5"x1.06"x0.38") has a seek button, reset control, and an on/off switch. Personal listening has never sounded better! Ideal for ballgames, studyhall, and workouts. Battery and nugget style earphones included.



RF DETECTION DISK \$15.00

Are you being bugged? Curious about the RF near your radios? Ever wonder how much wave you get from your microwave? This little unit illuminates into blinking mode when near any RF. Cell phones, PCS phones, cordless phones, hand held transceivers - they all activate the detection disk. (Don't worry, your unit in standby mode won't activate the disk - transmissions and incoming calls cause it to blink!) Compact RF disk can be worn on a neck chain, attached to your key ring, hung from your rear view mirror, or shoved in your pocket until you want to use it! Detects RF 1 Mhz to 2.5 Ghz, and is only activated at close range. Uses a CR-2032 battery - yes, it is included! (Light may be hard to see in bright areas.)

PHOTON II MICROLIGHT

The popular photon microlight has been improved. These super-bright (better than 8 candellas!) LED lights are visible over a mile away. The LED is secured in a tough ABS case and offers a squeeze button for quick use, and a constant on slide switch for prolonged lighting needs. The lithium batteries last a very long time (10 year shelf life!) and are included. The light won't burn out because it is an LED! Specify your choice of five incredible bright colors. Great for home or office use, popular with fire and rescue professionals, pyrotechnicians, stage performers, and dimly lit restaurant patrons. PHOTON II microlights include a keyring and come in ruby red (\$13.50), amber yellow (\$13.50) orange (\$13.50), sapphire blue (\$17.50), diamond white (\$17.50), turquoise (\$17.50), and emerald green (\$17.50). Includes two replaceable 2016 lithium batteries.



mini keyboard \$10.00
A very small computer keyboard (measures less than 5-3/4" x 9-3/4") that takes up minimal desk space. Uses a PS2 connector, and keyboard enclosure is black. Great for applications requiring a complete keyboard in a limited space, and an ideal solution for those wanting something lightweight and compact for transporting. Great for home or work applications! optional keyboard adapter: PS2 to 5 pin DIN \$3.95



Geophone

vibration sensing kit

Detect a fly stomping across the desk! Well maybe not that sensitive, but almost. These vibration sensors made by Geosource® were used in oil exploration to determine geological statistics. They are made with a magnet suspended in a coil and are very sensitive to vibration. Compact size, the unit measures approx. 1.6" high and 1.2" dia. The kit includes a geophone vibration sensor along with parts to build a basic detector that will light an LED. In addition we include a schematic that will show you how to operate a relay. The sensitivity is adjustable, so you can set it to detect elephants and other small creatures. Similar units were used by our armed forces to detect enemy troop movements...the perfect device to alert you to the pitter patter of little Leroy's feet! Unit sensitivity can be set high enough to detect a business card dropped on a table, and we've made it work with vibrations up to 40 feet away! Earthquake or Aunt Agatha...you decide! It's a fun gadget with many uses. COMPLETE GEOSOURCE KIT...\$9.95 GEOSOURCE UNIT ONLY...\$7.95

Lighted Screwdriver Supertool! \$9.95

At first glance, this appears to be an ordinary screwdriver, but press a button on the base and two lights illuminate the area you are working on. Nifty, huh? But wait, there's more! The seven interchangeable bits are stored right there at the base of the screwdriver (6 storage slots) for easy access. No handles to unscrew or tool boxes to dig through. Hey, you ain't seen nothin' yet...remove the bit and the magnetic retrieval tool telescopes from the screwdriver shaft! Incredible!!! Of course, the comfort grip handle and rugged construction are icing on the cake! Definitely a 'gotta have it' tool!

www.gatewayelec.com



8123 PAGE BLVD * ST. LOUIS, MO 63130 * (314)427-6116
9222 CHESAPEAKE DR. * SAN DIEGO, CA 92123 * (619)279-6802
2525 FEDERAL BLVD. * DENVER, CO 80211 * (303)458-5444
MAIL ORDERS CALL TOLL-FREE 1-800-669-5810
FAX ORDERS (314)427-3147

rv1099

ANIMAL SOUNDS PIANO KIT \$29.95
This of the sounds project kit has ten keys for playing notes scale and eight buttons to select the associated with each note. Select the piano mode and the kit will synthesize piano sounds for each key. OR select one of seven different animal voices including cat, dog, pig, bird, chicken, duck, and sheep. Old MacDonald never had a choir like this! The circuit features an auto power-off function, a demo mode, and easy step-by-step instructions. Requires 2 AA batteries not included.

Passive Infra-red Talking Motion Detector III! \$27.50

"Stay out of that refrigerator!", "Watch your step!", "Do your homework", "Don't touch that remote!" ... The possibilities are mind-boggling with this talking motion detector. You speak into it to record your message (upto 12 seconds long), turn the unit on, and instantly your voice (or your mother-in-laws) reminds anyone in the vicinity that you were expecting them. Message can be changed with the flip of a switch. Uses 4 AA batteries (not included), or an external power source (built-in jack). May be used independently (80 db output) or with an amplified speaker to blast your message throughout the house. Approx 4"x 3-1/2"x 1-1/2".

THE FINE PRINT - PRICES SUBJECT TO CHANGE WITHOUT NOTICE * GATEWAY IS NOT RESPONSIBLE FOR PRINTING ERRORS * MASTERCARD, VISA AND DISCOVER ACCEPTED * YES, WE'LL TAKE YOUR CHECK - SORRY, NO C.O.D.'s * \$10 MERCHANDISE MINIMUM ON MAIL ORDERS * SUPPLY OF SOME ITEMS IS LIMITED * PRICES DO NOT INCLUDE SHIPPING * UPS GROUND SHIPPING/HANDLING WITHIN THE CONTINENTAL U.S. (ITEMS REQUIRING ADDITIONAL AMOUNTS ARE NOTED)...\$5.00 FOR THE FIRST ITEM, \$0.50 FOR EACH ADDITIONAL ITEM. RESTOCKING CHARGE MAY BE ASSESSED ON RETURNED ITEMS. * Why doesn't glue stick to the inside of the bottle?



Events CALENDAR

APRIL 2

CT - SOUTHTON - Hamfest. Southington ARC, Chet Bacon KA1ILH, 860-628-9346. E-Mail: chet@chetbacon.com
Web: <http://www.chetbacon.com/sara.html>
NC - KINSTON - Hamfest. Down East Hamfest Assn., Doug Burt W4OFO, 252-524-5724

APRIL 8

WA - SPOKANE - Hamfest. Lilac City ARC, Warren Kelsey KJ7BB, 509-534-8443

APRIL 9

NC - RALEIGH - State Convention. Raleigh ARC, Chuck Littlewood K4HF, 919-872-6555. E-Mail: k4hf@arrl.net Web: <http://www.rars.org>
WI - STOUTTOWN - Hamfest. Madison Area

Repeater Assn., Paul Toussaint N9VWH, 608-245-8890. E-Mail: n9vwh@arrl.net

APRIL 15

AL - ALBERTVILLE - Hamfest. Marshall County ARC, Buddy Smith KC4URL, 256-593-2516. E-Mail: kc4url@airnet.net

APRIL 16

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>
MI - GROSSE POINTE - Hamfest. South Eastern MI ARA, Jerry Rosner N8FGK, 313-331-3336. E-Mail: n8fgk@amsat.org

APRIL 21-22

AR - LITTLE ROCK - Little Rock Hamfest, Jim Blackmon K5VZ, 870-246-7833 (h) or 870-246-6734 (w). Fax: 870-246-6736. E-Mail: lrhamfest@usa.net
Web: <http://www.aristotle.net/~ares/hamfest/>

APRIL 22

NH - NASHUA - Hamfest. Res Ctr Church. NE Antique RC 617-923-2665

APRIL 29

AL - MOULTON - Hamfest. Bankhead ARC, Web: <http://www.n4idx.org>
IA - DES MOINES - Hamfest. Des Moines RAA, Duane Bower WB0UCY, 515-287-6542. E-Mail: duaneab@uswest.net

MAY 2000

MAY 6

WI - CEDARBURG - Hamfest. Ozaukee RC, Joe Holly AA9HR, 262-377-2137; E-Mail: aa9hr@execpc.com. Skip Douglas, 262-284-3271

MAY 6-7

AL - BIRMINGHAM - Hamfest. Glenn Glass KE4YZK, 205-681-5019. E-Mail: ke4yzk@bellsouth.net Web: <http://www.bro.net/barc/slideshow/index.html>

MAY 7

MD - HAGERSTOWN - Hamfest. Antietam Radio Assn., Tina Jones KB8ZQM, 304-728-7769. E-Mail: kb8zqm@intrepid.net
Web: <http://www.qsl.net/w3cwc>
NY - YONKERS - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053. E-Mail: wb2slq@juno.com
Web: <http://www.metro70cmnetwork.com>

MAY 12-13

NH - ROCHESTER - Hamfest. Fairgrounds. Hoss Traders, Joe, 207-469-3492

MAY 19-20-21

OH - DAYTON - ARRL National Convention. Dayton ARA, Dave Coons, WT8W, 937-849-0604. E-Mail: wt8w@arrl.org
Web: <http://www.hamvention.org>

MAY 21

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

MAY 27-28

WY - CASPER - State Convention. Casper ARC, Warren (Rev) Morton WS7W, 307-235-2799 or 307-237-9301. E-Mail: mortonwg@aol.com
Web: <http://w3.trib.com/~carc/hamfest.html>

JUNE 2000

JUNE 2-3-4

NY - ROCHESTER - Atlantic Division ARRL Convention. Harold Smith K2HC, 716-424-7184. E-Mail: rochfst@frontiernet.net
Web: <http://www.rochesterhamfest.org>

JUNE 3-4

OR - SEASIDE - Northwestern Division ARRL Convention. Convention Center. VE testing. Talk-in: 146.660 (-600). Randy Stinson K27T, 503-297-1175

JUNE 4

VA - MANASSAS - Hamfest. Ole Virginia Hams ARC, Jack McDermott N4YIC, 703-330-7987. E-Mail: N4YIC@arrl.net or patnjack@erols.com
Web: <http://www.qsl.net/olevahams/>

JUNE 10

NC - WINSTON-SALEM - Hamfest. Forsyth ARC, John Kippe N0KTY, 336-723-7388. Web: <http://members.xoom.com/w4nc/hamfest.htm>
PA - BLOOMSBURG - Eastern PA Section Convention. Columbia-Montour ARC, George Law N3KYZ, 570-784-2299. E-Mail: n3kyz@epix.net
Web: <http://www.bafn.org/~cmarc>

JUNE 11

IL - WHEATON - Hamfest. Six Meter Club of Chicago, Joseph Gutwein WA9RIJ, 630-963-4922 or 708-442-4961. E-Mail: wa9rij@mc.net
Web: <http://cyberconnect.com/orion/smcc.html>

JUNE 18

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 & 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

JULY 2000

JULY 7-8-9

UT - BRYCE CANYON - State Convention. UT Hamfest Committee, Kathy Rudnicki N7JSH, 801-547-9218

JULY 8

GA - GAINESVILLE - State Convention. Lanierland ARC, Ken Johnson N24Q, 706-335-9658. E-Mail: nz4q@aol.com
MO - KANSAS CITY - Hamfest. PHD ARA, Bob Roske WA0CLR, 816-436-0069. E-Mail: wa0clr@worldnet.att.net
Web: <http://members.tripod.com/~PHDARA/>

JULY 9

Roger's Systems Specialist

24895 Avenue Rockefeller
Valencia California 91355

"We Have Great Connections"

Computer • Telecommunications
Network • Audio • Video

www.rogerssystems.com

Category 5 Patch Cable

TE-038-L5	3ft. Straight Patch	\$1.75
TE-068-L5	7 ft. Straight Patch	\$2.00
TE-128-L5	14ft. Straight Patch	\$4.00
TE-258-L5	25ft. Straight Patch	\$5.00
TE-358-L5	35ft. Straight Patch	\$7.00
TE-508-L5	50 ft. Straight Patch	\$10.00
TE-758-L5	75ft. Straight Patch	\$17.00
TE-108-L5	100 ft. Straight Patch	\$20.00

USB Cables

CC-USB-6	6ft. USB "A" to "A" M/M	\$5.00
CC-USB-AB6	6ft. USB "A" to "B" M/M	\$5.00
CC-USB-PP	6ft. USB to IEEE Printer Cable	\$29.00
CC-USB-AB10	10ft.USB "A" to "B" M/M	\$6.00
CC-USB-AB15	15ft.USB "A" to "B" M/M	\$8.00
CC-USB-X10	10ft. USB Extension	\$6.00

USB Accessories

CC-USB-8	USB (2) to 2x8 pin w/ Bracket	\$5.00
CC-USB-9	USB (2) to 2x5 pin w/ Bracket	\$5.00
USB-PCI	USB x2 PCI Add on Card	\$27.00
USB-KB-104	USB 104-Key Kybrd Win98/PS2	\$24.00
USB-MOUSE	3-Button USB Mouse 4200dpi	\$12.00
USB-CAM	C-IT USB Cam w/ Software	\$69.00

Network Cards

NT-TBT-10	10-Base 16Bit ISA Slot Card	\$12.00
NT-TBT-100	10/100 32-Bit PCI Slot	\$19.00
NT-TBT-200	10-Base 32-Bit PCI Slot	\$12.00
NT-TBT-3C905B	3COM 3C905B-TX 10/100 PCI	\$62.00
NT-8460B	INTEL Pro+ 10/100 Express	\$55.00

External SCSI Case

TM-CASE-HDS \$15.00

Limited to stock on hand

50 Pin centronics pass through connector
Push button I.D. setting, On/Off switch
Internal Fan, 50P Ribbon, 30watt Power Supply



Acer

KEYBOARD & MOUSE

KB-449	Acer PS/2 Win. Keyboard	\$8.00
TM-290-PS	Acer PS/2 2-button 6pin din	\$5.00

**COMBO
BOTH FOR \$12.00**



Acer

\$10.00

cat. no. TM-177

ACER AMPLIFIED SPEAKER SET W/
CABLES & POWER SUPPLY

Patch Panels

PP-24P-5	24 Port Cat5 Patch Panel	\$59.00
PP-48P-5	48 Port Cat5 Patch Panel * SPECIAL *	\$79.00
PP-12P-5	12 Port Cat5 Patch Panel	\$42.00
PP-64P-5	64 Port Cat5 Patch Panel	\$255.00

All Category 5 568B Wiring

- \$20.00 min. order required
- Add \$4.50 shipping for prepaid orders
- Prices subject to change without notice
- All major credit cards accepted
- Special offers only valid on items in stock
- California residents add tax
- Call for quantity discounts
- No out of state checks accepted

800-366-0579 661-295-5577 Fax 661-295-8777

Events CALENDAR

IL - PEOTONE - Hamfest. Kankakee Area Radio Society, Don Kerouac K9NR, 815-939-7548. E-Mail: k9nr@juno.com Web: <http://www.w9az.com>

JULY 16

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 G 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

MO - WASHINGTON - Hamfest. Zero Beaters ARC, Dave Neal N0PNC, 314-532-2477 (days) or 314-458-3254 (eve). E-Mail: Dave_Neal@msc.com Web: <http://zbarc.usmo.com/>

PA - KIMBERTON - Hamfest. Mid-Atlantic ARC, Bill Owen W3KRB, 610-325-3995. E-Mail: gem@op.net Web: <http://www.marc.org/hamfest.html>

JULY 22

NH - NASHUA - Hamfest. Res Ctr Church. NE Antique RC 617-923-2665

JULY 29-30

OK - OKLAHOMA CITY - State Convention. Central OK Radio Amateurs, Harold Miller KB1ZQ, 405-672-7735 or 405-650-9963. E-Mail: n1lpn@swbell.net Web: <http://www.geocities.com/heartland/7332>

JULY 30

OH - RANDOLPH - Hamfest. Portage ARC, Joanne Solak KJ30, 330-274-8240. E-Mail: jsolak@apk.net

AUGUST 2000

AUGUST 5

OH - COLUMBUS - Hamfest. Voice of Aladdin ARC, James Morton KB8KPJ, 614-846-7790. E-Mail: kb8kpj@cs.com

AUGUST 12

IL - QUINCY - Hamfest. Western Illinois ARC, Jim Funk, N9JF, 217-336-4191. E-Mail: jfunk@adams.net Web: <http://www.qsl.net/w9awe>

AUGUST 13

IA - AMANA - Hamfest. Cedar Valley ARC, Wayne Kolosik, K10FE, 319-393-4224. E-Mail: k10fe@usa.net
IN - GREENTOWN - Hamfest. Kokomo & Grant County ARCs, L.B. (Nick) Nickerson KA6NQW, 765-668-4814. E-Mail: ka6nqwnick@netusa1.net Web: <http://www.netusa1.net/~ka6nqwnick/hamfest.html>

AUGUST 20

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 G 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

AUGUST 26-27

MA - BOXBORO - NE Division ARRL Convention. Dave W1TQ, 978-649-3907

AUGUST 27

NY - YONKERS - Hamfest. Yonkers ARC, John Costa WB2AUL, 914-969-6548. E-Mail: wb2aul@aol.com

SEPTEMBER 2000

SEPTEMBER 17

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 G 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

SEPTEMBER 23

NY - HAMBURG - Western NY ARRL Section Convention. Harold Smith K2HC, 716-424-7184. E-Mail: info@buffalohamfest.org Web: <http://www.buffalohamfest.org>

SEPTEMBER 24

NY - YONKERS - Flea Market. Lincoln High School, Kneeland Ave. 9am-3pm. VE Exams. Talk-in: 440.425 PL 156.7, 223.760 PL 67.0, 146.910, 443.350 PL 156.7. Metro 70cm Network, Otto Supliski WB2SLQ, 914-969-1053. E-Mail: wb2slq@juno.com Web: <http://www.metro70cmnetwork.com>

OCTOBER 2000

OCTOBER 6-7

NH - ROCHESTER - Hamfest. Fairgrounds. Hoss Traders, Joe, 207-469-3492

OCTOBER 6-7-8

AZ - SCOTTSDALE - Southwestern Div. Convention. Scottsdale ARC, Walt Schuknecht

N7IZM, 480-947-0338. E-Mail: n7izm@arri.net

OCTOBER 15

MA - CAMBRIDGE - Flea at MIT. Albany and Main Sts. 9am-2pm. Talk-in: 146.52 G 449.725/444.725 W1XM/R PL 114.8 (2A). Nick Altenbernd KA1MQX, 617-253-3776 (9-5). Web: <http://web.mit.edu/w1mx/www/swapfest.html>

OCTOBER 21

NH - NASHUA - Hamfest. Res Ctr Church. NE Antique RC 617-923-2665

OCTOBER 29

NY - LINDENHURST - Hamfest. GSBARC & SCRC, Lenore Dunlop N2KYP, 516-785-0826. E-Mail: info@gsbarc.org Web: <http://www.gsbarc.org>

Subscribe to Nuts & Volts.
Check out our web site and take advantage of our special subscription offer.
<http://www.nutsvolts.com>
For new subscribers OR renewals!



Cool Wireless Goodies

World's Smallest TV Transmitters



We call them the 'Cubes'.... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency drift with performance that equals law enforcement models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Audio units include sound using a sensitive built-in mike that will hear a whisper 15 feet away! Units run on 9 volts and hook-up to most any CCD camera. Any of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air! These are the units that are being built into hats, papers, cigarette packs and sold for big \$\$!!
C-2000, Basic Video Transmitter.....\$89.95 C-3000, Basic Video & Audio Transmitter.....\$149.95
C-2001, High Power Video Transmitter.....\$179.95 C-3001, High Power Video & Audio Transmitter.....\$229.95

CCD Video Cameras



Top quality Japanese Class 'A' CCD array, over 440 line resolution, not the off-spec arrays that are found on many other cameras. Don't be fooled by the cheap CMOS single chip cameras which have 1/2 the resolution, 1/4 the light sensitivity and draw over twice the current! The black & white models are also super IR (Infra-Red) sensitive. Add our invisible to the eye, IR-1 illuminator kit to see in the dark! Color camera has Auto gain, white balance, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. Run on 9 VDC, standard 1 volt p-p video. Use our transmitters for wireless transmission to TV set, or add our IB-1 Interface board kit for audio sound pick-up and super easy direct wire hook-up to any Video monitor, VCR or TV with AV input. Fully assembled, with pre-wired connector.

CCDWA-2, B&W CCD Camera, wide-angle lens\$69.95
CCDPH-2, B&W CCD Camera, slim fit pin-hole lens.....\$69.95
CCDC-1, Color CCD Camera, wide-angle lens\$129.95
IR-1, IR Illuminator Kit for B&W cameras\$24.95
IB-1, Interface Board Kit\$14.95

Mini Radio Receivers



Imagine the fun of tuning into aircraft a hundred miles away, the local police/fire department, ham operators, or how about Radio Moscow or the BBC in London? Now imagine doing this on a little radio you built yourself - in just an evening! These popular little receivers are the nuts for catching all the action on the local ham, aircraft, standard FM broadcast radio, shortwave or WWV National Time Standard radio bands. Pick the receiver of your choice, each easy to build, sensitive receiver has plenty of crystal clear audio to drive any speaker or earphone. Easy one evening assembly, run on 9 volt battery, all have squelch except for shortwave and FM broadcast which has handy SCA output. Add our snazzy matching case and knob set for that smart finished look.

AR-1, Airband 108-136 MHz Kit\$29.95
HFRC-1, WWV 10 MHz (crystal controlled) Kit\$34.95
FR-1, FM Broadcast Band 88-108 MHz Kit\$24.95
FR-6, 6 Meter FM Ham Band Kit\$34.95
FR-10, 10 Meter FM Ham Band Kit\$34.95
FR-146, 2 Meter FM Ham Band Kit\$34.95
FR-220, 220 MHz FM Ham Band Kit\$34.95
SR-1, Shortwave 4-11 MHz Band Kit\$29.95
Matching Case Set (specify for which kit)\$14.95

Touch-Tone Reader



Read touch-tone numbers from any radio, phone line, tape recorder - any audio source! Decoder called numbers on scanners, radio shows, anywhere touch-tones are used. Memory stores up to 256 digits, an 8 digit display window scrolls anywhere in memory. Memory good for 100 years, even with power off! Runs on 7 to 15 VDC. Available in kit form with optional matching case set or fully assembled in case set. We sell tons of these to private investigators!

TG-1, Tone-Grabber Touch Tone Reader Kit\$99.95
CTG, Case for Tone-Grabber Touch Tone Reader\$14.95
TG-1WT, Tone-Grabber, fully assembled with case\$149.95
AC12-5, 12 Volt DC Wall Plug Adapter\$9.95

Order Toll-free: 800-446-2295

Sorry, no tech info, or order status at 800 number

For Technical Info, Order Status
Call Factory direct: 716-924-4560

Super Pro FM Stereo Transmitter



Professional synthesized FM Stereo station in easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set freq with Up/Down buttons, big LED display. Input low pass filter gives great sound (no more squeals or swishing from cheap CD inputs!) Limiters for max 'punch' in audio - without over mod. LED meters to easily set audio levels, built-in mixer with mike, line level inputs. Churches, drive-ins, schools, colleges find the FM-100 the answer to their transmitting needs, you will too. Great features, great price! Kit includes cabinet, whip antenna, 120 VAC supply. We also offer a high power export version of the FM-100 that's fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped outside the USA, or within the US if accompanied by a signed statement that the unit will be exported.
FM-100, Pro FM Stereo Transmitter Kit\$249.95
FM-100WT, Fully Wired High Power FM-100.....\$399.95

Tiny Transmitters



Gosh, these babies are tiny - that's a quarter in the picture! Choose the unit that's best for you. FM-5 is the smallest tunable FM transmitter in the world, picks up a whisper 10' away and transmits up to 300'. Runs on tiny included watch battery, uses SMT

parts. FM-4 is larger, more powerful, runs on 5-12 volts, goes up to a mile. FM4.5 operate in standard FM band 88-108 MHz. FM-6 is crystal controlled in 2 meter ham band, 146.535 MHz, easily picked up on scanner or 2 meter rig, runs on 2 included watch batteries. SMT (surface mount) kits include extra parts in case you sneeze & loose a part!
FM-4MC, High Power FM Transmitter Kit\$17.95
FM-5, World's Smallest FM Transmitter Kit\$19.95
FM-6, Crystal Controlled 2M FM Transmitter Kit ...\$39.95
FM-6, Fully Wired & Tested 2M FM Transmitter\$69.95

AM Radio Transmitter



Operates in standard AM broadcast band. Pro version, AM-25, is synthesized for stable, no-drift frequency and is settable for high power output where regulations allow, typical range of 1-2 miles. Entry-level AM-1 is tunable, runs FCC maximum 100 mw, range 1/4 mile. Both accept line-level inputs from tape decks, CD players or mike mixers, run on 12 volts DC. Pro AM-25 includes AC power adapter, matching case and bottom loaded wire antenna. Entry-level AM-1 has an available matching case and knob set that dresses up the unit. Great sound, easy to build - you can be on the air in an evening!
AM-25, Professional AM Transmitter Kit\$129.95
AM-1, Entry level AM Radio Transmitter Kit\$29.95
CAM, Matching Case Set for AM-1.....\$14.95

RAMSEY ELECTRONICS, INC.

793 Canning Parkway Victor, NY 14564

See our complete catalog and order on-line with our secure server at:

www.ramseyelectronics.com

Doppler Direction Finder



Track down jammers and hidden transmitters with ease! This is the famous WA2EBY DF'er featured in April 99 QST. Shows direct bearing to transmitter on compass style LED display, easy to hook up to any FM receiver. The transmitter - the object of your DF'ing - need not be FM, it can be AM, FM or CW. Easily connects to receiver's speaker jack and antenna, unit runs on 12 VDC. We even include 4 handy home-brew "mag mount" antennas and cable for quick set up and operation! Whips can be cut and optimized for any frequency from 130-1000 MHz. Track down that jammer, win that fox hunt, zero in on that downed Cessna - this is an easy to build, reliable kit that compares most favorably to commercial units costing upwards of \$1000.00! This is a neat kit!!
DDF-1, Doppler Direction Finder Kit\$149.95

FM Stereo Radio Transmitters

No drift, microprocessor synthesized! Excellent audio quality, connect to CD player, tape deck or mike mixer and you're on-the-air. Strappable for high or low power! Runs on 12 VDC or 120 VAC. Kit includes case, whip antenna, 120 VAC power adapter - easy one evening assembly.
FM-25, Synthesized Stereo Transmitter Kit\$129.95

Lower cost alternative to our high performance transmitters. Great value, easily tunable, fun to build. Manual goes into great detail about antennas, range and FCC rules. Handy kit for sending music thru house and yard, ideal for school projects too - you'll be amazed at the exceptional audio quality! Runs on 9V battery or 5 to 15 VDC. Add our matching case and whip antenna set for nice 'pro' look.
FM-10A, Tunable FM Stereo Transmitter Kit\$34.95
CFM, Matching Case and Antenna Set\$14.95
FMAC, 12 Volt DC Wall Plug Adapter.....\$9.95

FM Station Antennas



For maximum performance, a good antenna is needed. Choose our very popular dipole kit or the Comet, a factory made 5/8 wave colinear model with 3.4 dB gain. Both work great with any FM receiver or transmitter.
TM-100, FM Antenna Kit\$39.95
FMA-200, Vertical Antenna\$114.95

RF Power Booster



Add muscle to your signal, boost power up to 1 watt over a freq range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat finished look, add the nice matching case set.
LPA-1, Power Booster Amplifier Kit\$39.95
CLPA, Matching Case Set for LPA-1 Kit\$14.95
LPA-1WT, Fully Wired LPA-1 with Case\$99.95

Dinky Radios



Everyone who sees one of these babies says they just gotta have one! Super cute, tiny (that's a Quarter in the picture!) FM radios have automatic scan/search tuning, comfortable ear bud earphones and we even include the battery. The pager style unit looks like a shrunken pager and even has an LCD clock built-in. The crystal clear sound will amaze you! Makes a great gift.
MFMT-1, World's Smallest FM Radio.....\$11.95
PFMR-1, Pager Style LCD Clock & FM Radio\$12.95

VISA MasterCard AMERICAN EXPRESS DISCOVER

ORDERING INFO: Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

WESTERN TEST SYSTEMS

WE BUY AND SELL

Inquiries 307-635-2269 • Fax 307-635-2291

Orders 800-538-1493

2701 Westland Court, Unit B, Cheyenne, Wyoming 82001

OSCILLOSCOPES & ACCESSORIES

OSCILLOSCOPES

TEK 2445 150 MHz 4-channel Oscilloscope	\$1,400.00
TEK 2465 300 MHz 4-channel Oscilloscope	\$2,250.00
TEK 7104 1 GHz 2-Channel Oscilloscope, w/7A29,7A29-04,7B10,7B15	\$3,000.00
TEK 7844 400 MHz Dual Beam Oscilloscope with 7A24,7A26,7B80,7B85	\$900.00
TEK 7904 500 MHz Oscilloscope, with 7A24,7A26,7B80,7B85	\$900.00
TEK SC503 10 MHz Dual Trace Storage Oscilloscope, TM500 series	\$375.00

PROBES

HP 1122A Probe Power Supply	\$150.00
HP 54701A 2.5 GHz 10X FET Probe, s for 54700 series oscilloscope	\$1,000.00
TEK 1101 Accessory Power Supply, for FET probes	\$200.00
TEK A6901 Ground Isolation Monitor	\$200.00
TEK A6902B Voltage Isolator, DC-20 MHz, 20 mV-500 V/div	\$600.00
TEK P6046 100 MHz Differential Probe	\$500.00
TEK P6201 900 MHz 1X/10X/100X FET Probe	\$450.00
TEK P6202A 500 MHz 10X FET Probe	\$250.00
TEK P6701-opt.02 O/E Converter, 450-1050 nm/0-1 mW: DC-700 MHz, ST conn.	\$175.00

CALIBRATION

TEK 067-0587-02 Signal Standardizer Calibration Fixture	\$750.00
TEK SG503 Level Generator, s 250 kHz-250 MHz, TM500 series	\$600.00

WAVEFORM GENERATORS

FUNCTION

HP 3310B 5 MHz Function Generator, variable phase trigger	\$350.00
HP 3312A 13 MHz Function Generator	\$500.00
HP 3314A-001 20 MHz Function Generator, HPIB	\$1,500.00
HP 3325A 21 MHz Synthesized Function Generator, HPIB	\$1,000.00
HP 3325A-002 21 MHz Synthesized Function Generator, HV output option	\$1,500.00
HP 8165A-002 Prog. Signal Source, p 1 mHz-50 MHz, log swee	\$1,250.00
HP 8904A-001,002,004 Multifunction Synthesizer, DC-600 kHz	\$2,500.00
TEK AWG5102 Arb.Waveform Gen., 20 MS/s, 12 bits,50ppm synthesis <1MHz	\$900.00
TEK AWG5105-opt.02 Arbitrary Waveform Generator, dual channel option	\$1,250.00
TEK DD501 Digital Delay & Burst Gen., for function & pulse gen's	\$275.00
TEK FG501 1 MHz Function Generator, TM500 series	\$225.00
TEK FG502 11 MHz Function Generator, TM500 series	\$300.00
TEK FG503 3 MHz Function Generator, TM500 series	\$250.00
TEK RG501 Ramp Generator, TM500 series	\$175.00
WAVETEK 288 20 MHz Synthesized Function Generator, GPIB	\$750.00

PULSE

BERKELEY NUCLEONICS 7085B Digital Delay Generator, 0-100 mS, 1 nS res.,5 Hz-5 MHz	\$750.00
HP 8007B 100 MHz Pulse Generator	\$600.00
HP 8012B 50 MHz Pulse Generator, variable transition time	\$600.00
HP 8080A/81A/83A/84A 300 MHz Word Generator	\$800.00
HP 8080A/91A/92A/93A 1 GHz Single Channel Pulse Generator	\$950.00
HP 8112A 50 MHz Programmable Pulse Generator, HPIB	\$4,000.00
HP 8115A 50 MHz Dual Channel Pulse Generator, HPIB	\$2,750.00
HP 8116A 50 MHz Pulse / Function Generator, HPIB	\$3,500.00
HP 8116A-001 50 MHz Pulse / n Function Generator, HPIB; burst optio	\$3,900.00
TEK PG502 250 MHz Pulse Generator, Tr<1nS, TM500 series	\$600.00
TEK PG505 100 kHz Pulse Generator, 80 V peak, TM500 series	\$275.00
TEK PG508 50 MHz Pulse Generator, TM500 series	\$400.00
WAVETEK 802 50 MHz Pulse Generator	\$300.00

VOLTAGE & CURRENT

VOLTMETERS

FLUKE 845AR High Impedance Voltmeter / Null Detector	\$400.00
HP 3456A 6-1/2 Digit Voltmeter, HPIB	\$500.00
HP 3457A 7-1/2 digit Voltmeter, HPIB	\$1,200.00
HP 3478A 5-1/2 digit Multimeter, HPIB	\$600.00
KEITHLEY 181 6-1/2 digit Nanovoltmeter, 10 nV sensitivity, GPIB	\$900.00
SOLARTRON 7081 8-1/2 digit Voltmeter	\$3,250.00
TEK DM5010 4-1/2 digit Multimeter, TM5000 series plug-in	\$300.00
TEK DM501A 4-1/2 digit Multimeter, TM500 series plug-in	\$225.00

CALIBRATION

FLUKE 510A AC Reference Standard, 10 VRMS, 0-10 mA	\$450.00
FLUKE 515A Portable Calibrator, DC/AC/Ohms, line & battery power	\$900.00
FLUKE 5220A Transconductance Amplifier, DC-5 kHz, 0-20 A	\$3,000.00
VALHALLA 2703 AC Volt.Std., 0-120V/10 Hz-100 kHz;120-1200V/10 Hz-1 kHz	\$1,500.00

VOLTAGE SOURCES

HP 6114A Precision Dual Range Power Supply, 20 V 2 A / 40 V 1 A	\$850.00
HP 6115A Precision Dual Range Power Supply, 50V 0.8A / 100V 0.4A	\$850.00
KEITHLEY 228 Programmable Voltage/Current Source	\$1,900.00

CURRENT METERS & SOURCES

HP 4140B Picoammeter / DC Voltage e Source, without test fixtur	\$2,000.00
HP 6177C DC Current Source, to 50 V, 500 mA	\$500.00
HP 6181C DC Current Source, to 100 V, 250 mA	\$500.00
HP 6186C DC Current Source, to 300 V, 100 mA	\$750.00
KEITHLEY 225 Current Source, 0.1 uA-100 mA, 10-100 V compliance	\$500.00
KEITHLEY 227 Current Source, 1 uA-1 A, 0-50 V compliance	\$800.00
TEK CT-5 High Current Transformer for P6021/A6302, to 1000A	\$375.00
TEK P6022 AC Current Probe w/termination, 935 Hz-120 MHz, 6 A pk	\$275.00

IMPEDANCE & COMPONENTS

L.C.R.

BOONTON 62AD 1 MHz Inductance Meter, 2-2000 uH	\$550.00
BOONTON 72BD 1 MHz Capacitance Meter, 3-1/2 digit display	\$650.00
HP 4282A-101 3-1/2 digit LCR Meter, 120 Hz / 1 kHz / 10 kHz test, HPIB	\$1,500.00

STANDARDS

E.S.I. SR-1 Standard Resistor, various values	\$125.00
E.S.I. SR1010 Resistance Transfer Standards, 1 Ohm-100 K/step	\$550.00
E.S.I. SR1050-1M Resistance Transfer Standard, 1 Megohm/step	\$2,000.00
GR 1404-A 1000 pF Reference Standard Capacitor	\$700.00
GR 1406 Standard Air Capacitors, GR900 connector, 0.1% acc.	\$375.00
GR 1432-U 4-Decade Resistor, 0-111,10 Ohms, 0.01 Ohm resolution	\$100.00
GR 1433-J 4-Decade Resistor, 0-11,110 Ohms, 1 Ohm resolution	\$150.00
GR 1433-K 4-Decade Resistor, 0-1,110 Ohms, 0.1 Ohm resolution	\$150.00
GR 1433-L 4-Decade Resistor, 0-111,100 Ohms, 10 Ohms resolution	\$150.00
GR 1433-N 5-Decade Resistor, 0-11,111 Ohms, 0.1 Ohm resolution	\$200.00
GR 1433-X 6-Decade Resistor, to 111,111.0 Ohms, 0.1 Ohm res.	\$250.00

HI & LO RESISTANCE

HP 4328A Milliohmeter	\$1,200.00
-----------------------	------------

T.D.R.

TEK 1503B-03,04 T.D.R., 0-50,000 ft., chart recorder & battery power	\$3,000.00
TEK 1503-opt.04 Time Domain Reflectometer, 0-50,000 feet,chart recorder	\$1,400.00

POWER SUPPLIES

SINGLE OUTPUT

HP 6200B Dual Range Supply, C 0-20 V 0-1.5 A / 0-40 V 0-750 mA CVC	\$200.00
HP 6207B 0-160 V 0-200 mA CV/CC Power Supply	\$200.00
HP 6256B 0-10 V 0-20 A CV/CC Power Supply	\$250.00
HP 6263B 0-20 V 0-10 A CV/CC Power Supply	\$400.00
HP 6266B 0-40 V 0-5 A CV/CC Power Supply	\$400.00
HP 6267B 0-40 V 0-10 A CV/CC Power Supply	\$550.00
HP 6274B 0-60 V 0-15 A CV/CC Power Supply	\$650.00
HP 6281A 0-7.5 V 0-5 A CV/CC Power Supply	\$150.00
HP 6282A 0-10 V 0-10 A CV/CC Power Supply	\$200.00
HP 6289A 0-40 V 0-1.5 A CV/CC Power Supply	\$200.00
HP 6299A 0-100 V 0-750 mA CV/CC Power Supply	\$200.00
HP 6384A 4.0-5.5 V at 8 A CV/CL Power Supply	\$125.00
HP 6443B 0-120 V 0-2.5 A CV/CC Power Supply	\$450.00
HP 6574A 0-60 V 0-35 A CV/CC Power Supply	\$1,675.00
HP 6672A 0-20 V 0-100 A CV/CC Power Supply,HPIB, 191-250VAC line	\$2,750.00
KEPCO ATE 36-30M 0-36 V 0-30 A CV/CC Power Supply	\$900.00
KEPCO ATE 36-8M 0-36 V 0-8 A CV/CC Power Supply	\$375.00
LAMBDA LK-352-FM 0-60 V 0-15 A CV/CC Power Supply	\$600.00
SORENSEN DCR 600-0.75B 0-600 V 0-750 mA CV/CC Power Supply	\$550.00
SORENSEN DCS 40-25 0-40 V 0-25 A CV/CC Power Supply	\$650.00
SORENSEN SRL 20-12 0-20 V 0-12 A CV/CC Power Supply	\$400.00
SORENSEN SRL 60-8 0-60 V 0-8 A CV/CC Power Supply	\$600.00
TEK PS501-1 Power Supply, 0-20 V, s 2 mV res., 400 mA, TM500 series	\$175.00

MULTIPLE OUTPUT

HP 6205C Dual Power Supply, 0-40 V 300 mA & 0-20 V 600 mA, CV/CL	\$300.00
HP 6228B Dual 0-50 V 0-1 A CV/CC Power Supply	\$450.00
HP 6237B Triple Output Supply, to +/-20 V 0.5 A & 0-18 V 1 A	\$375.00
HP 6253A Dual 0-20 V 0-3 A CV/CC Power Supply	\$450.00
HP 6255A Dual 0-40 V 0-1.5 A CV/CC Power Supply	\$450.00
KEPCO MPS-620M Triple Output Supply, dual 0-20V 1A tracking & 0-6V 5A	\$250.00
LAMBDA LPD-422-FM Dual 0-40 V 0-1 A CV/CC Power Supply	\$300.00

LAMBDA LPT-7202-FM Triple Output Power Supply	\$450.00
TEK PS5010 Programmable Triple Power Supply, TM5000 series	\$650.00
TEK PS503A Dual Power Supply, TM500 series	\$200.00

MISCELLANEOUS

ACME PS2L-500 Programmable Load, 0-75 V / 0-75 A / 500 Watts max.	\$350.00
ELGAR 501C/400SD AC Power Source, 45 Hz-5 kHz, 500 VA, 0-135 VAC	\$1,150.00
HP 59501B HPIB Isolated DAC/Power Supply Programmer	\$175.00
KEPCO BOP 20-20M Bipolar Op Amp/Power Supply, to 20 V 20 A	\$675.00
KEPCO BOP 36-5M Bipolar Op Amp/Power Supply, to 36 V 5 A	\$400.00
KEPCO BOP 50-2M Bipolar Op Amp/Power Supply, to 50 V 2 A	\$400.00
TRANSISTOR DEVICES DAL-50-15-100 Programmable Load, 0-50 V, 0-15 A, 100 Watts max.	\$200.00

TIME & FREQUENCY

UNIVERSAL COUNTERS

HP 5314A-001 100 MHz/100 nS Universal Counter; TCXO reference option	\$275.00
HP 5315A-001 100 MHz/100 nS Universal Counter; TCXO reference option	\$450.00
HP 5315A-002,003 100 MHz/100 nS Univ. Counter; batt. power & 1 GHz C-ch.	\$650.00
HP 5315A-003 100 MHz/100 nS Univ. Counter, 1 GHz C-channel option	\$550.00
HP 5315B 100 MHz/ 100 nS Universal Counter	\$500.00
HP 5316A 100 MHz/100 nS Universal Counter, HPIB	\$600.00
HP 5316A-001,003 100 MHz/ 100 nS Univ. Counter, HPIB, TCXO, 1 GHz C-ch.	\$750.00
HP 5316B 100 MHz/ 100 nS Universal Counter, HPIB	\$750.00
HP 5370A 100 MHz/ 20 pS 11 digit Universal Time Interval Counter	\$750.00
PHILIPS PM6672/411 120 MHz/100 nS Universal Counter, C-channel 70-1000 MHz	\$450.00
TEK DC5004 Programmable 100 MHz/100nS Counter/Timer, TM5000 series	\$250.00
TEK DC5009 Programmable 135 MHz Univ. Counter/Timer, TM5000 series	\$400.00
TEK DC5010 350 MHz / 3.125 nS Universal Counter, TM5000 series	\$950.00
TEK DC503A 125 MHz/100 nS Universal Counter, TM500 series	\$275.00
TEK DC509 135 MHz/ 10 nS Universal s Counter, TM500 series	\$275.00

FREQUENCY COUNTERS

EIP 545A 18 GHz Frequency Counter	\$750.00
FLUKE 7220A-010,131,351 1.3 GHz Counter; battery power, OCXO, and res. mult.	\$500.00
HP 5340A 18 GHz Frequency Counter	\$450.00
HP 5342A 18 GHz Frequency Counter	\$1,250.00
HP 5343A-001 26.5 GHz Frequency Counter, OCXO reference	\$3,500.00
HP 5345A/5355A/5356B 26.5 GHz CW/Pulse Frequency Counter	\$3,500.00
HP 5351B-001 26.5 GHz Frequency Counter, HPIB, OCXO reference	\$4,250.00
HP 5364A Microwave Mixer / Detector, for modulation domain an.	\$3,000.00
HP 5385A-004 1 GHz Frequency Counter, HPIB; OCXO ref. osc. option	\$800.00

STANDARDS

HP 105B Quartz Oscillator, 0.1 / 1.0 / 5.0 MHz, battery power	\$1,500.00
HP 5087A-opt.032 Distribution Amplifier, 12 outputs at 5 MHz	\$1,750.00

AUDIO & BASEBAND

SPECTRUM ANALYSIS

HP 3586C Selective Level Meter, 50 Hz-32.5 MHz, 50 & 75 ohms	\$1,200.00
TEK 7L5L3/R7603 Spectrum Analyzer, 20 Hz-5 MHz, 10 Hz min. res.,w/frame	\$1,500.00

DISTORTION ANALYZERS

HP 8903A Audio Analyzer, 20 Hz-100 kHz	\$1,500.00
--	------------

RMS VOLTMETERS

FLUKE 8922A True RMS Voltmeter, 180 uV-700 V, 2 Hz-11 MHz	\$450.00
---	----------

OSCILLATORS

TEK SG502 Sine/Square Osc., 5 Hz-500 kHz, 70 dB step atten., TM500	\$200.00
--	----------

MISCELLANEOUS

HP 3575A-002 Phase-Gain Meter, 1 Hz-13 MHz, dual display	\$850.00
HP 461A Amplifier, 20 dB or 40 dB gain, 1 kHz-150 MHz	\$125.00
HP 465A Amplifier, 20/40 dB, 5 Hz-1 MHz, 1/2 Watt/50 Ohms	\$125.00
HP 467A Power Amplifier, X1/X2/X5/X10, DC-1 MHz, 10 W output	\$375.00
KROHN-HITE 3103 High/Low Pass Filter, 10 Hz-3 MHz, 24 dB/octave	\$350.00
KROHN-HITE 3200 High Pass / Low Pass Filter, 20 Hz-2 MHz, 24 dB/octave	\$275.00
KROHN-HITE 3202 Dual HP/LP/BP/BR Filter, 20 Hz-2 MHz, 24 dB/octave	\$450.00



90 DAY WARRANTY PARTS AND LABOR • 10 DAY INSPECTION TEST EQUIPMENT WANTED CALL OR FAX LIST • OPEN ACCOUNTS



KROHN-HITE 3342R Dual HP/LP Filter, 0.001 Hz-99.9 kHz, 48 dB/octave	\$900.00
ROCKLAND 852 Dual Highpass/ Lowpass Filter, 0.1 Hz-111 kHz	\$900.00
TEK AM502 Differential Amplifier, 0.1 Hz-1 MHz, TM500 series	\$475.00
WAVETEK 716 Brickwall Filter	\$1,500.00

RF & MICROWAVE

SPECTRUM ANALYZERS

HP 11517A/18A/19A/20A Mixer Set, 12.4-40.0 GHz, for HP 8555A/8569A	\$500.00
HP 11970A WR28 Harmonic Mixer, 26.5-40 GHz	\$1,100.00
HP 11970K WR42 Harmonic Mixer, 18.0-26.5 GHz	\$1,100.00
HP 11970Q WR22 Harmonic Mixer, 33-50 GHz	\$1,400.00
HP 11970U WR19 Harmonic Mixer, 40-60 GHz	\$1,400.00
HP 70620B Preamplifier, 1.0-26.5 GHz, for 70000 series	\$3,900.00
HP 8559A/853A-001 Spectrum An., 0.01-21 GHz, 1 kHz res., w/rackmount frame	\$3,750.00
HP 8565A-100 Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res	\$3,250.00
HP 8568B Spectrum Analyzer, 100 Hz-1.5 GHz, 10 Hz min. res.	\$8,500.00
HP 8569B Spectrum Analyzer, 10 MHz-22 GHz, 100 Hz min. res. bw.	\$7,500.00
TEK TR502 Tracking Generator, 0.1-1800 MHz, for 7L13/7L14	\$950.00
TEK WM782V WR15 Harmonic Mixer, 50-75 GHz	\$1,500.00

NETWORK ANALYZERS

HP 11650A Network Analyzer Accessory Kit, APC7	\$600.00
HP 35676A Reflection/Transmission Test Kit, 5 Hz-200 MHz	\$1,000.00
HP 85020A Directional Bridge, 10-4300 MHz, N(f) test port	\$650.00
HP 85027C Directional Bridge, 0.01-18 GHz, N(f) test port	\$1,750.00
HP 85054A Type N Calibration Kit, for HP 8510 series	\$1,800.00
HP 8511A Frequency Converter, 45 MHz-26.5 GHz, for HP 8510	\$6,500.00
HP 8756A Scalar Network Analyzer	\$2,500.00
HP R85026A WR28 Detector, 26.5-40 GHz, for HP 8757 series	\$1,200.00
WILTRON 560-98KF50 SWR Autolester, 10 MHz-40 GHz, for Wiltron 560 series	\$1,800.00

SIGNAL GENERATORS

FLUKE 6060A Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res., GPIB	\$1,900.00
FLUKE 6060A/AN Synthesized Signal Gen., 10 kHz-50 MHz, 10 Hz res., GPIB	\$1,500.00
FLUKE 6060B/AB Synthesized Signal Gen., 0.1-1050 MHz, 10 Hz res.	\$1,900.00
GIGATRONICS 1018 Synthesized Signal Gen., 50 MHz-18 GHz, 1 MHz res.	\$4,500.00
GIGATRONICS 600/6-12 Synthesized Source, 6-12 GHz, 1 kHz res., GPIB	\$2,500.00
GIGATRONICS 840-18 Freq. Multiplier, 18-26 & 26-40 GHz outputs 0 dBm	\$2,750.00
GIGATRONICS 875/50 Levelled Multiplier, x4, 50.0-75.0 GHz output, -3 dBm	\$2,500.00
GIGATRONICS 875/86 Levelled Multiplier, 26.5-40.0 & 50.0-75.0 GHz outputs	\$3,750.00
GIGATRONICS 900/2-8 Synthesized Signal/Sweep Gen., 2-8 GHz, 1 MHz res., GPIB	\$2,500.00
HP 11720A Pulse Modulator, 2-18 GHz, 80 dB on/off ratio	\$450.00
HP 85100V Frequency Mult., 10-15 GHz in / 50-75 GHz out >0 dBm	\$3,750.00
HP 8640B Signal Generator, 0.5-512 MHz, AM, FM, pulse modulation	\$950.00
HP 8656B-001 Synth. Signal Gen., 0.1-990 MHz, 10 Hz res., OCXO ref.	\$2,500.00
HP 8657A-002 Signal Generator, 0.1-1040 MHz, 10 Hz res., HPIB	\$3,250.00
HP 8660C/86602B-002 Synth. Sig. Gen., 1-1300 MHz, FM / Phase mod. w/86635A	\$2,750.00
HP 8660C/86603A/86633B Synthesizer, 1-2600 MHz, 1 Hz res., AM / FM	\$3,250.00
HP 8660D/86603A/86632B Synthesizer, 1-2600 MHz, 1 Hz res., AM / FM	\$4,500.00
HP 8672A Synthesized Signal Generator, 2-18 GHz, +3 dBm output	\$5,500.00
HP 8673D-H16 Synth. Signal Generator, 50 MHz-26 GHz, AM/FM	\$18,500.00
HP 8673E Synthesized Signal Generator, 2-18 GHz, +8 dBm output	\$9,500.00
HP 8673G-004, 008 Synth. CW Signal Generator, 2-26 GHz, >+8 dBm output	\$12,500.00
HP 8684B Signal Generator, 5.4-12.5 GHz, AM/ WBFM/ Pulse	\$3,500.00

SWEEP GENERATORS

HP 8341B-004 Synthesized Sweeper, 10 MHz-20 GHz, +10 dBm, rear output	\$14,500.00
HP 8350A/83545A-002 Sweep Oscillator, 5.9-12.4 GHz, 70 dB step attenuator	\$4,000.00
HP 8601A Generator/Sweeper, 0.1-110 MHz, +20 dBm levelled	\$400.00
HP 8620C Sweep Oscillator Frame	\$550.00
HP 8622B-002 RF Plug-in, 10-2400 MHz, +13 dBm levelled, 70 dB atten.	\$1,250.00
HP 86230B RF Plug-in, 1.8-4.2 GHz, +10 dBm unlevelled	\$375.00
HP 86241A-001 RF Plug-in, 3.2-6.5 GHz, +8 dBm levelled	\$300.00
HP 86242D-004, 008 RF Plug-in, 5.9-9.0 GHz, +10 dBm levelled	\$300.00
HP 86245A-001 RF Plug-in, 5.9-12.4 GHz, +17 dBm levelled	\$600.00
HP 86250D RF Plug-in, 8.0-12.4 GHz, +10 dBm levelled	\$500.00
HP 86260A-H04 RF Plug-in, 10.0-15.0 GHz, +10 dBm unlevelled	\$500.00
HP 86290A-004 RF Plug-in, 2.0-18.0 GHz, +7 dBm levelled, rear output	\$1,750.00
HP 86290B-004 RF Plug-in, 2.0-18.6 GHz, +10 dBm levelled, rear output	\$1,850.00

WAVETEK 962 Sweep Generator, 1.0-4.0 GHz, markers, +12 dBm unlvld.	\$1,250.00
WILTRON 6647M Sweep Generator, 10 MHz-20 GHz, +10 dBm levelled	\$4,500.00

POWER METERS

ANRITSU MP-81B/ML-83A Power Meter, 75-110 GHz (WR10), -20 to +20 dBm	\$2,500.00
BOONTON 42B/41-4E Analog Power Meter, with 1 MHz-18 GHz sensor	\$450.00
HP 435B/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz	\$900.00
HP 435B/8481B Power Meter, 0 to +43 dBm, 10 MHz-18 GHz	\$1,500.00
HP 435B/8482H Power Meter, -10 to +34 dBm, 100 kHz-4.2 GHz	\$900.00
HP 436A-022/8481A Power Meter, -30 to +20 dBm, 10 MHz-18 GHz, HPIB	\$1,400.00
HP 8477A Power Meter Calibrator, for HP 432 series	\$500.00
HP 8900D/84811A Digital Peak Power Meter, 10 MHz-18 GHz, 0-+20 dBm	\$2,300.00
HP K486A WR42 Thermistor Mount, 18.0-26.5 GHz, for 432 series	\$350.00
HP Q8486A Power Sensor, 33.0-50.0 GHz, WR22, for 435/6/7/8	\$1,500.00
HP R486A WR28 Thermistor Mount, 26.5-40 GHz, for 432 series	\$350.00
HP R8486A WR28 Power Sensor, 26.5-40 GHz, for HP 435/6/7/8	\$1,500.00

RF MILLIVOLTMETERS

RACAL 9303 TRMS Level Meter, 10 kHz-2 GHz, -77 to +23 dBm, GPIB	\$875.00
--	----------

AMPLIFIERS, MISCELLANEOUS

ENI 1040L Amplifier, 55 dB gain, 10-500 kHz, 400 Watts	\$2,750.00
HP 415E SWR Meter	\$200.00
HP 8406A Comb Generator, 1/10/100 MHz increments, to 5 GHz	\$500.00
HP 8447A Amplifier, 20 dB, 0.1-400 MHz, 5 dB NF, +6 dBm output	\$375.00
HP 8447E Amplifier, 22 dB, 0.1-1300 MHz, +13 dBm output	\$750.00
HP 8447F-H84 Dual Amp, 25 dBG 0.1-1300 MHz & 28 dBG 9 kHz-50 MHz	\$900.00
HP 8901A Modulation Analyzer, 150 kHz-1300 MHz	\$2,500.00
HP 8901B-1,2,3 Modulation An., 0.15-1300 MHz, rear input, OCXO, ext.LO	\$3,000.00
HP 8970A Noise Figure Meter	\$4,000.00
RF POWER LABS ML50 Amplifier, 2-30 MHz, 47 dB gain, 50 Watts, metered, 28V	\$350.00
ROHDE & SCHWARTZ ESH2 Test Receiver, 9 kHz-30 MHz	\$5,000.00

COAXIAL & WAVEGUIDE

AMERICAN NUCLEONICS AM-432 Cavity Backed Spiral Antenna, LHC, 2-18 GHz, TNC(f) "NEW"	\$95.00
AVANTEK AMT-400X2 WR28 Active Doubler, 13-20 GHz +10 dBm in, +10 dBm out	\$450.00
BAYTRON 3-28-300/10 WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$300.00
BIRD 6735-300 1 kW Load, 25-1000 MHz, LC(f), with wattmeter	\$650.00
BIRD 8201 500 Watt Oil Cooled Load, DC-2.5 GHz, N(f)	\$350.00
BIRD 8251 1 kW Oil-Dielectric Load, DC-2.4 GHz, N(f)	\$500.00
CONTINENTAL MW. RAE28-K-M WR28 x K(m) Endfire Adapter	\$225.00
FXR/MICROLAB S3-02N Triple Stub Tuner, 200-1000 MHz, 100 Watts max., N(m/f)	\$125.00
FXR/MICROLAB SL-03N Stub Tuner, 0.3-6.0 GHz, 100 Watts max., N(m/f)	\$75.00
GR 874-LTL Constant Impedance Trombone Line, 0-44 cm, DC-2 GHz	\$400.00
HP 11590A-001 Bias Network, 1.0-18.0 GHz, APC7	\$450.00
HP 11636A 2-Way Power Divider, DC-18 GHz, N(m/f)	\$300.00
HP 11692D Dual Directional Coupler, 22 dB, 2-18 GHz	\$800.00
HP 3321K Programmable Step Atten., 0-70 dB, DC-26.5 GHz, 3.5mm	\$475.00
HP 33327L-006 Programmable Step Attenuator, 0-70 dB, DC-40 GHz, 2.9mm	\$1,000.00
HP 774D Dual Directional Coupler, 20 dB, 215-450 MHz	\$275.00
HP 777D Dual Directional Coupler, 20 dB, 1.9-4.1 GHz	\$275.00
HP 778D-011 Dual Dir. Coupler, 20 dB, 100-2000 MHz, APC7 test port	\$450.00
HP 8431A 2-4 GHz Band Pass Filter, N(m/f)	\$150.00
HP 8472A Crystal Detector, 10 MHz-18 GHz, negative polarity, SMA	\$175.00
HP 8494G-002 Programmable Step Attenuator, 0-11 dB, DC-4 GHz, SMA	\$350.00
HP 8495H-002 Programmable Step Attenuator, 0-70 dB, DC-18 GHz, SMA	\$400.00
HP 8496A-002 Step Attenuator, 0-110 dB, DC-4 GHz, SMA	\$375.00
HP 8497K-004 Programmable Step Attenuator, 0-90 dB, DC-26.5 GHz	\$750.00
HP K382A WR42 Direct Reading Attenuator, 0-50 dB, 18-26.5 GHz	\$2,900.00
HP K422A WR42 Flat Broadband Detector, 18.0-26.5 GHz	\$350.00
HP K532A WR42 Frequency Meter, 18.0-26.5 GHz	\$450.00
HP K870A WR42 Slide Screw Tuner, 18.0-26.5 GHz	\$275.00
HP K914B WR42 Moving Load, 18.0-26.5 GHz	\$300.00
HP Q752D WR22 Directional Coupler, 20 dB, 33-50 GHz	\$650.00
HP R382A WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$2,250.00
HP R422A WR28 Crystal Detector, 26.5-40 GHz	\$400.00
HP R532A WR28 Frequency Meter, 26.5-40 GHz	\$500.00
HP R752C WR28 Directional Coupler, 10 dB, 26.5-40 GHz	\$450.00
HP R752D WR28 Directional Coupler, 20 dB, 26.5-40 GHz	\$450.00
HP R914B WR28 Moving Load, 26.5-40 GHz	\$250.00
HP V365A WR15 Isolator, 25 dB, 50-75 GHz	\$750.00
HP V752D WR15 Directional Coupler, 20 dB, 50-75 GHz	\$650.00
HP X870A WR90 Slide Screw Tuner	\$150.00
HUGHES 45712H-1000 WR22 Frequency Meter, 33-50 GHz	\$900.00
HUGHES 45714H-1000 WR15 Frequency Meter, 50-75 GHz	\$900.00
HUGHES 45716H-1000 WR10 Frequency Meter, 75-110 GHz	\$900.00

HUGHES 45721H-2000 WR28 Direct Reading Attenuator, 0-50 dB, 26.5-40 GHz	\$1,000.00
HUGHES 45724H-1000 WR15 Direct Reading Attenuator, 0-50 dB, 50-75 GHz	\$1,000.00
HUGHES 45732H-1200 WR22 Level Set Attenuator, 0-25 dB, 33-50 GHz	\$250.00
HUGHES 45772H-1100 WR22 Thermistor Mount, -20 to +10 dBm, 33-50 GHz	\$400.00
HUGHES 45773H-1100 WR19 Thermistor Mount, -20 to +10 dBm, 40-60 GHz	\$650.00
HUGHES 45774H-1100 WR15 Thermistor Mount, -20 to +10 dBm, 50-75 GHz	\$750.00
HUGHES 45775H-1100 WR12 Thermistor Mount, -20 to +10 dBm, 60-90 GHz	\$800.00
HUGHES 45776H-1100 WR10 Thermistor Mount, -20 to +10 dBm, 75-110 GHz	\$850.00
HUGHES 47316H-1111 WR10 Tuneable Detector, 75-110 GHz, positive polarity	\$600.00
HUGHES 47741H-2310 WR28 Phase Locked Gunn Osc., 32.000 GHz, +18 dBm	\$2,000.00
HUGHES 47742H-1210 WR22 Phase Locked Gunn Osc., 42.000 GHz, +18 dBm	\$2,750.00
HUGHES 47974H-1000 WR15 SPST PIN Switch, 250 MHz speed, 60-62 GHz response	\$375.00
KRYTAR 2616S Directional Detector, 1.7-26.5 GHz, K(f/m)/SMC	\$200.00
M/A-COM 3-19-300/10 WR19 Directional Coupler, 10 dB, 40-60 GHz	\$450.00
MICA C-121S06 Circulator, 17.5-24.5 GHz, SMA(f/m/m)	\$75.00
MIDWEST MICROWAVE 3537 DC Block, 0.1-12.4 GHz, SMA(m/f) "NEW"	\$40.00
MINI-CIRCUITS ZFDC-20-4 Directional Coupler, 19.5 dB, 1-1000 MHz, SMA(f)	\$25.00
NARDA 3000-SERIES Directional Couplers	\$150.00
NARDA 3022 Bi-Directional Coupler, 20 dB, 1-4 GHz	\$375.00
NARDA 3090-SERIES Precision High Directivity Couplers	\$225.00
NARDA 368BMM Coaxial High Power Load, 500 Watts, 2.0-18 GHz, N(m)	\$500.00
NARDA 3752 Coaxial Phase Shifter, 0-180 deg./GHz, 1-5 GHz	\$1,000.00
NARDA 3753B Coaxial Phase Shifter, 0-55 deg./GHz, 3.5-12.4 GHz	\$1,000.00
NARDA 4000-SERIES SMA Miniature Directional Couplers	\$75.00
NARDA 4226-10 Directional Coupler, 10 dB, 0.5-18.0 GHz, SMA(f)	\$275.00
NARDA 4227-16 Directional Coupler, 16 dB, 1.7-26.5 GHz, 3.5mm(f)	\$325.00
NARDA 4242-20 Directional Coupler, 20 dB, 0.5-2.0 GHz, SMA(f)	\$100.00
NARDA 4247-20 Directional Coupler, 20 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 4247B-10 Directional Coupler, 10 dB, 6.0-26.5 GHz, 3.5mm(f)	\$200.00
NARDA 5070-SERIES Precision Reflectometer Couplers	\$300.00
NARDA 562 DC Block, 10 MHz-12.4 GHz, 100 V max., N(m/f)	\$65.00
NARDA 765-10 10 dB Attenuator, 50 Watts, DC-5 GHz, N(m/f)	\$165.00
NARDA 768-10, 20 dB or 20 dB Attenuator, 20 Watts, DC-11 GHz, N(m/f)	\$120.00
NARDA 792FF Variable Attenuator, 0-20 dB, 2.0-12.4 GHz	\$375.00
NARDA 794FM Direct Reading Variable Attenuator, 0-40 dB, 4-8 GHz	\$375.00
OMNI-SPECTRA 2085-6010-00 Crystal Detector, 1-18 GHz, negative polarity, SMA(m/f)	\$50.00
PAMTECH KYG1014 WR42 Junction Circulator, 18.0-26.5 GHz	\$250.00
SONOMA SCIENTIFIC 21A3 WR42 Circulator, 20 dB, 20.6-24.8 GHz	\$75.00
TRG B510 WR22 Direct Reading Attenuator, 0-50 dB, 33-50 GHz	\$1,000.00
TRG V551 WR15 Frequency Meter, 50-75 GHz	\$600.00
TRG W551 WR10 Frequency Meter, 75-110 GHz	\$750.00
WAVELINE 100080 WR28 Terminated Crossguide Coupler, 30 dB	\$200.00
WEINSCHEL DS109 Double Stub Tuner, 1-13 GHz, N(m/f)	\$150.00
WEINSCHEL DS109LL Double Stub Tuner, 0.2-2.0 GHz, N(m/f)	\$150.00

COMMUNICATIONS

HP 3780A-001 Pattern Generator / Error Detector, 1 kb/s - 50 Mb/s	\$1,000.00
HP 59401A HPIB Bus Analyzer	\$375.00
TEK 1410R NTSC Gen., w/SPG2 sync generator, TSG7 color bars	\$800.00
TEK 1411R PAL Gen., w/SPG12 sync; TSG11 color bars; TSG13 linearity	\$750.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG13, TSG15, TSG16	\$1,000.00
TEK 1411R PAL Test Gen., w/SPG12, TSG11, TSG12, TSG13, TSG15, TSG16	\$1,100.00
TEK 1411R-opt.04 PAL Test Gen., w/ SPG12, TSG11, TSG13, TSG15, TSG16	\$1,400.00
TEK 147A NTSC Test Signal Generator, with noise test signal	\$800.00
TEK 148 PAL Insertion Test Signal Generator	\$700.00
TEK 520A NTSC Vectorscope	\$750.00
TEK 521A PAL Vectorscope	\$750.00

MISCELLANEOUS

FLUKE 2180A RTD Digital Thermometer	\$500.00
HP 7090A Measurement Plotting System	\$1,500.00
P.A.R. 5208-95.98 Two-Phase Lock-in Amp., 2 Hz-100 kHz, GPIB	\$1,500.00
TEK TM5003 5000-series 3-slot Programmable Power Module	\$450.00
TEK TM5006 5000-series 6-slot Programmable Power Module	\$600.00
TEK TM504 500-series 4-slot Power Module	\$175.00
TEK TM506 500-series 6-slot Power Module	\$250.00
TEK TM515 500-series 5-slot Traveller Power Module	\$250.00

INTERNET SECURITY COMPUTER SECURITY

The latest tricks and methods hackers use on the Net to pirate software (warez), and hack websites. Includes examples, countermeasures, password defeats, Packet-Switched Networks, UNIX, Sprintnet, X.25, anonymous FTP, brute force techs, lots of tips. More! \$29. wrds=29.4K

INTERNET TRACKING & TRACING: Scammers, spammers, stalkers, infectors, and others hide behind the Internet's anonymity to commit serious offenses. Learn from master hackers best methods to track, trace IDs and origins, and to protect your own privacy. More! \$29. wrds=17.0K

INTERNET FRAUDS DATABASE: Internet cons, scams and related frauds now rake in \$2+ billion annually! Most are done anonymously with impunity. Details how they're done, how to ID them, how to protect yourself. More! \$25. wrds=19.1K

COOKIE TERMINATOR: \$25. wrds=8.4K
Any 2 for \$49.3 for \$64

ATM SECURITY

100+ ATM crimes, abuses, vulnerabilities, defeats exposed - TEMPEST, mag stripes, false fronts, supercool, More! Case histories, labeled internal photos, figures. \$39. wrds=41.0K

PBX SECURITY

PBXs hacking losses of \$5-\$10 billion/yr! Detailed vulnerabilities (especially for out-dial), countermeasures. Exclusive author interview in Forbes! \$24. wrds=17.4K

CELLPHONE/CORDLESS GUIDE

How cellphones operate; mods. Vulnerabilities to hack attack; countermeasures. Cloning details for NAMS, ESNs, etc, control data formats, computing encoded MINs, ESNs, SIDHs, Op Sys, PROMs, forcing ACK, test mode and resets, cable diagrams, scanning, tracking, scanner restorations, freq allocations, roaming, step-by-step to keypad-reprogram 100+ popular cellphones. One FREE database search. Plus much on Cordless phones. More! \$49. wrds=80.0K

PAGER (BEEPER) MANUAL: How Pagers work, different types and uses, freqs, advantages over and uses with cellphones, and tips and tricks. How phreaks hack Pagers; countermeasures. Plus plans for a **Personal Pocket Paging System** (xmitter and receiver). More! \$29. wrds=11.7K Both for only \$69

THE DIRTY-2 DOZEN!

24+ Hot Hack/Phreak Expose! Disks! See Web CATALOG NOW!

TOP SECRET

2430 Juan Tabo, NE, #259, ABQ, NM 87112
P.O. Box 23097 ABQ, NM 87192
Fax: 505-292-4078 (all hours, orders only) Voice: 505-237-2073 (9-7 M-S)

FREE FULL WEB CATALOG: www.tsc-global.com

Established in 1971 by John Williams, MSE, former DOD weapons engineer and NIH physicist. Featured on CBS '60 Minutes', Forbes, New York Times. Add \$5 total S/H (US, Canada). Postal MO is fastest! VISA, MC OK. No CODs. 10% OFF All Orders over \$100. \$2.00 OFF All New Orders over \$20 placed by Mail or Fax. wrds=Estimated Word Count

Sold for legal educational purposes only. Some publications are controversial! We take no responsibility for anything we publish. See Catalog for WARRANTY, SPECIAL PROJECTS and all other applicable policies.

Describes in detail how computers penetrate each other, and how VIRUSES, TROJAN HORSES, WORMS are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary FLUSHOT+ protection system. Internet advice, password defeats, glossary - much more! Manual + PC Disk! \$39. wrds=49.5K

THE HACKER FILES: Expose 3 HD PC disks filled with choice raw, colorful, highly informative hacker, phreaker text files covering many topics! \$39.
Both for only \$69

BEYOND VAN ECK TEMPEST

Remote eavesdropping plans of TV video "noise" signals. Range up to 1 KM. Describes how Van Eck systems work, and are also used in surveillance of computer systems. Plus TVRO vs phone privacy detailed! \$29. wrds=14.9K. Van Eck Demo Tape is \$29. (15 min). Both for only \$49!

CALLER ID & ANI SECURITY

How they work and the many vulnerabilities of Caller ID, ANI, *69, *57, Call Blocking, *67, et al. Describes ESS, SS7, CNA, CMA, DNR, Diverters, Centrex! \$25. wrds=15.2K

FAX MACHINE SECURITY

All known methods used to hack/fax and countermeasures. Includes computer fax modems, crimes, interceptions, fax servers, fax-on-demand, protocols, parameters, compression, encryption, and fax surveillance-type mods. More! \$29. wrds=29.0K

MANY MORE TITLES!

(See Catalog for prices & descriptions)

POWERFUL STOCK SOFTWARE

BEYOND PHONE COLOR BOXES

ANSWER. MACHINE SECURITY

CASINO SECRETS

CHECK & M.O. SECURITY

CREDIT CARD SECURITY

CONS & SCAMS DATABASE

SOCIAL ENGINEERING

POLYGRAPH SECRETS

BY AN ORDER OF THE MAGNITUDE

ULTIMATE SUCCESS MANUAL

STEALTH TECHNOLOGY

SIMPLE/CHEAP SECURITY ELEC.

SECRET & SURVIVAL RADIO

POWER METER SECRETS

As reported on "60 MINUTES" 6th Edition! Details devices that can slow down (even stop) power meters while loads draw full power - great science project! Devices plug into one outlet and normal loads into other outlets. Describes meter creep, overload droop, pole meters, etc. \$29. wrds=10.4K

SPM THE VIDEO: Now its easier to learn about KW-HR Power Meters than ever before! This educational video shows you how they work and their anatomy. Demonstrates SPMEM device and external magnetic methods used to slow and stop meters! Hosted by a top expert in the field. From the novice to the pro, an excellent source of info on these exciting devices! Great in combo with our SPM-related manuals! \$29. (20 min)

THE I.G. MANUAL: Details external magnetic ways (applied to meters) outlaws use to slow down and stop power meters while drawing full loads. \$25. wrds=4.9K

KW-HR METERS: How watt-hour energy meters work, calibration, error modes (many), ANSI Standards, etc. Demand and Polyphase Meters. Experimental results to slow, stop power meters by others. \$25. wrds=24.2K
Any 2 for \$49.3 for \$64, all 4 for \$79

VOICE MAIL SECURITY

VMS are hacked to penetrate PBXs to make outgoing calls, get free VMB usage, secretly read/change/delete messages, control/damage the VMS (or its PBX) itself. Details how they do it, countermeasures. A must for users, sysops, security personnel! \$29. wrds=14.2K

THE "GOLDFINGER"

THE "SILKWOOD"

SECRETS OF SOLDERLESS BBS

HIGH VOLTAGE DEVICES

MIND CONTROL

UNDER ATTACK!

RADIONICS MANUAL

HEAL THYSELF!

SECRET & ALTERNATE IDS

CRYPTANALYSIS TECHNIQUES

GOVERNMENT LAND GRAB

ROCKET'S RED GLARE

VORTEX GENERATOR

SURVIVAL GUNS & AMMO


THE ULTIMATE DRIVER

Plus Many More - Order Today!


HAM GEAR FOR SALE

WANTED: ROCKWELL-Collins HF-80 equipment, 851S-1, 237B-3 log periodic, Collins literature. Jim Stitzinger 805-259-2011, 805-259-3830 (fax), bfl-jfs@smartlink.net

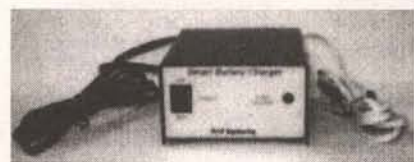DRAKE TR7 & R7 service kit extender boards and digital jumper card. Same as originals, \$63.20. Bob 509-765-4721. rsrolfne@atnet.net



THE SMART BATTERY CHARGER for lead acid or gel cell batteries. Can be left connected to the battery INDEFINITELY, will not overcharge! Standard kit is 12V @ 1 amp. This kit is 100% complete. For the kit order #150-KIT at \$59.95. For an assembled and tested unit, order #150-ASY at \$79.95. CA residents add 7.75% sales tax. Add \$6.50 per unit shipping. MC/VISA accepted. A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. 714-952-2114, FAX 714-952-3280.

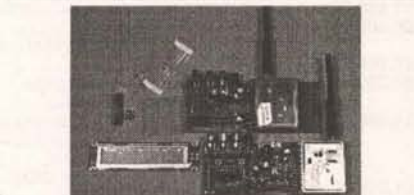

GET FULL control of frequencies from 2.2GHz to 2.7GHz on your existing RF link or Matco transmitters and receivers. These easy-to-assemble kits are fully PIC controlled, have an easy-to-read LCD and store set frequencies in memory. Kits are \$59.95 ea. or \$99.95 ea. pre-assembled. Additional price breaks are available when sold with transmitter and receiver combination. Visit our website at: www.atvcam.com

LML RADIO & electronics. Let us be your one stop shop for all your radio equipment, test equipment & other surplus needs. Free catalog. Call 909-873-1319 or fax on demand 24 hr. 909-820-1885 & our new web catalog: <http://members.aol.com/hrh6/LMLinc> or LML, 424 E. Shamrock, Rialto, CA 92376.


50KW RF GENERATORS. Designed by Westenhous. WL6426 water cool tube. Mike, 828-684-7672. [HTTP://WWW.CHI GEOR.COM](http://WWW.CHI GEOR.COM)

PRACTICAL ANTENNA HANDBOOK, by Joseph Carr. The most popular book on antennas ever written, widely known as "the antenna builder's bible." This Third Edition is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works. Only \$49.95! 10% discount to Nuts & Volts subscribers. Call 1-800-783-4624 to order using Visa or MasterCard.



LOW COST WSHFAX WEATHER FAX FOR PC/CLONES. This unit is featured in Chapter 5 of the Fifth Edition of the WEATHER SATELLITE HANDBOOK. It will process both HF and satellite weather FAX. For KIT order #200-KIT for \$159.95. For assembled unit order #200-ASY for \$189.95. Add \$6.50 S/H per order. Software is included. Tuning indicator included, compatible with JV FAX 7.0. Visa & MC accepted. For more information, send LSASE (55¢) to: A&A Engineering, 2521 W. La Palma #K, Anaheim, CA 92801. To order call, 714-952-2114. Fax 714-952-3280.

SECRETS OF RF CIRCUIT DESIGN From Joseph Carr, one of today's most respected electronics authors, comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits. Only \$29.95! 10% discount to Nuts & Volts subscribers. Call 1-800-783-4624 to order using Visa or MasterCard.

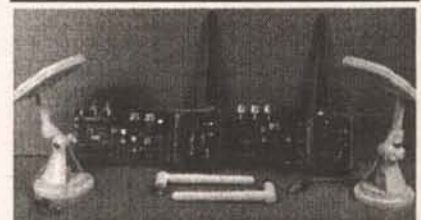

ATV-2400, 2.4GHz 8 channel designed for legal use in ham bands. EZATV, www.4atv.com

HAM GEAR WANTED

ARC-5 RECEIVERS and original manuals. John Broussard, 312 Guilbeau, Breau Bridge, LA 70517.

CB - SCANNERS

HALCON COMMUNICATIONS Wholesale only: Cobra, Uniden, Midland, Galaxy, CTE, Super Star, Kenwood, Yaesu, Icom. Free catalog, Free call 1-800-683-6999.

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT

Visit www.alfaelectronics.com for complete info

Call 1-800-526-2532 for Order and Free Catalog



DMM
DMM-89S (\$179.00): true rms, AC/DC (V, A), Ω, bar graph, freq, capac., dBm, logic, diode
DMM-23T (\$99.95): 4 1/2 digit, true rms, high resol. (10μV, 10nA, 10mΩ), hFE, diode, contin.
DMM-20 (\$74.95): AC/DC (V, A), Freq, cont., Capac, Induct., Ω, hFE, diode, duty cycle
DMM-122 (\$59.95): DC/AC (V, A), Ω, hFE, diode, capacitance, freq, logic, continuity
DMM-123 (\$44.95): DMM + capacitance, DC/AC (V, A), Ω, hFE, diode, continuity
DMM-10 (\$19.95): 3 1/2 digit, DC/AC V, Ω, hFE, diode, signal output (+3V, -0.5Vsq., 50% duty)



LCR/COUNTER
CAP-15 (\$49.95): 3 1/2 digit, 0.1pF-20mF, 9 Ranges, 0.1pF resolution, zero adjustment
LCR-24 (\$119.95): 0.1μH-200H, 0.1pF-2000μF, 0.01Ω-20MΩ, diode test. New Model.
LCR-131D (\$219.95): autorange, 0.1μH-10kH, 0.1pF-10mF, 1mΩ-10MΩ, Q Factor, serial/parallel, 120Hz/1kHz testing mode.
FC-1200 (\$129.95): 1.25GHz counter, Handheld, 8 digits display, 10ppm accuracy, sensitivity 5mV (130-350MHz), 30mV (440MHz)

TRUKE SPECIALTY
12B \$ 94.95
70-III \$ 99.00
73-III \$125.00
75-III \$155.00
77-III \$173.00
79-III \$195.00
87-III \$325.00
92B-III \$1,445
96B-II \$1,695
99B-III \$2,095
105B \$2,495
123-III \$1,130
863E \$555
867B \$740
• AC Current Probe \$34.95
• DC/AC Current Probe \$79.95
• Mini AC Clamp \$59.95
• AC Clamp w/temp \$89.95
• DC/AC Clamp \$109.95
• Thermometer \$69.95-\$89.95
• IR Thermometer \$189.95
• Sound Level Meter \$169.95
• Tachometer \$169.95-\$219.95
• EMF Tester \$69.95
• Pressure Meter \$299.95
• Watt Meter \$129.95
• High Voltage Probe \$59.95
• pH Meter \$79.95
• Light Meter \$79.95-\$89.95



Single Output DC Power Supplies
• Constant current, constant voltage mode
• Short Circuit and overload protected
Analog Meters Display
PS-303 (\$159.00) 30V/3A
PS-305 (\$219.95) 30V/5A
PS-812 (\$399.95) 60V/5A
PS-1610 (\$289.00) 16V/10A
PS-8107 (\$399.95) 30V/10A
Digital Volt, Analog Current
PS-8200 (\$179.95) 30V/3A
PS-8201 (\$239.95) 30V/5A
Digital Volt & Current Display
PS-8300 (\$199.95) 30V/3A
PS-8301 (\$259.95) 30V/5A



Triple Output
• Independence or Tracking operation
• Parallel to double current output (PS-8102 & PS-8103 only)
Triple Output (Analog displays)
PS-8102 (\$399.95) 30V/3A/30V/3A
PS-8103 (\$489.95) 30V/5A/30V/5A
Digital Displays
PS-8202 (\$499.95) 30V/3A/30V/3A
PS-8203 (\$549.95) 30V/5A/30V/5A

AUDIO/RF/FUNCT. GEN.
RF Generator • SG-4160 (\$124.95) 100kHz-150MHz sinewaves in 8 ranges
• SG-4162AD (\$229.95) with 6 digit counter
Audio Generator • AG-2601 (\$124.95) 10Hz-1MHz, 0.8Vpp sine, 0-10Vpp squarewave
• AG-2603AD (\$229.95) with 6 digit counter
Function Generator • FG-2100A (\$154.95) 0.2Hz-2MHz, 5mV-20Vpp
• FG-2103 (\$329.95) Sweep 0.5Hz-5MHz

GW/INSTEK

20 MHz Scope 100MHz Cursor


Triple Output

Single Output

Programmable

FUNCTION GENERATOR

BENCHTOP DMM

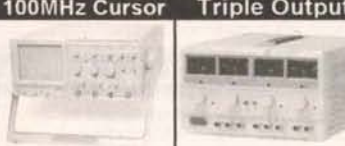

• OS-620 \$304.95
• Most economical scope
• Dual CH/X-Y operation
• 1 mV/div sensitivity
• Z-axis input, CH1 output
• TV syn, ALT trigger
• 2 probes (x1, x10)

• OS-6103 \$1199.95
• Cursor Readout & meas
• Dual CH / Delay sweep
• 10 panel setting memory
• Time base auto-range
• Z-axis modulation input
• 2 probes (x1, x10)

• 2 variable out 0-30V, 0-3A
• One fixed 5V, 3A output
• Auto track, serial, parallel
• Const. volt, current mode
• 4 analog or 2 digital display
PC-3030 (\$499.95)
PC-3030D (\$549.95) digital

• Const voltage, current mod
• Voltage regulation <0.01%
• Current regulation <0.2%
PS-1830 (\$198.95) 18V/3A
PS-1850 (\$214.95) 18V/5A
PPT-1830C (\$1,499.95) 18V/3A
PPT-3615C (\$1,499.95) 36V/1.5A

• Auto serial/parall (PPT ser)
• Auto track (PPT series),
• IEEE-488.2 and SCPI
compatible command set
PPS-1860C (\$1,149.95) 18V/6A
PPS-3635C (\$1,149.95) 36V/3.5A
PPT-1830C (\$1,499.95) 18V/3A
PPT-3615C (\$1,499.95) 36V/1.5A

FG-8015G (\$157.95)
• 0.02Hz-2MHz
• Sine/Sqr/Tri/Pulse/Ramp
FG-8020G (\$209.95)
• 0.02Hz-2MHz w/counter
FG-8050 (\$449.95) Sweep
• 0.05Hz-5MHz w/counter
• INT/EXT AM/FM mod

ALFA ELECTRONICS
P.O. BOX 8089
PRINCETON, NJ 08543-8089

TEL: (800)526-2532 / (609) 897-1135
FAX: 609-897-0206
E-mail: sales@alfaelectronics.com

Call / Write / Fax / Email for FREE CATALOG
Visa, MC, AMEX, COD, PO Accepted. OEM Welcome.
1 Year Warranty (2 Years for GW/Instek)

SALES & SERVICE: CB equipment, modification kits, meters, antennas, mics, radios, transistors, repairs & hard-to-find items. Complete list \$4. D&R Electronics, 10 Park St., Thomaston, CT 06787. 860-283-9492 or RTed821836@aol.com

240+ CHANNEL CB/HAM/COMMER-CIAL radios: AM/FM/SSB/CW export/domestic: RCI, Motorola, Uniden, Cobra, Alinco, Kenwood. Mics, antennas, linears, meters, books, night scopes, and tons more stuff! Catalog \$3. MAXTECH, Box 8086, New York, NY 10150. 718-547-8244.

SHOOTING STAR, Palomar, Superstar, Galaxy, Uniden, Cobra, exports, police & fire & military scanners, microphones, power supplies, antennas, modifications, repairs, more!! 15 yrs. in same location, 5 page picture price sheets \$1 (refundable). Galaxy, Box 1202, Akron, OH 44309. (Also, Red Devil & Messinger Products.)


KONNEX DISTRIBUTING. Call 1-888-777-7874. PO Box 451372, Los Angeles, CA 90045. CBs, antennas, meters, transistors. Best prices. Credit card acceptable.

CB, EXPORT RADIOS, AMPLIFIERS. Texas Star, Palomar, Falcon, Connex, Galaxy Superstar, Cobra, sound modules, microphones, surveillance/counter-surveillance. Catalog \$2 refundable. Specify catalog 505. **WIZARD ELECTRONICS**, PO BOX 8, IRON CITY, TN 38463.

CB MODIFICATIONS! Frequencies, books, kits, high-performance accessories, plans, repairs, amplifiers, 10-meter conversions. The best since 1976! Catalog \$3. CBCI, Box 1898NV, Monterey, CA 93942. www.cbciintl.com

COMPUTER HARDWARE

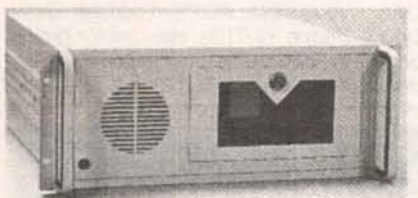WE CARRY a variety of cables, switch boxes, accessories, and adapters to connect PCs, printers, Mac's, networks, telecommunications, and audio/video equipment. We offer: custom cables, free catalogs, and same day shipping on most orders. Visit our website at www.rogerssystems.com or call 1-800-366-0579.



19" RACKMOUNT ATX PC chassis, \$169 (with ad). 972-242-8087, www.cti-tx.com



SONY PLAYSTATION GAME ENHANCER, mod-chip function plays backup COPY of CD. You do not need to have original loaded to play backup. Simply plug the enhancer in back of playstation! Skips both Sony logos, many preloaded cheat codes, type in more found on the Internet. Memory management function, view video/movie files from CD, PC computer link port \$29. Quantity prices available. 240 save game memory card \$25. Order now 847-657-1160 or on-line www.saveware.com

CRTs CHEAP. Buy direct from the manufacturer. Save money. Mfg. all CRT types since 1950. **3 year warranty.** Reg-Res 19" tubes \$75; 25" \$100; hi-res 13" tubes from \$80. We specialize in **hi-resolution** video/computer CRTs. T.M.C. 215-226-0749/215-223-0388.

PC CABLES: http://www.cablesusa.com 100s of hard-to-find new cables and parts, pictures, free technical information. Low prices, RS232, SCSI, keyboard, network, VGA, Cat-5, USB, Firewire, fast secure online ordering & browsing. 954-418-0817.



LOW-COST 12-BIT A/D KITS. \$59 LPT: Analog! PC printer-port interface acquires 8 analog signals. Also features two 12-bit D/A's, current sources for sensor excitation and digital I/O lines. QuickBasic and VB software included. 1-channel A/D only \$39. http://www.tgn.net/~adnav/ or E-Mail: adnav@tgn.net



433MHz PII system with Intel CELERON/A 128K cache MMX CPU, 6.2 gigabyte hard drive, 44X CD-ROM, 1.44 floppy, 32 megabytes SDIMM memory, 8MB AGP 3D video, 56K modem/voice/fax, 32 voice 3D sound, 360 watt speakers, multimedia keyboard, Internet mouse, ATX professional case, 2 year parts and labor warranty, with the best lifetime tech support to keep you and your computer happy! Only \$479! Everything installed with FULL versions WIN95B \$59, WIN98 \$119. Order now 847-657-1160 or on-line www.save-ware.com

C and H SALES COMPANY

2176 E. Colorado Blvd. • Pasadena, CA 91107

TOLL FREE:
1-800-325-9465

C & H SALES COMPANY HAS BEEN IN BUSINESS FOR OVER FIFTY YEARS. WE'RE THE BEST SOURCE FOR GREAT BUYS ON ITEMS LIKE THESE - AND MORE!

FREE
148 PAGE
CATALOG!

ELECTRONIC COUNTER

HEWLETT PACKARD, Model 5328A. Universal counter. Usable to 100 MHz, 100 ns single shot resolution. Has frequency, period, period average, ratio, totalize, scale functions. A built-in digital voltmeter allows measurements of input voltages. Two input channels provide individual slope, polarity and level settings. Has 9 digit LED readout. Input power 100-240 VAC 48-66 Hz 100 VA max. Dimensions: 17" wide x 17-1/4" deep x 3-1/2" high.

Stock #TE9808

\$250.00



SOLA CONSTANT VOLTAGE TRANSFORMER

SOLA ELECTRIC, #93-13-150. Harmonically neutralized constant voltage transformer. Rated at 500 watts. Input voltage 95 to 130 VAC 60 Hz. Output voltage 120 VAC. This unit is designed for rack or bench mounting. The meters on the front panel indicate output current and input/output voltage. A toggle switch is provided for selection of input or output voltage. The input voltage is connected at the rear of the unit via a covered electrical panel. Two standard 3-wire grounded electrical outputs are supplied on the front and rear panels. Dimensions: 19" wide x 14-1/4" high x 10-1/4" deep. Weight 59 lbs.

Stock #STR9900

\$225.00

MILLIOHMETER

HEWLETT PACKARD, Model 4328A. Designed to measure very low resistances. Measurement range 1m ohm to 100 ohms. Resolution 20 u ohms. Analog meter readout. Ideal for measuring contact resistance of switches or relays. This unit is also useful for measuring the resistivity of semiconductor devices. (Requires special 4 terminal probes which are not supplied, but probably are available from Hewlett Packard.) Power input: 115-230 VAC 48-66 Hz, 5 VA max. Dimensions: 5-1/8" wide x 11-1/2" deep x 6-1/2" high.

Stock #TE9812

\$200.00

ALTIMETER/BAROMETER

KOLLSMAN, #MC-2 MS28074-2. Scale type altimeter with barometric setting scale window. Altimeter scale range -1000 to 80,000 feet. Barometric range 28.1 to 31.0 inch of mercury. An adjustment knob is provided for scale setting to local altitude or barometric pressure. Has white numerals on a black background. Illumination is provided. Electrical input is rated 115 VAC 400 cycles. Pressure input port is female 7/16" X20 thread. Standard aircraft panel 3-1/8" mount. Dimensions: 2-17/64" sq. x 7-1/2" deep.

Stock #STOCK #IN9900

\$79.50

☒ Master Charge ☒ Visa ☒ American Express ☒ Discover

Call us first if you have surplus inventories of electronic, optical, or mechanical items for disposal

WE BUY & SELL!

Write in 40 on Reader Service Card.

Gibraltar Trade Center COMPUTER & TECHNOLOGY SHOWS

ATTENTION VENDORS

3 DAY
SHOW

\$65⁰⁰

PER 8' TABLE

- TREMENDOUS ADVERTISING SUPPORT
- IMPRESSIVE CROWDS
- EASY SET UP & TEAR DOWN
- CONVENIENT NEARBY HOTELS

TAKE A LOOK www.gibraltartrade.com

OVER 200
TABLES
ADMISSION
ONLY \$2.00
PER CARLOAD!



MT. CLEMENS, MI

NOVEMBER 19-21, 1999
DECEMBER 10-12, 1999
SUNDAY, DEC. 26TH 1999
(ONE DAY ONLY)

TAYLOR, MI

OCTOBER 29-31, 1999
NOVEMBER 26-28, 1999
DECEMBER 17-19, 1999

Gibraltar
TRADE CENTER, INC.

MT. CLEMENS, MI
I-94 & N. RIVER RD.
(EXIT 237) • 810-465-6440

TAYLOR, MI
I-75 & EUREKA RD.
(EXIT 36) • 734-287-2000

450MHz BAREBONE systems from \$250. 486 computers \$99. Brand new Pentiums from \$199. Motherboards \$20, 1.44/1.2 floppies, speakers \$10. Call 714-778-0450.

ISO-7816 PROGRAMMER READ & WRITE to ANY ISO-7816 device! *This ISO-7816 programmer is fully assembled and tested. The following is included: 1. Programmer module. 2. RJ11 data cable. 3. Com port adapter (com1 or 2). 4. UL approved power supply. Easy to understand instruction page. For IBM computers only, user must have a DX386 or better machine and use of the Internet. ONLY \$149.95 plus S/H. TO order, call 231-882-4079. *Type of software will allow programmer to work with any ISO-7816 device. Software for ISO-7816 devices are not provided, user must procure software and ISO-7816 devices. 90 day hardware warranty included!

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

TOSHIBA NOTEWORTHY hi-res 640x480 laptop video conferencing color cameras. Comes with adj. stand, wall power adapter, video conferencing/capture PCMCIA card bus card and video cable. Has focusable lens (macro to infinity), will run on two self-contained alkaline AA batteries. Size 3.5L x 2.4W x 1.1H. **NEW FACTORY BOXED** (ltd. qty.) \$125 each. Leave message 714-806-3268.

EVERYTHING NEW w/warranty! Motherboards with CPU 450MHz \$195, monitors 15" \$125. Pentium systems from \$195. Modems, multimedia kits, scanners, 2.5 gigabyte hard drive \$65. Call 714-778-0450. E-Mail: cci@surfside.net

COMPUTER SOFTWARE

MICROSOFT OFFICE97 Professional Edition. New factory sealed, unopened. **WORD, EXCEL, POWERPOINT, ACCESS** and **OUTLOOK** included. CD only. **ONLY \$49.95! FREE SHIPPING!** Quantity discounts available. bruce@msn.com

FREE IBM DISK CATALOG of quality Shareware and CD-ROMs. **MOM 'N' POP'S SOFTWARE <ASP>**, PO Box 15003-N, Springhill, FL 34609-0111. 352-688-9108. momnpop@gate.net

FORBIDDEN SUBJECTS³ hacking CD-ROM \$12 postpaid. Free troubleware diskette catalog. Amazing subject matter. No commercial or shareware here, just lots of technical fun! Peregrine Dynamics, 720 Portage Trl., Cuyahoga Falls, OH 44221-3035.

UNDERGROUND CDs: Health, hacking, phreaking, free energy, anti-gravity, time travel, many incredible electronic devices, and MP3 stuff: www.hi-tech-stuff.com

CAM & MOTION SW/HW: Z-trace, PCB toolpath. Plotcam motion control, step drivers. www.megabits.net/ddt MSG/FAX 407-452-7197, 407-459-2729. Heater@megabits.net

FORBIDDEN SUBJECTS³ hacking CD-ROM \$12 postpaid. Free hacking/phreaking/troubleware diskette catalog. Incredible subject matter. Peregrine Dynamics, 720 Portage Trl., Cuyahoga Falls, OH 44221-3035.

LIQUIDATION WINDOWS 95/98, Office suites \$10-69. 1,000 games \$25. Windows tutorials \$5. Mastering Windows 98 book \$10. 714-778-0450.

COMPUTER EQUIPMENT WANTED

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

HP CALCULATORS wanted: models 10, 70, calculator watch, others for private collection. Cash paid. Bob Morrow, 765-855-2348, rkmorrow@aol.com

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.**, 937-847-2300 OR fax 937-847-2350.

WANTED: TERMINALS + PRINTERS: DEC, Wyse, IBM, ADDS, Okidata, Data South, Epson, C.I.T.O.H., etc. Call for quote on any surplus computer equipment. Call Jeremy, 603-673-8077.

TEST EQUIPMENT

TEKTRONIX OSCILLOSCOPES: 434, \$125; 454, \$125; 454 w/cover, \$175; 465M like new with cover, \$350; 466/DM44, \$350; 7603/2-7A18/7B53A, \$250; 7603/2-7A26/7B53A, \$275; 7633R/2-7A26/7B53A, \$300; 7704A, \$175; 7904/7A19/7A26/7B53A/7B92A, \$600; 7A18A, \$50; 7A18, \$45; 7B53A new-in-box w/manual, \$85; P6019 probe kit w/134 amp & pwr. supply, \$150; P6021 probe kit w/134 amp & pwr. supply, \$150; P6021 probe, \$75. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, fax 520-760-7780. E-Mail: lcoppes@primenet.com

DISTORTION, ANAs: HP 339A, \$1,000; HP 334A, \$400; HP 331A, \$250; modulation anas., HP 8901A, \$900; HP 8901B rear inputs, \$1,200. A-Comm Electronics, 11891 E. 33rd Ave., Unit C, Aurora, CO 80010, 303-341-2283, fax 303-341-2293.

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 96 Page CATALOG. Outside the U.S.A. send \$3.00 postage.

Touchtone Keypad

Farbell # DU200P (A). Standard 12 button telephone keypad with touchtone (DTMF) circuitry. Field replacement for some GTE payphones. White plastic buttons with black numerals and letters. 11 color-coded leads, 9" long with spade lugs.

CAT # KP-11

25 for \$75.00

\$4.00 each

3/4" Protective Pads

Self-sticking 0.8" dia x 0.25" high black rubber discs. Use as feet, spacers, cushions and protectors. Packaged 36 per sheet.

CAT # RF-341

Minimum purchase 36 pcs.

360 for \$18.00 36 for \$3.60

Silent Footswitch

Control International, Inc. Quality, heavy-gauge metal footswitch designed for silent operation. S.P.S.T., normally-open, rated 11 Amps @ 250 Vac. No-slip rubber pad on top surface. 3' cable, 2 conductor 16 AWG, stranded wire. 3.56" X 2.73" X 1.36" high.

CAT # FSW-9

\$5.50 each

3000 MCD ULTRA-BRIGHT RED LED


Everlight # 383URC-2/TR1-C(R) Red, "Ultra-bright" T 1 3/4 LEDs "Tape-and-reel" parts. These are 5 mm diameter water-clear LEDs that light bright red at 20 ma.

CAT # LED-50

2 for \$1.00

100 for \$35.00
1000 for \$250.00

REDUCED PRICE! 185 Watt Power Supply

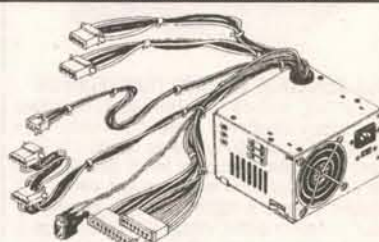

Compaq # 172417-002 (172432-001)

Input: 120/240 Vac (switchable)

DC outputs: +5V @ 18A, +3.4V @ 12A, +12V @ 6A, -5V @ 0.15A, -12V @ 0.15A.

Size: 6.5" x 5.75" x 3.85" Built-in fan. On/off switch on 20" lead. Power cord not included. UL, CSA.

CAT # PS-185

\$7.50 each

40 RPM Gearhead Motor

Pittman #

GM8212C127-R2.

Small, powerful gearhead motor.

187:1 ratio. No load specs: 40 RPM @ 19.1 Vdc, 130 mA. 24 RPM @ 12 Vdc, 160 mA. Overall dimensions 3" long X 1.37" diameter. 0.185" (3/16") diameter X 0.75" long shaft. A brass 0.56" diameter gear with 16 cogs is fastened to the shaft. 17" leads.

CAT # DCM-135

\$15.00 each

10 for \$125.00

S-VHS Video Tapes (Used)

Super VHS tape users! Save a bundle on name-brand S-VHS, T-120 tapes. These tapes were used for a brief period, then bulk erased. The record-protect tabs have been broken out, so you will have to cover the notch with a piece of tape, but they work great.



CAT # S-VHS

\$3.00 each

10 for \$28.00 • 100 for \$250.00

20 Character X 4 Line LCD

Optrex # DMC 20434-CEM

(PWB 20434-CEM)

5 x 8 dot format.

3" x 1" viewing area.

3.88" x 2.38" module.

Removed from new equipment. May have felt padding on metal bezel. 14 pin single row header is pre-attached. Spec/hook-up sheet included.

CAT# LCD-46

\$7.00 each

10 for \$60.00

Snap-In Capacitor

560 UF 400 Vdc - NICHICON CE

85° C LQ (M). 1.39" dia. X 1.83" h.


0.4" lead sp. CAT# EC-5640

10 for \$3.75 each

100 for \$3.00 each

\$4.00 each

Five LED Chaser

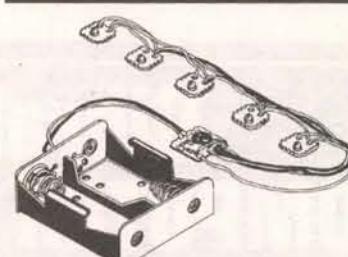

An inexpensive, eye-catching display. Five bright red LEDs flash sequentially at approximately 1 cycle per second. The LEDs are 3 mm diameter, T-1 size, clear in the off-state. Each led is mounted on its own 0.7" x 0.85" pc board and is part of a 20" string which can be positioned to suit your needs. The flash rate can be slowed or speeded with the addition of a pot or resistor. Operates on 3 Vdc, or higher with the addition of a resistor. We supply a simple modification sheet for changing flash rate. Includes a battery holder for two D cells.

CAT# CSR-5

\$2.75 each

10 for \$25.00

ORDER TOLL FREE

1-800-826-5432


MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
SHOP ON-LINE www.allelectronics.com
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

HEWLETT PACKARD 141T, \$300; 141T w/8552B, 8553B, \$850; 8552B, \$350; 1630A w/pods, \$300; 1741A, \$200; 1980B, \$300; 331A, \$75; 3325A opt. 1 & 2, \$850; 333A, \$175; 334A, \$200; 3330B/3571A, \$650; 33320H, \$200; 33322H, \$200; 3400A, \$85; 3455A, \$200; 3456A, \$350; 350D, \$35; 355E, \$50; 355F, \$50; 3575A opt. 1, \$300; 423A, \$75; 4260A, \$200; 435B/scales, \$250; 436A, \$500; 436A w/cable & 8484A, \$750; 436A/022, \$550; 456A, \$100; 5006A, \$200; 5257A, \$75; 5300A/5302A, \$100; 5314A, \$150; 5315B, \$300; 5326A, \$50; 5328A/11/96, \$150; 5335A, \$350; 5335A/10/20, \$500; 5335A/10/20/30/40, \$850; 5342A/1/3/11, \$900; 5342A/1/11, \$800; 5345A no opt. \$250; 5383A, \$200; 54100A w/pods, \$1,250; 54201D, \$650; 59401A, \$75; 8660C with opts 1, 5, 100, 86603A, 86635A, 86632B, \$2,500. All with 30-day warranty, 10-day inspection. **Coppes Enterprises, 520-749-8471, fax 520-760-7780. E-Mail: lcoppes@primenet.com**

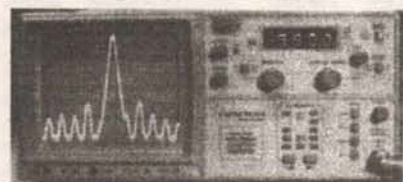

ENGINEER TESTED: Spectrum analyzers, frequency counters, frequency standards, meters, scopes, generators, curve tracers, and more. **VISA, MASTER-CARD, AMEX.** "Performance tested." **NIST calibrated.** Warranted. **New & used.** Contract engineering. Gary N6ZD. [HTTP://TECH-SERVICES.COM](http://TECH-SERVICES.COM) 831-385-7519.

FEITEK PROVIDES repair, calibration and traceable certifications of test equipment. Free estimates. We buy, sell and trade all makes of test equipment. Visa and MasterCard accepted. Check out our inventory and specials at WWW.FEITEK.COM 2752 Walton Road, St. Louis, MO 63114, 314-423-1770.


HP 4815A Z-meter: Expert restoration or verification to HP/QA factory specs. Former HP tech/supv, tel 908-852-7989 or E-Mail: GeoSA4815@compuserve.com Webpage: <http://ourworld.com/puserve.com/homepages/GeoSA4815>

KENTRONIX TEST EQUIPMENT SPECIALS. Check our WEB site at <http://www.kentronix.com> for monthly specials. We are also looking to buy test equipment, coaxial and waveguide components, manuals, etc. Contact Brian at 732-681-3229 or FAX 732-681-3312. E-Mail: brian@kentronix.com

TEKTRONIX DC5010 350MHz counter, \$400; HP 606B sig. gen., \$250; GR1606A RF bridge, \$250; Wavetek 5081. 1 step attenuator DC-1GHz, 0-81db, 10, 1, .1db steps, 50 ohm, \$100; HP K422A detector, \$150; Tektronix LC130, LC meter, \$150; Krohn-Hite 3323 solid state variable, hi pass low pass, band reject dual filter 10Hz-100KHz, \$450; Wavetek 182A 4MHz function gen., \$150; HP 5004A signature ana., \$150. A-Comm Electronics 303-341-2283, fax 303-341-2293, sales@a-comm.com

AILTECH EATON NM37/57A EMI receiver 30MHz-1000MHz, \$1,000; HP 8640B, \$1,000; HP 8640B opt 02, \$1,500; HP 8165A programmable signal source 1mhz-50MHz, HPIB, \$900; HP 8620C, 86290B, 2-18.6GHz, sweeper and frame, \$2,200; PTS 040 .1-40MHz synthesizer, \$500; PTS 200 1-200MHz freq synthesizer, \$600; HP 4935A TIMS, \$900; Sencor SC61 wave ana. 0-60MHz scope freq and PK-PK digital read out useable to 100MHz, \$450. A-Comm Electronics 303-341-2283, fax 303-341-2293.

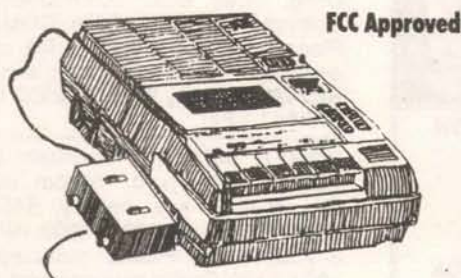TELEPHONE LISTENING DEVICE WITH 12 HR. RECORDER



FCC Approved

Record telephone conversations in your office or home. Starts automatically when phone is answered, records both sides of phone conversation. Recorder stops when phone is hung up. \$99.95 + \$7 shipping. For telephone listening device separately \$19.95 + \$2 ship.

For comprehensive 50 page catalog of Micro Video, VHF transmitters, Surveillance, and Counter-surveillance and much more! Send \$3.00

Call 407-725-1000

USI CORP

P.O. Box N2052 Melbourne, FL 32902
COD'S OK

Write in 42 on Reader Service Card.


Programmers Designers Engineers Hackers

Are you an expert with Microchip's®
PIC® Microcontroller Series?

If you're really good at writing .asm code using MPLAB and MPASM for the 16C/F series and have a strong electronics background in digital circuits, you are invited to use your talents and possibly do some design work for us.

We're a multi-million dollar international electronics company in search of a few good independent subcontractors who can work at home to help us develop some brand new products for the security industry, on a fast track basis. If you already have some neat products you think we may be interested in, let us know.

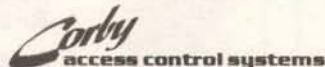Please send your complete technical qualifications and a detailed list of abilities and achievements to: glenn@corby.com and be sure to put "NV99" in the subject header.



HP 4800A Vector Z meter, \$850; HP 5340A, 18GHz ctr opt 010, \$1,200; HP 3581C level meter, \$800; HP 8363B sig. gen., 2.3-6.5GHz, \$1,500; HP 618C sig. gen., \$400. A-Comm Electronics 303-341-2283.

TEST EQUIPMENT for sale/wanted (NEW/USED): RF, Microwave, video and fiber optic. Cable TV, Broadcast TV, satellite and related industries. Wavetek, Tektronix, Hewlett Packard and other manufacturers. Spectrum analyzers, signal level meters, sweep systems, TDRs, OTDRs, and much more. **PTL Test Equipment, Inc.** Phone 561-747-3647 FAX 561-575-4635. E-Mail: PTLTE@aol.com <http://www.PTLTEST.com>


POOR MAN'S Spectrum Analyzer/Monitor Receiver Kit. 2 to 1,700 MHz. Basic kit only \$98. Now available with switched resolution filters, tracking generator and direct digital frequency readout. Works with ANY scope or IBM compatible computer. Send stamped envelope for details. Science Workshop, Box 310B, Bethpage, NY 11714. <http://www.science-workshop.com>

HP 4944A, TIMS, \$400; HP 5423A structural dynamics ana., \$1,000; Tektronix 620 XY display, \$300; HP 461A, \$150; HP 465A, \$150; HP 7475A, RS232 plotter, \$150. A-Comm Electronics 303-341-2283, fax 303-341-2293, sales@a-comm.com

FOR THE BEST PRICES ON PROFESSIONAL TOOLS, CALL ELECTRO-TOOL



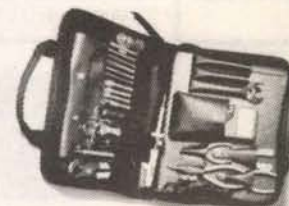platt - Case - Deluxe Polypropylene. Chemical Resistant. Tools by CooperTools and others. 800T Case, complete with tools ... \$419.95
800T Case Only ... \$121.80




platt - Case - Cordura Exterior. Two exterior pockets & one literature pocket. 660ZT Case, complete with tools ... \$223.00
660ZT Case Only ... \$59.45
Optional Sperry meter #DM6510 as shown ... \$65.00



Weller WCC100 - Electronically controlled station, temperature adjustable from 350°F-850°F. Zero voltage circuit-safe for sensitive components, 40 Watt pencil ... \$97.90



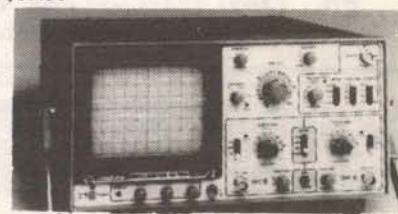OptiVISOR - Superior magnification, Optical Glass Prismatic lenses (not plastic). Select any one of (6) magnifications ... \$24.00



GoldStar - 20 MHz Dual Trace Oscilloscope OS-9020A-Large 6" rectangular, high sensitivity: 1mV/div, high accuracy: ±3%, stable, low-drift design, 8 divisions of displayed dynamic range and accurate, distortion-free waveform measurements ... \$372.00

Electro Tool, Inc.



9103 Gillman, Livonia, MI 48150
Customer Service: (734) 422-1221
ORDERS ONLY: 1 (800) 772-3455
FAX: (734) 422-3432



"Tools American Made."

DESOLDER STATIONS: PACE:
MBT100 \$225, **MBT200** \$325, **PPS100** \$200, **PPS85** base for **MBT250** \$350, **MBT220** \$700. **Weller DS100** \$200, **DS1000** \$250. **Hot tweezer** \$50, **ultrasonic cleaner** \$75, **hot plate** \$75, **digital solder pot** \$150. **Hakko 850**, **Pace MP-1**, **hot air SMD** \$700, **solder stations: digital readout Weller EC2000** \$100, **EC2002M** \$225 new, **WTCN** \$50, **EC1301** \$50 nu, **TC201** \$50 nu, **EC1201AFE fumex pencil** \$75, **WCP1** electric rotary sponge \$25 310-515-2058.


IFR 1200 with spectrum normal 2MHz, Birdie 250KHz to 1GHz, \$5,500. 661-269-0555.

LOWEST COST LCD'S ON EARTH



VIDEO LCD

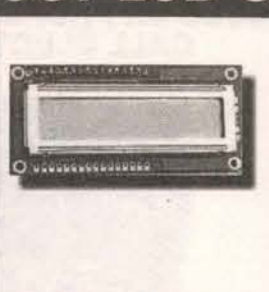4 Inch Video NTSC \$150
Sharp P/N 4LU4E
Composite NTSC & RGB Input
12:00 OR 6:00 Viewing Angle
Integrated Backlight & Inverter
Extended Temp: -10 to +60 C
Brightness: 260 nits
Power Consumption: 4.3 Watts
Contrast: 50 to 1



CHARACTER LCD

OPTREX DMF-5005SN-EW
240 x 64 Graphic EL Backlit STN \$30
OPTREX DMF-5005N
240 x 64 Graphic Reflective STN \$30
SANYO DM2023-7G1
2 x 20 Character Reflective STN \$8
SHARP LM20A21
2 x 20 Character Reflective STN \$8
VIKAY 2035TNLD NOTW-D
2 X 16 Character LED Backlit STN \$8



LCD MONITOR

10.4" DSTN or 12.1" TFT
Analog SVGA Input
Autosync
Auto Sizing
Automatic Expansion of VGA
images to SVGA (On 12.1")
Very Aggressive Pricing
Starting under \$500!



TOUCH MONITOR


EarthVue 10.4
10.4" VGA TFT
Analog VGA Input
105 Nit Brightness
RS-232 Touch Screen Option
Only 9.9"W x 7.7"H x 1.5"D
Ideal For Factory Automation
Fully Articulating Ball Mount
Only \$1095 With Touch



LCD DISPLAYS

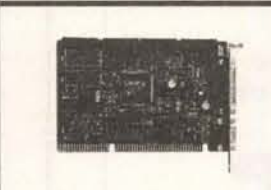6.3" Mono STN \$60
9.4" Mono Reflective \$60
8.4" TFT \$250
9.4" DSTN \$150
10.4" TFT \$350
10.4" DSTN \$240

NoteBook Screens
340 Models in Stock
Obsolete Screens Stocked
Hard To Find LCD? Call!



CONTROLLERS

ISA
PCI
PC/104
NTSC
Analog VGA
Complete LCD Kits with LCD,
Controller & Cable Starting
under \$200



EARTH

Computer Technologies

"The World Leader In LCD Recycling"

Ph: (949) 361-2333 Fax: (949) 361-2121

<http://www.flat-panel.com>

Write in 43 on Reader Service Card.

BRUEL & KJAER BUY, SELL, BEST PRICES. EXCALIBUR ENGINEERING, 3198-C AIRPORT LOOP DRIVE, COSTA MESA, CA 92626. 714-540-0169, FAX 714-540-5417.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 OR fax 937-847-2350.

POWER METERS: Wavetek 1034A, 10MHz-20GHz, +10, -50dbm AC with rechargeable new battery, \$450; HP 436A, 8484A, opt 022, \$1,000; HP 432A, 8478B, \$400; Pacific measurements 1009, \$150; Pacific measurements 1036, -40, +10dbm, \$150. A-Comm Electronics 303-341-2283, fax 303-341-2293, sales@a-comm.com

WE BUY & sell test & measurement equipment. <http://www.a-comm.com>

EQUIPMENT CLEARANCE. Electronic test, avionics test, NDT. Most 8 yrs old+. For list, E-Mail: amslsovt@sover.net Andrew Smith, AMSL, Vermont, USA 802-254-9459.

OSCILLOSCOPES: OFFERS accepted, Hewlett Packard 1725A, \$200; 1740A \$150; 1741A \$200; Tek 7904 w/7A26, 7A24, 7B80, 7B85 with manual, \$600. 1101 probe supply, \$65, 4 available, 1142A probe control power module, \$250, 4 available; Hitachi V 422 o'scope w/manual & probes \$250; TEKTRONIX 7104 w/7A29, 7B10, 7B15 1GHz, 2 channel o'scope \$2,350. **Psitech Plus** 707-745-4804.

AFFORDABLE HP power sensor repair! Most 8481As repaired for \$255 or less. We also handle 478As and many others. Call or fax for more information. Willamette RF, Inc., 541-754-7226, FAX 541-753-4629.

NEW, FASTER POCKET TESTBENCH, tiny, inexpensive, portable RS-232 instrument, with scope, logic, counter, generator modes. Oricom Technologies, 303-449-6428. www.sni.net/~oricom

PEPPER SYSTEMS: High quality test equipment. <http://home.earthlink.net/~peppersys> 214-353-0257, (fax 214-902-9511). E-Mail: peppersys@earthlink.net

HEWLETT PACKARD: Programmable signal generator 8656A opt 001, 002 w/ HP installed attenuator 11810A, \$850; 1024MHz signal generator 8640B opt 002, 003, \$1,200; audio analyzer 8901A, \$550, 8901B modulation analyzer, \$1,250; spectrum analyzer 141T, spectrum analyzer frame, \$300. Offers accepted. Psitech Plus 707-745-4804. Check our new www.psitech-plus.com


EQUIPMENT SALE: Hewlett Packard 3336C synthesizer & level generator with options 004, 005, \$1,000; Wavetek 3001 signal generator, \$300; Hewlett Packard 8015A opt 03, \$350; 8015A \$250; HP 3403C opt 03 TRMS voltmeter, \$300, 3403C \$200; HP 3763A error detector, \$300. Offers accepted. Psitech Plus 707-745-4804. Check our new www.psitech-plus.com

TEK TM500: AM503/A6302, \$650; AM503/A6303, \$1,000; DC504, \$75; DC509, \$100; DC5009, \$200; DM501, \$65; DM501A, \$85; FG5010, \$500; PG501, \$50; SC502, \$200; TM5006, \$300; TM501, \$50; TM503, \$65; TM506, \$85; TM515, \$85. All with 30-day warranty, 10 day insp. **Coppes Enterprises**, 520-749-8471, fax 520-760-7780. E-Mail: lcoppes@primenet.com

POWER SUPPLIES: EMI TCR 10S90, \$200; EMI TCR 150S7, \$250; EMI TCR 40S25, \$250; EMI 20S50, \$250; Fluke 4216A, \$150; Fluke 4265A, \$200; Fluke 4265A/GPIB, \$250; 6186C, \$300; 6265B, \$150; 6267B, \$250; 6521A, \$500. All with 30-day warranty, 10-day insp. **Coppes Enterprises**, 520-749-8471, fax 520-760-7780. E-Mail: lcoppes@primenet.com

SECURITY

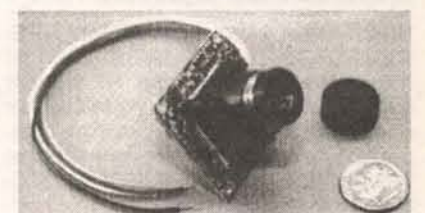STOP THEM from listening in or recording your telephone conversations with the **TELEPRIVACY-PLUS**. Send \$49 to Vakis, 1402 Pine Ave., Niagara Falls, NY 14301.



B/W 430 LINE CCD CAMERA with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. Price @ 10 pcs., \$44 each. Enclosure: \$8; optional lens: \$18. Dealers welcome. **MATCO, Inc.** 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com Website: www.mat-co.com



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

Miniature Transmitters and Receivers

2 Button / 3 Channel Transmitter



RF300T

1....\$22.95
5....\$19.95 ea
10....\$16.95 ea

RF300XT

1....\$25.95
5....\$22.95 ea
10....\$19.95 ea

- 300' (XT), 150' (T) Range
- Frequency: 318 MHz
- 59,049 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.8 ma
- Fully Assembled in Case
- Dimensions: 1.25" x 2.0" x .5"
- Push both buttons for the 3rd Channel
- Slide Button Cover Included

4 Button / 15 Channel Transmitter



RF304XT

1....\$27.95
5....\$24.95 ea
10....\$21.95 ea

- 250' Range
- Frequency: 318 MHz
- 6,561 Settable Security Codes
- 12 Volt Battery and Keychain Included
- Current Draw: 4.6 ma
- Fully Assembled in Case
- Dimensions: 1.35" x 2.25" x .5"
- Push combination of buttons to achieve up to 15 channels

2-4 Data / 3-15 Channel Receivers



RF300RL RF300RM

1....\$27.95
5....\$24.95 ea
10....\$22.95 ea

RF304RL RF304RM

1....\$29.95
5....\$26.95 ea
10....\$23.95 ea

- Compatible with 300/4 Transmitters
- 11-24 volts DC Operating Voltage
- 13 ma. Current Draw
- Latching (L) or Momentary (M) Output
- Kits Available (subtract \$5.00 ea.)
- Dimensions: 1.25" x 3.75" x .5"
- 2 (300) / 4 (304) Output Data Lines
- Binary to Dec / Hex Converter can achieve up to 15 channels

- Alarm Systems
- Garage / Gate Openers
- Lighting Control

- Magic Props
- Medical Alert
- Monitoring Systems

- Industrial Controls
- Surveillance Control
- Motor Control

- Schematics Available
- Receiver Board Layout Available
- Custom Design Consulting Available


Visitect Inc.

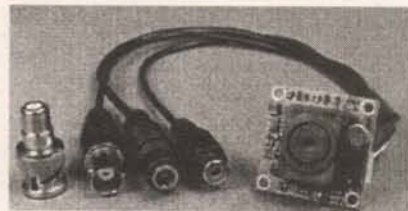(510) 651-1425 Fax: (510) 651-8454
P.O. Box 14156, Fremont, CA 94539

Email: Support@Visitect.Com
Visa / Mastercard, COD



CONVERTS PC MONITOR to SECURITY MONITOR. The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size, 4-1/2" x 2-1/2" x 3/4". Over 600 lines of resolution, twice that of standard TV monitor! High quality audio output feeds speakers directly. Excellent grey-scale conversion; works well with B/W inputs. Power supply included; \$69 each. Dealers welcome. **MATCO, Inc.,** 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com Website: www.mat-co.com



B/W BOARD camera w/audio, \$49 @ qty 10, 1.27" x 1.27". Enclosure available for \$10. **Matco, Inc.,** 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com



SALE! PS 102: Built-in pin hole CCD, lens size: 3.6mm. 5-1/2" (D) x 1.7" (H). \$79 @ 5 pcs., \$72 @ 10 pcs. Distributors welcome. **Matco, Inc.,** 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com




SPECIAL! IC 113: PIR motion detector with audio! W/ NO/NC alarm output. CCD camera with audio can be turned on by detector. 5-1/4" (L) x 2-3/4" (W) x 2" (D). \$89 @ 5 pcs., \$82 @ 10 pcs. **Matco, Inc.** 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com




AS-1004, FCC approved. 2.4GHz transmitter & receiver with audio! Capable handling total of 4 wireless cameras, range: >300'. Built-in camera, 400 TV line. \$189 a pair @ 5 pcs., \$179 @ 10 pcs. Additional camera \$119 @ 10 pcs. **Matco, Inc.** 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com

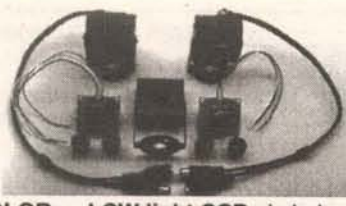CONSUMERTRONICS 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS.** Catalog \$3. PO Box 23097, Albuquerque, NM 87192. **www.tsc-global.com**



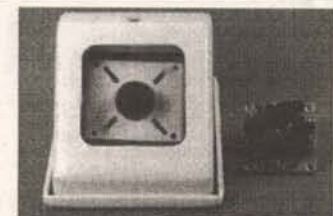COLOR — LOW light CCD pin hole and standard lens available, only 1.27" x 1.27", \$109. Sony sensor with audio. **Matco, Inc.,** 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com



WEATHERPROOF ENCLOSURE for board cameras, fits all 30-42mm color/back & white cameras, \$59. **Matco, Inc.,** Schaumburg, IL 1-800-719-9605 Fax: 630-350-9546. E-Mail: nsales@mat-co.com Web site www.mat-co.com

SURVEILLANCE-COUNTERSURVEILLANCE: I buy and sell used equipment. **Steve** 410-879-4035.

SEEKING DISTRIBUTORS FOR SECURITY PRODUCTS. **Matco, Inc.,** Schaumburg, IL 630-350-0299. **www.mat-co.com**

WIRELESS VIDEO audio Wavecom Jr., \$95; Wavecom Sr., \$140; Baby monitor, \$180. Tel 1-800-600-4974, **www.aljon tech.com**

SATELLITE EQUIPMENT

THE BEST is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at **www.acdinc.com** for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

Quality Used Test Equipment

90 DAY WARRANTY Parts & Labor - 10 DAY TRIAL PERIOD

HEWLETT PACKARD

11570A, Accessory Kit (use for 8405A calibration)	\$300
11720A, Pulse Modulator, 2-18 GHz, >80dB on/off ratio	\$400
11975A, 2-8GHz Amplifier (use w/ 11970 series mixers)	\$1750
214B, 10 MHz Pulse Generator, 200W Pulse/50 ohms	\$700
2225A, ThinkJet Printer, HP/IB	\$125
239A, Audio Oscillator, 0.025% (-93dB) THD	\$250
3314A, Arbitrary/Function Generator	\$1250
3325A-2, 21MHz Synth Func Gen, 40Vp-p, HP/IB	\$850
3332Z, Prog Attenuator, DC-18GHz, 0-110dB	\$200
3403C, Digital RMS Voltmeter, 2 Hz-100 MHz	\$150
3421A-201/4462A, Data Acquisition Control Unit, HP/IB	\$325
3455A, 6.5 digit Multimeter, HP/IB	\$250
3456A, 6.5 digit Multimeter, HP/IB	\$450
3468B, 5.5 digit Multimeter, HP-IL	\$300
3478A, 5.5 digit Multimeter	\$350
3488A, Switch/Control Unit	\$350
3497A, Data Acquisition/Control Unit	\$150
3498A, Data Acquisition Extender	\$300
3852A, Data Acq/Control Unit	\$800
435A, Power Meter w/sensor cable	\$200
436A-02-022, Power Meter w/ sensor cable, HP/IB	\$550
44462A/63A, 8 Chan MUX/2 Chan Actuator (3421A)	\$135
491C, Amplifier, 2 GHz-4GHz, 1 Watt, 30dB Gain	\$250
5004A, Signature Analyzer	\$200
5180A, Waveform Recorder, 20MHz	\$500
5314A, 100 MHz Counter	\$150
5315B, 100 MHz Counter	\$200
5316B, 100 MHz Counter, HP/IB	\$275
5328A-011-020-030, 512 MHz Counter w/DVM, HP/IB	\$225
5334A-060, 100 MHz Counter, front & rear input, HP/IB	\$300
5334B, 100 MHz Counter, HP/IB	\$400
5335A, 200 MHz Counter, HP/IB	\$575
5335A-10-40, 200 MHz Counter, Oven Oscillator, HP/IB	\$725
5342A, Microwave Counter, 18GHz, Oven Osc, HP/IB	\$900
6034A, Dig Autoranging Pwr Sup, 60V/10A/200W, HP/IB	\$650
6034L, Dig Autoranging Pwr Sup, 60V/10A/200W, HP/IB	\$575
6110A (Harrison), Pwr Sup, 3KV @ 6mA	\$150
6253A, Dual Pwr. Sup., 0-20V@3A	\$275
6255A, Dual Pwr Sup, 0-40V@1.5A	\$350
6267B, Pwr Sup, 0-40V @ 10A	\$450
6268B, Pwr Sup, 0-40V@30A	\$600
6271B, Pwr Sup, 0-60V@3A	\$225
6284A, Pwr Sup, 0-20V@3A	\$100
6289A, Pwr Sup, 0-40V@1.5A	\$100
6294A, Pwr Sup, 0-60V@1A	\$100
6515A, Pwr Sup, 0-1.6KV@5mA (cable kit incl)	\$200
7550A, Graphics Plotter, HP/IB	\$200
7570A, Draft Pro Plotter, HP/IB	\$250
8111A, 20 MHz Pulse/Function Generator, 16Vp-p	\$1250
8160A, 50MHz Programmable Pulse Generator, HP/IB	\$1600
8447A, RF Amp, 0.1-400MHz, 20dB gain, +6dBm out	\$300
8472A, Crystal Detector, 0.01-18 GHz	\$100
8481A, Power Sensor, 0.1-18 GHz, -30 to +20dBm	\$475

8496H, Programmable Attenuator, DC-18 GHz, 0-110 dB	\$375
8501A, Storage Normalizer (use w/8505A)	\$750
8504A, Transistor Test Fixture Kit	\$500
8513D, 3.5MM Test Port Cable Set (new) use on 8515A	\$475
8566A, Spectrum Analyzer, 100Hz-22GHz, HP/IB	\$12500
8568B, Spectrum Analyzer, 100Hz-1.5GHz, HP/IB	\$7500
8569B, Spectrum Analyzer, 0.01-22GHz, HP/IB	\$5000
8640B, Signal Generator, 0.5-512 MHz, AM/FM/Pulse	\$700
8660C/8663B/86603A, 2.6GHz Synth Sig Gen	\$1800
8662A, Synthesized Signal Generator, 0.1-1280 MHz	\$15500
8672A opt 4 & 8, Synth Signal Generator, 2-18GHz	\$4000
8903B-001, Audio Analyzer, 20 Hz-100 KHz, rear input	\$1500
9411B, Switch Controller, HP/IB	\$450
9413A, VHF Switch	\$450
E1407A, VXI A/B-C-Size Active Adapter	\$200

TEKTRONIX

1240-05(4)DI's, Logic Analyzer w/ (4) P6460 probes	\$650
2465B, 400 MHz O'Scope, 4-channel	\$3600
7854, Keyboard Only	\$125
7A24, 400MHz Dual Trace Amplifier	\$175
7B92A, 500MHz Dual Time Base	\$125
A6302, Current Probe	\$300
AM503, Current Probe Amplifier	\$250
P6136, 10X probe, 350 MHz, use w/2400 series o'scopes	\$100
P6452, Data Acquisition Probe (use w/ DAS9100)	\$150
P6460, Data Acquisition Probe (for 1240/1241 Analyzer)	\$150
PG502, 250 MHz Pulse Generator, use w/TM500 series	\$300
PS503A, Triple Pwr Sup, 0 to +/-20V@1A, 5V@1A	\$150
TD5460-IM, 350 MHz Digital O'Scope, 4-Channel, extra memory, includes 2 new P6138A probes & manuals	\$4500
TD540A-1F-IM, 500 MHz Digital O'Scope, 4-Channel, extra memory, 1.44 floppy, 4 new P6139A probes, manuals	\$8000

MISCELLANEOUS

AstroMed ASC902, Medium Gain Amplifier Plug-in	\$100
Boonton 92BD, RF Millivoltmeter, 10KHz-1.2GHz	\$250
Clarostat 240C, Power Decade Resistor, 0-1,111,110 ohm	\$150
Eaton DSR5-5DA, 7-Decade Synchro/Resolver Std	\$800
EIP 545A-05-08, Microwave Counter, 10 Hz-18 GHz	\$550
EMI TCR160T30, Pwr Sup, 0-160V@30A	\$700
Fluke 6010A, Synthesized Func Gen, 10Hz-11MHz, GPIB	\$225
Fluke 8922A, Digital RMS Voltmeter, 2 Hz-11 MHz	\$400
GenRad 1538A, Strobosc, 110-1500 RPM strobe	\$350
Heise 711B, Digital Pressure Gauge, 0 to 30 PSI, .05%	\$350
Interface 553, Mil-Std-1553 Analyzer	\$850
Kepco BHK1000-0.2M, Pwr Sup, 0-1000V @ 200mA	\$275
Microdyne 1400-MR Telemetry Receiver w/Plug-ins	\$800
PAR 128, Lock-in Amplifier, 0.5Hz-100KHz	\$500
RF Power Labs M102L, RF Amp, 30Hz-100MHz, 2W	\$450
Sorensen DCR20-115B, Pwr Sup, 0-20V @ 115A	\$475
Sorensen SRL40-25, Pwr Sup, 0-40V@25A	\$475
Wavetek 178, 50MHz Programmable Waveform Synth	\$900
Wavetek 271-02, 12MHz Pulse/Func Gen, GPIB	\$400
Wavetek 859, 50 MHz Prog Pulse Generator, GPIB	\$575

Come visit us at our new website: **www.testequipmentplus.com**



TEST EQUIPMENT PLUS
(520) 575-6967, FAX (520) 575-6936
3331 W. Bright Terrace, Tucson, AZ 85741



Write in 46 on Reader Service Card.

World Passing You By?

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind; this is information you need to know!



Examples Include:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.
11 EMAC WAY, CARBONDALE, IL 62901
618-529-4525 Fax 457-0110 BBS 529-5708
World Wide Web: **http://www.emacinc.com**

1985 - 1998
OVER
12
YEARS
OF SERVICE

Write in 45 on Reader Service Card.

PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS



See Table Of Contents: **http://www.sq-1.com**
Secure Online Ordering is Available

PIC is a trademark of Microchip Technology Inc.

SQUARE 1 ELECTRONICS

Voice (707) 279-8881 Fax (707) 279-8883

http://www.sq-1.com



SEXTANT

Aircraft or marine navigation. No case. AS-IS **\$50**



SINGER CSM-1 COMMUNICATIONS SERVICE MONITOR



RF signal source: 0 to 600MHz in 100MHz steps plus 100Hz vernier. RF output: 110 to 0 dBm, built-in oscilloscope monitor. Inputs: RF, detected, vertical, horizontal, AM/FM. Outputs: audio, tone, RF.

Functions: generate 2mV to 2mV. AGC: manual or auto. **\$295**

TELEGRAPH KEYER

Unique item for military collectors. J37 telegraph key, new in original government package. **\$49.95**




AN/URM-120 50 OHM THRU-LINE RF WATTMETER


Frequency range: 2MHz to 1000MHz. Power range: 10 watts to 1000 watts. USWR≤1.08 to 1. Uses three plug-in coupler elements (included). CU-753 2 to 30MHz 50 to 100 watts CU-754 25 to 250MHz 10 to 500 watts CU-755 200 to 1000MHz 10 to 500 watts. Connector: Type N. Case included. Size: 7"Wx6-5/8"H x7-1/5"D. Weight: 6.5 lbs. **Price: \$395**

LAMBDA LK344A-FM POWER SUPPLY

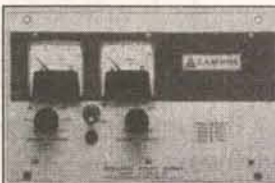Front panel voltage and current meters. Con-vection-cooled, no blower. Voltage adjustable from 0 to 60 VDC at a maximum current of 4A. Regulation 0.015% or 1mV. Line or load. Series/parallel operation. Remotely programmable by voltage or resistance. Less than 500µV RMS ripple. Constant current/constant current. **NEW Price: \$395**



NEW LOWER PRICE: \$295

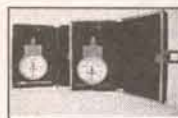

JONES MODEL 1600-1 TACHOMETER

Instrument tachometer centrifugal mechanical tach measures RPM scale 0-500 RPM, coupling shaft 1/8" accessories, various size rubber tipped drive couplings, case new. Also Jones Model 1600-7 RPM scale 0-11,000 RPM w/accessories. **New \$35/ea. or 2 for \$50**

HP 8640B SIGNAL GENERATOR OPT 003



CONDITION CODE "A"

Frequency: 500KHz to 512MHz. Indicates to 1024MHz. Requires external frequency doubler for 1024MHz (supplied with unit). Readout can be used as a frequency counter. Accuracy: 6.5 digits expandable to X10 and X100. Output: 145dBm to +19dBm (0.5 to 512MHz). Modulation: AM, FM, pulse, 400 and 1KHz, 1mV to 1V internal. Has input and output of modulation sources.

**BEST
BUY**

**\$1,095
\$775**

Write in 47 on Reader Service Card.

SATELLITE RADIO BOOK AND GUIDE. New book covers all Audio Services, SCPC, Subcarriers, FM Squared, Facsimile, Press Services, Weather Services. Simple how-to-receive instructions. \$16.95 plus \$3 Priority Mail. UNIVERSAL ELECTRONICS, 4555 GROVES ROAD, #12, COLUMBUS, OH 43232. 614-866-4605.

FREE SATELLITE TV SYSTEM! Now is the time to get a small dish. Call 626-568-0903 and give certificate number 0141002. www.iwantadish.com



FREE BIG dish catalog. Low prices! Systems, upgrades, parts, and "4DTV." Skyvision, 1010 Frontier Dr., Fergus Falls, MN 56537. www.skyvision.com Call 1-800-543-3025.

CABLE TV. Join us on the INTERNET to buy and sell cable TV equipment, electronic equipment, DSS equipment, satellite equipment, telephony equipment, and much more. Major equipment dealers and wholesalers online. Auctions, classified ads, discussion forums, chat rooms, and dealer links for all types of equipment. Dealers and vendors call or visit our site for ad rates and links. **WWW.GOCABLETV.COM** or call 1-800-451-0083.



BEST PRICING on 18" satellite TV systems for home and RV. DISH Network programming, multi-room viewing options, accessories & more. www.skyvision.com Call 1-800-543-3025.

SATELLITE EQUIPMENT available: Receivers \$25 and up; 20-25 LNB \$30; C-KU feed horns \$65. Call 757-599-4408.

FREE FLYER on DBS files, hacking, hardware info. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Bill 1-800-879-9657.

MILITARY SURPLUS ELECTRONICS

AUDIO - VIDEO - LASERS

SYNC-A-LINK UNIVERSAL video sync generators. For more details phone or fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.

FREE LASER CATALOG. Helium-Neon, Argon, ruby, visible laser diode modules, lightshows, holography, laser pointers. Lowest prices. Midwest Laser Products, PO Box 262, Frankfort, IL 60423. 815-464-0085 **www.midwest-laser.com**

TOSHIBA NOTEWORTHY hi-res 640x480 laptop video conferencing color cameras. Comes with adj. stand, wall power adapter, video conferencing/capture PCMCIA card bus card and video cable. Has focusable lens (macro to infinity), will run on two self-contained alkaline AA batteries. Size 3.5L x 2.4W 1.1H. **NEW FACTORY BOXED** (ltd. qty.) \$125 each. Leave message 714-806-3268.



ANTIQUE VIDEO TRANSFER SERVICE: transfer any 2" QUADRUPLIX tape. Affordable fast! Phone/fax 415-821-7500 or 415-821-3359. 5001 Diamond Heights Blvd., San Francisco, CA 94131-1621.

WANTED: PRO video equipment, VCRs, switchers, cameras, etc. Advanced Media 702-874-1911.

ATV 2.2GHz to 2.7GHz wireless video data link module tuner & transmitter 100mW. Picotronic, web: <http://members.aol.com/picotronic/atv.htm>

LASER SHOW SYSTEMS AND COMPONENTS. Hobby and professional projectors. **www.redline-lasers.com**

BROADCAST VIDEO equipment wanted: all types, new or old. Please call, Jon with info. 1-800-539-2859.



SYNC-A-LINK's 3-D Scopers™ digital color CCD cameras for stereoscopic imagery. At a reasonable cost. Phone or Fax 918-479-6451 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352.



STEREOSCOPER VR is a stereo multiplexer that creates 3D stereoscopic video from two genlock cameras. Stereoscopers VR comes with LCS glasses and driver. 90 day warranty \$247 or write to Sync-A-Link, PO Box 4, Locust Grove, OK 74352. Phone or fax 918-479-6451.



CONVERTS PC MONITOR TO SECURITY MONITOR. The VGA-801 accepts standard NTSC or PAL inputs for display on any existing VGA/SVGA computer monitor. Small compact size, 4-1/2" x 2-1/2" x 3/4". Over 600 lines of resolution, twice that of standard TV monitor! High quality audio output feeds speakers directly. Excellent grey-scale conversion; works well with B/W inputs. Power supply included; **\$69 each.** Dealers welcome. MATCO, Inc., 1-800-719-9605; Fax 847-619-0852; E-Mail: sales@mat-co.com Website: www.mat-co.com



TZPC-175 Converters

\$39.00

20-lot



**THE BEST
DEALER
PRICING**


- ✓ Call for other models
- ✓ One stop shop
- ✓ Same day shipping
- ✓ One full year warranty

Centurion: CF-3000 (Brand New) True, 99-Channel

\$49.00

20-lot

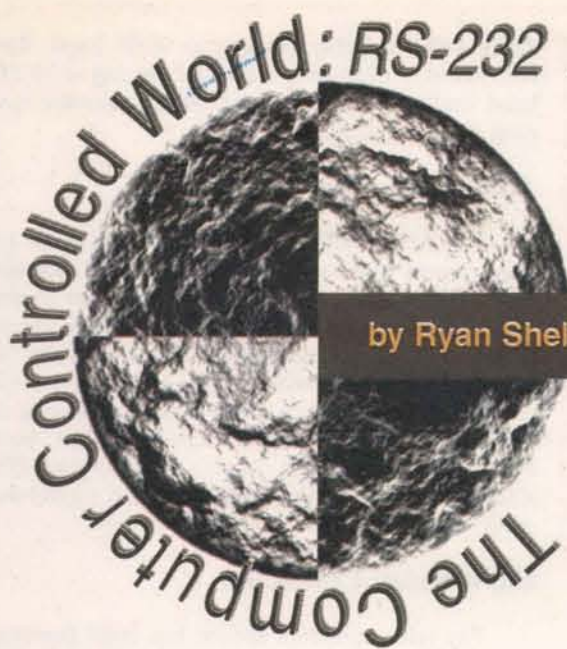**Intek Electronic
Systems
405-634-1535**



RS-232 Network Control Methods and Applications

Utilizing the BASIC Stamp II SX

by Ryan Sheldon, National Control Devices • (417) 646-5644 • www.controlanything.com

Managing a graphical user interface complete with working buttons, menus, and a user-friendly display, controlled with a simple three-button interface.

When I was 17, my father owned a Porsche 930 Turbo. It had the highly sought-after factory slant nose and had been optimized for performance to the point that it was no longer street legal. It was rarely driven, as it was one of those few cars that actually appreciated in value. On a quiet summer evening, my dad asked me if I wanted to go for a ride. I had only ridden in it twice before, and was not about to say no.

We went about five miles outside my hometown to a deserted country road where he stopped. He opened the door, pulled the keys out of the ignition (glancing at me with distrust), and walked over to my passenger-side door. As he opened it, he handed me the keys and said, "I know you'll be careful, but I want to remind you that this car is dangerous." I could not believe he was actually letting me drive the very car my brother and I spent hours helplessly drooling over while parked uselessly in our garage.

As I put it in first, I took off rather slowly. When I approached 50 miles per hour, I shifted into second. As the engine started to wind, I shifted into third, but soon had to slow down as I was not use to taking curves in this car. I jokingly asked my dad what fourth gear was for, and he said, "I've only used it a few times myself." I have never driven any car before, or since, with as much excitement and enthusiasm as I had that day.

But now, 10 years later, I no longer get any sort of thrill by driving a machine that can propel you from a dead stop into a tree in record time. I like to think my personal tastes have evolved into something that gives me a different kind of power. But I was recently reminded of that same youthful thrill in the form of Parallax's BASIC Stamp II SX. Similar in that it is fast (very fast), it can be somewhat intimidating (to the inexperienced driver), and it has more program memory than I will ever need (a useless fourth gear of sorts).

The BASIC Stamp — in my humble opinion — is the micro-miracle of the 90s. Without exception, it is the fastest and easiest way to provide a tiny intelligent brain for the toughest of projects. And now, with the release of the BASIC Stamp II SX, the Stamp has been optimized for performance using the latest of available micro-microprocessors.

Like a Porsche 930 turbo, it does not take long to get use to having, and it is addic-

tive in the best possible way. I hope to share my addiction with others because it allows me to do things quickly and easily. And if you've never used the Stamp before, then take comfort in the fact that I have only used it for a total of 10 hours before writing this article.

So why not go full bore and give the Stamp something tough. After all, if you're going to get behind the wheel of a sports car, you better be ready to drive. You're not going to have any fun by driving it like a ninny. So let's use this mighty micro to cause some real trouble. I think I have just the thing...

The Project

In this project, I will put the Stamp SX in charge of managing a graphical user interface. Not your basic "change full-screen graphic images" kind. This is the real thing, with working buttons, menus, and a user-friendly display, controlled with a simple three-button interface. Oh, and in case I forgot to mention, the user interface has to really do something ... in this application, it has to switch 16 video signals into two monitors and control a bank of eight relays from the three-button interface. And speaking of a useless fourth gear, I managed to get the job done with 10 spare I/O pins, and plenty of free program memory.

Truly GUI

There are some applications where only a true GUI will do (Graphical User Interface, GUI is pronounced "gooey"). The graphical elements shown in Figure 1 are stored as icons, which is basically an image that is divided into a lot of smaller images. The vacuum florescent display controller supports a command set that allows you to position these smaller images just about anywhere on the VFD screen.

Once this page of icons is stored into

the VFD controller, the Stamp II SX is used to control how these icons will appear on the screen, strategically positioning each graphical element on the screen to build a user interface. I drew these icons using PhotoShop 5 and I stored them into the VFD display controller using our VFD Loader Utility. Drawing the icons took about an hour, storing them

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
RELAYS	VIDEO1	VIDEO2	RUN	YES	NO	SET	ON	OFF	CLR						
RELAYS	VIDEO1	VIDEO2	RUN	YES	NO	SET	ON	OFF	CLR						

Figure 1

Figure 2

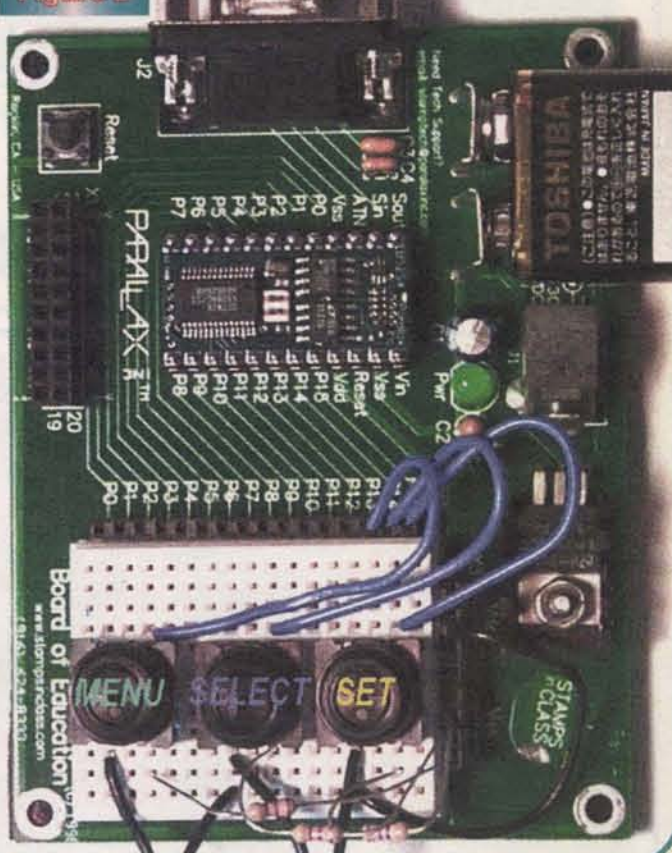


Figure 4

ON	OFF	OFF	OFF	VIDEO1	1	2	3	4	5	6	7	8
1	2	3	4	RELAYS	9	10	11	12	13	14	15	16
5	6	7	8	VIDEO2	1	2	3	4	5	6	7	8
ON	OFF	OFF	OFF		9	10	11	12	13	14	15	16

Figure 3

VIDEO1	VIDEO1	VIDEO1
RELAYS	RELAYS	RELAYS
VIDEO2	VIDEO2	VIDEO2

into the controller took about 15 seconds ... this is the very reason why I don't complain about my computers being slow.

The image shown in Figure 1 may be modified by your favorite paint program. It's possible to make the interface look a lot prettier, but I was a little anxious to make it work as I had just received my Stamp II SX from Parallax.

Three-Button Interface

Three buttons are used to switch 16 video signals into two outputs and actuate/de-actuate a bank of eight relays. As shown in Figure 2, the buttons are mounted on Parallax's Board of Education, a rather useful tool for quick prototypes.

The "Menu" button on the left is used to switch menus. Each time the button is pushed, the menu cycles between Video 1, Video 2, and Relays as

shown in Figure 3. When the menu is set to Video 1 or 2, the middle and right buttons are used to switch video input sources, up to 16. I will discuss that in more detail later in this article. Figure 4 shows video input 7 routed to video output 1, and video input 12 routed to video output 2.

When the menu button is switched to Relays, the center button is used to select one of the eight relays while the right-most button is used to toggle the selected relay on and off. Figure 4 also shows relays 1 and 5 on. Note that "SET" appears in place of relay 7. Pushing the center button moves the "SET" marker between each of the eight relays.

Wiring External Devices

The BASIC Stamp II SX is wired to three buttons and three external devices, leaving 10 I/O lines available for other functions. Figure 5 shows the

ASEL video switcher running at 9600 baud, the R85 five-amp eight-relay controller running at 19.2K baud, and a vacuum florescent display controller running at 38.4K baud.

16x2 Video Switching

The ASEL video switcher is used to route 16 video inputs to two video outputs under software control. The ASEL has 16 composite video inputs and two composite video outputs as shown in Figure 6. The ASEL is capable of switching video, audio, or just about any other analog signal source in the ± 5 -volt range. The ASEL is easily controlled by any of the BASIC Stamp series micro-controllers from Parallax. Any computer capable of generating RS-232 data at 1200 or 9600 baud can also control the ASEL video switcher.

Eight-Relay Controller

The relay controller shown has eight five-amp relays (10-amp relays are also available). The relay controller is ideal for controlling lights, small motors, speakers, telephone lines, or just about anything. External devices can be wired to each relay as normally open (where the device is normally off and switched on) or normally closed (where the device is always on and switched off). The RS-232 input is optoisolated. A third data wire may be connected to the relay controller if your computer needs to ask the relay controller what the current on/off status is of each relay.

VF Display Controller

The vacuum florescent display and controller is capable of storing up to 127 full-screen images, or 123 pages of icons, or any combination of images and icons. The VF display controller is easily controlled using simple ASCII character codes. It is possible to copy stored images to the display screen, plot pixels, scroll images, and use 20 different sizes of icons for large text fonts, complex graphical user interfaces, or animation.

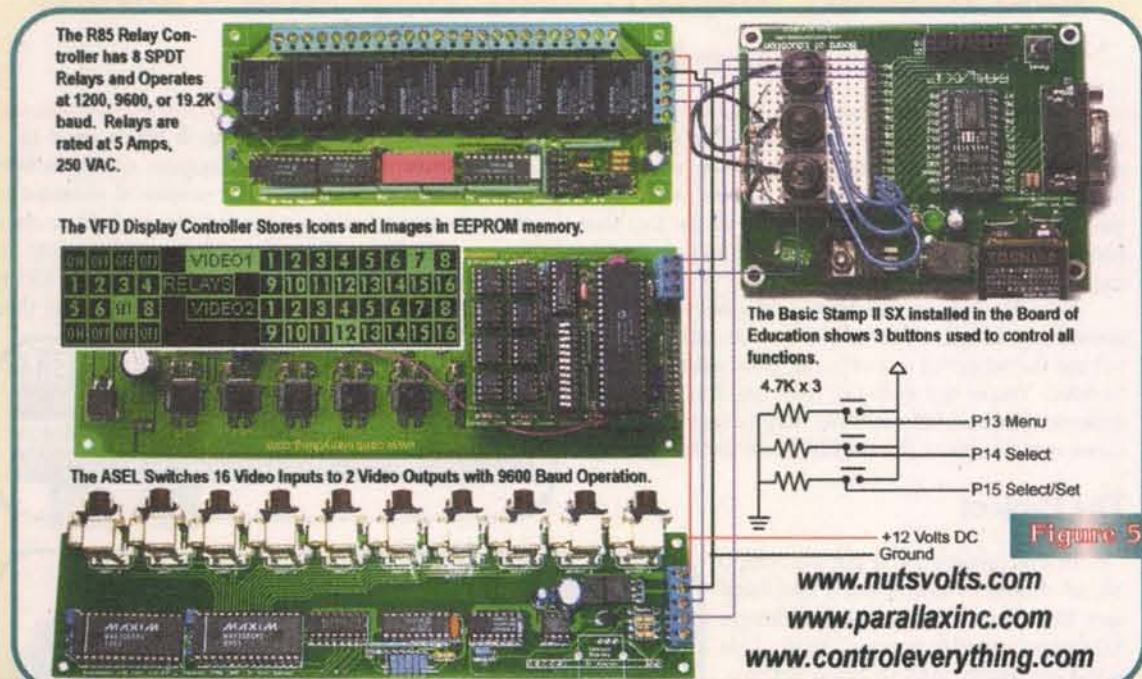


Figure 5

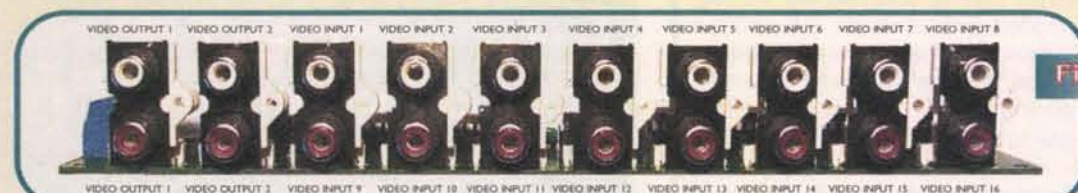


Figure 6

BASIC Stamp II SX Firmware

The firmware can be downloaded from my web site at www.controleverything.com. Go to the "articles" link and download the November 1999, Stamp on Steroids file: NOV99.ZIP. This file contains the template image used for the GUI and the BASIC Stamp II SX source code.

Controlling the ASEL Video Switcher

The BASIC Stamp II SX is used to control the ASEL 16x2 video switcher from the user interface.

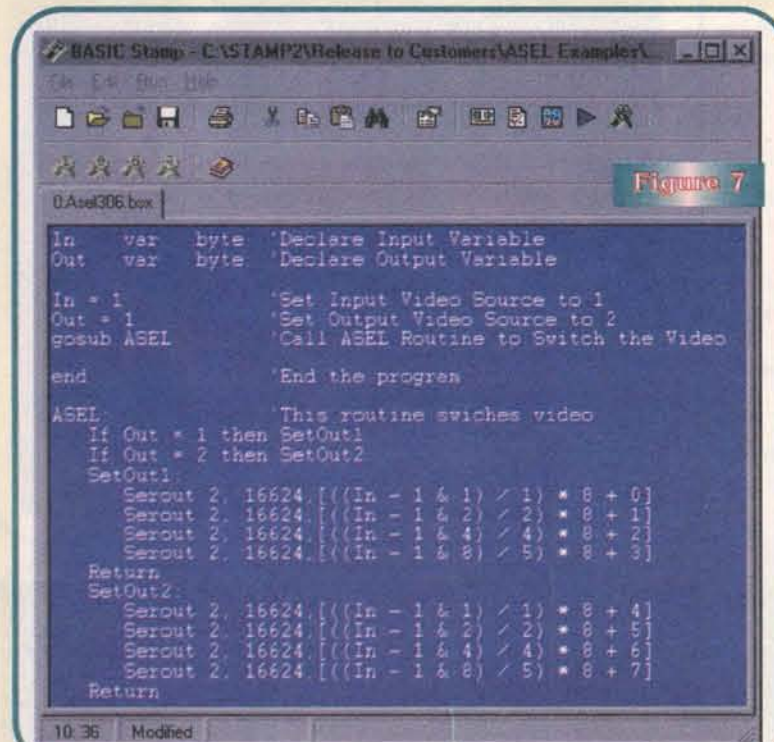


Figure 7

wiring of all devices to the Board of Education. The wiring only takes about 10 minutes. The Stamp II SX supports many baud rate options. The Stamp is connected to the

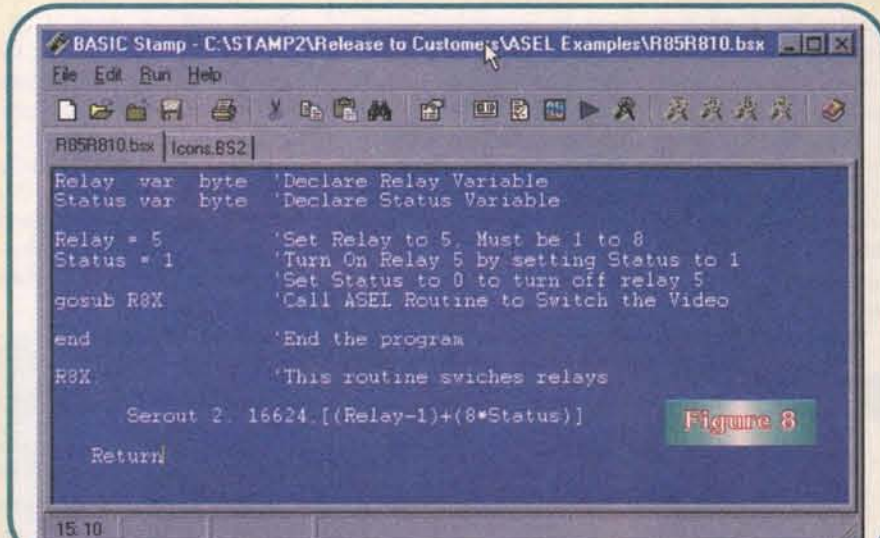


Figure 8

In an effort to simplify the video switching operations, I have simplified the code so you can get an idea of what must be done to switch video from the BASIC Stamp II SX. Figure 7 was taken from Parallax's BASIC Stamp Editor version 1.091 beta.

Controlling the Relay Driver

The relay driver is also very easy to control from the Stamp II SX. The screen shot shown in Figure 8 provides a few short lines of code to show how it is done:

Controlling the VF Display

Only two commands are ever used to control the vacuum fluorescent display. The clear screen command is issued when the program is first run, and the Paste Icon command is used to generate the graphical user interface. Figure 9 shows how to send these commands using the BASIC Stamp II SX. The VF display controller supports many other commands such as plotting pixels, brightness adjustment, image/text scrolling, full-screen image copy, as well as many text functions.

While any of Parallax's BASIC Stamp series micro-controllers can control the VF display, I would recommend using the BASIC Stamp II SX version. Its high processor speed means shorter character spacing, making it noticeably faster for most display operations.

Accessing the Buttons

The Stamp also has a very powerful button function, allowing you to monitor and de-bounce inputs using a single instruction. Because I am inexperienced in using most of the Stamp's functions, I chose to write my own code for this rather than spend any time learning how their command works. Figure 10 provides a stripped-down version of a program that I used to monitor each of the three buttons. When a button is pressed, the program waits for the user to release the button before an operation is performed.


Program Logic

One thing that I have always taken for granted when programming on a desktop computer is that I can often be lazy about how I write my code. Because so many resources are available to me on a desktop computer, I can write routines that are rather inefficient, require less thinking, and usually use up more code space. This is not good programming practice when using a microcontroller such as the BASIC Stamp. But because I was pressed for

time, I thought I would give it a shot just to see how the Stamp II SX holds up. The routine shown in Figure 11 is used to change menus every time the

always welcome and encouraged. Or, if you have a story idea, just let me know. If I like it, I'll run with it.



NV

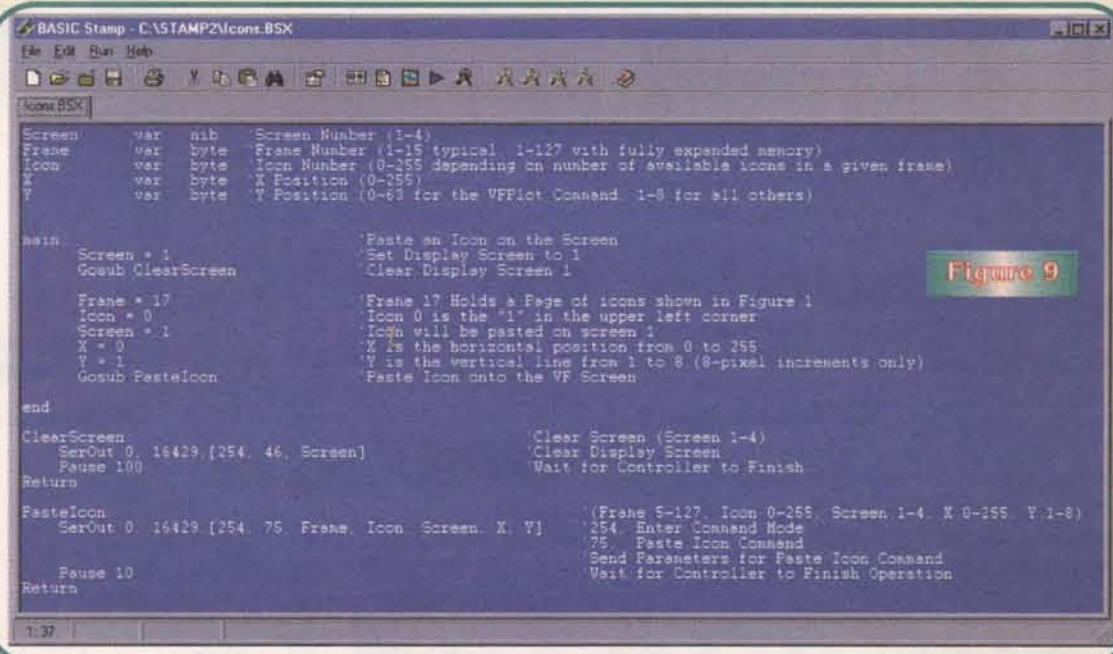

menu button is pushed (see Figure 3 to see how the graphics change when the menu button is pushed). Pasting stored icons onto the VF screen changes the menu.

If I were to write this routine efficiently, it would only redraw the images that actually change on the screen. Instead, I chose to scrap the use of logic and clear all buttons, then draw the menu item that was selected. This means the Stamp has to do twice as much work, but only uses a few logic instructions to get the job done. Surprisingly, the menu button is VERY responsive. The Stamp and display keep up with normal to fast button presses with little effort.

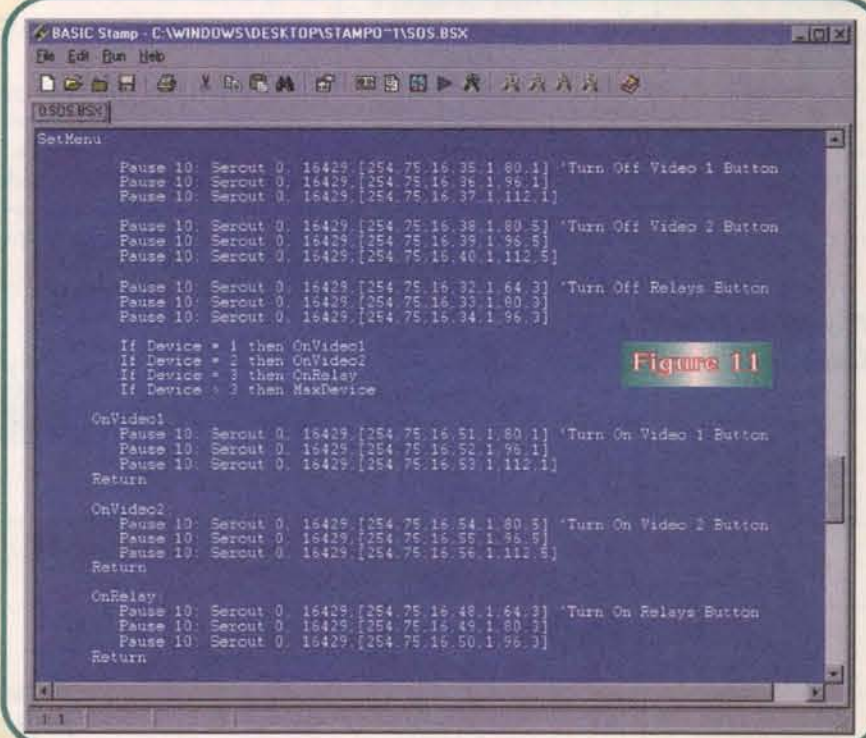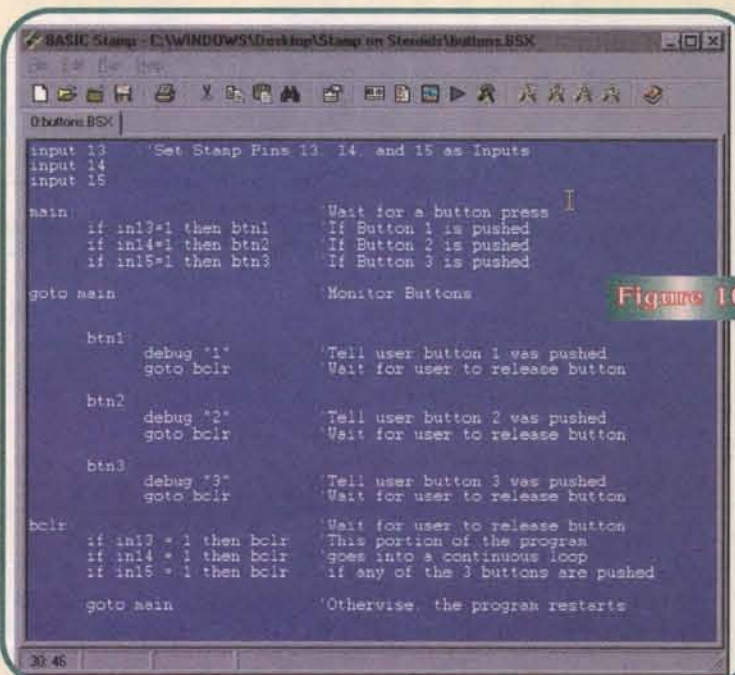I hope you have enjoyed this month's article, maybe even learned a little something. I know I have. I would like to encourage you to call or write if you have any questions about this or any of my previous articles. Feedback is



NUTS AND VOLTS SUBSCRIBERS WITH A CURRENT SUBSCRIBER NUMBER MAY ORDER ANY NCD DEVICE AT THE 10 PIECE PRICE. LIMIT ONE DEVICE PER SUBSCRIBER NUMBER PER MONTH. VISIT WWW.CONTROLEVERYTHING.COM FOR SOFTWARE, MANUALS, AND PRICES.

NEW CONTACT INFO:
 Ryan Sheldon
 National Control Devices
 P.O. Box 455
 Osceola, MO 64776
 Phone: (417) 646-5644
 FAX: (417) 646-8302
 ncdryan@aol.com
 www.controlanything.com

SOURCES:

BASIC Stamp II SX, Board of Education
 Parallax, Inc.
 3805 Atherton Road, #102
 Rocklin, CA 95765
 Phone: (888) 512-1024
 FAX: (916) 624-8003
 www.parallaxinc.com
 info@parallaxinc.com

ASEL Video Switcher, R85 Relay Controller, VF Display/Controller
 National Control Devices
 P.O. Box 455
 Osceola, MO 64776
 Phone: (417) 646-5644
 FAX: (417) 646-8302
 www.controlanything.com
 ncdryan@aol.com

Here is an interesting exercise: One day when you have copious amounts of free time, try counting the number of batteries in your house. This means counting every battery, including the one that backs up the clock in your digital refrigerator.

I tried this once and never completed it — I literally lost count somewhere near 200 batteries! Believe it or not, this is average for a hardware hacker. With all of the batteries in our lives, it is natural that a growing number of them will be rechargeable NICADs (Nickel-CADmium).

Portable power tools, test instruments, laptop computers, and portable phones usually top the list of common rechargeable devices in our homes and offices. The sealed nicad cell is an electrochemical system which converts, in a reversible way, chemical energy into electrical energy. To accomplish this, the nicad battery uses a nickel

Usually nicad battery packs are a set of individual cells wired in series and wrapped in a plastic sleeve. The batteries are charged and discharged in series. If a single cell in the pack becomes weak, shorts out, or opens, the entire pack is rendered useless.

Even worse, many appliance manufacturers glue the pack into a proprietary plastic case which only fits the device it is intended to power. The net result is that when these batteries fail, either the entire battery pack or the device itself is discarded. The terrible irony is that doing this can negate any advantage of purchasing a rechargeable device in the first place!

Walk through a hamfest or a flea market, and you will literally find hundreds of wonderful

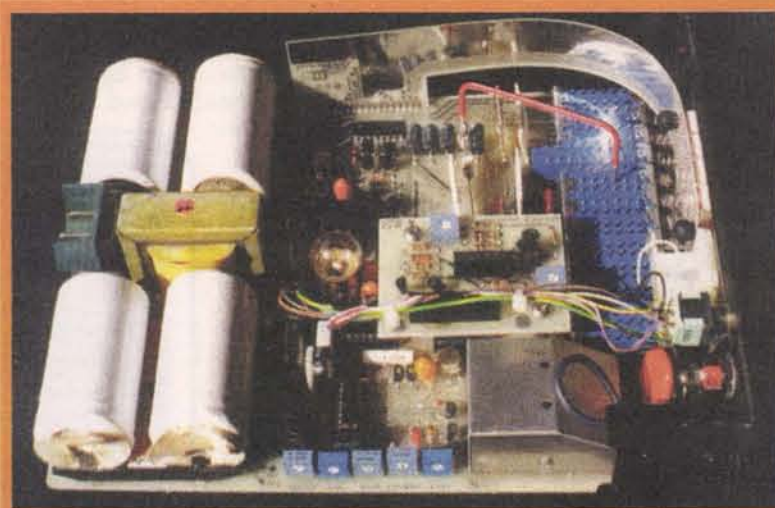


Figure 2: Dead Fluke meter, needs new NiCads.

REVIVING NICAD-POWERED DEVICES

positive electrode with a cadmium negative electrode in a potassium hydroxide electrolyte.

Nicads are strange animals. We often kill them with kindness. Unlike their lead-acid cousins, they really don't like to be kept charged up all of the time. Unfortunately, it is far more likely we will do exactly that — a rechargeable screwdriver is usually left in its charging stand until we need it. The problem is that nicad batteries are notorious for developing the dreaded "memory effect." Nicads suffering from the "memory effect" will appear to be fully charged, but when a load is drawn off them, will quickly drop below their rated capacity and die out. This phenomenon is not as much a characteristic of nicads in general, but more because of the way they are packaged.

devices suffering from nicad battery failure at bargain prices.

Our project this month is to look at some ways we can salvage these from the scrap heap and recycle them back into active duty. Dig through your toolbox and electronic junkbox, and pull these out for another look.

NICAD WAKE-UP CALL

After many cycles of operation, nicads often develop small internal short circuits as the potassium hydroxide electrolyte forms tiny "dendrites" which bridge the nickel-cadmium electrodes. These shorts inhibit the cell's ability to achieve a full charge. When this happens, the cell is usually

discarded.

One of the simplest ways you can breathe new life into a "dead" nicad battery pack is to hit it with a short duration overvoltage. One of my favorite tricks is to take a 12-volt power supply with a good current rating of several amps and connect it across the nicad battery pack in series with an old metal file. By dragging the positive lead across the file, you send intermittent high-current spikes through the battery pack, burning off any internal shorts in the batteries. Many times the battery pack will accept a charge after this seemingly rough treatment (Figure 1). This works on battery packs from 4.8 volts to 9.6 volts. Use a higher voltage supply for higher-voltage battery packs.

Be sure to wear eye protection when performing this operation!

REPLACEMENT


If a cell fails to open, or shows obvious signs of electrolyte leakage, it is a total loss. Your choices here are to either replace the defective cell, or the entire battery pack. Battery packs that are sealed in a plastic sleeve can often be accessed by carefully slitting the sleeve open with a razor blade, exposing the individual cells. If the pack is in a hard plastic shell, it may be possible to cut the shell open with a Dremel tool, or even carefully pry it apart along the glue line with a screwdriver. Camcorder and cellphone batteries often are constructed in this manner.

One good tactic is to purchase a battery pack for the device which is designed for standard alkaline batteries and fill it with nicad cells instead. This will allow you to test and replace individual defective cells in the future, instead of throwing away entire (mostly good) battery packs. Because nicads are rated at 1.2 volts instead of 1.5 for disposable alkaline batteries, it may be necessary to check and make sure the device will still function properly on the slightly lower voltage of the combined nicad pack. It usually will for anything less than a 12-volt battery.

CONDITIONING

Newer nicad battery chargers employ a "conditioning cycle" which is little more than a controlled discharge of the battery pack through a load before the charging cycle commences. The reason for this is to allow all of the cells to reach a completely discharged state before they are recharged. In a series-connected battery pack, some cells are likely to discharge before others. The weak sisters may actually charge negatively if the remaining cells continue to push current

Figure 1: Reviving Shorted NiCad Cells — Drag lead quickly across file.

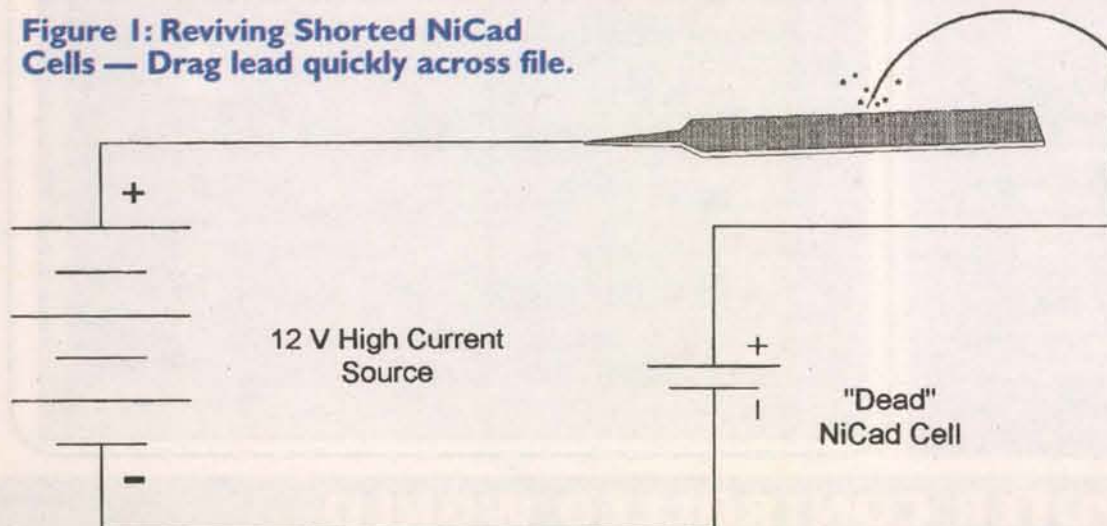

through the pack under a big load.

Stronger cells may not become completely discharged before the total pack voltage drops below nominal operating voltage for the device it is powering. Discharging the pack completely will help ensure that all of the cells will have an opportunity to be charged equally. You can simulate this by connecting the battery pack to a suitably-rated light bulb and waiting until the light goes out before recharging the battery pack.

EXAMPLES

Take a look at the Fluke 8000A multimeter I picked up at a local hamfest for \$5.00. When plugged into AC power, it emitted a high-frequency whine, and displayed random digits. The seller had decided it was a total loss. However, when I opened it up, I discovered it was powered by four "D" nicads floating across a constant charging supply when plugged into AC utility power.

The high-frequency charging supply had insufficient output to run the meter. Since it had not spent much time in portable use, the constant AC charging supply had literally cooked the batteries. The nicads were visibly leaking and read no voltage at all. Because the multimeter depended on the batteries to provide the DC operating voltage, the failure of the batteries caused the meter to quit operating. Replacing the nicads put the meter back on the workbench (Figure 2).

Many low-cost power tools have internal nicad battery packs. My 10-year-old Sears electric

screwdriver and 3/8" portable drill began to show symptoms of nicad failure when an all-night charge only yielded five minutes of run time. Using a torx screwdriver to open the cases revealed internal battery packs consisting of "C" size cells which were easily replaceable, saving these two tools from the landfill. With luck they may last another 10 years (Figure 3).

CHARGING NICADS

Cyclic Use:

It is recommended that nicads be charged at semi-constant or constant current charging at the 0.1 I (I/10) rate for 15 hours. Overcharging at I/10 for long periods of time can be done at room temperature without causing damage. For example, a 1200 mAh nicad can be charged at 120 mA for 15 hours or longer. Using Ohm's Law, a five-volt charging supply would need a 42-ohm resistor in series with the nicad cell to deliver this current ($E/I=R$, so $5/120 = 41.66\Omega$).

Cell sizes ranging from 1/3AA to SC can also be quick-charged for 4.5 to six hours at the 0.25 I (I/3- I/4) rate. Quick-charging larger cells (C-cell and up) requires a controlled charge circuit because of the heat and gas generated during overcharge.

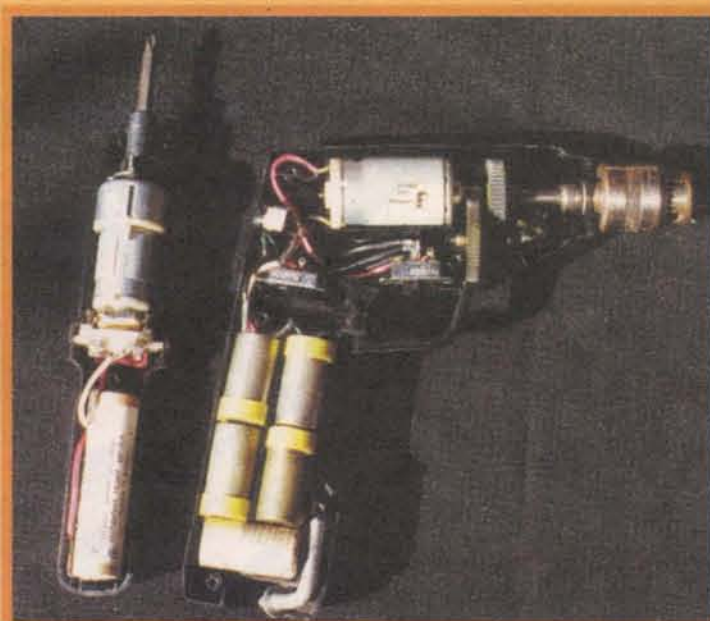


Figure 3: Don't toss out "dead" power tools, repair them!

Stand-by Use:

A trickle charge between 0.02 I and 0.05 I (I/50- I/20) is sufficient to keep a battery fully charged. At 0 degrees Celsius to 45 degrees Celsius (32 degrees F to 113 degrees F), this charge rate will minimize heating effects during overcharge and prolong battery life.

The most common problem with inexpensive rechargeable tools is that there is no current limiting in the charger. Keeping nicads on constant high charge will eventually heat them up until they self-destruct.

A cheap and dirty method of limiting current to nicads in standby charge mode is to insert a light bulb (or suitable series resistor) in series with the charger. The light bulb filament will gradually dim and increase its resistance as the battery pack reaches full charge and thereby tapers off the supply current to the battery pack. You may need to experiment with various light bulbs until you find one that exhibits the correct charging characteristics.

Proper care and maintenance of nicads will allow hundreds of recharge cycles. They are an environmentally-friendly alternative to continuously disposing of alkaline or carbon-manganese batteries. With occasional replacement, the devices they power can be used almost forever. Certainly, if you have over 200 batteries to replace, nicads make good sense!

Remember, have fun whatever you do! **NV**

Nickel Cadmium Standard Cell Specifications*

Size	Capacity mAh	Dia. (mm)	Height (mm)	Weight (gm)	Charge Current (mA) I / 10	Fast Charge Current (mA) I / 3	Time (Hrs)
1/3 AAA	50	10.5	16.0	3.5	5	15	4-6
1/3 AA	110	14.5	17.0	8.0	11	33	4-6
N	150	12.0	29.5	9.0	15	45	4-6
AAA	200	10.5	44.5	10.0	20	60	4-6
1/3 AF	225	17.0	17.0	12.0	23	340	7-8
2/3 AA	270	14.5	30.0	14.0	27	400	1
2/3 AF	500	17.0	28.0	20.0	50	750	1
AA	600	14.5	50.0	24.0	50	900	1
1/2 SC	650	23.0	26.0	29.0	65	945	1
4/5 SC	1000	23.0	34.0	42.0	100	1500	1
3/5 C	1100	26.0	30.0	44.0	110	1650	1
AF	1200	17.0	50.0	34.0	120	1800	1
SC	1400	23.0	43.0	53.0	140	2100	1
C	2000	26.0	50.0	75.0	200	—	—
1/2 D	2300	34.0	38.0	80.0	220	—	—
2/3 D	2500	34.0	44.0	110.0	250	2500	1
D	4000	34.0	61.0	160.0	400	6000	1
F	7000	34.0	91.0	230.0	700	—	—
SF	10,000	43.0	91.0	400.0	1000	—	—

*There may be slight variations in overall length and height of cells due to differences in mounting tabs and contacts, and in the thickness of cell coverings.

PRINTED CIRCUIT BOARDS

QUALITY PRODUCT

FAST DELIVERY

COMPETITIVE PRICING

We will beat any competitor's prices!!!

- * UL approved
- * Single & Double sided
- * Multilayers to 8 layer
- * SMOBC, LPI mask
- * Reverse Engineering
- * Through hole or SMT
- * Nickel & Gold Plating
- * Routing or scoring
- * Electrical Testing
- * Artwork or CAD data
- * Fast quotes

10 pcs (3 days) 1 or 2 layers **\$249**

10 pcs (5 days) 4 layers **\$695**
(up to 30 sq. in. ea.) includes tooling, artwork, LPI mask & legend

PROTOTYPE THROUGH
PRODUCTION

PULSAR, INC

9901 W. Pacific Ave.
Franklin Park, IL 60131

Phone 847.233.0012

Fax 847.233.0013

Modem 847.233.0014

yogii@flash.net • flash.net/~yogii

Write in 163 on Reader Service Card.

DIGITAL SATELLITE TV REVOLUTION!

KNOWLEDGE is POWER!

- A clear explanation of all aspects of digital satellite TV
- Communication fundamentals and standards
- Digital compression, MPEG-2, DVB, error correction
- Uplink, satellite and receive system operation
- Internet operation and satellite delivery of data
- Installing fixed and tracking dishes
- Retrofitting older systems and mobile systems
- Conventional and IF distribution systems
- Troubleshooting and repair ... and much more ...

www.baylin.com
or... call 800-483-2423

ORDER via Internet or Send \$60 plus \$5 s/h to:

Baylin Publications, 1905 Mariposa, Boulder, CO 80302
MASTER, VISA & AMEX /COD orders accepted

FREE CATALOG - Satellite TV books, videos and software



486 pages, 8-1/2" x 11"

**JUST
PUBLISHED!**

Telephone: 303-449-4551
FAX: 303-939-8720

Write in 164 on Reader Service Card.

Nuts & Volts Magazine/NOVEMBER 1999 47

POWERPOINTING YOUR PROJECTS

Part 3

by Steve Daniels

From Idea to Project

Before we begin to lay out a board, we need to go through several essential planning steps.

* Make sure that the circuit works

This usually involves setting it up on a breadboard like the one shown in Figure 2.

The prototype board provides a convenient way to quickly make changes in component values or in the circuit design, and it has built-in buses and terminations for a power supply.

* Do a first cut at the final layout

The template will give us the ability to move component outlines around on-screen, but it is still a good idea to work things out on the breadboard beforehand. In doing your layout, think first about the terminations going off the board — to switches, controls, batteries, and the like — and position these first. Then locate the rest of the components to accommodate the external connections.

Remember that our PC board will have two levels: a component side and a solder side. While this means that the designer must think on two levels, it also makes

prototyping easier.

You can run connections under components, anticipating that these will later be traces on the solder side of the board. Note the wires going under the chips in Figure 2.

Last month, we built a template in PowerPoint for doing layout drawings and PC board etch patterns. This month, we will put the template to use by doing a board layout for the schematic that we created in Part 1 (see Figure 1). Then we will produce an etch pattern, create a PC board, and mount it in an enclosure. The finished device will be

* Select an enclosure and figure out the dimensions of the board

The application will dictate the kind of case. The amount of space that the components occupy on the breadboard will indicate how big the case should be and how big a board is needed. I chose a standard plastic case available from RadioShack and measured inside it to figure out how large a board it would accommodate.

Now that we have a possible layout and know the size and shape of the board, we can create an "x-ray" drawing. This drawing will show both the components and the interconnecting wiring. Open the template and save the file with a new name. Leave Snap To Grid off and start with Zoom at 200%. Now see Figure 3.

a) Using the guides to establish the size, draw an outline of the board. I usually draw individual

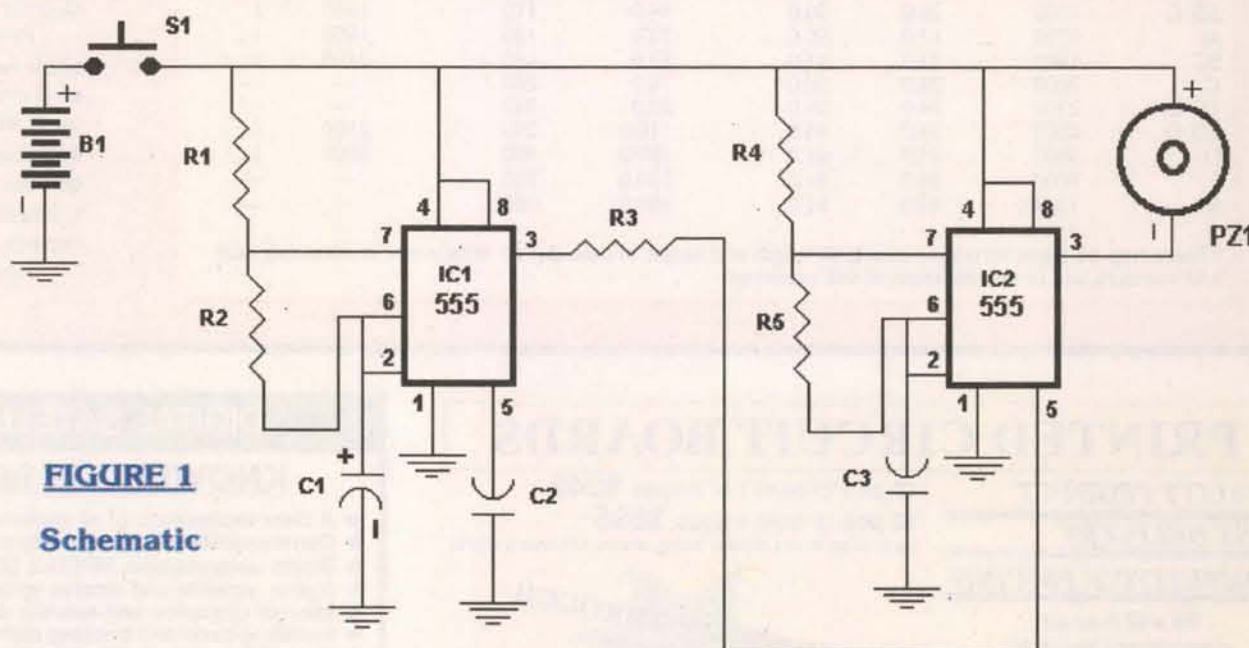


FIGURE 1
Schematic

R1 - 8.2K
R2 - 33K
R3 - 1K
R4 - 4.7K
R5 - 10K

C1 - 22 mfd. electrolytic
C2 - .01 mfd. mylar
C3 - .05 mfd. mylar

S1 - SPST Pushbutton
PZ1 - Piezoelectric Speaker Element, Radio Shack 273-091 or similar
B1 - 9 volt battery

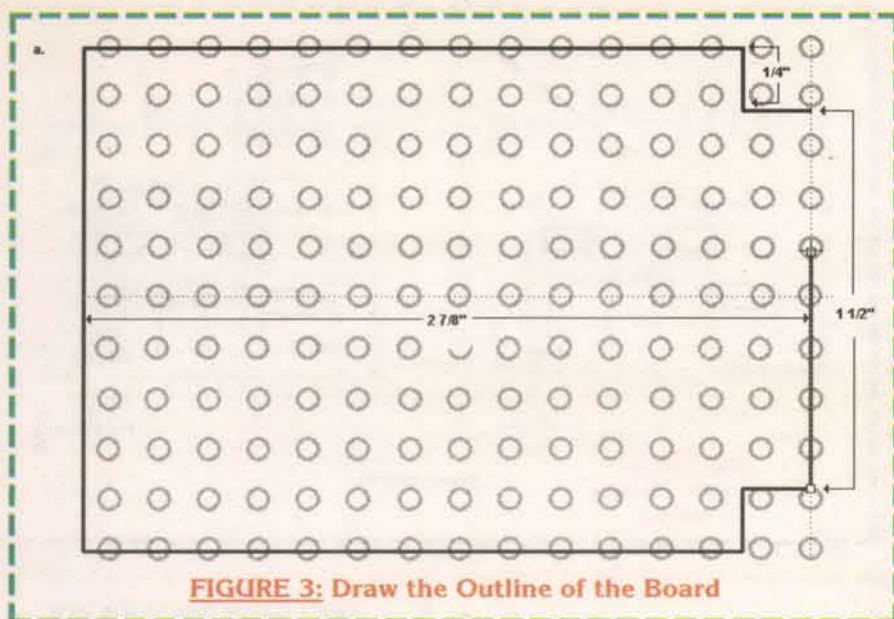


FIGURE 3: Draw the Outline of the Board

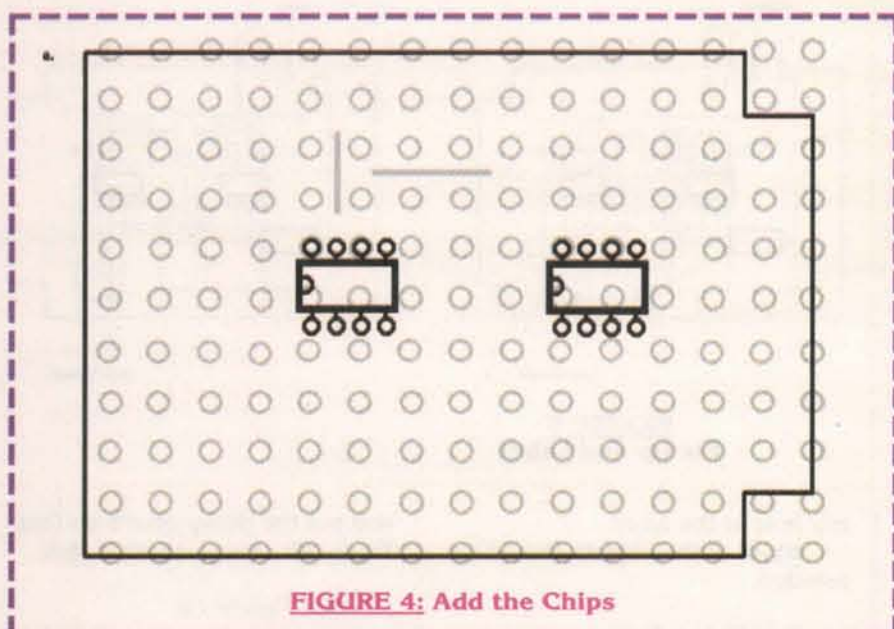


FIGURE 4: Add the Chips

lines as shown and group them rather than drawing a polygon. For convenience, place the outline more or less in the center of the array. Hide the guides.

See Figure 4.

a) Begin to populate the board

by copying two eight-pin DIP outlines and two trace lines from the library area and placing them within the board outline. Use the holes of the array to orient the chips with respect to each other. This board won't be very tightly packed, so "eyeball" positioning of the chips is okay; if it were more

complicated, you might want to do some measuring with the guides to establish exact locations. It should be clear now why I emphasized No Fill for the component outlines: You have to be able to see through to the holes in the array and to the traces that we will add in the next step.

See Figure 5.

a) Establish the lines connecting pin 4 and pin 8 of each chip by copying horizontal and vertical line segments as needed and moving them into place.

b) This shows a typical shortcut.

c) When you have made the connections, bring the chip outlines to the front.

Now let's look to place the pads for the off-board items: the switch, the battery clip, and the piezo element. The top left seems

a reasonable area for the first two since the battery clamp is on the left side of the case. The connections for the element should go on the lower left near pin 3 of IC2.

See Figure 6.

a) Do you remember how you were cursing under your breath at all the finicky details of making the template? It pays now, doesn't it! If you went all the way, you should even have the polarity symbols available.

b) Draw traces to these pads now and add the traces for the power to the chips. We'll make adjustments later, if necessary, but it is around these connections that we will work out everything else. Always bring outlines and pads to the front as you connect traces to them.

Now we can add components and wire.

See Figure 7.

a) Refer to your breadboarded layout when you are positioning component outlines. If you were careful to run traces under components where necessary, things should fall into place. The negative side of the electrolytic falls on top of the ground trace, so just shorten the trace, terminate it on the top side of the pad, and continue from the bottom side.

b) Wire the components together. With practice, it will become clear where you should just extend a line to make a connection and where you need to draw a new one.

Yes, I know that I changed a number of traces that we had laid down in the beginning; I said that we might have to, remember? Let's take a look at what changed and

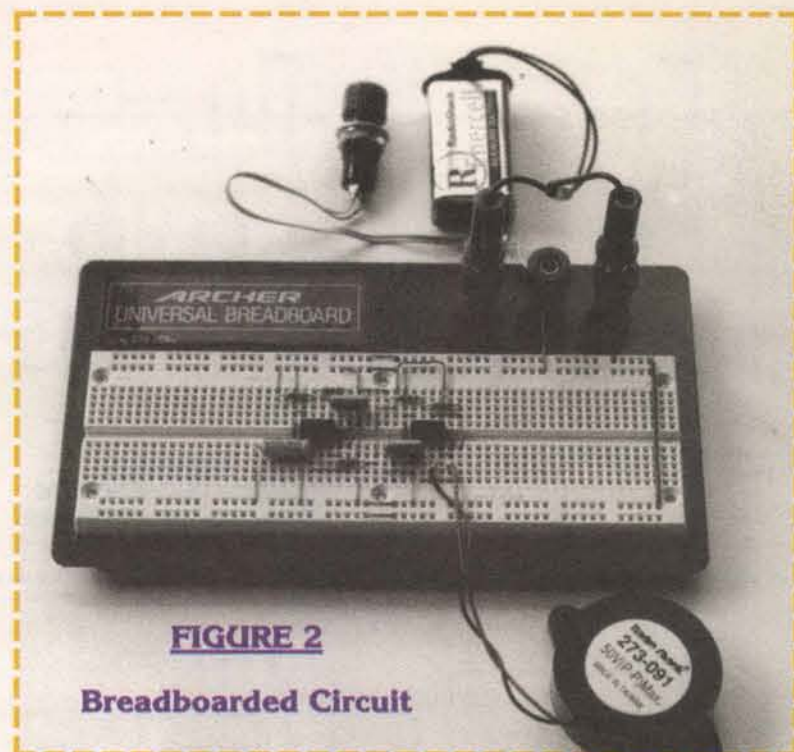


FIGURE 2

Breadboarded Circuit


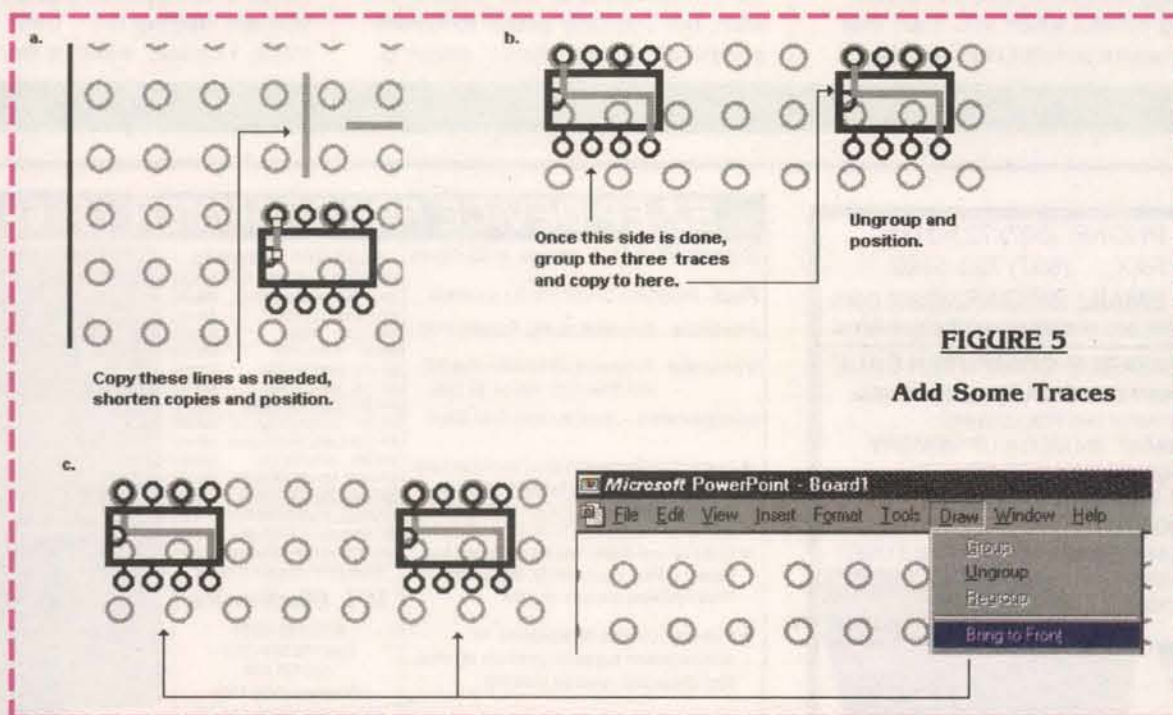
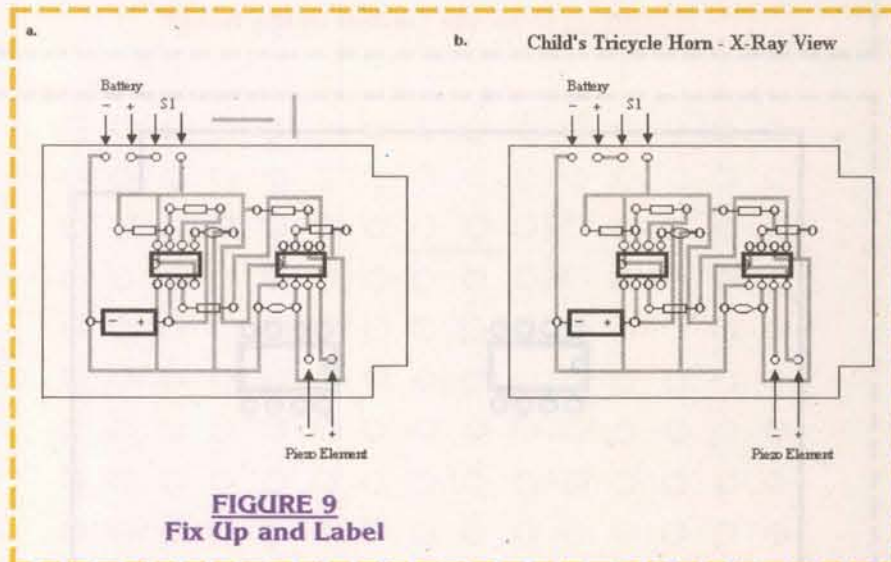
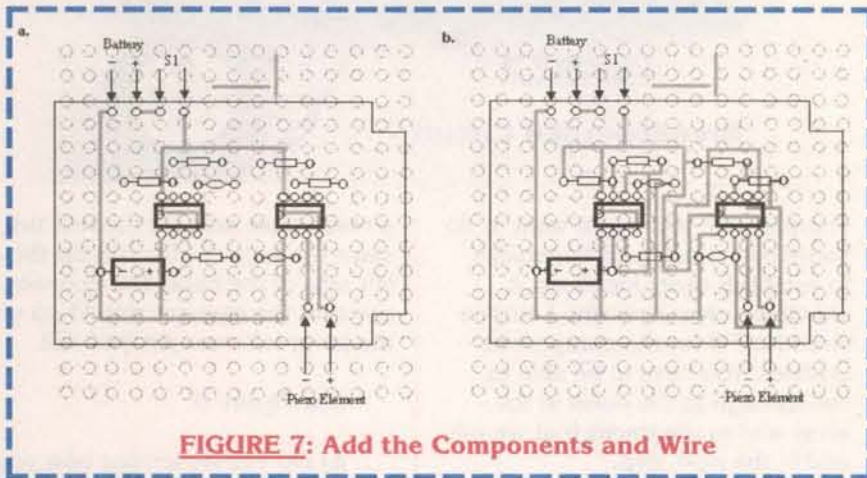
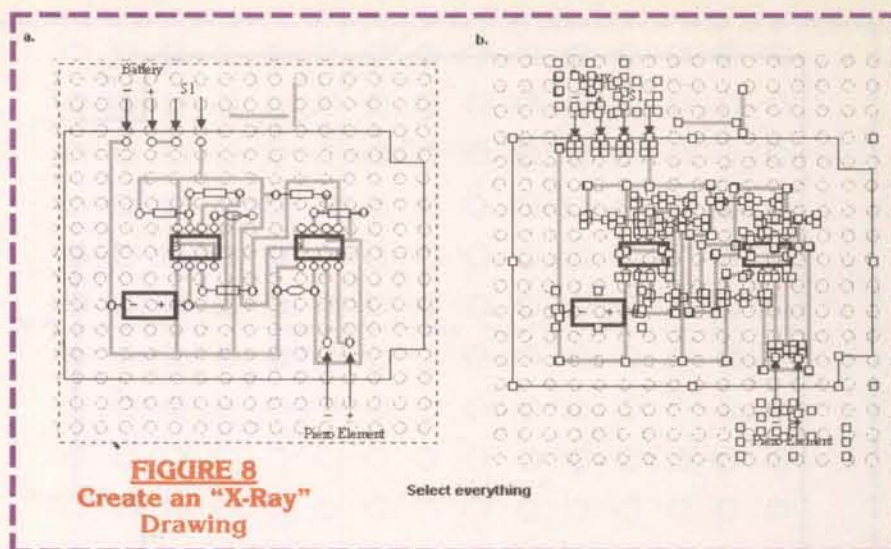


FIGURE 5

Add Some Traces

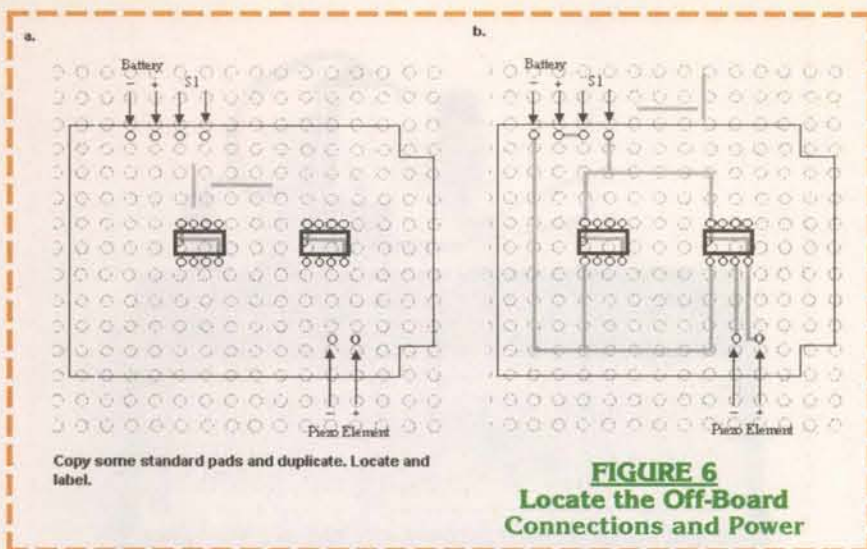

why, because the changes illustrate very typical problems in board design.

As the schematic shows, we need to get the output from pin 3 of IC1 to the control voltage input, pin 5, of IC2. This is not possible without using jumpers if the trace carrying V+ to pin 8 of IC2 remains where it is in Figure 7(a). By threading that trace under the resistor going to pin 3 of IC1, we leave a path open to the top row of IC2. The other big change from the breadboard layout was routing the trace connecting pins 2 and 6 of IC2 under the chip; this required redrawing the trace connecting pins 4 and 8. Now everything

routes easily.

You won't always be able to avoid jumpers — especially as your boards get larger — but you can minimize the number by planning carefully and using a little creativity with the template.

What we have at this point is an "x-ray" drawing; it shows both the layout of parts on the component side and the traces underneath the board. Let's start to turn this into a finished drawing.

See Figure 8.

a) "Rubber Band" all of the objects that comprise the board, being careful when you start that the mouse pointer isn't touching

any hole in the array.

b) All of the objects should be selected.

See Figure 9.

a) Group all the objects. Create a new slide and copy the grouped objects to it.

b) Now ungroup the drawing, remove the un-needed sample traces and label the slide.

You may add designations to the components at this point if you wish, but I usually prefer to create a separate "parts layout" drawing

and put the designations on that. To do this, create another slide.

See Figure 10.

a) Copy the drawing from Figure 8 to this slide. Ungroup it and delete the connecting lines. You may find that you need to increase the zoom and rubber band some objects to remove traces that are underneath component outlines. One caution at this point: It is easy to accidentally move a component outline while you are zipping from trace to trace. I usually select a few traces

BRIGAR ELECTRONICS
7-9 ALICE ST.
BINGHAMTON, NY 13904



PHONE: (607) 723-3111
FAX: (607) 723-5202
EMAIL: BRIGAR2@aol.com
<http://members.aol.com/brigar2/brigar.html>

15" SVGA COLOR MONITOR
Various Manufacturer
IBM PC/XT or Higher compatibles
.26 mm dot pitch - Max resolution
1280 x 1024 Includes power cable
Weight 32 lbs.

Removed
from svce.
Mint cond.
SALE
PRICE
\$ 69.95



UNBEATABLE COMPUTER SALE
IBM COMPATABLE CPU'S VARIOUS MFG.
COMES WITH THE FOLLOWING:
■ 486 66MHZ ■ 4 MEG & UP MEMORY
■ 170 TO 540 MEG HARD DRIVES.
■ 3-1/2" 1.44 MB FLOPPY DRIVE
■ KEYBOARD
THE COMPUTERS ARE OBVIOUSLY USED
BUT IN GREAT
CONDITION.

**BLOW
OUT
\$ 59.95**



EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- www.m2l.com

Fast - Programs 27C010 in 23 seconds

Portable - Connects to PC Parallel Port

Versatile - Programs 2716-080 plus EE
and flash (28, 29) to 32 pins

Inexpensive - Best for less than \$200

• Correct implementation of manufacturer
specified algorithms for fast, reliable
programming.

• Easy to use menu based software has
binary editor, read, verify, copy, etc.
Free updates via bbs or web.

• Full over current detection on all
device power supplies protects against
bad chips and reverse insertion.


• Broad support for additional devices
using adapters listed below.



Available Adapters

EP-PIC (16C5x, 61, 62x, 71, 84)	\$49.95
EP-PIC64 (16C82-5, 72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751, C51)	\$39.95
EP-11E (88HC11 E/A)	\$59.95
EP-11D (88HC711D3)	\$39.95
EP-16 (16B1 EPROMs)	\$49.95
EP-Z8 (286E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (83x, 24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (IC22x10, 18v8)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
EP-TSOP (TSOP EPROMs)	\$59.95

M²L Electronics

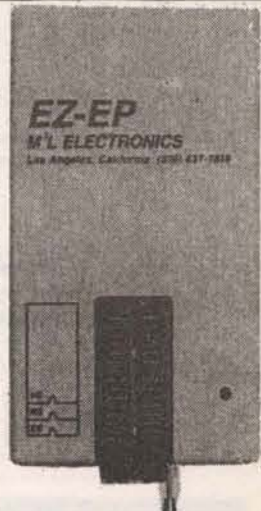970/259-0555
Fax: 970/259-0777
250 CR 218
Durango, CO 81301
CO orders please add 7%
sales tax.
<http://www.m2l.com>



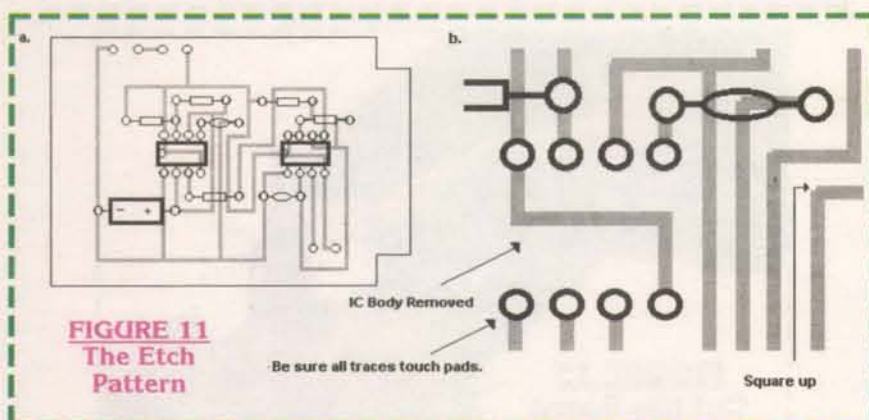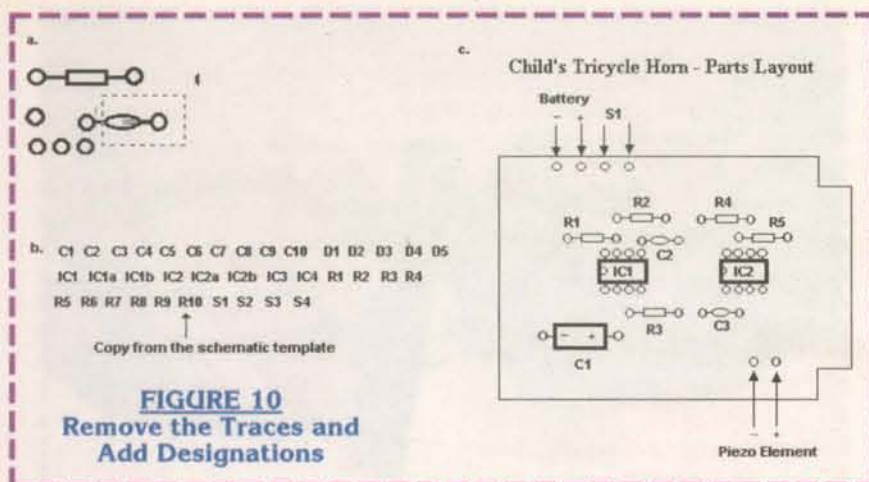

at a time, delete them, and then save my work before deleting any more.

b) We created some designations back in the schematic template, so grab a handful of these and copy them to the slide.

c) Designations in place, slide labeled.

Betcha thought we would never get around to creating an etch pattern ... it is done in the same way that we created the parts layout, only we delete the component outlines. To be more precise, we delete the bodies of the components, but leave their pads, since they indicate where to drill.

See Figure 11.

a) Copy the x-ray view draw-

ing to a new slide and remove everything external to the trace pattern.

b) Go to 400% zoom. Ungroup one outline at a time and delete each component body. Be patient ... you do not want to accidentally move any of the pads that you were so careful to set up.



See Figure 12.

a) Now we have an etch pattern.

b) Change the color of all the traces to black. I was able to do this in one step by rubber-banding everything and clicking as shown in Format/Colors and Lines.

See Figure 13.

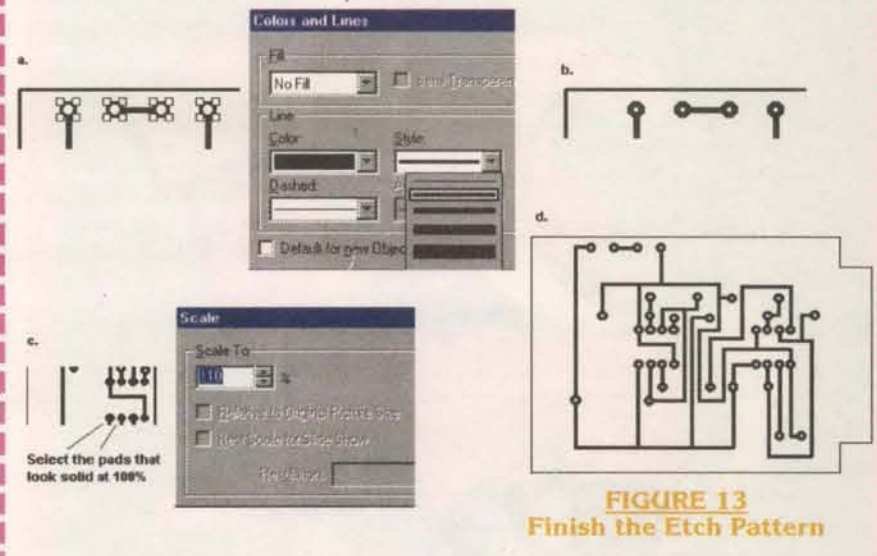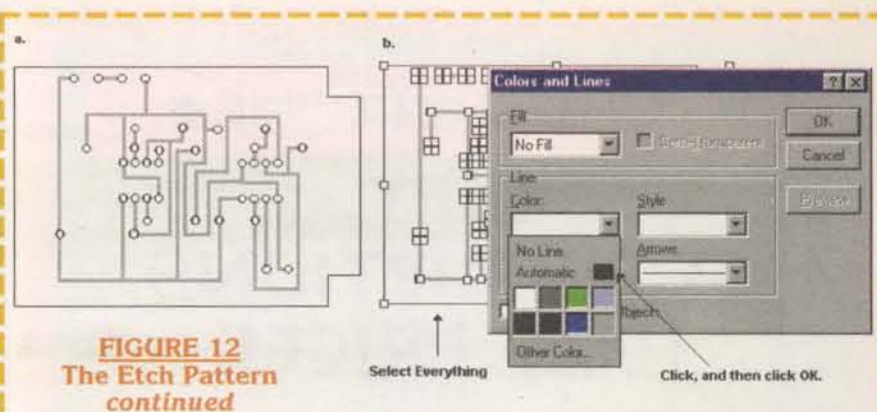a) Now select all the pads and change the line style to the second



thinnest.

b) This is what they look like at 200% zoom; at 100% some will look solid.

c) Since it is nice to be able to view our drawings at 100%, select all of the holes that still look solid at this zoom level and scale them up 10%. Doing this also gives us a more easily visible hole when the pattern is printed.

d) Try printing the slide. If the result looks like this, let's make a board!

There are about as many ways of transferring an etch pattern to a board as there are hobbyists. A way that works for simple boards and isn't technically complex

begins with printing the pattern to transparency film such as you can get from any stationery store. Now use a steel rule and a scribe to mark the outline of the board on a piece of single-sided copper clad phenolic (Figure 14). Use a nibbling tool to cut the piece to size (Figure 15). The material in the photos came from a RadioShack kit p/n 276-1576, which also contains etchant, a resist pen, and solvent for stripping the resist (Figure 16). The plastic case that holds these items doubles as a bath.

Clean the board thoroughly using a sponge and a little household cleanser (Comet or similar), and dry it. Now you want to tape the board over the etch pattern

THERE IS A FREE LUNCH AFTER ALL — 500 resistors sent absolutely free with order of \$10.00 or more. Sell them to your friends for 1¢ or 2¢ and treat yourself to a \$5.00 or \$10.00 lunch! Spend \$25.00 and we'll send 1,500 (Lunch for 2).

ER Digital Multimeter	\$17.95	1N4005 (600V-1A) (100)	\$4.95
ER Analog Multimeter	6.95	1N914 (75V-10mA) (100)	2.95
SO-239 Connector	.95	1N4148 (75V-10mA) (100)	2.95
PL-259 Connector	.95	2N3904 (NPN) (100)	6.00
6-pc Precision Screwdriver Set	1.50	2N3906 (PNP) (100)	8.00
10 Pair Alligator Clip Leads	2.95	2N3055 (NPN) GP	.65
10 T 1 3/4 LEDs (green, red, yellow)	1.25	2N5239 (NPN) HV GP Amp	1.50
12V - 60Amp Starter Switch	9.50	2N5684 (PNP) 50A-300W Hi-Pwr Amp	3.00
Pocket Telescoping Magnet	2.95	2N5686 (NPN) 50A-300W Hi-Pwr Amp	3.00
40-pc Carbon Steel Tap & Die Set	19.95	Set of 4 Wax Carvers/Picks	3.95
AA Ni-Cad Battery	.95	6" Plastic Vernier Caliper	1.50
1# 60/40 Solder	7.95	Pad of 56 Stick-on Feet	2.50
30W Solder Iron	2.95	4" Black Tie Wraps (100)	2.50
XLR-3 Pin Male Connector	2.00	12-1/2W - 1.5K Rheostat	4.75
XLR-3 Pin Female Connector	2.25	50V-2A Bridge Rectifier	.75
Mini Toggle Switch SPDT On-Off-On	.50	2-Way Splitter (5-900 MHz)	.95
Mini Toggle Switch DPDT On-Off-On	.60	RL45 Connector	.25
Full Size Toggle DPDT 15A-3/4 HP	2.00	Banana Plugs (Red or Black)	.30
3-Wire Trailer Connector (M&F)	3.25	Universal 1 Amp AC/DC Adapter	4.95
4-Wire Trailer Connector (M&F)	3.95	with 7 Different Voltages	
Mini Snap-In Rocker Switch 6A	.45		
1N4001 (50V-1A) (100)	4.95		

Add \$3.50 for shipping and handling. CA Buyers add 7.75% Sales Tax.

HYATT ELECTRONICS, 371 N. Johnson Ave., El Cajon, CA 92020
Tel. (619) 444-2434 • Fax (619) 444-1987

World's Smallest 68HC11 Microcontroller Module!

MicroStamp11™

NEW!


- tiny 1-inch x 1.4-inch module
- 5V regulator, 8MHz crystal
- choice of 8K or 32K EEPROM
- plugs into your breadboard like a DIP
- all I/O lines brought out to versatile 20-pin connector
- easy programming/code-loading with Docking Module
- 8K Starter Package #MS11SP8K...\$49*
- 32K Starter Package #MS11SP32K...\$60*
- additional modules from \$34 each

*Includes MicroStamp11, documentation, PC software, serial cable & Docking Module. Add \$5 for shipping & handling.

Technological Arts

Phone: (416) 963-8996

www.technologicalarts.com

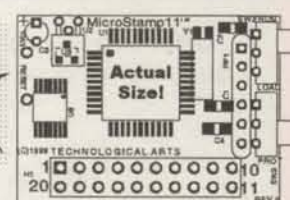

Possible Applications:

- remote telemetry
- micro robotics
- smart sensors
- many more!

Visa/MasterCard
Discover/Amex

Fax: (416) 963-9179

✱ SANTA SPECIAL ✱

GIFT SUBSCRIPTIONS HALF PRICE!!



That's right!

Buy or renew your own subscription to **Nuts & Volts** at the regular price, and order a second subscription to give to a friend or family member and pay *half* the regular rate!!

Along with your regular price subscription order, include the name and address of the person to receive the gift subscription, and we'll send them a special holiday card announcing their gift.

Offer applies to any length, PREPAID USA-delivered subscriptions only!! Half price offer cannot be used to extend one subscription.

NUTS & VOLTS MAGAZINE

430 Princland Court, Corona, CA 92879

909-371-8497 • 909-371-3052 FAX

Subscription Order ONLY Line 1-800-783-4624

E-Mail: subscribe@nutsvolts.com

Offer expires January 1, 2000

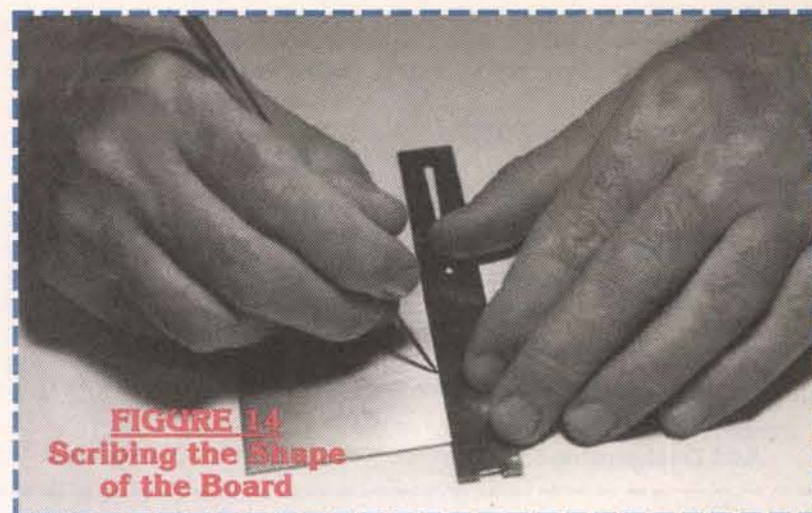


FIGURE 14
Scribing the Shape
of the Board

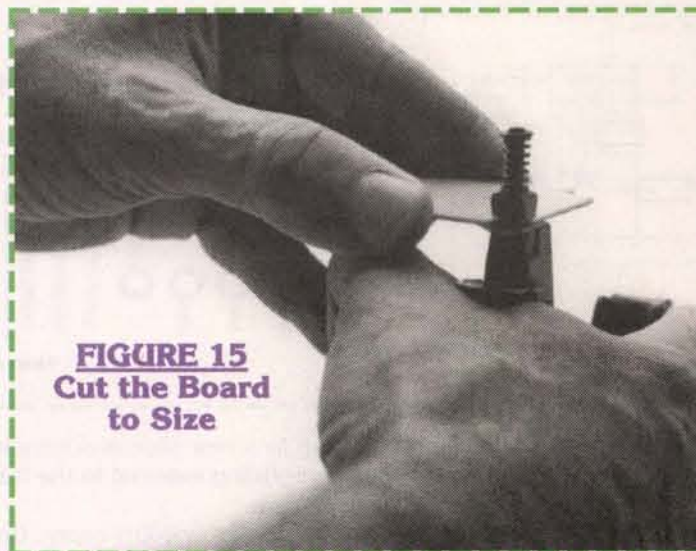


FIGURE 15
Cut the Board
to Size

(Figure 17) using ordinary transparent tape. If the text on the slide isn't backwards, you have the correct side up. Now turn the whole works over (Figure 18) and use a scribe to put a dent in the copper to mark the center of each pad.

Peel the board away from the drawing, but keep the drawing in front of you as a guide (it will be upside down now). With the resist pen, duplicate the drawing pattern on the copper (Figure 19). Your pads need not be perfectly circular, because the dents we made will position the drill precisely later.

Do use a steel rule to help keep your lines as straight and thin as possible. Follow the directions that come with the kit to etch the board and strip the resist ink.

Drilling and Stuffing

The kit comes with a 1/16th inch drill bit. This is fine for many of the larger holes that you will sometimes need to drill in a board, but it is too large for small component leads and IC pins. I use a number 59 drill and my trusty Dremel tool. Drill through each

FASTER THAN MOTOROLA

Two-way radio jamming equipment 800/900MHz. Stop illegal surveillance. **Pager jammers 900MHz.** Stop pagers from going off during school or church service. **Cellular phone jammers.** Stop cellars from going off during school or church service. **PCS jamming, PCS phones.** Lojack/teletrack/boomerang. Stop illegal tracing/anti-surveillance. Cordless phone jammers 49MHz/900MHz • Radar jammers Xband • Nextel jammers • Car alarm jammer • CB radio jammer • Garage door jammer • RC radio jammers • AM/FM radio • HF/VHF/UHF radios • 1/8000MHz jamming equipment.

This equipment is designed for anti-surveillance customers: embassies, schools, churches, governments, law enforcement.

IF YOU DON'T SEE WHAT YOU WANT, WE WILL BUILD IT FOR YOU!!

We sell only to specific organizations or for export. Anyone implying illegal activity will be denied assistance and will be reported to law enforcement.

Jam RF • 954-561-8128 or www.jamrf.com

FIGURE 16
The RadioShack Kit



Child's Tricycle Horn - Etch Pattern

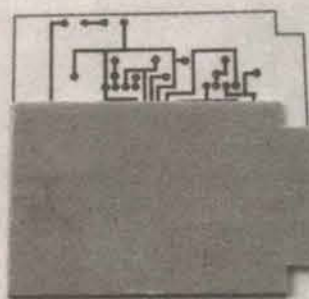


FIGURE 17
Tape Down the Board

RadioShack plastic box that I had in my stock. This one has been pulled from their stores but, if you want to duplicate what you see, you can still get it through the RSU (RadioShack Unlimited) program. You ask for part number RSU 11907698, pay for it at the store, and they ship the item to your home in a few days. I have tried this service for a few things in the catalog, and it has worked as advertised.

The piezo element is screwed to the case with 4-40 hardware. The board is mounted on a pair of female standoffs, RadioShack p/n 276-195.

I originally conceived this device as an add-on for a kid's tricycle, so I wanted the sort of handlebar-mounted switch that is typical of a horn. I couldn't find one in a store, so I cobbled one from a RadioShack push button part number 275-646 and a cap from a soda bottle. I made a hole in the top of the cap large enough to pass the button, connected a couple of wires to it and ran these out a small hole in the side. I filled the bottom of the cap with auto body filler and stuck a hose clamp (from any hardware store) into this

pad exactly where you made the center indentation earlier. Figure 20 shows the completed board, stuffed and ready to mount in a box. You will notice that the leads to the piezo element and the battery clip are tacked to the board with epoxy cement. This is just a precaution to keep them from breaking, because they take a good deal of flexing during assembly.

See Figure 21.

I mounted the works in a

ELECTRONIC TEST EQUIPMENT BOUGHT & SOLD

90 DAY WARRANTY PARTS & LABOR • 10 DAY RIGHT OF RETURN, OPEN ACCOUNTS

Altech Type 32, Precision Attenuator, 0-100dB	\$300	HP 8672A, Frequency Synthesizer, 2-18GHz	\$4,500
Argosystems AS210, Frequency Calibration System	\$2,000	HP 8684D, Signal Generator, 5.4-18GHz	\$2,000
Austron 2100R, Loran-C Frequency Monitor	\$250	HP 8697A, RF Plug-In, 26.5-40GHz	\$250
Bird 4381, RF Power Analyzer, Opt. 832	\$200	HP 8743A, Reflection Transmission Test Set	\$200
Boonton 82AD, Modulation Meter	\$450	HP 8743A/018, Reflection Transmission Test Set, 18GHz	\$300
Boonton 92BD, Digital RF Millivolt Meter	\$250	HP 8750A, Storage Normalizer, Includes Cable	\$250
Boonton 518-A4, Q Standard	\$100	HP 8753B, Network Analyzer, Opt. 002,006,010	\$8,000
Boonton 2500, DC Range Calibrator	\$250	HP 8756A, Scalar Network Analyzer	\$1,500
Boonton 4G, Power Meter Sensor, .01-26.5GHz	\$200	HP 8901A, Modulation Analyzer	\$1,000
Boonton 4300, Power Meter, 2 Channel	\$800	HP 8903B, Audio Analyzer, Opt. 001	\$2,000
Bruel & Kjaer 1612, Bandpass Filter	\$250	HP E3817A, DC Power Supply, 0-40V, 1A	\$250
Calit. Inst. 101T, AC Power Source	\$200	HP P486A, Power Sensor, 12.4-18GHz	\$100
Eaton 380K11, Frequency Synthesizer, 1-2000MHz	\$2,000	HP X486A, Power Sensor, 8.2-12.4GHz	\$100
EIP 371, Source Locking Microwave Counter, 18GHz	\$1,000	Hughes 8010H, TWT Amplifier, 3-8GHz	\$1,000
EIP 545A, Microwave Counter, 18GHz, Opt. 02,05,08	\$1,000	Huntron 5100DS, Computer Controlled Troubleshooting System	\$1,200
EIP 578, Source Locking Microwave Counter, 26.5GHz	\$2,200	Keithley 192, Programmable DMM, 6.5 Digits, HP/IB	\$600
EIP 931, Microwave Source, .01-18.6GHz, Opt. 9320	\$5,000	Keithley 195A, Digital Multimeter	\$300
ESI 296, Auto LCR Meter	\$800	Keithley 614, Electrometer	\$700
Fuke 515A, Portable Calibrator	\$800	Krohn-Hite 3202, Filter, LP, HP, BP, Unused	\$350
Fuke 540B, Thermal Transfer Standard	\$500	Leeds & North 1091, Capacitor Decade, .001uF-1uF	\$150
Fuke 5450A, Programmable Resistance Calibrator	\$1,000	Micronetics NSI-52640W, Noise Source, 26.5-40GHz	\$350
Fuke 6010A, Frequency Synthesizer, 10Hz-11MHz	\$300	Micro Sciences ICT-101, IC Tester	\$300
Fuke 6080A/AN Frequency Syn.	\$4,000	Ming HT-21, Handy IC Tester	\$100
Fuke 8520A, Digital Multimeter	\$250	Narda 5082, High Directivity Bridge, 2-18GHz	\$300
Fuke 8922A, True RMS Voltmeter	\$250	Narda 5292 Directional Coupler, 1-18GHz	\$200
Fuke A55, Thermal Converter	\$200	Racal Dana 1515, Delay Pulse Generator	\$500
General Microwave 478A, Peak Power Meter	\$700	Racal Dana 1992, Frequency Counter, High Stab.	\$500
General Radio 1557, Vibration Calibrator	\$400	Simco A300, Aerostat Anti-static	\$100
Gigatronics 6008-12, Frequency Synthesizer	\$1,000	Sorensen DCS-33-33, Power Supply, 0-13 volts	\$500
Gigatronics 910, Frequency Synthesizer, .05-26GHz, Opt. 03/06	\$8,000	Tek 0-33 Amps	\$100
Guideline 9154C, Transvolt Standard Cell	\$300	Tek 134, Probe Amplifier for P6021 & P6022	\$100
Guideline 9577, Precision DMM, 7.5 Digits	\$300	Tek 1470, NTSC Color Sync & Test Sig. Generator	\$500
Hitachi V-212, Scope, 20MHz, Dual Trace	\$200	Tek 1503/01/05, TDR, Scale in Meters	\$1,000
HP 1122A, Probe Power Supply	\$200	Tek 1503B, TDR with Opt. 03, Battery Pack	\$2,400
HP 11590A, Bias Network	\$250	Tek 178, Linear IC Test Fixture, For 577	\$150
HP 11604A, Universal Extension	\$100	Tek 2245A, Scope, 100MHz, 4 Channels	\$800
HP 11605A, Flexible Arm	\$100	Tek 2246, Oscilloscope, 4-Channel, 100MHz, Cursors	\$1,200
HP 11638A, Calibration Kit, Type N	\$600	Tek 2432, Scope, Digital, 300MHz, 4 Channel, HP/IB	\$2,000
HP 11665B, Modulator	\$250	Tek 2445A, Scope, 150MHz, 4 Channel	\$1,200
HP 11869A, Adaptor for Plug-In 8350A/B	\$350	Tek 2445B, Scope, 150MHz, 4 Trace, HP/IB	\$1,500
HP 11970A, Harmonic Mixer, 26.5-40GHz	\$600	Tek 305DMM, Scope, 100MHz, Dual Trace, DMM, battery	\$500
HP 11970K, Harmonic Mixer, 18-26.5GHz	\$600	Tek 318, Logic Analyzer w/accessories	\$500
HP 11970Q, Harmonic Mixer, 33-50GHz	\$600	Tek 338, Logic Analyzer	\$400
HP 1630D, Logic Analyzer w/pods	\$500	Tek 464, Scope, 100MHz Dual Trace, Storage	\$400
HP 1630G, Logic Analyzer, 65 Channels	\$500	Tek 492, Spectrum Analyzer, Opt. 01/02	\$4,500
HP 16530A/16531A, Digital Scope Card, 16500A System	\$500	Tek 492/02, Spectrum Analyzer	\$4,000
HP 214B, Pulse Generator	\$1,000	Tek 492BP, Spectrum Analyzer	\$8,500
HP 33102A, Microwave Switch, 100MHz-18GHz	\$100	Tek 492P, Spectrum Analyzer, Opt. 01,02	\$5,000
HP 3314A, Function Generator, Opt. 001	\$1,500	Tek 576, Curve Tracer	\$1,800
HP 3325A, Function Generator	\$1,000	Tek 577, Curve Tracer w/177 Fixture	\$1,000
HP 3325A/0102, Function Gen., Opt. 01/02	\$1,500	Tek 604, XY Monitor	\$100
HP 3332H, Programmable Attenuator, DC-18GHz	\$250	Tek 7D20, Programmable Digitizer PI	\$600
HP 3336C, Synthesizer, Level Generator	\$1,000	Tek 7S11, Sampling Unit w/S4 Head, DC-14GHz	\$800
HP 3400A, RMS Voltmeter, 10Hz-10MHz	\$100	Tek A610, Current Probe, 2-500 Amps	\$200
HP 3403C, True RMS Voltmeter	\$200	Tek DC503, Universal Counter Timer TM500	\$100
HP 3456A, Digital Multimeter	\$600	Tek DC504, Counter/Timer TM500	\$100
HP 35689A, S-Parameter Test Set for 3589A	\$1,400	Tek DM502A, Autorangeing DMM	\$150
HP 3582A, Spectrum Analyzer, .02-25.5KHz	\$1,800	Tek FG501, Function Generator, 1MHz	\$100
HP 4140B, Picoammeter, DC Source	\$2,000	Tek FG502, Function Generator, .1Hz-11MHz	\$250
HP 4274A, Multi-frequency LCR Meter, Opt. 001,002,003	\$2,000	Tek P6046, Differential Probe	\$300
HP/IB, Includes Test Fixture	\$2,000	Tek P6201, FET Probe Kit, 900MHz	\$400
HP 4342A, Q-Meter	\$1,000	Tek P6202A, FET Probe, 500MHz unused	\$300
HP 435B, Power Meter	\$350	Tek P6602, Temperature Probe for DM5110, DM511	\$150
HP 436A/022, Power Meter, HP/IB	\$500	Tek PG506, Scope Cal System w/TG501, SG503, New Style	\$1,500
HP 5005B, Signature Multimeter	\$350	Tek PG508, Pulse Generator, 50MHz	\$300
HP 5006A, Signature Analyzer	\$300	Tek PS503A, Dual Power Supply	\$150
HP 5334A/020, Universal Counter w/DVM	\$600	Tek SC502, Scope, 15MHz, Dual Trace	\$200
HP 5335A/010, Frequency Counter	\$600	Tek SG502, Sig. Gen. 5Hz-50KHz	\$200
HP 5335A/030, Frequency Counter, 1300MHz	\$800	Tek TDS410, Digitizing Oscilloscope, 150MHz	\$2,800
HP 5340A, Frequency Counter, 18GHz	\$600	Tek TDS410A, Digitizing Scope, 200MHz, Opt. 13,1F	\$3,000
HP 5340A, Frequency Counter w/Opt. 01/02/011	\$800	Tek TM503, 3 Slot Power Module	\$100
HP 5342A, Microwave Counter	\$1,000	Tek WM490A, Waveguide Mixer, 26.5-40GHz	\$800
HP 5345A, Frequency Counter, Opt. 012	\$400	Tek WM490K, Waveguide Mixer, 18-26.5GHz	\$800
HP 5350A/010/002, Microwave Frequency Counter	\$2,000	Texscan SSG2000, Freq. Syn., 100KHz-2GHz, AM, FM	\$1,800
HP 54100D, Digital Scope, 1GHz	\$2,000	Ungar 4624, Solder, Desolder Station	\$250
HP 54200A, Digital Storage Scope	\$800	Vu-Data 5110, Semiconductor Tester, In/out Circuit	\$150
HP 54601A, Digital Scope, 100MHz, 4 Channel	\$1,200	Wavetek 178, 50MHz Programmable Waveform Syn.	\$1,000
HP 6112A, Power Supply, 0-40V, 0.5A	\$200	Wavetek 180, Sweep/Function Generator	\$200
HP 8015A, Pulse Generator, .1Hz-50MHz, 30V	\$500	Wavetek 185, Sweep Function Gen., .0001-5MHz	\$400
HP 8165A, Programmable Signal Source, .0001-50MHz	\$1,000	Wavetek 1084, Signal Gen. Sweeper, 3.5-4.5GHz	\$300
HP 8165A, Programmable Signal Source, Opt. 02/03	\$1,200	Wavetek 1910, XY Monitor, Dual Trace	\$400
HP 8350A, Sweep Oscillator Mainframe	\$1,000	Wavetek 452, Filter, Dual HiLo, 1Hz-10KHz	\$450
HP 8350B, Sweep Oscillator Mainframe	\$1,500	Wavetek 907, Signal Generator, 7-11GHz	\$600
HP 8354A, RF Plug-In, 2-8.4GHz	\$1,200	Wiltron 610D, Sweeper Mainframe	\$250
HP 8354A, RF Plug-In, 5.9-12.4GHz	\$1,200	Wiltron 6213D, RF Plug-In, 10MHz-4.2GHz	\$400
HP 8410C/8412B, Network Analyzer w/8411A/Opt. 18, 18GHz	\$800	Wiltron 6219D, RF Plug-In, 2-8GHz	\$200
HP 8411A, Frequency Converters	\$250	Wiltron 6223D, RF Plug-In, 4-12.4GHz	\$250
HP 8414A, Polar Display	\$100	Wiltron 6229D, RF Plug-In, 7.9-18.5GHz	\$300
HP 8444A, Tracking Generator	\$500	Wiltron 62FF75, VSWR Bridge, 10-1000MHz	\$150
HP 8445B, Spectrum Anlyz., Automatic Pre-Selector	\$300	Wiltron 6NF50, Autotester, 1-1500MHz, for 640	\$100
HP 8447E, Amplifier, 1-1300MHz, Gain 22dB	\$600	Wiltron 7B50, Detector, 1-1500MHz, for 640	\$100
HP 8501A, Storage Normalizer, w/cable	\$800		
HP 8503C, 3.5mm Calibration Kit	\$1,000		
HP 8505A, Network Anlyz. w/8501A & 8503A, Opt. 05	\$4,000		
HP 8502B, Directional Bridge, 10MHz-26.5GHz	\$1,200		
HP 8557A, Spectrum Analyzer, 01-350MHz	\$800		
HP 8559A, Spectrum Analyzer, 01-21GHz	\$2,000		
HP 8559A/853A, Spectrum Analyzer, Digital, 01-21GHz	\$3,000		
HP 8569A, Spectrum Analyzer, 10MHz-22GHz	\$5,000		
HP 86220A, RF Plug-In, 10-1300MHz	\$500		
HP 86241A, RF Plug-In, 3.2-6.5GHz	\$400		
HP 86250A, RF Plug-In, 12.4-18GHz	\$400		
HP 86290A, RF Plug-In, 2-18GHz	\$1,200		
HP 86290B, RF Plug-In, 2-18GHz	\$1,400		
HP 8643A, Synthesized Frequency Generator	\$6,000		
HP 8660C, Freq Syn w/86603A & 86635A, 2.6GHz	\$2,500		
HP 86601A, RF Plug-In, 110MHz	\$300		
HP 86602A, RF Plug-In, 1300MHz	\$500		
HP 86603A, RF Plug-In, 2600MHz	\$800		

WANTED: YOUR EXCESS TEST EQUIPMENT

Turn your excess test equipment into cash!
Call or Fax your list for a quote.

PHELPS INSTRUMENTS

2631 Hillside Ave., Norco, CA 91760
909-279-7347 • FAX 909-279-7323



FIGURE 18
Mark the Hole Centers
on the Copper

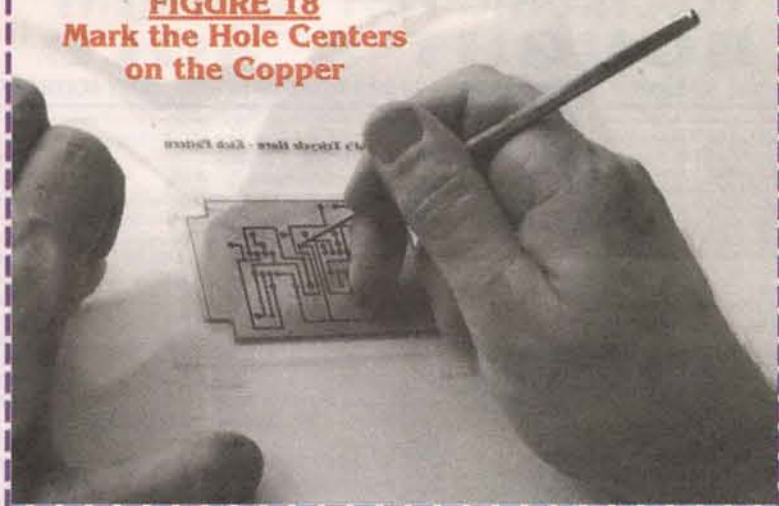


FIGURE 21
Mounted in
Case

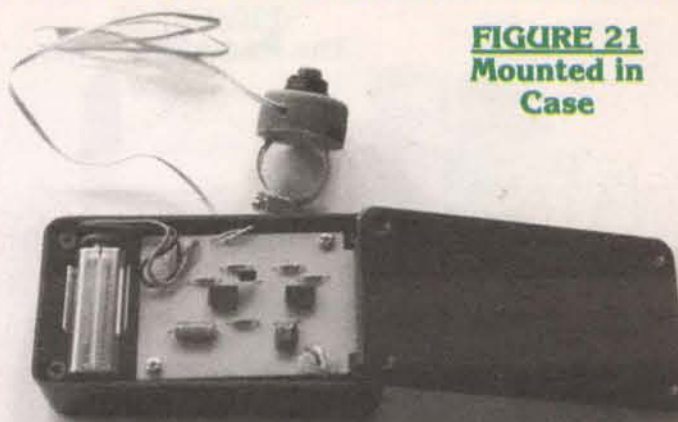


FIGURE 19
Draw the Pattern


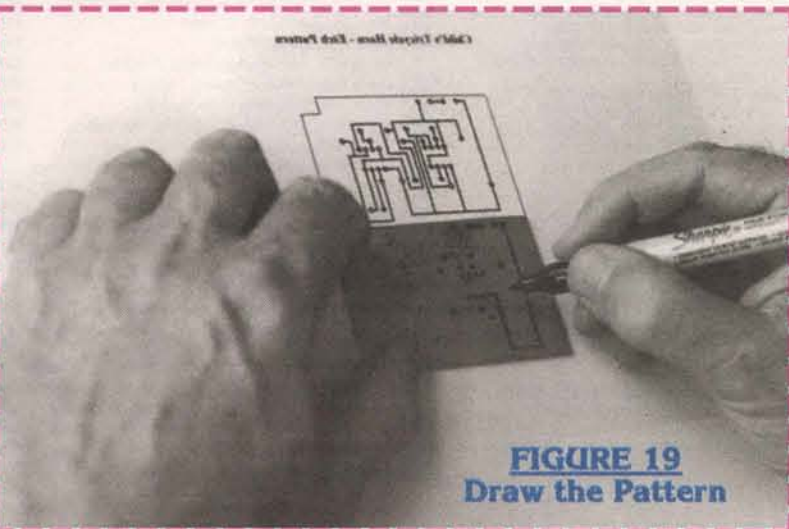



FIGURE 20
The Completed Board

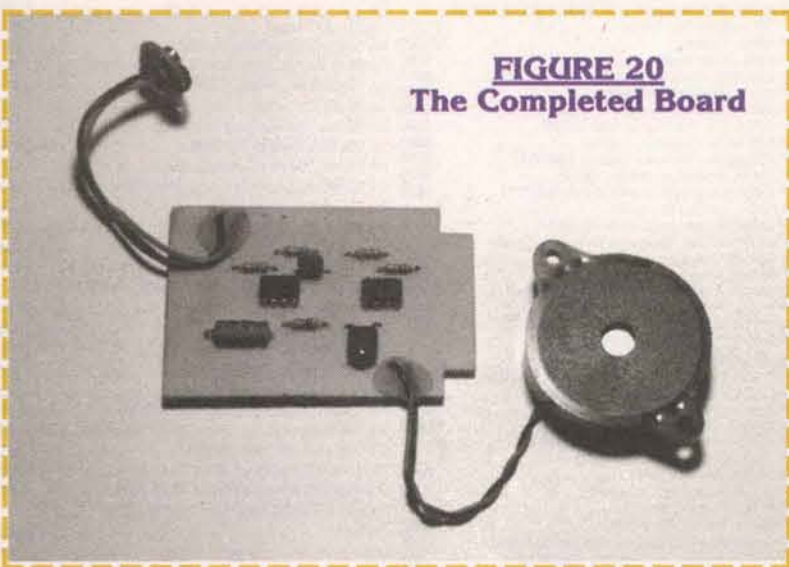

material while it was drying. As you can see, it fits nicely. To be able to secure the box to a handle-bar or other support, I cut a cou-

ple of slots in the cover of the case and threaded a larger hose clamp through them. Figure 22 shows the whole thing in place, and in

FIGURE 22
Get Outta My Way!!

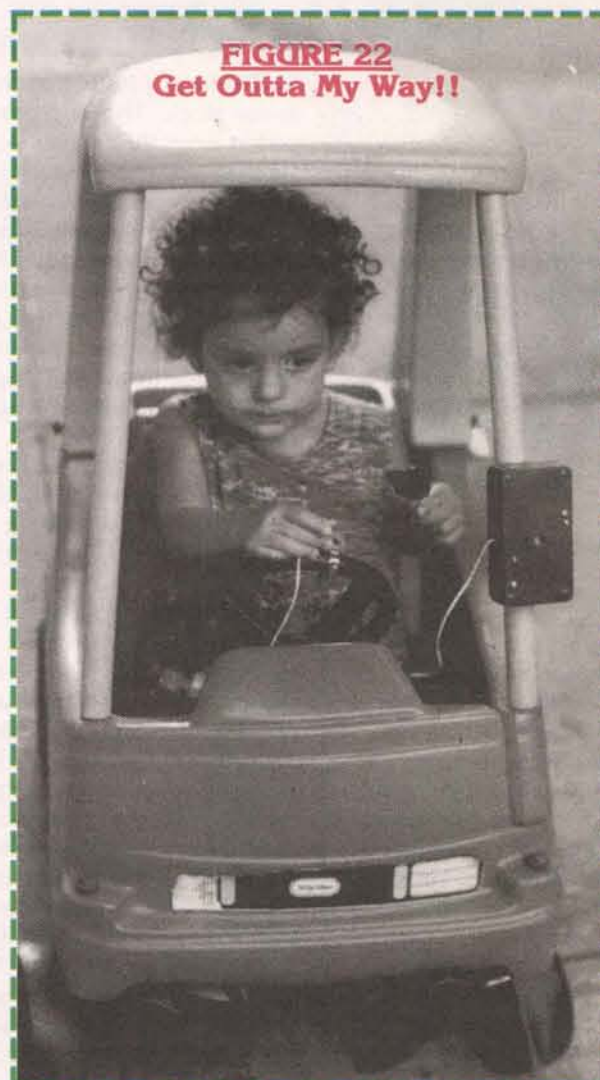

use by a future road warrior.

I hope that you enjoy using these PowerPoint tools for your projects, and I welcome comments and suggestions at Stevedanls@AOL.COM. Completed copies of the schematic and/or PC board templates are available as Power-

Point 7.0 files. Send your E-Mail address with a check or money order for \$10.00 for each template to: Small Bear Electronics, 123 Seventh Avenue, Suite 156, Brooklyn, NY 11215; or check out <http://home.netcom.com/~smallbearelec>. **NV**



"PROGRAMMING AND CUSTOMIZING BASIC STAMP COMPUTERS"

by Scott Edwards

Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.

ONLY \$34.95


Order Today!



**SECRETS OF
RF CIRCUIT
DESIGN**

2 Great Books
by Joseph Carr

**PRACTICAL
ANTENNA
HANDBOOK**

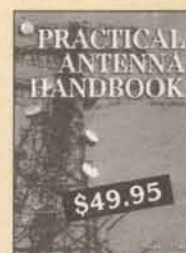

As a paid subscriber to *Nuts & Volts*, you'll receive **10%** off the list price!!

(See ad on page 92 for ordering details and other titles currently available.)

2539 W. 237th Street, Bldg. F, Torrance, CA 90505
 Order desk only: USA: (800) 872-8878 CA: (800) 223-9977
 L.A. & Technical Info: (310) 784-5488 Fax: (310) 784-7590
 OEM INQUIRIES WELCOME

TIMELINE INC.

Over 14 years and 32,000 customers and still growing

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

LIQUID CRYSTAL DISPLAYS

240x64 dot LCD with built-in controller.
 AND 4021ST-EO. Unit is EL back-lit. \$59.⁰⁰ or 2 for \$109.⁰⁰ or
 OPTREX DMF5005 (non back-lit) \$49.⁰⁰ or 2 for \$89.⁰⁰
 20 character x 8 line 7/16" x 2 1/8" The built-in controller allows you to do text and graphics.

Alphanumeric—parallel interface

16x1.....\$6.00	20x2.....\$8.00	32x2.....\$8.00
16x1 (lg. char.).....\$8.00	20x4.....\$8.00	40x1.....\$8.00
16x2.....\$6.00	20x4 (lg. char.).....\$10.00	40x2.....2 for \$20.00
16x2 (lg. char.).....\$10.00	24x2.....\$8.00	40x4.....\$20.00
16x4.....\$12.00	32x4.....\$10.00	4x2.....\$5.00

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

Graphics and alphanumeric—serial interface

size	Mfr.	price	size	Mfr.	price
640x480 (backlit)	Epson	\$20.00	480x128	Hitachi	\$10.00
640x400 (backlit)	Panasonic	\$15.00	256x128	Epson	\$20.00
640x200	Toshiba	\$15.00	240x128 (backlit)	Optrex	\$20.00
480x128 (backlit)	ALPS	\$10.00	240x64	Epson	\$15.00
			160x128	Optrex	\$15.00

6" VGA LCD 640X480, Sanyo LMDK55-22 \$19⁰⁰

MONITORS

9" COLOR SVGA MONITOR \$169.⁰⁰
 Fully Enclosed - Tilt and swivel type.

MONITORS

Non-Enclosed TTL

Comes with pinout, 12V at 1.4 Amp input • Horizontal frequency 15KHz • Ability to do 40 and 80 column.
5 inch Amber \$19.00 • 7 inch Amber \$19.00
9 inch Amber or Green \$19.00

5" COLOR MONITOR \$29.⁰⁰

• Flat Facplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible
 • 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.
 • Open Frame Construction • Standard Interface Connector • Degaussing Coil included • Mfr. Samtron

2 for \$49⁰⁰

HACKER CORNER

IBM™ Wireless Modem \$49⁰⁰

Use with laptop computer to send and receive voice, data, and FAX over standard cellular networks. Includes complete system of cellular radio transceiver, modem, handsfree JABRA headset, antennas, and complete operating and modem software for DOS/Windows. Interfaces with laptop using PCMCIA type II or III slot and included cable (SVDC systems). Ideal for sending data or FAX from the work site or your car. Provides an advanced graphical user interface for modem operation and handsfree voice conversations. Complete with full manual specifications. Features Include: • 14 Kbps data rate for cellular AMPS data connections • 19.2 Kbps data rate with CDPD service • Group 3 VIX fax protocol • Dual NAM support for cellular AMPS communications • Full duplex operation • Operating range: Transmitting 824 Mhz to 849 Mhz, Receiving 860 Mhz to 894 Mhz

4 INCH LCD MONITOR \$49.⁰⁰

Compact (4.4" x 3.8" x 1.4") TFT active matrix LCD color monitor including fluorescent backlight. Analog RGB and composite sync input with switchable horizontal / vertical viewing. Low power consumption and long life backlight make it ideal for security and door phone use. Single 8 VDC supply and good resolution allow mobile operations or use with laptops. Standard ribbon cable - Molex connector interface. Complete specifications included.

EMBEDDED 486 COMPUTER \$79⁰⁰ 2 for \$149⁰⁰

Complete enhanced Intel 486SX-33 based computer in ultra small (9-7/8" x 6-5/8" x 3-1/8") case. Ideal for embedded operations or as a second computer. Features include: • One 16 bit ISA slot • 3 serial ports plus dedicated printer port • Parallel optical coupled adapter port • Built in IBM PC/AT keyboard port • On board VGA video and port • Uses standard SIMM up to 32 MB • BIOS is PC/AT compatible

Unit has a backup Ni-Cd battery system in case of power failure (5 min. backup time) and lockable front cover to prevent floppy drive access. Mounting / interface provisions for standard 3.5" laptop floppy and 2.5 inch hard drives. Comes with very comprehensive manual.

SONY Miniature Color LCD Display (LCX005BKB) \$29⁰⁰

• 1.4 CM (0.55 inch) Diagonal Full Color Display • Built In Horizontal and Vertical Drivers • Delta Dot Pattern for High Picture Quality • 537 dots (H) x 222 dots (V) • Compatible with NTSC & PAL Format and Sync Inputs • 12 VDC Operation with -1 to +17 V RGB Signal and Driver Input Voltage • Excellent Display for Virtual Reality Projects, Viewfinders, and Miniature Test Equipment Displays • Pin Outs and Specification Included • Unit Requires Clock, Synchronization and Video

1.8cm (0.7 inch) unit LCX009AKB 827H x 228V \$29⁰⁰

CELL SITE TRANSCIVER \$29⁰⁰ 2 for \$49⁰⁰


These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 MHz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

NTSC COMPOSITE 4" LCD MONITOR \$69⁰⁰

SONY PLAYSTATION MODCHIPS. Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

SURPLUS LASER EQUIPMENT: New & used industrial, medical, scientific, and entertainment laser systems. <http://www.timepassage.com> sales@timepassage.com

CABLE TV

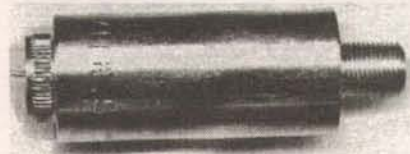

NOTCH FILTERS 110, 108.5, 106.5, 97.5 75dB deep notch. \$19.95 ea., 1-5 qty. \$15.95 ea., 6-10 qty. \$11.95 ea., 11-20 qty. \$9.95 ea., 21 or more qty. Call 24 hr. order and information hot line 516-389-3536.

POSITIVE NOTCH FILTERS. All channels available. Starting at \$16 each. Order by single channel #. Top quality non-tunable metal cylinder type. 75dB deep on the notch. Need to block the video on a cable channel? Order a negative notch filter. We carry a large stock on all channels for dealers and vendors. VISA, MASTERCARD, DISCOVER, and UPS COD for established customers. Quantity pricing on 5 or more. 100 pcs. \$7 each. Open 8am to 5pm CST, Monday-Friday. All sales must comply with FCC 1996 Cable Act. On the web go to WWW.GOFILTERS.COM "THE FILTER COMPANY." Call for all orders 1-800-235-8080.

RAW CONVERTERS: We have the best quality to your cable needs. PIO-5135 \$45; Zenith ST-1600 \$75; S/A 8590 (10-B) \$65 each; S/A 8590 (11-B) \$75 each; Comto 5503 VIP (450 MHz) \$35 each; Comto 5503-A only \$2 each. Call for others not listed. 405-631-5153.

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

GENUINE UNMODIFIED JERROLD DPBB 7312. 410-485-7772. E-MAIL: CLEWIS7298@AOL.COM

DTV & DISH NETWORK INFORMATION (33 pages) only \$15. Call toll-free 1-877-856-0923. Plus cable television reference guides for all systems, call 1-877-880-0197.

NEW! CABLE converter electronic service equipment and supplies for most cable converter boxes. Highest service, lowest prices. Call Ken Erny Electronics. 24 hr. order and information hot line 516-389-3536.

ALL YOUR cable needs, wholesale prices. All makes and models, dealers welcome. Call now 1-877-449-3737. Fast service Mon-Fri 9:00-5:00 EST. 24 hour msg. 30-day guarantee.

DISCOUNT CABLE converters, bullet snoopers, all makes and models: Genuine unmodified General Instrument, Jerrold, Tocom, Scientific Atlanta, Zenith, Pioneer, Panasonic and more. Best warranty. Free catalog 1-800-243-0962.

ATTN. DEALERS: Are you a current dealer or just getting started? Buy factory direct & save. New 125 channel volume control converter, 800MHz tuner. Also available non-volume converters. Call for lot pricing. A & S Wholesale, 1-800-370-0801.

PC BOARD ASSEMBLY. Thru hole only. Small or large quantities OK. Call Network Sales. 616-683-0500.

UNMODIFIED CABLE CONVERTERS. Zenith ST1600, ST1086, ST300, Panasonic 175, 145 vol. & non-vol. Regal RR-92 & RC 83, DP5, DP7, DRZ, 5503 VIP, SA 8580. Guaranteed low prices. Please call for more converters 405-631-1856.

WANTED: GENUINE RAW UNMODIFIED CABLE TV CONVERTERS. TOP CASH PAID. CALL 708-715-6118.

CABLE TV. Unmodified converters DP5 \$35; DPBB7 \$80; 8500 series \$15, etc., good prices over 100 pcs. Minimum 10 pcs. any qty., plus all major brands available. Lowest price new/refurbished/field pulls. Phone: 1-800-929-1549.



FUSION ELECTRONIC SECURITY

1-800-323-8746

WEBSITE: WWW.FUSIONELECTRONICS.COM
 E-MAIL: FUSION@FUSIONELECTRONICS.COM

1376 NW 22 AVE.
 MIAMI, FL 33125
 TEL (305) 635-7060
 FAX (305) 635-3175

MONITOR

\$93⁰⁰

BLACK & WHITE
 12" 1000 LINES
 ECL - 1202
 MANY SIZES AVAILABLE

BLACK & WHITE BULLET CAMERA

\$79⁰⁰

WATERPROOF
 420 LINES
 .1 LUX
 ECL - 377

DIGITAL COLOR CAMERA

\$99⁰⁰

DIGITAL COLOR (DSP)
 350 LINES
 2 LUX
 ECL - 551

MINI DIGITAL COLOR CAMERA

\$98⁰⁰

350 LINES
 ECL - 554
 2 LUX
 METAL HOUSING

COLOR MICRO BOARD CAMERA

\$87⁰⁰

DIGITAL (WITH DSP)
 350 LINES
 32 MM x 32 MM
 2 LUX • PINHOLE LENS
 ECL - 456P

PIR CAMERA

\$96⁰⁰

HIDDEN (COVERT)
 420 LINES
 .1 LUX
 WORKING PIR

2.4 GHZ VIDEO TRANSMITTER

\$89⁰⁰

1000' • 4 CHANNELS
 ECL - 240MT
 2.5" x 1.5" x .5"

4 CHANNEL RECIEVER

\$135⁰⁰

2.4 GHZ
 WITH POWER SUPPLY
 ECL - 240DSR

ALUMINUM WALL BRACKET

\$12⁰⁰

13" ADJUSTABLE P/T
 ECL - 205

BLACK & WHITE MINI DOME

\$59⁰⁰

3.5" • 420 LINES
 .1 LUX
 ECL - 372

OUTDOOR ALUMINUM HOUSING

\$34⁰⁰

WITH HEAT SHIELD
 ECL - 601S

BLACK & WHITE CAMERA

\$65⁰⁰

420 LINES
 .1 LUX
 ECL-371

BLACK & WHITE MICRO BOARD CAMERA

\$38⁰⁰

420 LINES
 32MMX32MM
 .1 LUX
 ECL - 11P
 PINHOLE LENS

PLASTIC WALL BRACKET

\$4⁸⁵

7" ADJUSTABLE P/T
 ECL - 206

MINI METAL BRACKET

\$6⁵⁰

SWIVEL HEAD
 CAMERA MOUNT
 ECL - 203AL

WE HAVE MONTHLY SPECIALS!

RAINBOW • SPECTO/CSI • GBC • CHUGAI/COMPUTAR • ATV • NVT • PHILIPS • BURLE • JVC •

ECLIPSE • PANASONIC • SILENT WITNESS • VIDEOLARM • SONY • SAMSUNG • PELCO • RAINBOW • SPECTO/CSI • GBC • CHUGAI/COMPUTAR • ATV • NVT • PHILIPS • BURLE • JVC •



REFILL INKS FOR INKJET PRINTERS

Refill your old cartridge and save. All refill kits come with instructions and needed materials for refilling inkjet cartridges. Success guaranteed. Available for the following:

CANON BC-01, BC-02 CANON BJ10e, APPLE STYLEWRITER, BJ-200 Single, Black, \$8.00. **CANON BJC-600** (BC-201) Single Black or Single Colors (3 refills) \$8.00. **CANON BJ-130/300/330 & IBM Exec Jet** (Cart #BJL-481 & BJL-642) Black - 3-bottle kit \$22.00. **CANON BJC-210/240** (BC-05 Cart) 3-color kit (3 refills each color for BC-05) \$24.00. **CANON BJC-4000** and Apple Stylewriter 2400 Black 3-bottle kit (3 refills BC-20, 9 refills BCI-21 black, 30 refills BCI-11 black, 10 refills BCI-10) \$19.00. **CANON BJC-4000/BJC70** and Apple Stylewriter 2400 Tri-color kit - 6 refills each color for BCI-21 or 15 refills each color for BCI-11 \$24.00. **CANON BJC-800/820/880** 3-bottle kit (for BJL-643B) \$19.00. **CANON BJC-800/820/880** 3-bottle tri-color kit (Cart #BJL-643CMY) \$24.00. **EPSON STYLUS COLOR PRINTER** - (Cart S020034) Single Triple black \$19.00; Tri-color kit (Cart S020036) 2 refills each color \$24.00. **EPSON STYLUS COLOR II** - (S020047) Triple Black \$19.00 (S020049). Tri-color (2 refills each color) \$24.00. **EPSON STYLUS COLOR 400, 500, & 600** (S020093) Triple black (7 refills total) \$19.00. **EPSON STYLUS COLOR 200, 500** (S020097) Tri-color 3 refills each color \$24.00. **EPSON STYLUS COLOR 400, 600, 800, 1520** Tri-color (S020089) 3 refills each color \$24.00. **EPSON STYLUS 800/1000** (S020025) 3-refill kit, black, \$19.00. **EPSON STYLUS COLOR 440 AND 640** Black refill kit. (S020187) 4 refills plus free vacuum bottle \$19.00. **EPSON STYLUS COLOR 440, 640, AND 740** (S020191) Color refill kit. 4 refills of each color \$24.00. **HP DESKJET 500/550/560** (51608A, 51633A, 51626A) Black single refills \$8.00. **HP DESKJET 500/550/560**. Black 3-bottle kit \$19.00. **HP DESKJET 500C/550C/560C**. Tri-color kit (5 refills each color) \$24.00. **HP DESKJET 1200C, DESIGNJET 650** (Cart #HP 51640B) Black Three pack (3 refills) \$19.00. **HP DESKJET 1200C/1600C, DESIGNJET 650** (Cart #HP 51640 C,M,Y). Tri-color kit (one refill each color) \$24.00. **HP DESKJET 600/660** (HP 51629A) Black three pack \$19.00. **HP DESKJET 600C/660C**. (HP 51649A) Tri-color (5 refills each color) \$24.00. **HP DESKJET 855C/1600C** (HP 51645A) Black three pack \$19.00. **HP DESKJET 855C** (HP 51641A) Tri-color kit (2 refills each color) \$24.00. **HP PAINTJET and PAINTJET XL** (51606A) Black 3-bottle kit \$19.00. **HP PAINTJET and PAINTJET XL** (51606C) Tri-color kit \$24.00. **HP PAINTJET XL300** (C1645A & C1656A) Black 3-refill kit \$19.00. **HP PAINTJET XL300** Tri-color kit (1 refill each color) HP 51639C,M,Y \$24.00. **HP THINKJET, QUIETJET, KODAK DICONIX 150** (51604A or 92261A) black 5 refills \$9.00. **IBM/Lexmark/Execjet/4076** (1380620) black 3-refill kit \$19.00. **IBM/Lexmark ExecJet IIC, WinWriter 150 C** (Cart #1380619) 4 refills each color \$24.00. **Lexmark 3200, 5000, 5700, 7000, 7200, Optra 45 and Z51** (12A1970) 3 refills Black \$19.00. **Lexmark 3200, 6000, 5700, 7000, Optra 45 and Z51** (12A1980) 4 refills each color \$24.00. **SNAP AND FILL SYSTEM** - Permits refilling HP 51626A (black for HP 500-series) and HP 51629A (black for HP 600-series) cartridges without making a hole in the cartridge. Consists of special cartridge holder, syringe, plastic tubing, and directions. **STARTER KIT** - with ink for 3 refills \$28.00. **EXTRA INK FOR SNAP & FILL SYSTEM** (black only) 4-oz. bottle \$18.00; 8-oz. bottle \$34.00. Specify whether for HP 51626A or HP 51629A.

HARD-TO-GET PRINTER RIBBONS



Gorilla Banana, Commodore 1525 \$8.00; Adam Coleco \$12.00; TI-850/855 \$6.00; Centronics 700 Zip Pack \$5.00; C. Itoh Prowriter Jr., Riteman C+/F+ \$6.00; Riteman Inforunner \$8.00; Commodore MPS-801 \$5.00; MPS 803 \$5.00; Decwriter LA30/36 \$4.00; Apple Scribe \$4.00; Mannisman Tally Spirit 80, Commodore 1526 \$5.00; Epson JX-80 4-Color \$14.00. Printronix P-1013 \$11.00; Star SJ144 color 3-pack \$29.00. ALSO HEAT & TRANSFER RIBBONS AND PAPER FOR PRINTING T-SHIRTS.

Over 300 different ribbons in stock. All ribbons new, not re-inked. Fully guaranteed. Order directly or send SASE for complete list.

Add \$4 per order shipping. CA residents add 7.75% sales tax. On ribbon orders over \$50 deduct 10% dis-

H.T. ORR Computer Supplies

249 Juanita Way, Placentia, CA 92870-2216

714-528-9822 • 800-377-2023 • FAX 714-993-6216

<http://www.extremeplay.com/occomp/orr.htm>

Write In 50 on Reader Service Card.

CABLE CONVERTERS, DBS, remotes, schematics, etc., free flyer. Smart card socket \$5 ea. New Atmel 89C52 \$10 ea. Jake 419-385-3100.

PLAIN CONVERTERS: Brand-new, the most reliable in the market today. V-Master 3800 only \$75 each, refurbish Panasonic-TZPC-175, \$39. Minimum 10-lot, 1 full year warranty, same day shipping. 405-634-1535.

CABLE CONVERTERS. Original equipment with remote. Like new, ready to go. Lowest prices. Guaranteed. Limited models. Call now 412-833-0773.

THE BEST is back to stay. Master code recovery. 16c5x, 16c62x, PALS, GALS, other microcontrollers, etc. Check out our web page at www.acdinc.com for details or call 703-764-5361 or write Advanced Circuit Designs, Inc., 5765-F Burke Centre Parkway, Suite 317, Burke, VA 22015.

PLAYSTATION MOD chips. New Dino mode program. Works with all models up to 900x. Color instructions. Seven wire hook up, does not come with wires. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

CALL US TOLL FREE FOR ALL YOUR CABLE NEEDS. OFFICE HOURS: M-F 9AM-5PM EST. COD ONLY, FREE SHIPPING ON FIRST ORDER. TOLL FREE 1-877-282-7641.

TOCOM UNMODIFIED 5503 cable converters, untouched, \$6 ea. 10 lot min. Call 706-657-4445.

GENUINE UNMODIFIED JERROLD DPBB7312 FOR SALE 10 LOT MIN. CALL 708-715-6118.

CABLE PARTS & EVERYTHING. Best prices & quantity discounts. WE DON'T SELL BOXES. 1-800-MODULE-0.

SONY PLAYSTATION MODCHIPS. Allows playing of CDR backups & imports. \$10 + \$3 shipping. 619-590-9320.

CABLE PARTS! Computer parts. Call for great prices or visit us on the Web: [HTTP://WWW.CB-Electronics.com](http://WWW.CB-Electronics.com) or call 1-800-436-8630.

CABLE BROKERS IS HAVING ITS FINAL BLOWOUT OF THEIR WAREHOUSE. THE FOLLOWING UNMODIFIED EQUIPMENT IS AVAILABLE TO OTHER BROKERS AND CABLE COMPANIES IN 100 LOT; ZENITH ST 1083-5 \$5; DUAL CABLE INPUT, ST 1600 99 CHANNEL DC \$30; TOCOM 5503A \$2; VIP \$18; 07 \$25, PI 5135 \$60. V5S8 \$50. 2014 \$70; 8600, 8590, 8570 \$30. You must prepay shipping ON ALL ORDERS \$175. CALL 1-800-219-8618.

CABLE CONVERTERS & equipment for the lowest prices guaranteed. 30-day money back guarantee & 1-year parts and labor. COD & credit cards welcome. 1-800-711-0187.

CABLE CONVERTERS. One stop for all your cable needs. New plain converter and original factory equipment with remote. We also carry PICs, EPROM, and MC68HC705C8ACP and remote. Lowest price guaranteed. 1-800-387-1981.

CABLE TV. Join us on the INTERNET to buy and sell cable TV equipment, electronic equipment, DSS equipment, satellite equipment, telephony equipment, and much more. Major equipment dealers and wholesalers online. Auctions, classified ads, discussion forums, chat rooms, and dealer links for all types of equipment. Dealers and vendors call or visit our site for ad rates and links. WWW.GOCABLETV.COM or call 1-800-451-0083.

BRAND NEW basic converters, 550MHz w/remote, \$19.95 ea. 10 lot min. Call 706-657-4445.

UNMODIFIED CABLE converters. SA 8590, \$39.95 ea. 10 lot min. Call 706-657-4445.

ZENITH UNMODIFIED converters. ST 1000-288, \$16 ea. 10 lot min., ST 1086, \$25 ea. 10 lot min., ST 1600, \$59.95 ea. 10 lot min. Call 706-657-4445.

TELEPHONE/FAX

12 HOUR fully automatic heavy duty professional **TELEPHONE RECORDER, \$79** including shipping. Send check or money order to: **VAKIS**, 1402 Pine Ave., Niagara Falls, NY 14301.

PHONE SYSTEMS WANTED!!! We buy AT&T MERLIN, SYSTEM 25/75/85 and other AT&T phone systems. Please call for a quote or fax us your equipment list. **KEYWAYS, INC.**, 937-847-2300 or FAX 937-847-2350.

FOR SALE: All items new in MFG box. Toshiba, computer, telephony-system, PC Strata, DK 424, Iwatsu-build Adix, vs to suit your needs. Cortel Co., Aries, digital, key-system, ADKS 144, ACB cards for many applications. Send for mfg. items list. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711.

MFG. COMPUTER telephony integration. We have strategy DK Aries, key system ADKS 144. Send for full detail and mfg. items list. 3U hot swap, backplane assemblies. 6U computer telephony assembly. Ohio Service Supply Co., PO Box 8802, Canton, OH 44711-8802.

CABLE TV. Join us on the INTERNET to buy and sell cable TV equipment, electronic equipment, DSS equipment, satellite equipment, telephony equipment, and much more. Major equipment dealers and wholesalers online. Auctions, classified ads, discussion forums, chat rooms, and dealer links for all types of equipment. Dealers and vendors call or visit our site for ad rates and links. WWW.GOCABLETV.COM or call 1-800-451-0083.

TIMELESS PRODUCTS

The Best Prices and Service • In Business over 15 years!

Phone 218-346-6660 Fax 218-346-6664

CABLE TV CONVERTERS

WILL NOT DECODE

New! "TP 125 V"
128 Channel Converter with Volume

Special Prices for
TP1550PC
Call for Details

Panasonic still available!

- REFURBISHED CONVERTERS ALSO AVAILABLE •
- QUALITY REPAIR DEPARTMENT FOR ALL YOUR TUNER REPAIRS •
- REMOTES AVAILABLE FOR MOST CABLE BOXES •

DEALERS ONLY • GREAT QUANTITY PRICES • NO DECODER SALES

COMPONENTS

RF TRANSISTORS, TUBES, SD1446, MRF455, MRF454, 2SC2290, 2SC1969, 2SC2166, 2SB754, TA7222AP, 2SC1947, TIP42C, KIA7217, MRF422, MRF448, MRF247, MRF317, SAV7, SAV17, 3-500ZG, 4CX250B, 572B, 3CX400A7/8874, 3CX3000A7, 4CX400A, silver mica caps, resistors, electrolytics, etc. Westgate 1-800-213-4563.

CASH PAID FOR ICs. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.,** 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. www.electronicsurplus.com


NEW SURPLUS ICs: (250) AY-3-1015D @ \$5; (275) CD10105BE @ \$0.35; (104) ICM7217IIJI @ \$4.75; (65) MM54104N @ \$9; (325) MM74C901N @ \$0.35. Doppler Systems, 480-488-9755 or dave@dopsy.com

SEE OUR ad on 4-channel 2.4GHz wireless system in the AdMart section on page 74. Matco, Inc.

WANT TO Buy: ICs, military & aircraft relays, diodes, transistors, Cannon, TRW, Amp, Burndy, Deutsch, Bendix connectors, electronic test equipment & most components. Hoffer Electronic Ent., 818-718-1165, FAX 818-341-5506. E-Mail: Hoffer1165@aol.com



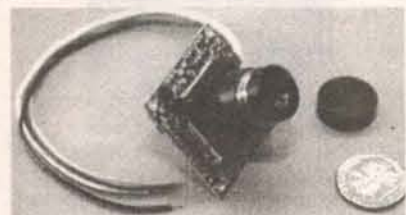AMAZING! 35¢ ALL TOGGLE SWITCHES. Brand new. Rated 6A/125V. Hardware included. 1/4" panel hole. SPDT or DPDT on-on, or on-off-on. Minimum 100pcs./package. Add \$6 freight. Gateway Products Corporation, PO Box 936397, Margate, FL 33093, 954-227-9300. VISA/MC, no COD.



B/W 430 LINE CCD CAMERA with optional black low-profile swivel adjustable enclosure. Pin hole or Std. lens type. 6, 8, and 12mm lens are available. 1/3" CCD, 3.6mm/F2.0 lens included; 9-14 VDC, 0.08 lux, IR sensitive; 1.27" x 1.27" x 0.5"D pinhole or 1" deep standard. Price @ 10 pcs., **\$44 each.** Enclosure: \$8; optional lens: \$18. Dealers welcome. MATCO, Inc. 1-800-719-9605. Fax 847-619-0852. E-Mail: sales@mat-co.com Website: www.mat-co.com

DIAMOND-TIPPED BURS for Dremel-type tools. Set of 20, in case, \$8 postpaid (check, MO). John Hill, 5734 Vickie Dr., Winston-Salem, NC 27106. Visit Honest John's Electronic Barn on the web! <http://soar.to/honestjohn>

NEC SUPER caps .47 farad, 5.5V. cap measures .840D x .45H. Mounted on small PC board measuring 1.070 x .920 w/current limiting charging resistor and polarity protection diode. 100 pcs., \$25 (qty. avail.) leave message 714-806-3268.

MICROCONTROLLERS

Programming and Customizing BASIC Stamp Computers. By well known author Scott Edwards, originator of the *Nuts & Volts* Stamp Applications column. Only \$34.95. **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

Sell Nuts & Volts in your store and earn \$\$\$! Contact us for details. 909-371-8497



PIC MICROCONTROLLER PROGRAMMER KIT. Super value at \$19.95 + \$4.95 shipping. See our web site for the complete range of PICs that can be programmed. Includes PCB, parts and instructions. P16PRO shareware must be downloaded from the web. Amazon Electronics, tel 1-888-549-3749. Lots of other products. www.electronics123.com

ANTIQUE ELECTRONICS

WESTERN ELECTRIC wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. **FREE OFFER** 1-800-251-5454.

WANTED: FOR historical museum, pre-1980 microcomputers, magazines, and sales literature. Floyd, VA 24091-0341 (540-763-3311/540-382-2935).

RADIO TUBES and phono. needles. 870-347-2281.

Tired of Expensive Inkjet Cartridges ? Save 90% on Inkjet Inks !

Printer	# of Refills		Cost/Refill		Kit Price	
	Black	Color	Black	Color	Black	Color
HP 500 Series, 400, Officejet 300, 350, Fax	7	14	4.71	2.85	32.95	39.95
HP 600 Series, Officejet 500, 570, 600	7	14	4.71	3.21	32.95	44.95
HP 820C, 855C, 870C, 1000C, 1150C, Copier 120, 210	6	12	6.67	3.33	39.95	39.95
HP 720C, 722C, 712C, 880C, 890C, 895C 1120C, 1170C	6	12	6.67	3.75	39.95	44.95
Canon BJ-10, 200, 210, 240, 250 Apple SWriter 1200, 1500	14	20	2.15	2.00	29.95	39.95
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	60	60	0.50	0.67	29.95	39.95
Canon BJC-6000	14	8	2.85	1.67	39.95	39.95
Canon BJC-600, 610, 620 Apple SWriter Pro	20	13	1.50	3.07	29.95	39.95
Epson Stylus Color, Color Pro, Pro XL	12	12	2.50	3.33	29.95	39.95
Epson Stylus Color II, IIs, 1500 (Black)	15	15	2.00	2.66	29.95	39.95
Epson Stylus Color 500, 200	20	17	1.50	2.35	29.95	39.95
Epson Stylus Color 400, 600, 800, 850, Photo	20	17	1.50	2.65	29.95	44.95
Lexmark JP 1000, 1020, 1100, ExecJet II, IIs, Medley 4C	10	17	3.00	2.35	29.95	39.95
Lexmark JetPrinter 5700, 5000, 7000, 7200, 3200	15	17	2.67	2.35	39.95	39.95
Compaq IJ700, IJ900, Xerox XJ8C, XJ9C	15	17	2.67	2.35	39.95	39.95
Xerox Home Center 450C, XJ6C Inkjet	22	12	1.36	3.33	29.95	39.95

SAVE 30 - 50% on New Compatible Cartridges!

Printer	BLACK CARTRIDGE	COLOR CARTRIDGE
(CALL FOR OTHERS NOT LISTED)		
Canon BJC-4000 Series, C2500, C3000, C3500, C5000	\$5.50	\$12.95
Apple StyleWriter 2400, 2500	\$5.50	\$12.95
Canon BJC-600, 610, 620 Apple StyleWriter Pro	\$4.95 (9cc)	\$4.95 @ (9cc)
Hi-Capacity Canon BJC-600, 610, 620	\$5.95 (15cc)	\$5.95 @ (12cc)
Canon BJC-70, BJC-80	\$9.95 (3-pak)	\$14.95 (3-pak)
Epson Stylus Color, Color Pro, Pro XL	NEW PRICING \$10.95	\$17.95
Epson Stylus Color II, IIs	\$12.95	\$17.95
Epson Stylus Color 500, 200	\$12.95	\$17.95
Epson Stylus Color 400, 600, 800, 850, 1520, Photo	\$12.95	\$17.95
Epson Stylus Color 440, 640, 740	\$12.95	\$17.95

- **BULK Inks, Refill Accessories**
- **Glossy card stock & Coated Paper**
- **School & Government PO's Welcome**
- **2 - 3 Day Shipping**

Quality Inks for:
HP • Epson • Lexmark
Canon • Apple • DEC

Inkjet Southwest



Call or see us online!

Monday - Friday
8:30 - 5:30 PST 11:30 - 8:30 EST

www.inkjetsw.com

1-800-447-3469

(480) 668-1069 Fax

(480) 668-0959

ACP's 94th GIANT COMPUTER SWAP★MEET

Orange County's Original! Be a Seller...for your space Call Mary

All Day Sunday 8am-2pm

Nov 28th

FREE Admission & Parking Shop 100's of Sellers

in ACP's Giant Parking Lot !!!

Advanced Computer Products, Inc.

ACP SUPER★STORE
Since 1976

**1310 E. Edinger
Santa Ana, CA
714-558-8813**



CRYSTAL SETS. Parts, plans, books, kits. Largest source in the world. Catalog \$2. B. TURKE, PO Box 22288, Hollywood, FL 33022.

AVIATION ELECTRONICS

BUY, SELL, trade, avionics equipment, Collins, King, Sperry; test equipment, IFR, Litton LTN series INUs. 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net

PUBLICATIONS

Discount electronics books. See the NV Bookstore ad on page 92.



OUT-OF-PRINT TECHNICAL BOOKS.
www.johnsontechbooks.com
805-525-8955. sales@johnsontechbooks.com

CABLE TV CONVERTERS



Raven-85 plain converter: 85 channel, Ch-3 output, PG Lock, HRC/STD and sleep timer

Raven-99 plain converter: 99 channel, Ch-3 output, PG lock, MFT/Fine tuning, HRC/STD and sleep timer

Raven-135 converter: Volume control, 135 channel, Ch-3/4 output, PG lock, HRC/STD and sleep timer, audio & video output through RCA jacks

Raven-125 converter: Volume control, 125 channel, Ch-3/4 output, PG lock, HRC/STD (by remote unit) and sleep timer, audio & video output thru RCA jacks

FREE BROCHURES & PRICE LIST

CALL (310) 515-5085 or
FAX 1-800-579-5000
PCW Company

PRACTICAL ANTENNA HANDBOOK, by Joseph Carr. The most popular book on antennas ever written, widely known as "the antenna builder's bible." This Third Edition is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works. Only \$49.95! **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

Programming and Customizing BASIC Stamp Computers. By well known author Scott Edwards, originator of the *Nuts & Volts* Stamp Applications column. Only \$34.95. **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

SECRETS OF RF CIRCUIT DESIGN From Joseph Carr, comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits. Only \$29.95! **10% discount to Nuts & Volts subscribers.** Call 1-800-783-4624 to order using Visa or MasterCard.

ROBOTICS

ROBOT BOOKS.COM visit our web site for reviews of robotics books, plus robot kits, toys, movies, and magazines! www.robotbooks.com

ARobot KIT from Arrick Robotics uses the BASIC Stamp II. Quality metal construction. Easy to assemble and very expandable. \$235. <http://www.robotics.com/arobot>

www.futurerobots.com ROBOTICS for active security systems is now possible for the amateur electronic experimenter to design and build. Come and see the future of home robotics and read Lab Note 116 Design Concepts for Various Types of Guard Robots. Also other technical articles about active security robot and systems.



H-BRIDGE MOTOR controllers. 12V (\$25) and 24V (\$35) versions. 35A average, 50A peak PWM out. Many features. Compact. Approximately 3.75" by 5.5". 570-735-5053. <http://members.tripod.com/~divelec>

CONTROL STEPPER MOTORS FROM PC. <http://www.timepassage.com>


BIPOLAR STEPPER driver (chopping type): automatic current reduction when idle. 3 amp per phase, 12-40V, full or half step, opto isolated inputs, \$75 in quantities of 1 or 2, \$65 in quantities of 3 or more. www.brewingtons.com

PLANS — KITS — SCHEMATICS

QUICK-BUILD PROTOBOARDS. PIC instrumentation chips, kits, telephone electronics, pocket testbench. Oricom Technologies, 303-449-6428. www.sni.net/~oricom

MAKE YOUR OWN PHOTOVOLTAIC CELLS! Incredibly easy, cheap, compact, and versatile. Complete instructions. wclark@infoave.net

The Pocket Programmer

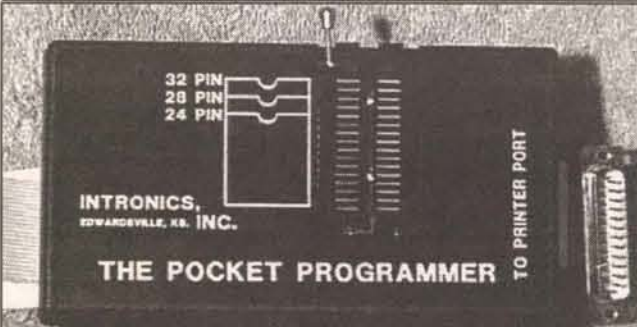

The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs E(E)prom, Flash & Dallas Ram. 27(C)/28(C)/28F/ 29F/29CXXXX & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, MCU's 874X, 875X, 40-Pin X 16 & Serial Eprom's, PLCC, 5-Gang, 82/74 Prom's and Eprom Emulator to 32K X 8. Only \$129.95

Same Name, Address & Phone Number for 16 Years.... Now isn't that Amazing ?

Intronics, Inc.

Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add \$5.00 COD
Tel. (913) 422-2094 Add \$4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge / Amex

COMPUTER PARTS

NEW ARRIVAL!

Super Deal on new Pentium II PC System-Fully Y2K Compliant.

BAREBONES SYSTEM

\$245

Mainboard + ATX case, 56K V.90 Fax/Modem, 8MB AGP Video, 3D sound, 10/100 network adapter, removable hard drive kit, floppy drive, speakers, keyboard, and mouse. (CPU, memory, & hard drive not included...available below.)

Memory		Other Add-ons	
SDRAM PC-100 32MB/64MB	\$51/89	40x CD-ROM	\$39
128MB/256MB	\$155/299	4.3 GB Hard Drive	\$95
		8.4 GB Hard Drive	\$124
Packard Bell Upgrades		10.8 GB Hard Drive	\$149
VIDEO: 512K Kit	\$18	Processors	
1MB Kit	\$49	Intel Celeron 400/500 MHZ	\$89/195
CACHE: 128K Kit	\$18	Intel PII 400/450 MHZ	\$209/230
512K Kit	\$49	Intel PIII 500 MHZ	\$290
CPU: Intel 486 DX2-66	\$25		
Intel Pentium Overdrive	\$59		

NOTE: Prices subject to change without notice.

LA PAZ ELECTRONICS INTERNATIONAL
P.O. Box 261095 San Diego CA 92196
Tel. 858.586.7610 * Fax. 858.586.1482

Order Line: 800.586.4199 Visit Our Website @ www.lapazelectronics.com

ENCYCLOPEDIA OF electronic surveillance schematics: Schematics with parts identification, \$20; **Amateur's guide to wiretapping**, \$10. VHS, 1370 Trancas Street, #201, Napa, CA 94558.



RUNNING LIGHTS KIT. Ideal for Christmas decorations etc. 8 LEDs switch on in 10 push button selectable patterns. 8 speed levels for a total of 80 combinations. Includes PCB, parts and instructions. \$15.95 + \$4.95 shipping. Can operate light bulbs with 8x TRIACs (\$6 extra). Amazon Electronics, tel 1-888-549-3749. Lots of other products. www.electronics123.com

CONSUMERTRONICS 120+ exciting manuals: Electronics, computers, Internet, phones, energy, radionics, financial (including stocks), crime-fighting, security, survival, phenomena, **SPECIAL PROJECTS**. Catalog \$3. PO Box 23097, Albuquerque, NM 87192. www.tsc-global.com



CIRCUIT BOARDS. Low-cost, precision-made PC boards from your CAD program files (no photoplots required). Single and double-sided with contour routing. Ideal for RF/analog/digital prototypes. Full details at <http://www.pcbmilling.com> E-Mail: feedback@pcbmilling.com FAX: 703-818-0071.

LASER LIGHT SHOW KITS & SOFTWARE. <http://www.timepassage.com>

MANUALS — SCHEMATICS WANTED

MISCELLANEOUS ELECTRONICS FOR SALE

HIGHEND EQUIPMENT 203-744-4111. OK INDUSTRIES DEMO BLOWOUT. If it is not listed just give us a call, chances are we have it! **SOLDER STATIONS:** total rework, forced convection, hot air. MTR5000 (retail \$4,595) sell \$1,700; MTR4000 (retail \$3,995) sell \$1,400; MTR3001 (retail \$2,495) sell \$900; BTR2001 (retail \$1,595) sell \$500; FCR2001 (retail \$1,850) sell \$700; BTR1000 (retail \$825) sell \$300; SMT1160 (retail \$995) sell \$400; SA2000 (retail \$395) sell \$140; SA1000 (retail \$295) sell \$100; SA500 (retail \$145) sell \$50. **PUR-AIR:** Fume exactors. EP101 (retail \$1,695) sell \$200; EP051 (retail \$595) sell \$100. **JEM:** Batch ovens JEM310 (retail \$7,995) sell \$2,500; JEM210 (retail \$4,995) sell \$1,000. **PICK & PLACE:** Chip placers, vacuum pencils, fluid dispensers. SMT8501 (retail \$4,595) sell \$1,500; SMT880 (retail \$2,200) sell \$500; FD1000 (retail \$495) sell \$150; VP100 (retail \$395) sell \$100. **BOARD ETCHER:** SSP-75A (retail \$995) sell \$300. **ALWAYS BUYING: VIDEO, RADIO, PHONE SYSTEMS, COMPUTERS, STEREO, AND BROADCAST EQUIPMENT.**

FREE FLYER on DBS, cable TV, phones, credit cards, schematics, health items. Bill 1-800-879-9657.

PRIMECELL

IF YOU NEED NEW BATTERIES FOR YOUR ELECTRONIC EQUIPMENT
DON'T PITCH EM - SEND THEM FOR REBUILDING ! - SAVE \$ \$

CUNARD ASSOC. INC., 9343 US RT 220, Bedford, PA 15522

- WE INSTALL NEW NI-CAD OR NI-MH BATTERIES INTO YOUR ORIGINAL CASE.
- WE IMPROVE CAPACITY TO BETTER THAN ORIGINAL.
- WE FIX WHAT CAN'T BE FOUND. (OR AFFORDED)
- WE PROVIDE QUICK SERVICE. / EXTENDED LIFE FOR OLDER EQUIPMENT
- WE OFFER FREE QUOTES. / FREE RETURN IF QUOTE IS REFUSED.
- WE PROPERLY DISPOSE OF YOUR OLD CELLS BY RECYCLING.
- WE GIVE YOU A 12 MONTH WARRANTY.
- WE WILL BE HERE WHEN YOU NEED US / EST. 1986
- WE SAVE YOU **** MONEY **** \$ \$ \$ \$



• NO JOB IS TOO LARGE OR TOO SMALL VOLUME DISCOUNTS AVAILABLE

GENERAL ELECTRIC

19A704850P(1200mAh) \$ 34.95
19A704860P(1800mAh) \$ 39.95
PL19D429763(777)G1/3 \$ 37.95
19A705293P 344A4506P \$ 34.95
MAXON SA-1155 1160 \$ 39.95
TAD 1450 1510 1520 \$ 21.95

MOTOROLA

P200 HT600 MT1000
NTN 4585 4824 5414 \$ 37.95
NTN 5447 5521 5545 \$ 37.95
NLN 5860 NTN 4327 \$ 39.95

MIDLAND

70-B10 B16 B19 B21 \$ 39.95
B25 B26 B32 B36 B60 \$ 39.95

UNIDEN

APX650 1050 \$ 29.95
1000 1010 1070 \$ 34.95
1100 1200 Series \$ 38.95
BP205 650mAh \$ 19.95
BP200 1500mAh \$ 24.95
SC150 1500mAh \$ 22.95

ICOM

BP2 / BP3 / BP22 \$ 18.95
BP5 / BP23 / 24 \$ 24.95
BP7 / CM7 / BP8 \$ 32.95
BP180 / CM79 \$ 34.95

YAESU

FNB 3 4 12 14 16 \$ 32.95
FNB19 21 26 27 38 \$ 32.95
FNB 10 1117 25 35 \$ 23.95

RADIO SHACK

HTX Packs \$ 29.95
New 8.4V pack & chgr
1500mAh nimh \$ 34.95

KENWOOD

PB2 / KNB3 \$ 29.95
PB21/21H \$ 14.95
PB25/H26 \$ 24.95

CORDLESS DRILLS

Any brand 7.2V \$ 18.95
Any brand 9.6V \$ 29.95
Any brand 12.0V \$ 32.95
Any brand 14.4V \$ 37.95
Any Brand 18.0V \$ 45.95

COMPUTER PACKS

Send battery for quote.

FOR INFORMATION ABOUT YOUR REQUIREMENTS CONTACT US:
PHONE OR FAX: (814) 623-7000 E-MAIL TO: PRIMECELL@AOL.COM
SEND YOUR PACKS FOR FREE QUOTATION VIA UPS, RPS OR US MAIL
VISIT OUR WEB SITE <http://members.aol.com/primecell/primecell.htm>

BATTERY REBUILD SERVICE

MANY OTHERS AVAILABLE - WRITE OR CALL

FREE CATALOG

ADD \$ 4.50 SHIPPING & HANDLING PER ORDER



Write In 55 on Reader Service Card.

HARD-TO-find parts; big screen tubes \$135; 13", 19", 25" \$25; electronic tuners \$20; RF modulators \$5; modules, knobs, flybacks. Call 912-272-6561. Scarborough TV, 1422 Old River Rd., East Dublin, GA 31027.

LASERS, SCANNERS & SOFTWARE. <http://www.timepassage.com>

NEC SUPER caps .47 farad, 5.5V. cap measures .840D x .45H. Mounted on small PC board measuring 1.070 x .920 w/current limiting charging resistor and polarity protection diode. 100 pcs., \$25 (qty. avail.) leave message 714-806-3268.

DEC EQUIPMENT WANTED!!! We are buying DEC systems, boards, terminals, drives and peripherals. Also Scientific Micro Systems (SMS), DSD, Datability, Dialog, other DEC compatibles, and Computer Output Microfilm (COM) units. Please call for a quote or fax us your equipment list. We buy, sell, and trade. **KEYWAYS, INC.,** 937-847-2300 OR fax 937-847-2350.

PC CABLES: <http://www.pccables.com> connectors, RS232, IDC, SVHS, ribbon cable, DB9, DB15, loopback, null modem, jumpers, SCSI, screws, rails. Secure online catalog, ordering, browsing. 954-418-0817.



SOLAR-POWERED FAN HAT. Baseball type hat with solar powered fan. Great for sports fans, golfers, etc. Available in red or blue. \$19 plus \$2.00 shipping. CA residents add 7.75% sales tax. Visa/MC/Disc/Amex OK. H.T. Orr Computer Supplies, 249 Juanita Way, Placentia, CA 92670. 714-528-9822, 1-800-377-2023, FAX 714-993-6216.



*Check out Santa's Special on Page 52 and
our Winter Special on Page 92*


ADDRESSABLE STEPPER MOTOR CONTROLLER

The PARAMAX stepper motor controller is a PC parallel port based addressable controller capable of simultaneous operation of 4 uni-polar stepper motors ranging in voltages from 5 to 12 volts at up to 2 amps per phase. The PARAMAX stepper motor controller includes 8 digital inputs with a data throughput rate of 500k bytes per second. Using the unique PARAMAX addressing method, up to 256 controllers can simultaneously function from a single parallel port. The programming package includes libraries that allow you to create applications both under Windows and DOS. Included libraries are: C++, Pascal, Delphi, Basic and utilities for DOS and Windows.

Also available at:
FORD ELECTRONICS, INC
(714) 521 - 8080

Part Number: JWP1X-1A

\$199.95

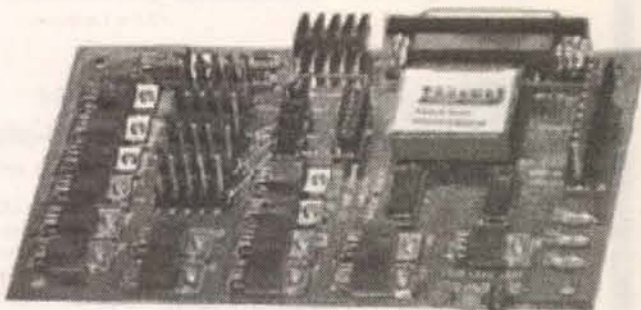

PARAMAX INC.
(800) 473 - 8080

Come and visit us on the internet at:
www.paramax.net

Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase, and 3-D Surface plots
- Real-Time Recording and Post-Processing modes

Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research

System Requirements

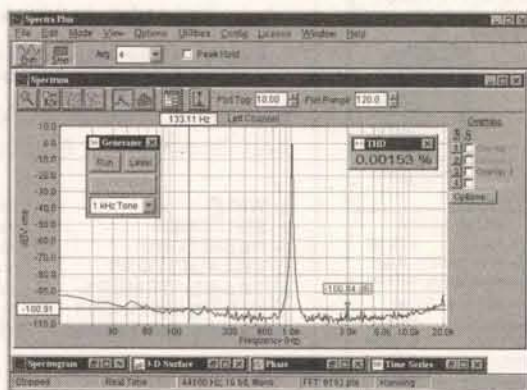- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



Priced from \$299

(U.S. sales only – not for export/resale)

DOWNLOAD FREE 30 DAY TRIAL!

www.spectraplus.com

PHS Pioneer Hill Software
24460 Mason Rd.
Poulsbo, WA 98370
a subsidiary of Sound Technology, Inc.



Spectra Plus
FFT Spectral Analysis System

Sales: (360) 697-3472

Fax: (360) 697-7717

e-mail: pioneer@telebyte.com

Write in 56 on Reader Service Card.

Serial in, graphics out. Almost too easy.


These serial displays take RS-232 at 2400 or 9600 baud and produce stunning text and graphics on a supertwist LCD screen. See our complete line at www.seetron.com. All models are in stock for immediate delivery.

G12032 120x32-pixel LCD SGX-120L \$99.00

Same size as 2x16 text LCD
Editable font(s) in 4 sizes
Up to 6 screens in EEPROM
Easy terminal protocol



(3.2 x 1.4 in.)

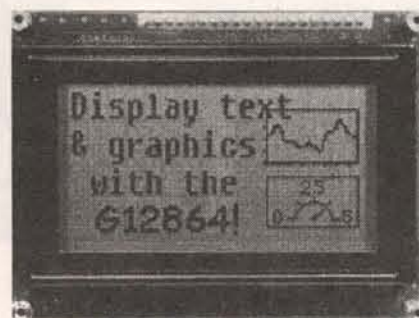

(3.7 x 2.8 in.)

G12864 128x64-pixel LCD \$199.00 BGX-128L-1

Large, sharp LCD
Editable font(s)
Up to 14 screens in flash
Separate text, graphics layers
DB9 connector built in
AC adapter jack built in
Easy terminal protocol

www.seetron.com

Scott Edwards Electronics, Inc. ph 520-459-4802 fx 520-459-0623 nnv@seetron.com

Write in 57 on Reader Service Card.

NUCLEAR ELECTRONICS (NIM, CAMAC), PMTs, optics, high vacuum, and high voltage components and equipment. Guaranteed quality at reasonable cost. OE Technologies, Box 703, La Madera, NM 87539. Ph: 505-583-2482, Fax: 505-583-9190, E-Mail: oetech@newmexico.com <http://www.oetech.com>



ANAHEIM WIRE PRODUCTS. DISTRIBUTOR OF ELECTRICAL WIRE AND CABLE since 1973. Items available from our stock: Hook up wire, Automotive primary wire, GXL, SXL, Plenum cable, Teflon wire, Multi-conductor cable, Irradiated PVC, SO-CORD, Mil-Spec wire, Building wire, Welding cable, Battery cable, Telephone wire, Shrink tubing, Cable ties, Connectors. Wire cut & strip to specs. If interested, please call **1-800-626-7540**, FAX: 714-771-5043. Visa/MC/Amex. SEE US ON THE INTERNET: <http://www.anahemwire.com> OR E-Mail: info@anahemwire.com

HIGH QUALITY TOOLS AND STAINLESS STEEL HARDWARE. European and American screwdrivers, nut-drivers, pliers, hex-keys, balldrivers, and more! Wiha, Bondhus, and Knipex. Stainless cap screws, machine screws, nuts, washers, U-bolts, and eyes. Free catalog. Robert Mink Import-Export, Box 6437V, Fair Haven, NJ 07704. Telephone or fax **732-758-8388**. E-Mail: w2tv@csi.com

MISCELLANEOUS ELECTRONICS WANTED


WANTED: TUBE HiFi/commercial amps, preamps, corner/horn speakers. Altec, Marantz, McIntosh, Western Electric, etc. 405-737-3312 fax 405-737-3355.

WESTERN ELECTRIC wanted: 1920s-1960s. Amplifiers, mixers, pre-amps, speakers, tubes, etc. FREE OFFER 1-800-251-5454.

WANTED: TUBES, radios, transmitters, receivers, gyros, bearings, connectors, relays, lamps, synchros. Hyness Company, 709B Delair Road, Cranbury, NJ 08512-4212. Phone: 609-395-1116, FAX 609-395-1117.

WANTED: MANUAL/parts/programming software for Uniden UHF handheld model #SPU480K. Call Bill at 610-587-4107.

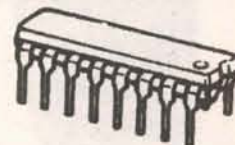WANTED: AVIONICS test equipment, IFR, 600A, 401L, others, Collins, King, Sperry, North Atlantic, Litton INUs LTN series, rate and tilt tables, air data test sets, 941-625-3222 P, 941-625-0494 F, E-Mail: avionics@afcon.net



WANTED: EXCESS ELECTRONIC COMPONENTS, BOARD-LEVEL COMPONENTS; MILITARY COMPONENTS; ICs, MEMORY, TRANSISTORS, DIODES, CAPS, RELAYS, ETC. CALL **LA PALMA SEMICONDUCTOR, 714-523-8892 FAX 714-523-8898**.

HIGHEST PRICES PAID: I will pay the following prices for Western Electric tubes: 211A/D/E new \$300, used \$175; 212A/D/E new \$750, used \$275; 274A/B (engraved base) new \$250, used \$200; 300B (engraved base) used \$550; 422A new \$50, used \$25; 437A new \$50, used \$25; and many more. Also buying Western Electric, and other audio tube and equipment literature. Call or send us your list. Toll free tel/fax: 1-888-715-8823. Don Singerhouse/Singerhouse Sound, LLC, PO Box 321, New Richmond, WI 54017. E-Mail: singtube@frontiernet.net

WANTED: X-BAND radar equipment. Military, civilian, working or not, parts, TMs, etc. Box 10215, Pittsburgh, PA 15232.

CASH PAID FOR ICs. Military or commercial integrated circuits, transistors, diodes, any semiconductors. **ELECTRONIC SURPLUS, INC.**, 5363 Broadway, Cleveland, OH 44127. 216-441-8500 or fax 216-441-8503, since 1946. www.electronicsurplus.com

NEEDED: WATER cooled induction heaters, hi-voltage supplies, variable 0-60KV, 0-10mA. Contact Ian, phone 864-882-6580.

WANTED: STANCOR/Chicago PCO/PSO-150, PCC-55, PCC-200. Also audio equipment by Langevin or Fairchild. R. Robinson, POB 1425, Wallingford, CT 06492. 203-949-0871. Richmix@erois.com

BBS & ONLINE SERVICES

EDUCATION

Lowest Dealer Price Available

	5+	10+	20+
Refurb. Panasonic 145 Regal w/Remote	\$45	\$40	\$35
BC4535 86 Channel	\$38	\$35	\$30
Oak Sigma 99 Channel	\$30	\$28	\$25
75 Channel Converter	\$45	\$40	\$35
Zenith ST1600 w/Remote	\$18	\$18	\$18
Panasonic Converters Model-175 (550MHz)	\$75	\$70	\$65
	\$65	\$55	\$45

Six month's warranty on this model only

Call us today to satisfy all your cable equipment needs!

SAM'S ELECTRONICS
1-405-631-1856

All Cable Equipment is unmodified.

BUSINESS OPPORTUNITIES



COUNTER-SURVEILLANCE=\$250 HR! Electronic eavesdropping is unbelievably widespread! Are you sure you're safe? Learn how others (without prior experience) earn \$250 HR in the fascinating field of COUNTER-SURVEILLANCE! For FREE catalog call: 1-800-732-5000.

RADIO SHACK dealership for sale. Located in the beautiful San Jacinto mountains of Southern California in forested Idyllwild. This store has been successful since 1980. If you have been looking for a chance to get out of the city and still be involved in electronics, here is your opportunity. Call Tom at 909-659-2029 for more information.

REPAIRS — SERVICES

ENGINEERING CONSULTING. Product development from conceptual to manufacturing stages. Digital, analog, and RF expertise. Microcontroller designs for HC05xx, HC11xx, and PIC families. Software design for IBM PC, XLINX and Altera FPGA design. In-house schematic capture and PWB. Hicks Electronic Design, PO Box 7366, Loveland, CO 80537-0366. Toll Free 1-888-849-6792 E-Mail: steve@hicksengineering.com website: www.hicksengineering.com

PC BOARDS REPAIRED. Prices start at \$5. Minimum 5 of one type. Network Sales, 616-683-0500.

PATENT YOUR HARDWARE/SOFTWARE INVENTIONS. Experienced registered patent agent can help you. Quick, efficient, economical, confidential service. Call 909-599-0801.

WELD ALUMINUM WITH PROPANE! EZ, INEXPENSIVE, STRONG. DETAILS: WEEKS, 36 CAROLINA ST., TAYLORS, SC 29687. 1-800-547-WELD(9353) FAX 864-244-6349. <http://www.dura-fix.com>

PRINTED CIRCUIT design by professional with 30+ years: conventional, multilayer, downhole, fine line. Prototype and production fabrication. Reverse engineer existing 2-layer board. Toll free 877-236-3223. www.circuit-applied-tech.com

CABLE CONVERTER REPAIR: Quality repair service for all name brands. If you're tired of the runaround you're getting from the company you purchased it from, or they're out of business. Give us a call for fast and courteous service. Have model and problem ready. Sorry no box, chip, or IL repairs. **Highview Engineering** 815-245-3735 or E-Mail: HIGHENG1@AOL.COM ask for George.

PC BOARD ASSEMBLY. Thru hole only. Small or large quantities OK. Call Network Sales. 616-683-0500.

(E)EPROM PROGRAMMING done quickly and economically. One day turn around typical. Simple copy \$3 per device. Also prototyping, design, and consulting services available. Call or send SASE to: **Luzer Electronics, 4023 North Bayberry, Wichita, KS 67226. 316-687-2127, FAX 316-687-3103.**

PLAYSTATION MOD chips. New Dino mode program. Works with all models up to 900x. Color instructions. Seven wire hook up, does not come with wires. \$5 each, plus shipping charges. 10% discount for 10 or more. Call 703-764-5118 to place an order.

PICS, GALS READ if you've lost your masters. Programming service available. Call for info. Network Sales, 616-683-0500.

RADIO REPAIR! Reasonable charges. Jim Rupe, 998 Whipple, Grayland, WA 98547-0697. 360-267-4011. E-Mail: w7ddf@yahoo.com

We are looking for New Distributors for Nuts & Volts Magazine.

If you would be interested in selling Nuts & Volts in your store or on your newsstand, we have a great deal for you!

For complete information, ask for our New Distributor flyer.

Nuts & Volts Magazine
phone 909-371-8497
fax 909-371-3052
E-Mail
distributors@nutsvolts.com

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM
WE BUY TEST EQUIPMENT AND COMPONENTS.
VISIT US ON THE WEB AT WWW.ABCTEST.COM


HP 54501A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 4935A TRANS. IMPAIRMENT TEST SET	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5006A SIGNATURE ANALYZER	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG	\$400.00
HP 54200A 50MHZ SCOPE/WAVEFORM ANALYZER	\$700.00	EIP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPEMETER	\$550.00
HP 5370A 100MHZ U.T.I. COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3586C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR&CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPEC. ANALYZER	\$3500.00
HP 3437A 3.5DIGIT SYSTEM VOLT METER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK 7904 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ PROG. O-SCOPE FRAME	\$750.00
HP 3336C SYNTHESIZER/LEVEL GENERATOR	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 3325A SYNTHESIZER/FUNCTION GENERATOR	\$1000.00	TEK 7904 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5335A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A24 400MHZ VERTICAL PLUG	\$150.00
HP 8558B/181 100K-1500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7B80 400MHZ TIME BASE	\$75.00
HP 8559B/183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7B92A 500MHZ DUAL TIME BASE	\$125.00
HP 1740A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7512 SAMPLING PLUG	\$250.00
HP 6034A 60VDC-10A POWER SUPPLY	\$750.00	TEK 7L14 10KHZ-1.8GHZ SPEC. ANALYZER	\$1000.00
HP 6269B 40VDC-50A POWER SUPPLY	\$800.00	TEK AM503 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-12.5A POWER SUPPLY OPT.J01	\$1200.00	WAVETEK 145 20MHZ PULSE/FUNCTION GEN.	\$400.00
HP 6632A 20VDC-5A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN.	\$150.00
HP 6643A 45VDC-4.3A POWER SUPPLY OPT.J03	\$750.00	WAVETEK 955 7.5-12.4GHZ MICROSOURCE	\$1100.00

Write in 58 on Reader Service Card.

Digital Storage Oscilloscopes From \$99.00

ATC modules turn your PC into a full-function DSC, spectrum analyzer, logger, & DVM. Units DC to 50MHz. O-Scope II now in Windows 3.1, 95/98, NT and DOS.

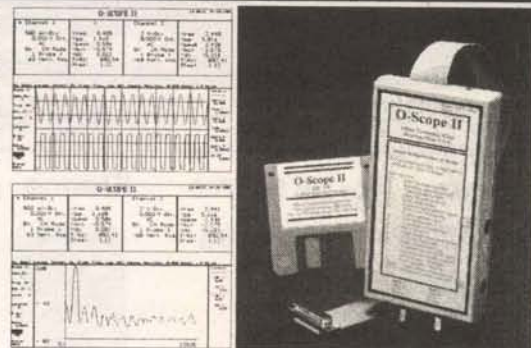O-Scope Ip \$189.
O-Scope II \$349.
Specialty probes call.



ATC is a stocking distributor for Pico Technology LTD which offers scope modules to 100MSPS, resolutions from 8 to 16 bit.

Pico offers PC based data loggers from 1 to 22 channels, 8 to 16 bit and the Enviromon environmental monitoring system.

Pico products - call

The DFA-5, **low cost differential amplifier**, cuts through common mode noise problems to reveal low voltage signals. With **NEW** gains from 1X to 1000X and band widths from 20KHz to 1.2MHz, DFA-5 is the test accessory to help you work with signals from **DFA5** 5 Volts to 5 microVolts. Only \$129.00.

Serial Port Problems ???
Check out **Serial !!** Our lowcost serial channel analyzer only \$99.00.

Allison Technology Corporation
2006 Finney Vallet Rd., TX. 77471 U.S.A.
800-980-9806 or 281-239-8500
<http://www.atcweb.com> atc@accesscomm.net

HOBBYISTS' ELECTRONIC SURPLUS

New Arrivals Daily!

FREE RESISTORS

We also service small & large OEM accounts.
We buy & sell excess electronic inventory.

(408) 573-7045

Check out our website
www.excess-solutions.com



Excess Solutions

Retail Store Location

430 E. Brokaw Rd.
San Jose, CA 95112

Write in 59 on Reader Service Card.

Nuts & Volts Magazine/NOVEMBER 1999 61

CALL TOLL FREE

(800) 292-7711
Orders Only

Se Habla Español

C&S SALES

Secure On-line Ordering @ cs-sales.com

**CALL OR WRITE
FOR OUR
FREE**

**64 PAGE CATALOG!
(800) 445-3201**

Digital Multimeters

Elenco Model M-1740



\$39.95

- 11 Functions:**
- Freq. to 20MHz
 - Cap. to 20µF
 - AC/DC Voltage
 - AC/DC Current
 - Beeper
 - Diode Test
 - Transistor Test
 - Meets UL-1244 safety specs.
- Model M-2760 - \$24.95**
(9 functions)

Elenco Model LCR-1810



\$99.95

- Capacitance 1pF to 20µF
- Inductance 1µH to 20H
- Resistance .01Ω to 2000MΩ
- Temperature -20°C to 750°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

Fluke 87III



\$319

Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

CCTV Cameras

Cameras have 420 lines (380 color) of resolution, 0.08 Lux, 3.6mm/F2 90° field of view. Power requirement is 12VDC @ 100mA (order SC-1).

MONOCHROME CAMERAS

COLOR CAMERAS



SC-12 - 35mm Lens (1.25"x1.25")



SC-15 - Pin Lens (1.25"x1.25")



SC-20 Pin Lens

SC-21 3.6mm Lens
360 Lines 1.25" x 1.25"
Infrared Sensitive, Audio Included

Accessories:

SC-1 - 12V 100mA adapter

SC-2 - 50' cable with connectors

\$6.00

\$19.00

\$109

Add \$10 for case

Call for complete catalog.

Test Equipment

**Quantity
Discounts
Available**

Elenco Sweep Function Generator with built-in frequency counter Model GF-8036

\$229.95



This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.2Hz to 2MHz.

10 Function 1.3GHz Universal Counter Elenco Model F-1300

- Frequency .05Hz - 1.3GHz 3 Ranges
- Period - Can read 60Hz to 60,000,000 F=1/T
- Totalize - Counts to 199,999,999
- RPM - 3 to 2099994 RPM
- Duty Cycle
- Max/Min/AVG with Time
- Stop-watch set 2 sec. to 100 hrs.
- Math Functions
- Timer - 2 sec. to 99 days
- Pulse Width - 0.1ms to 60000.6ms



\$229.95

20MHz Sweep / Function Generator with Frequency Counter Model 4040

- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep



21.5MHz Model 4070 **\$1295**
10MHz Model 4017 **\$325**
5MHz Model 4011 **\$255**

\$445

BK PRECISION

Elenco Handheld Universal Counter 1MHz - 2.8GHz Model F-2800



\$99

- Sensitivity:**
- <1.5mV @ 100MHz
 - <6mV @ 250MHz
 - <6mV @ 1GHz
 - <100mV @ 2.4GHz

Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter.

Elenco Quad Power Supply Model XP-581



4 Fully Regulated DC Power Supplies in One Unit

- 4 DC voltages:**
- 3 fixed: +5V @ 3A, +12V @ 1A, -12V @ 1A
 - 1 Variable: 2.5 - 20V @ 2A

\$85

B&K Frequency Counter Model BK-1875



**50Hz - 2.8GHz
3 Channels**

\$189

- Sensitivity:**
- <0.8mV @ 100MHz
 - <6mV @ 300MHz
 - <7mV @ 1GHz
 - <100mV @ 3GHz

Ultra sensitive synchronous detector bargraph and RF strength.

B&K Video Monitor Tester Model 1275



\$169

Great handheld unit to test PC and Mac monitors. The model 1275 is ideal for the field or the service bench. Small, portable and very effective, the 1275 generates crosshatch, dots, color bars and raster patterns in green, blue, red, black and white.

Soldering Station

Weller Low Cost Soldering Iron Model WLC-100




- Variable power control produces 5-40 watts.
- Ideal for hobbyists, DIYers and students.
- Complete with 40W iron.

\$34.95

Elenco Oscilloscopes

Free Dust Cover and 2 Probes

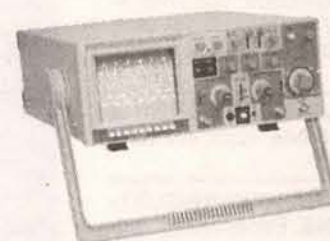

S-1325	25MHz	Dual Trace	\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz	Dual Trace	\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$749
S-1390	100MHz	Delayed Sweep	\$995

DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s Analog/Digital	\$695
DS-303	40MHz/20Ms/s Analog/Digital	\$995
DS-603	60MHz/20Ms/s Analog/Digital	\$1295

Tekk Radios

Pro-Sport FRS Two-Way Radio Model PRO-SPORT+

Talk up to
2 miles!

Available
in Yellow,
Blue & Black

No
License
Required

- 1/2 Watt Output, 14 Channels.
- TX & RX LED/LCD Indicators.
- Large LCD Display.
- 38 Privacy (CTCSS) Tones.
- Removeable Antenna.
- Water Resistant.
- 500mW Output.
- Palm Sized.



PRO SPORT Model
\$109.95 set of 2

\$69 each
or
\$125
Set of 2

PC Repair

A+ Certification Self-Study Course™

Model XK-305

\$379

DOS/WIN Exam
DOS 6.2
Windows 3.1 Installation and Configuration
Windows 3.1 Application Support
Windows 3.1 Devices and Drivers
Windows 3.1 Networking and Troubleshooting
Windows 95 Installation and Deployment
Windows 95 Basic Configuration
Windows 95 Troubleshooting and Optimization
Includes all the technical material, knowledge and interactive exercises needed to pass the A+ exams and excel in the competitive PC repair marketplace.

Introduction to PC Repair Self-Study Course™

Model XK-301

\$179

COURSE CONTENTS
Introduction to Computers
IBM PCs and Clones
PC Assembly/Disassembly
Introduction to MS-DOS
Introduction to Windows 3.1
Introduction to Windows 95
Introduction to Networks
Introduction to the Internet
Provides you with the easiest and most effective way to learn the fundamentals necessary for a profitable and successful career as a PC Repair Technician. Ideal for individuals new to the IT profession and as instruction prior to studying for A+ certification.

Elenco Technician Tool Kit Model TK-1500

\$49.95

28 tools plus a DMM contained in a large flexible tool case with a handle ideal for everyone on the go.



Elenco Educational Kits

Model AR-2N6K



**2 Meter / 6 Meter
Amateur Radio Kit**

\$34.95

Model AM-780K




**Two IC
Radio Kit**

\$11.95



**Model AK-700
Pulse/Tone
Telephone Kit**

\$15.95

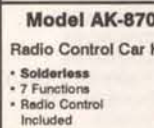

**Model AK-870
Radio Control Car Kit**

- Solderless
- 7 Functions
- Radio Control Included




\$24.95



**Model M-1005K
Digital Multimeter Kit**

\$19.95

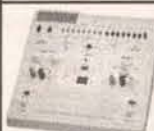

**Model XK-150
Digital / Analog
Trainer**

\$89.95

Guaranteed Lowest Prices

UPS SHIPPING: 48 STATES 5%
OTHERS CALL FOR DETAILS
IL Residents add 8.25% Sales Tax
SEE US ON THE WEB

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710
<http://www.cs-sales.com>



15 DAY MONEY BACK GUARANTEE

2 YEAR FACTORY WARRANTY

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

presented quite a spectacle to the neighbors.

I have since admonished my son for "playing" with the tubes (especially on bicycles) after pointing out some of the hazards he had let himself in for on that little escapade. But I did promise him we would do some higher level experimentation.

After I described the Tesla coil to him he has asked me about little else. Then I saw your article in *Nuts & Volts*, and I thought "perfect timing," perfect for halloween! At this rate, who knows what he will be cooking up in the garage by the time he is 15!

Greg Hultman, via Internet

Dear Nuts & Volts:

I happened to see the Sept. '99 issue in *Barns & Nobles* — the cover instantly caught my eye. I

love the article on the Tesla coil.

There were little bits of information in the article that I had not known. For example, the difference in connecting the grounds to the different coils.

I downloaded the software from the website at the end of the article, which was an added bonus. I like reading about exciting electronics stuff — Tesla coils, HV devices. I think I'm going to subscribe, thanks for a great, fun issue.

Joseph Gallo, via Internet

Dear Nuts & Volts:

Thanks for including the article on the Tesla coil. I would like to add a reminder that some neon sign transformers are internally grounded ... Beware of metal edges on tables, etc., in the area of the coil or Jacob's ladder when it is operating. They act as simple receivers and can provide a nasty shock, espe-

cially where the ends of the edge terminate. Sometimes, you can see a spark there as the edge resonates to the RF field. As an experiment, one could try to duplicate the work of Hertz with a simple loop receiver. It would be better to have such phenomena under "control" rather than as chance.

The Jacob's ladder can be made "hotter" by bridging the ladder with a high-voltage capacitor such as a Leyden jar. Unfortunately, this also causes the assembly to act as a spark gap transmitter with the wires of the ladder being the "aerial."

I have learned some of this from "the school of hard knocks." I have been extremely lucky ... There is really no reason for others to "re-invent the square wheel."

via Internet

Newsbytes

YEAR 2000 EDITION OF ANSWERS, RADIOSHACK'S NEW CATALOG

This edition of *ANSWERS* contains more pages and products than any RadioShack catalog in history. Inside you will find nearly 400 pages describing thousands of consumer electronics products available at more than 7,000 RadioShack stores and participating dealers across the US.

The catalog has been significantly expanded to include hundreds of unique and hard-to-find personal electronics products, parts, and components available through RadioShack Unlimited. This special order program gives customers access to more than 100,000 additional items not stocked in RadioShack stores.

While RadioShack has always been the store to turn to for much-needed items for the home or office, *ANSWERS* features some cool things you didn't even realize you needed — the kind of products that make life a little easier.

If you have questions about RadioShack or any of its products, please feel free to call Tony Magoulas, RadioShack Media Relations Manager at 817-415-4852.

MICROCHIP TECHNOLOGY RELEASES 1999 TECHNICAL LIBRARY CD-ROM

Microchip Technology, Inc., introduces the new 1999 *Technical Library CD-ROM*, a complete selection of technical documentation on Microchip's PICmicro® eight-bit microcontrollers and associated development tools; non-volatile memory devices; secure data products; and related microperipheral products including RFID, analog, and system supervisor ICs. The CD-ROM replicates the popular Microchip web site (www.microchip.com), and can be viewed via an HTML browser.

The 1999 *Technical Library CD-ROM* provides an extensive collection of Microchip product specifications, application notes and related source codes, development systems, and software support for embedded control applications, programming specifications, user's guides, and more.

The CD-ROM contains the most current release of Microchip's popular MPLAB™ Integrated Development Environment Software, which gives users the flexibility to edit, compile, emulate, and program PICmicro MCU devices all from a single user interface.

To request a free copy of the 1999 *Technical Library CD-ROM*, contact any authorized Microchip distributor or call Microchip's literature line at 480-786-7668.


A DEGREE ON A DISK!

Electro Science Applications Inc.

EM FORMULARY

File Formulas Conversions Data Search Tables Windows Help

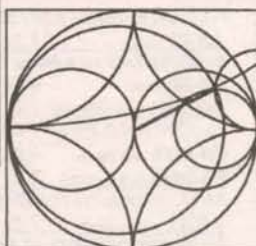smith chart
smith chart
snells law
solar array area
solenoid B
solenoid inductance
solid angle
space charge current
space loss
specific absorption rate
specific impulse
sphere capacitance



- 500+ formulas and simulations
- Unit conversions and data tables
- Physical constants
- Electronics, communications, radar
- Antennas, filters, optics
- Physics, math, space science
- Practical and educational

Self-contained and intuitive, you'll be up and running in minutes. Fast menu and hyper-linked access to equations and data. Current version 1.7 works with Windows 3.1, 95, or 98.

ELECTRO SCIENCE APPLICATIONS, INC.
P.O. BOX 11158, TORRANCE, CA 90510

To order, call (310) 539-2422 or E-Mail esa@earthlink.net.
Send \$29.95 check or money order (CA residents add 8.25% sales tax).
Foreign orders add appropriate shipping charge.

Electronic and RF design services also available.
Visit us at <http://www.esap.com>

Write in 211 on Reader Service Card.

Weeder Technologies

ON-LINE CATALOG

www.weedtech.com

Pro-Kit

PO Box 2426, Ft. Walton Beach, FL 32549

Voice/Fax 850-863-5723

Stackable RS-232 Kits

Digital I/O - 12 I/O pins individually configurable for input or output. DIP switch addressable; stack up to 16 modules on same port for 192 I/O points. Turn on/off relays. Sense switch transitions, button presses, 4x4 matrix decoding using auto-debounce and repeat. **\$32**

Analog Input - 8 input pins. 12-bit plus sign self-calibrating ADC. Returns results in 1mV steps from 0 to 4095. Software programmable alarm trip-points for each input. DIP switch addressable; stack up to 16 modules on same port for 128 single-ended or 64 differential inputs. **\$49**

Home Automation (X-10) - Connects between a TW523 and your serial port. Receive/transmit all X-10 commands with your home-brewed programs. Full collision detection with auto re-transmission. **\$39**

Caller ID - Decodes the caller ID data and sends it to your serial port in a pre-formatted ASCII character string. Example: "12/31 08:45 850-863-5723 Weeder, Terry <CR>". Keep a log of all incoming calls. Block out unwanted callers to your BBS or other modem applications. **\$35**

Touch-Tone Input - Decodes DTMF tones and sends them to your serial port. Keep a log of all outgoing calls. Use with the Caller ID kit for a complete in/out logging system. Send commands to the Home Automation and/or Digital I/O kits using a remote telephone. **\$34**

IR Remote Control Receiver

Learns and responds to the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. 7 individual output pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action. **\$32**

Telephone Call Restrictors

Two modes of operation; either prevent receiving or placing telephone calls (or call prefixes) which have been entered into memory, or prevent those calls (or call prefixes) which have "not" been entered into memory. Use touch-tone phone to program.
Block out selected outgoing calls. Bypass at any time using your password. **\$35**
Block out selected incoming calls. Calls identified using Caller ID data. **\$46**

Phone Line Transponder

7 individual output pins are controlled with buttons 1-7 on your touch-tone phone. Automatically answers telephone and waits for commands. Monitor room noises with built in mic. "Dial-Out" pin instructs unit to pick up phone and dial user entered number(s). Password protected. **\$49**


DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Decodes all touch-tones and displays them on a 16 character LCD. Holds the last 240 digits in non-volatile memory. Connect directly to radio receiver's speaker terminals for off-air decoding of repeater codes, or numbers dialed on a radio program. **\$55**

Write in 210 on Reader Service Card.

STAMP APPLICATIONS

by Lon Glazner

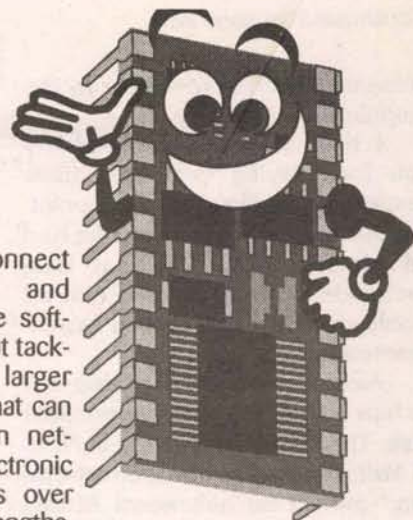

Putting the Spotlight on BASIC Stamp Projects, Hints, and Tips

A Multi-Drop Stamp-Based Network

There's been a lot of talk these last few years about the Internet and the creation of an information super-highway here in America. With all of the attention paid to the phenomena of the world wide web, I thought it was high time to bring the BASIC Stamp into this arena of networked electronics.

Overview

Think of STAMP Net as your very own information super-"dirt road." Okay, so it's not as cool or revolutionary as the Internet. You won't be able to exchange jokes with your co-workers when you're supposed to be slaving away for the boss. In fact, it'll be pretty slow and somewhat application specific. But for those of you who have considered automating your house with BASIC Stamps, or centralizing the control of some manufacturing equipment, STAMP Net should get you on your way.

The STAMP Net design consists of both the hardware communication architecture, as well as a software communication protocol required to connect a group of BASIC Stamp2 SXs (BS2-SX) together over an RS-485 network.

Defining the Design

We have a unique opportunity with this design. Typical engineering revolves around problem solving. Parts are selected, and software is written to solve a specific problem with time-to-develop and system cost being considered. STAMP Net is not such a design. Instead, it could be considered a design looking for an application. It could be used as a greenhouse monitoring system, a home lighting control network, or maybe as the backbone of a workshop alarm. We simply have to develop a multiple BS2-SX network, and a generic communication protocol, both of which should be flexible enough to fit a myriad of applications.

My choice for the hardware is the relatively simple RS-485 electrical specification (the actual specification is TIA/EIA-485-A). This specification allows multiple receivers and transmitters (commonly referred to as drivers) on the same communication bus. Our system will be half-duplex (only one device transmitting at a time), and will operate using a Master-Multiple Slave protocol (a single Master unit will initiate all communication to multiple Slaves on the RS-485 bus).

Notice that I stated previously that RS-485 was relatively simple. With short distances and low speeds, the industry standard RS-485 transceivers (both a transmitter and receiver) function well without much in the way of impedance matching or transmission line effects. For this article, the RS-485 network will be only a few inches in length so that we can concentrate on the communication protocol. Next month, we'll extend the number of BS2-SXs on the network and lengthen the cables, which may bring into play a host of gremlins.


Figure 1 displays a very simplified RS-485 network in block diagram format. This is pretty much what we'll have hooked up at the end of this part of the design. Again, the main reason for this is so that

we can connect the parts and write a little software without tackling the larger problems that can occur when networking electronic components over long cable lengths.

The Nuts and Bolts of RS-485

RS-485 is often called a "differential-pair" multidrop network. The "differential-pair" refers to the fact that the inputs to an RS-485 receiver consist of a pair of inputs (input A and input B), and the receiver is designed to respond to voltage differences between the two inputs. Using a differential pair for detecting voltage threshold changes can significantly reduce noise effects in a system like this. The multidrop moniker refers to multiple devices residing on the network.

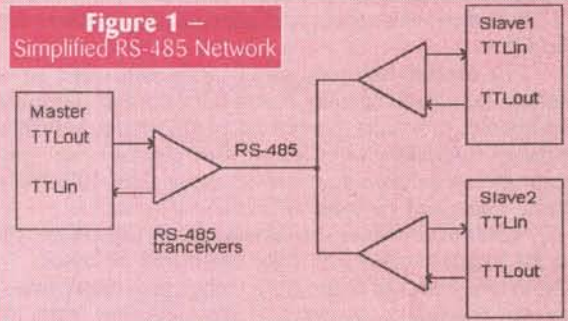RS-485 networks have been used across distances as great as 5,000 feet. The longer the distance your RS-485 network traverses, the greater your problems become with regards to noise, ground return losses, transmission line reflections,



Byte	Number	Description
Address	1	Address of unit message is intended for
Program	2	Program to be executed by receiving unit
Data 1	3	General purpose data byte
Data 2	4	General purpose data byte
Data 3	5	General purpose data byte
Data 4	6	General purpose data byte
Data 5	7	General purpose data byte
Checksum	8	Sum of all bytes in message

Table 1: Command and Response String Definition

Electro Mavin

Great Buys - Great Products - Great Gadgets
Check Out Our Great WebSite at

<http://mavin.com>

For Computer Items, Hobbist Projects,
Microwave Goodies and Some of the
Greatest Prices on the Web....

800-421-2442 or FAX 310-632-3557

E-Mail

john@mavin.com or mark@mavin.com

Mr. NiCd

NOVEMBER 1999 SUPER SPECIALS!

THE BEST BATTERIES IN AMERICA!

Packs & Charger for YAESU FT-50R / 40R / 10R:

FNB-40xh 5w-NiMH 7.2v 650mAh \$41.95
FNB-47xh (NIMH) 7.2v 1800mAh \$49.95
FNB-41xh (5w NiMH) 9.6v 1000mAh \$49.95

For YAESU FT-51R / 41R / 11R:

FNB-38 pack (5w) 9.6v 700mAh \$39.95

For YAESU FT-530 / 416 / 816 / 76 / 26:

FNB-26 pack (NIMH) 7.2v 1500mAh \$32.95
FNB-27s (5w NiMH) 12.0v 1000mAh \$45.95

For YAESU FT-411 / 470 / 73 / 33 / 23:

FNB-11 pack (5w) 12.0v 600mAh \$24.95
FBA-10 6-Cell AA case \$14.95

Packs for ALINCO DJ-580 / 582 / 180 radios:

EBP-20ns pack 7.2v 1500mAh \$29.95
EBP-22nh pk (5w) 12.0v 1000mAh \$36.95
EDH-11 6-Cell AA case \$14.95

For ICOM IC-21A / T22-42A / W31- 32A / T7A:

BP-180xh pk (NIMH) 7.2v 1000mAh \$39.95
BP-173 pack (5w) 9.6v 700mAh \$49.95

For ICOM IC-W21A / 2GXAT / V21AT: (Black or Gray)

BP-132s (5w NiMH) 12.0v 1500mAh \$49.95

For ICOM IC-2SAT / W2A / 3SAT / 4SAT etc:

BP-83 pack 7.2v 600mAh \$23.95

For ICOM 02AT etc & Radio Shack HTX-202 / 404:

BP-8h pack 8.4v 1400mAh \$32.95

BP-202s pack (HTX-202) 7.2v 1400mAh \$29.95

For KENWOOD TH-79A / 42A / 22A:

PB-32xh pack (NIMH) 6.0v 1000mAh \$29.95

PB-34xh pack (5w NiMH) 9.6v 1000mAh \$39.95

For KENWOOD TH-78 / 48 / 28 / 27:

PB-13 (original size) 7.2v 700mAh \$26.95

For KENWOOD TH-77, 75, 55, 46, 45, 26, 25:

PB-6X (NIMH, w/chg plug) 7.2v 1200mAh \$34.95

Mail, phone, & Fax orders welcome! Pay with
Mastercard / VISA / DISCOVER / American Express

Call 608-831-3443 / Fax 608-831-1082

Mr. NiCd - E. H. Yost & Company

2211-D Parview Road, Middleton, WI 53562

CALL OR WRITE FOR OUR FREE CATALOG!

Cellular / Laptop / Videocam / Commercial & Aviation packs tool

E-mail: ehyost@midplains.net

STAMP APPLICATIONS

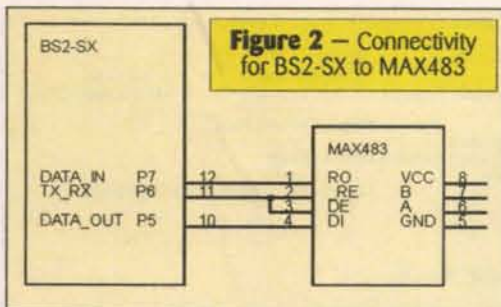


Figure 2 - Connectivity for BS2-SX to MAX483

and reduced data rates. At long distances this relatively simple network can become a significant engineering design. So try not to get too carried away with STAMP Net unless you've got some troubleshooting time on

your hands.

RS-485 is an electrical specification and not a communication protocol. In other words, RS-485 is defined by how its receivers and transmitters interact electrically, and what voltage levels and current loads they can operate within. How data is sent on an RS-485 network is, to a large degree, left up to the network designer. Of course, data rates are limited by the hardware used in an RS-485 design, which may affect aspects of any communication protocol.

There are a large variety of RS-485 transceivers on the market. Some provide physical isolation for your communication system, others are lower cost, very simple transceivers. I'm partial to the use of MAXIM Integrated Products, Inc., parts. They have a solid sample policy, which can be beneficial for some of the penny-pinching hobbyists out in Stamp land. I've also had success with their parts in the past. For these reasons, I'm selecting the low-cost MAX483 RS-485 low power transceiver for this design.

The MAX483 does not provide electrical isolation for this RS-485 network. Therefore, all circuit grounds are common, and should be connected via a conductive ground wire that runs the length of the network with the communication pair (A and B inputs/outputs). On the BS2-SX side, the MAX483 is interfaced via three wires. The first two are the receiver output (RO) which sends data to the BS2-SX from the RS-485 network and the data input (DI) which receives data from the BS2-SX and places it on the RS-485 network bus. The last connection is the receiver enable (asserted with a logic low) and driver enable (asserted with logic high) pins which can be tied together and connected to a single BS2-SX output. This last connection allows the BS2-SX to select the state of the RS-485 transceiver. Figure 2 is representative of this connectivity.

In STAMP Net, the Master unit will generally place its MAX483 in driver mode (TX_RX high), while all of the Slaves will remain in receive mode (TX_RX low), unless a command from the Master requires a response from one of the Slaves.

What's a Communication Protocol?

In today's world of high-speed telecommunication and cellular technology, I feel pretty silly describing what a communication protocol is. But I constantly hear engineers referring to electrical specifications as communication protocols. For instance, I've often heard the term RS-232 (which denotes voltage levels, as well as driver and receiver specifications in the same manner as RS-485) used to describe serial communication. When in actuality it only describes the

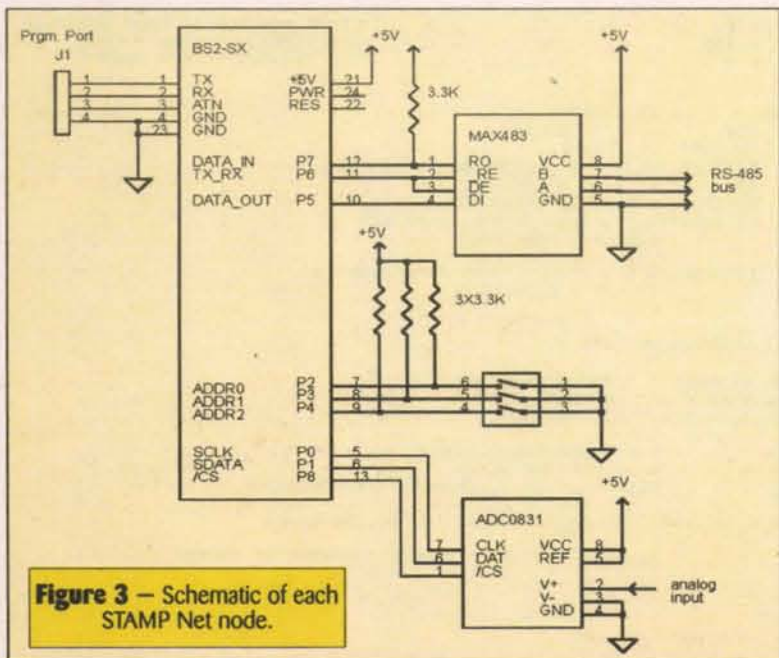


Figure 3 - Schematic of each STAMP Net node.

```

*****
'Master Program
'The Master program controls communication and data display. For a
'unit designated as a Master unit (address = 0) this program is
'used to poll the various slave units. If a unit is a Slave unit
'(address <> 0) then this program is where the unit waits for
'commands.
'($STAMP BS2SX,C:\Parallax\Analog.bsx)
'0:Master_Prgm.bsx

'I/O pin designations
AD_Clk CON 0
AD_Dat CON 1
AD_CS CON 8

'ADC0831 clock pin
'ADC0831 data pin
'ADC0831 chip select(asserted low)

'Communication Constants
Data_Out CON 5
TX_RX CON 6
Data_In CON 7
Baud CON 45

'TTL data out pin
'Receive enable(asserted low)
'TTL data in pin
'38.4kbps, 8N1 true data

'Internally used registers
Addr var byte
Comm_Flag var byte
Mstr var byte
S1 var byte
S2 var byte
S3 var byte
S4 var byte
S5 var byte
S6 var byte
S7 var byte

'Address of unit
'flag bits for unit
'Set for Master unit cleared for Slave
'Set if Slave # 1 is present on RS-485 bus
'Set if Slave # 2 is present on RS-485 bus
'Set if Slave # 3 is present on RS-485 bus
'Set if Slave # 4 is present on RS-485 bus
'Set if Slave # 5 is present on RS-485 bus
'Set if Slave # 6 is present on RS-485 bus
'Set if Slave # 7 is present on RS-485 bus

'Communication message string variables bytes(8 total)
Addr_Req var byte
Prgm_Req var byte
Dat1 var byte
Dat2 var byte
Dat3 var byte
Dat4 var byte
Dat5 var byte
Checksum var byte

'Unit address of message destination
'Request execution of this program
'Data byte 1
'Data byte 2
'Data byte 3
'Data byte 4
'Data byte 5
'Sum of previous bytes

'Storage Registers
Put_Addr var byte
Get_Addr var byte

'Put address location
'Get address location

'Working registers
Loop1 var byte
Work1 var byte
Work2 var byte
Work3 var byte
Work4 var byte
WorkBig var word

'For...Next variable
'General purpose register
'General purpose register
'General purpose register
'General purpose register
'Word sized general purpose register

'A/D registers
ResultA_D var byte
MaxA_D var byte
MinA_D var byte
AvgA_D var byte

'Result of A to D measurement
'Storage for maximum A to D result
'Storage for minimum A to D result
'Storage for avg. A to D result

*****
Main_Program:
Outs = %0000000100100000
Dirs = %0000000101100011

'Set output pin values
'Set pin direction values

Get_Address:
Comm_Flag = %00000000
Addr = (INL&%0011100)/4
If Addr <> 0 then No_Master
Mstr = 1

'Get unit address from P4-2

No_Master:
Pause 2000

'Addr and Comm Flag register Debug statements
'Debug "Address = ", BIN8 Addr,CR
'Debug "Comm Flag = ", BIN8 Comm_Flag,CR
'Pause 1000

If Mstr = 1 then Master_Program
Goto Slave_Program

*****
Master_Program:
For Addr_Req = 1 to 7
Pause 1000
Prgm_Req = 1
Checksum = Addr_Req+Prgm_Req+Dat1+Dat2+Dat3+Dat4+Dat5
Data_Out = HIGH
TX_RX = HIGH
Data_Out, Baud, [Addr_Req,Prgm_Req,Dat1,Dat2,Dat3,Dat4,
Dat5,Checksum]
PAUSE 1
TX_RX = LOW
Data_In, Baud, 500, No_Data, [Work1,Work2,Dat1,Dat2,Dat3,Dat4,
Dat5,Checksum]
'Enable receiver on RS-485

Work4 = Work1+Work2+Dat1+Dat2+Dat3+Dat4+Dat5
If Work4 <> Checksum Then Bad_Data

Work3 = %00000001
Work3 = Work3 << Addr_Req
Comm_Flag = Comm_Flag+Work3

'Set flag for unit that responds
'Set up pointer bit
'Rotate "1" into Slave location
'Add pointer bit to designate active

Slave
'Display incoming data
Debug "Address of Sender = ",DEC Addr_Req,CR
Debug "Data byte 1 = ",DEC Dat1,CR
Debug "Data byte 2 = ",DEC Dat2,CR
Debug "Data byte 3 = ",DEC Dat3,CR
Debug "Data byte 4 = ",DEC Dat4,CR
Debug "Data byte 5 = ",DEC Dat5,CR

Send_Next_Addr:
Next
Goto Done_Polling

Bad_Data:
Debug "Checksum Invalid Addr: ",DEC Addr_Req,cr
Goto Send_Next_Addr

No_Data:
Debug "No Data Returned Addr: ",DEC Addr_Req,cr
Goto Send_Next_Addr

Done_Polling:
Debug "Comm_Flag = ", BIN8 Comm_Flag,CR
Pause 3000
Goto Get_Address
    
```


RESOURCES

For more information on the BASIC Stamp, contact:

Parallax, Inc.

3805 Atherton Road, #102
Rocklin, CA 95765
phone (916) 624-8333
<http://www.parallaxinc.com>

Scott Edwards Electronics, Inc.

1939 S. Frontage Rd. Ste. F
Sierra Vista, AZ 85635
phone 520-459-4802
fax 520-459-0623
www.seetron.com info@seetron.com

Solutions Cubed

Lon Glazner
3029 Esplanade Suite F
Chico, CA 95973
E-Mail: lon@solutions-cubed.com
www.solutions-cubed.com
Phone: 530-891-8045
Fax: 530-891-1643

electrical requirements of a specific communication network or bus.

A communication protocol describes the manner in which data is exchanged. The electrical specification or drivers used to connect the data generators may be part of the protocol, but they do not define it. There are certain hardware and timing issues, as well as software issues that define a communication protocol.

From a hardware standpoint, we can describe STAMP Net as an RS-485 based multi-drop network. This will be a Master-Slave system with no more than one Master and no more than seven Slaves (this number could be greatly expanded, but we'll keep it small for now). Communication will be serial in nature, and will meet the format of eight data bits, no parity, and one stop bit, with true polarity (8N1,

with the start-bit defined by a logic "0" at the BS2-SX input). The data rate will be fixed at 38.4kbps. We'll be making use of the SERIN and SEROUT commands to perform the byte-by-byte transmission and reception of data.

The Master-Slave configuration is by far the easiest to implement. In this configuration, only a Master unit can initiate communication. In order for each Slave to report its current status, the Master would have to "poll" each existing unit. In a large network, this can prevent the Master-Slave concept from working. It would also be inappropriate to use a Master-Slave system if your Slave units are reporting time-critical information, such as failure conditions. But for something like a greenhouse monitor or a smaller network such as the one being designed here, the Master-Slave concept works well.

No communication protocol would be complete without a discussion of message types. Again, we're going to take the easy road, and limit the number of message types in our system to two. They will be the Master initiated Command and the Slave return of the Response. Each message will consist of eight bytes.

The software for the Master and Slave units will be identical in this design. In fact, the only difference between the Master and Slave units will be the address of the units. A unit with an address of "0" will default to the Master unit. Any other address (1 through 7) will default to a Slave. A Slave will always wait for communication and send its Response string to address "0." The Master, on the other hand, will poll units 1 through 7, and display their responses.

Next month, we'll add a little more functionality and a PC interface for the Master unit.

The Hardware

Since our Master and Slave units are going to be identical in software, we may as well make them identical in hardware. The addressing will be set with a three-position DIP switch. The RS-485 transceiver will be interfaced to as described by Figure 2, which will require an additional three I/O lines. Finally, I'm going to add an eight-bit analog-to-digital (A/D) converter, with a serial-peripheral-interface (SPI) which will require three more I/O lines. A schematic of this configuration is displayed in Figure 3.

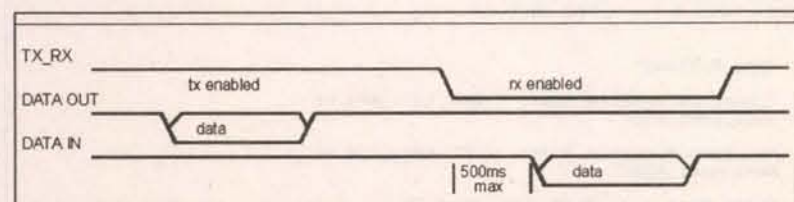


Figure 4 — Software Response Timing Requirement

```

Slave_Program:
  Debug   *Slave Program *.CR
  LOW     TX_RX
  SERIN   Data_In,Baud,[Addr_Req,Prgm_Req,Dat1,Dat2,Dat3,Dat4,Dat5,Checksum]

  If Addr_Req <> Addr Then Bad_Address
  Work4 = Addr_Req+Prgm_Req+Dat1+Dat2+Dat3+Dat4+Dat5
  If Work4 <> Checksum Then Bad_Sum
  RUN     Prgm_Req

Bad_Sum:
  Debug   *Checksum Invalid: *.cr
  Goto    Slave_Program

Bad_Address:
  Debug   *Wrong Address: *.DEC Addr_Req.cr
  Goto    Slave_Program

END
  
```

Code Listing 1: Master_Prgm.bsx

```

'Analog.bsx
'This is program 1 for the STAMP Net design. If this program
'is requested then 128 analog measurements are taken with the
'ADC0831 analog to digital converter. The maximum, minimum,
'and average result are returned to the Master unit.

'I/O pin designations
AD_Clk   CON    0      'ADC0831 clock pin
AD_Dat   CON    1      'ADC0831 data pin
AD_CS    CON    8      'ADC0831 chip select(asserted low)
AD_Samples CON 128     'Number of samples taken

'Communication Constants
Data_Out CON    5      'TTL data out pin
TX_RX    CON    6      'Receive enable(asserted low)
Data_In  CON    7      'TTL data in pin
Baud     CON    45     '38.4kbps, 8N1 true data

'Internally used registers
Addr     var    byte    'Address of unit
Comm_Flag var    byte    'flag bits for unit
Mstr     var    Comm_Flag.bit0 'Set for Master unit cleared for Slave
S1       var    Comm_Flag.bit1 'Set if Slave # 1 is present on RS-485 bus
S2       var    Comm_Flag.bit2 'Set if Slave # 2 is present on RS-485 bus
S3       var    Comm_Flag.bit3 'Set if Slave # 3 is present on RS-485 bus
S4       var    Comm_Flag.bit4 'Set if Slave # 4 is present on RS-485 bus
S5       var    Comm_Flag.bit5 'Set if Slave # 5 is present on RS-485 bus
S6       var    Comm_Flag.bit6 'Set if Slave # 6 is present on RS-485 bus
S7       var    Comm_Flag.bit7 'Set if Slave # 7 is present on RS-485 bus

'Communication message string variables bytes(8 total)
Addr_Req var    byte    'Unit address of message destination
Prgm_Req var    byte    'Request execution of this program
Dat1     var    byte    'Data byte 1
Dat2     var    byte    'Data byte 2
Dat3     var    byte    'Data byte 3
Dat4     var    byte    'Data byte 4
Dat5     var    byte    'Data byte 5
Checksum var    byte    'Sum of previous bytes

'Storage Registers
Put_Addr var    byte    'Put address location
Get_Addr var    byte    'Get address location

'Working registers
Loop1    var    byte    'For...Next variable
Work1    var    byte    'General purpose register
Work2    var    byte    'General purpose register
Work3    var    byte    'General purpose register
Work4    var    byte    'General purpose register
WorkBig  var    word    'Word sized general purpose register

'A/D registers
ResultA_D var    byte    'Result of A to D measurement
MaxA_D   var    byte    'Storage for maximum A to D result
MinA_D   var    byte    'Storage for minimum A to D result
AvgA_D   var    byte    'Storage for avg. A to D result
Num_Meas var    byte    'Storage for number of samples taken

*****
Main_Program:

Comm_Flag = %00000000
Outs      = %0000000100100000
Dirs      = %0000000101100011

'Set output pin values
'Set pin direction values

Get_Address:
Addr = (INL&%0011100)/4
'Get unit address from P4-2

WorkBig = 0
MinA_D = 255
MaxA_D = 0
'Clear average storage register
'Set minimum to max output
'Set maximum to min output

Measure_Analog:
For Loop1 = 1 to AD_Samples
  LOW     AD_CS
  PULSOUT AD_Clk,10
  SHIFTLN AD_Dat,AD_Clk,msbpost,[ResultA_D]
  HIGH    AD_CS
  WorkBig = WorkBig + ResultA_D
  If ResultA_D < MaxA_D Then Test_Min
  MaxA_D = ResultA_D

Test_Min:
  If ResultA_D > MinA_D Then Keep_Sampling
  MinA_D = ResultA_D

Keep_Sampling:
Next
AvgA_D = WorkBig/AD_Samples

'Debug *Average Storage = *.DEC WorkBig.cr
'Debug *Minimum A to D = *.DEC MinA_D.cr
'Debug *Maximum A to D = *.DEC MaxA_D.cr

Checksum = MaxA_D+MinA_D+AvgA_D
HIGH     Data_Out 'Set output high
HIGH     TX_RX    'Enable transmission on RS-485
SEROUT   Data_Out,[ $00,$00,MaxA_D,MinA_D,AvgA_D,$00,$00,Checksum]
PAUSE    1
LOW      TX_RX    'Enable receiver on RS-485

RUN      0
'Return to main program

END
  
```

Code Listing 2: Analog.bsx

STAMP APPLICATIONS

The Software

The software here is broken down into two main programs. These programs are basically the starting points for developing a versatile Stamp-to-Stamp communication interface.

The main program (Master_Prgm.bsx) begins by determining the address of the unit. If its address is a "0," then the Stamp defaults to a Master and begins polling for other units on the network. Any responses are displayed via a Debug command for this program. Additionally, the communication flag register (Comm_Flag) stores bits, which indicate which STAMP Net nodes are responding. This flag register would be an easy-to-use status register indicating any units that may be having communication problems on your network.

For Slaves, Master_Prgm.bsx is used to wait for commands from the Master unit. When a command is received, it is tested for a matching address and for a correct checksum. The address requirement is necessary for any BS2-SX to ignore commands to other BS2-SXs on the network. The checksum requirement allows BS2-SX slaves to ignore any corrupted data that they may be receiving. A Slave will always respond with a "0" for both the Address and Program bytes of a response string (see Table 1).

Notice that by selecting a set number of bytes for all commands and responses, I have made it easier to distinguish between commands from a Master and responses from other Slaves. And both can be processed and discarded, if need be, by the same software routine.

The second program (Analog.bsx) is the first of a set of network functional programs. This program interfaces to an ADC0831 eight-bit analog-to-digital converter; 128 samples are taken when this program is executed, and the maximum, minimum, and average measurements are returned via the RS-485 bus. This program is also responsible for responding to the Master unit.

Some communication protocol timing issues must be addressed by both pieces of software. You need to make sure that no two Stamps on the network are ever trying to transmit at the same time. For Analog.bsx, this is not a great concern. It takes long enough for the Slave BS2-SX to take all of its measurements (128 total) that the Master will be in receive mode prior to any data being sent out of the Slave executing Analog.bsx.

The time allowed for a Slave to respond to a Master unit's command is 500ms. This timing is excessive and could be reduced based on the

time required for the commands issued to be processed. But this early in the game, I decided to place no major time constraints on the Master-Slave interface. A diagram of what you would see at the interface between a Master unit and the MAX483 is displayed in Figure 4.

In Closing

The STAMP Net design is by no

means complete. The RS-485 interface must be tested over actual cables, and more program functions need to be added to the interface. But you can start to see the bare bones of a BS2-SX network beginning to take shape.

Next month, we'll extend out the cables to test our RS-485 network and add a little more functionality to the design. And, if time permits, we'll add a PC interface to the Master side


of the software.

I can already tell that the additional program memory available in the BS2-SX will lend itself to a much more complex system than would be possible with the sturdy BASIC Stamp 2. And while it's unlikely that I'll fully utilize the capabilities of the BS2-SX in the STAMP Net design, I'm sure there's a few Stamp enthusiasts out there that are up to the challenge. **NV**


Electronics made easy & affordable **velleman**

NEW PERSONALSCOPE™ HPS5


The Velleman **PERSONAL SCOPE™** is a portable fully-functional oscilloscope. At the cost of a good multimeter it gives you the best possible value for the money. The **PERSONAL SCOPE™** provides you with the **high sensitivity** (down to 5mV/div) often missing in higher or similarly priced units. Together with the other scope functions it makes this the ideal tool for students, hobbyists and professionals.

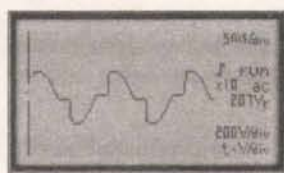


AC MAINS (e.g. phase control)

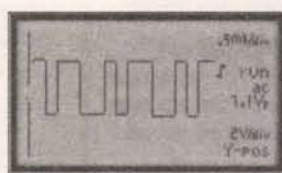

DIGITAL SIGNALS (e.g. pulse train)

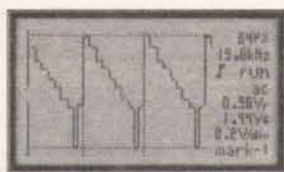

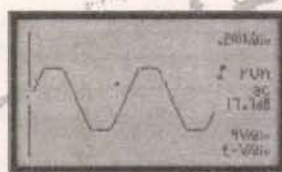TV AND VIDEO (e.g. composite video signal)



AUDIO SIGNALS (e.g. amplifier output clipping level)

SPECIFICATIONS:

- Maximum sample rate: 5MHz
- Input amplifier bandwidth: 1MHz (-3dB at 1V/div setting) 1Mohm // 20pF (standard probe)
- Vertical resolution: 8 bit (6 bit on LCD)
- LCD Graphics: 64 x 128 pixels
- dBm measurements: From -73dB tot +40dB (up to 60dB with X10 probe) ±0.5dB
- True rms AC measurement: 0.1mV to 80V (400Vrms with X10 probe) 2.5% accuracy
- Time base: 20s to 2µs / div in 22 steps
- Input sensitivity range: 5mV to 20V/div in 12 steps (up to 200V/div with X10 probe)
- Supply voltage: 9VDC / min 300mA adapter
- Batteries (in option): Alkaline type AA (5 pcs required) NiCd/NiMH rechargeable
- Battery life: Up to 20 hours with Alkaline batteries
- Safety: Meets IEC1010-1 600V CATII, pollution degree 1
- Dimensions: 105 x 220 x 35mm (4.13 x 7.95 x 1.38")
- Weight: 395g (14oz.) (excl. batteries)



OPTIONS:


- Insulated measurement probe x1 / x10: PROBE605
- Adapter for 110VAC: PS905USA

\$199.95

Probe not included



SERVICE & DEVELOPMENT

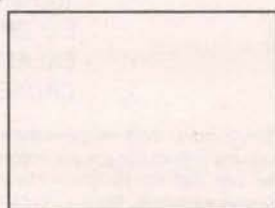

CAR DIAGNOSTICS



AUDIO TROUBLE SHOOTING

velleman

7415 Whitehall Street Suite 117
Fort Worth, TX 76118
(817) 284-7785 F: (817) 284-7712
www.velleman-kit.com email: velleman@earthlink.net


Questions ? Contact us for a list of US distributors or to get your **FREE** catalogue

Write in 37 on Reader Service Card.

AMATEUR ROBOTICS

NOTEBOOK


by Robert Nansel

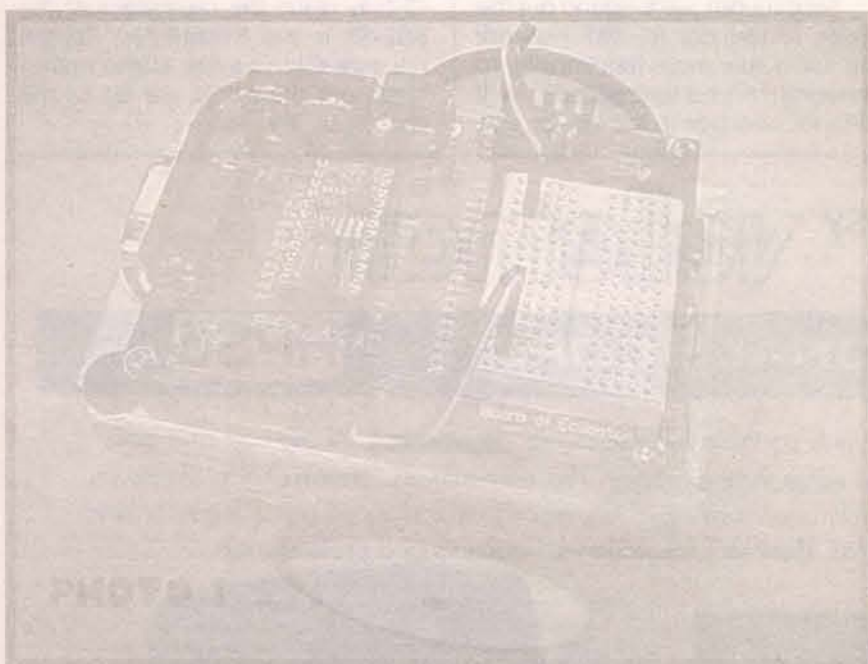

Last month, I presented PIC assembly code for a crude software-only I2C master. The code was to generate SDA and SCL waveforms that comply with the I2C specification for the purpose of developing and testing a software-only slave. Along the way, I showed how to use the START/STOP detector circuit (Sept. '99) for triggering a 'scope to get a stable display of the I2C waveforms.

The code sure wasn't pretty, but

it worked — mostly. In fact, the master code presented was brain-dead in a number of ways: It didn't pay attention to ACK pulses, bit arbitration, or clock stretching, and it assumed it alone controlled the I2C bus. Some stub functionality of clock stretching and bit arbitration were there, but commented out for later testing. Nevertheless, it did give me a simple, easily-modified I2C signal generator, which was all I really needed to get going on this iterative

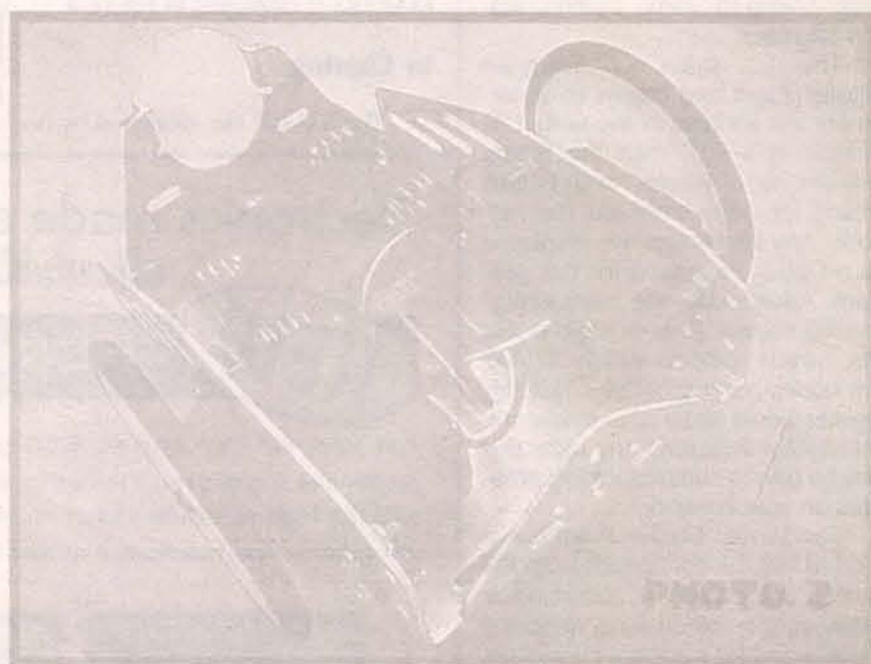

design process.

This time, I'll look at bit-level routines for an I2C slave. I'll also do mini reviews for two new robot kits, and say a few words about the loneliness of the Long-Distance Robot Builder.

Tweak the Master

Only minimal modifications need to be made to the code from last month for it to play nice with a slave. I'll just show the segment that contains

most of the changes (Listing 1), and outline what changes I made elsewhere. If anyone needs to get their hands on the full code, drop me a line.

Last time, the master simulated writing to I2C address 0111000. Combined with the write bit, the first byte transmitted after START was 01110000. The next byte was arbitrarily chosen to be 10110101.

Okay, the master must allow the slave to place data on SDA at the appropriate times. I wanted to test both reading and writing data to a slave; the address field works fine as a write, and the read can be the next byte in the datagram.

The I2C bus uses open-drain mode, so any time a one is output, it's the same as putting the line in a high-impedance state. Because of this, all the master has to do to allow the slave to place data on the bus is to send a second byte of all ones. The master still believes it is in sole control of SDA, but this change forces it to get out of the way so the slave can transmit data.

Notice in Listing 1 that I also changed the R/W bit to be a one instead of a zero. This reflects that this is to be a read operation. Thus, the whole datagram sent by the master is: S01110001A11111111AP, (where S, A, and P represent START, ACK, and STOP).

Since the master ignores everything the slave does, the value of R/W doesn't make any difference. Indeed, the slave code ignores R/W. I changed it all the same to make the datagram consistent with the I2C spec. During early testing, though, my choice had an interesting consequence (more on that later).

REMOTE CONTROL TV A/B SWITCH

SHOWDOWN



VS.



- HAS SEPARATE REMOTE FOR A/B
- MUST PLUG INTO AN A.C. OUTLET
- HAS EASILY DAMAGED R.F. RELAY
- A TO B ISOLATION IS MARGINAL
- POOR R.F. SHIELDING, CAN CAUSE DIAGONAL LINES IN TV PICTURE

- CONTROLLED BY EXISTING TV REMOTES
- NO A.C., RUNS A FULL YEAR ON 2 "AA"s
- 100% SOLID STATE, NOTHING TO BREAK
- EXCEPTIONALLY HIGH A TO B ISOLATION
- EXCELLENT R.F. SHIELDING, WILL NOT CAUSE INTERFERENCE IN TV PICTURE

QuikSwitch blows away the competition, both in quality and convenience! With its patented infrared receiver, QuikSwitch gives virtually any TV/VCR/CABLE/SAT remote the power to switch between A & B video sources! Switching is accomplished simply by holding down any button on any infrared remote for 2 seconds. A button such as "0" or "STOP" is used, one that will be ignored by the TV/VCR/etc. QuikSwitch has bright red & green A/B indicators, and runs for a full year on 2 "AA" alkaline batteries (not included). No A.C. outlet needed! What's more, QuikSwitch is a top quality R.F. device, with exceptional immunity to crosstalk and signal leakage. Why would you buy any other A/B switch? Order your QuikSwitch now and save!

QUIKSWITCH \$19.95 3-\$50 SPECIAL! 10-\$140

Shipping Charges Additional - 30 Day Money Back Guarantee - One Year Warranty

MILESTONE PRODUCTS

1-800-831-0184




```

** Test datagram write
entry:
-exit:

```

Listing 1

```

test1: call    i2c_init
test2: call    i2c_wait      ; Wait for bus free condition
      call    start        ; Create START condition
      movlw   0x71         ; Set to read from addr 0111000b
      movwf   i2c_out
      call    put_byte      ; Send the address + R/W flag
      call    get_ack
      movlw   0xFF         ; Set up data 11111111b
                          ; This is to test slave

      movwf   i2c_out
      call    put_byte      ; Send data
      call    get_ack
      call    stop         ; Create STOP condition
      goto    test2        ; repeat forever

```

The other changes I made to the master code were mainly cosmetic, a matter of changing labels and cleaning up the constants used for accessing SCL and SDA. The equates and #defines in the slave code (Listing 2) show the nature of what I did. All writes to TRISA are now indicated by use of W_SDA or W_SCL, and all reads from PORTA are indicated by R_SDA and R_SCL. I did these things to make the master and slave code a bit easier to read.

A Software-only I2C Slave

As I mentioned last time, the hard part of building an I2C slave in software isn't getting the slave to poll the bus lines often enough that START can be reliably detected; it's leaving enough processing cycles free for the slave to do other work besides monitoring the I2C bus. My current slave code does detect START reliably, but it doesn't even try to do any other work. I have some ideas how to fix this, though, and I'll talk about them later. Let's take a look first at the core routines of the slave.

When the bus is idle, the slave waits for a START condition in the idle routine. This short routine detects START in three to six cycles. Once START is detected, the slave must then wait for SCL to go low for

the first bit and, once that happens, the slave can start reading bits in from SDA.

In the interest of speed and readability, reading and writing bits are handled by inline macros. The macro `rcv_bit` takes as its parameter the bit number of the current byte being received and sets or clears the corresponding bit in the variable `i2c_in`. Likewise, the macro `xmt_bit` sets or clears the SDA line according to the state of the bit in `i2c_out` selected by the macro's bit number parameter. Both macros are invoked eight times; once each for bits 7 through 0 of the byte being sent or received.

"`rcv_bit`" first releases SCL (in case it was being stretched by the slave), then enters a loop that samples SDA and checks if SCL has gone high.

As always, if you have suggestions for improving Breadbot, if you've built a Breadbot, or if you have questions or comments about amateur robotics topics,

you can reach me at:

Robert Nansel
69 S. Fremont Ave. #2
Pittsburgh, PA 15202

E-Mail:

bnansel@nauticom.net

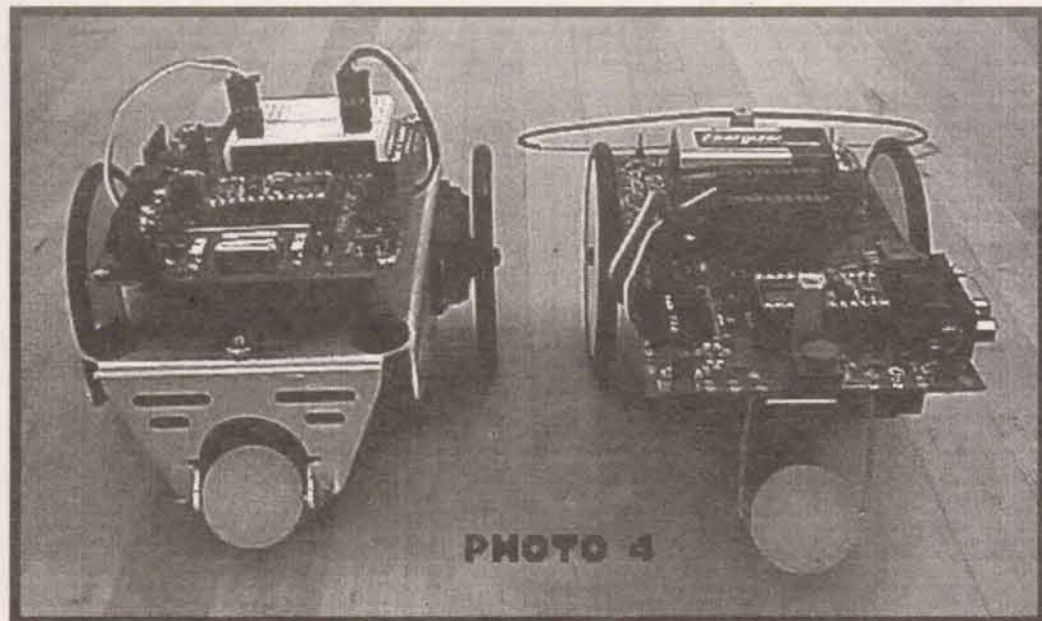


PHOTO 4

CABLE TV CONVERTERS

	5 lot	10 lot	20 lot	50+	100+
►Viewstar MXC - 2020 85 CH Plain Converter PG Lock HRC/STD SleepTimer	\$45.	\$40.	\$35.	\$30.	Call
►Century CTC - 3000 99 CH Plain Converter PG Lock HRC/STD SleepTimer	\$50.	\$45.	\$40.	\$35.	Call
►Panasonic TZPC 175 99 CH / Volume	\$67.	\$65.	\$62.	\$60.	Call
►View Master VM 125 V 125 CH / Volume	\$77.	\$70.	\$67.	\$65.	Call

All converters are factory new with remote control. Call us today for all your cable accessory needs.

DIRECT FACTORY SUPPLY, INC.
1-888-748-0946

E-MAIL YOUR REQUESTS TO: DIRFACSup@AOL.COM (No Descrambler Sales)

Once SCL rises, the sampled bit goes into the input buffer, and "`rcv_bit`" waits in a second loop for SCL to go low. This loop is three cycles, for a maximum 1.2 usec lag in recognizing the falling edge of SCL.

Finally, "`rcv_bit`" outputs a low on SCL to stretch the clock as long as

the receiver needs. Since the first thing "`rcv_bit`" does is to release SCL, and since the overall loop is short enough, this causes no trouble even with a master that doesn't recognize clock stretching.

"`xmt_bit`" is simpler. It first releases SCL, outputs the SDA level,

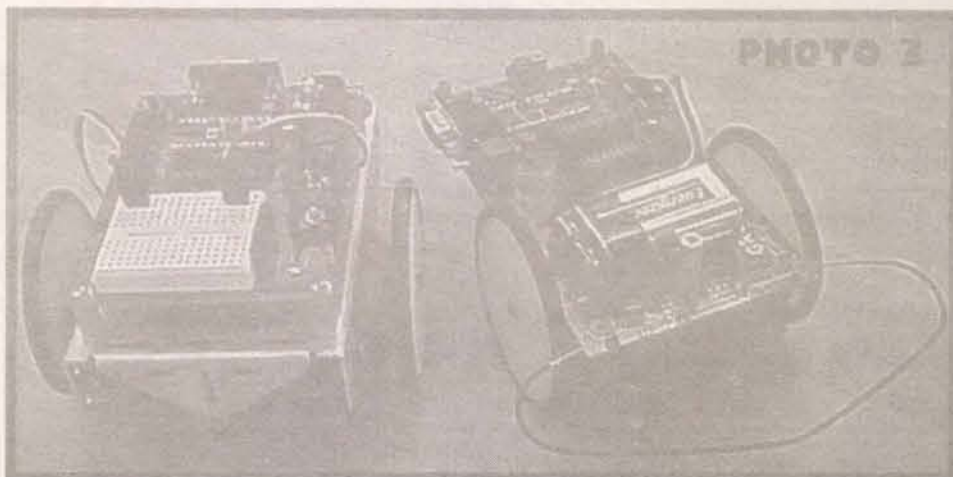


PHOTO 2

BIG POWER LOW COST



Dominoes are rugged, miniature encapsulated controllers that combine lots of analog and digital I/O with a fast control-oriented floating-point BASIC to provide a one-stop computation and control solution for cost-sensitive control tasks. Used stand alone or connected via RS-232/RS-485, Dominoes are true plug-and-go control.

Domino 1 features:

- Full floating-point ROMed BASIC
- 32-KB SRAM and 32-KB EEPROM
- 12 bits of parallel I/O
- 2 PWM outputs
- I²C bus
- 2-channel 12-bit ADC
- Serial port: 19.2-kbps RS-232A, RS-422, or RS-485
- +5 V @ 15 mA

Domino 2 has:

- everything in Domino 1 plus
- 16 more bits of high-current parallel I/O
- Hardware clock/calendar
- Wide-range power operation
- Hardware PWM output

\$99 to \$139

Visit our Web site for complete datasheets
www.micromint.com

To Order Call: **1-800-635-3355**

Micromint, Inc.

740 Florida Central Pkwy., Longwood, FL 32750
(407) 262-0066

title "slavetst.asm"

```
slavetst.asm - Respond to I2C Master test data pattern
(c) 1999 by Robert Nansel
This program is free software; you can redistribute it and/or
modify it under the terms of the GNU General Public License as
published by the Free Software Foundation. Details of the GNU
GPL can be found at www.fsf.org or by writing to the Free
Software Foundation, Inc., 59 Temple Place, Suite 330, Boston,
MA 02111-1307, USA.
It comes with ABSOLUTELY NO WARRANTY, implied or otherwise.
```

```
Revision history: v0.01.0 - 9/29/99
- basic bit-level slave routines
```

```
LIST P=16F84, F=INHX8M, R=DEC ; 16F84 Runs at 10 MHz
errorlevel 0,-305
INCLUDE "progra-1\mplab\p16F84.inc"
```

;; Registers

```
_CONFIG_CP_OFF & _WDT_OFF & _HS_OSC & _PWRTE_ON
```

;; Constants

```
i2c_clr equ 0xFC
i2c_set equ 0x03
idle_out equ 0x03
start_out equ 0x01
```

```
ack equ 0x00
no_ack equ 0xFF
```

```
SCL equ 0 ; Ser. Clock, bit 0 PortA
SDA equ 1 ; Ser. Data, bit 1 PortA
SDA_mask equ 0x02
```

```
#define R_SCL TRISA, SCL ; Read SCL, bit 0 PortA
#define R_SDA TRISA, SDA ; Read SDA, bit 0 PortA
#define W_SCL PORTA, SCL ; Write SCL, bit 0 PortA
#define W_SDA PORTA, SDA ; Write SDA, bit 1 PortA
```

;; Delay values

(these will eventually be used when invoking the delay macro)

```
F_Osc equ 10 ; 10 MHz XTAL
T_cyc equ 10000/((F_Osc*10)/4) ; T_cyc ns/cycle
T_buf equ ((47000/T_cyc)+5)/10 ; 4700 ns
T_hdsta equ ((40000/T_cyc)+5)/10 ; 4000 ns
T_low equ ((47000/T_cyc)+5)/10 ; 4700 ns
T_high equ ((40000/T_cyc)+5)/10 ; 4000 ns
T_susto equ ((40000/T_cyc)+5)/10 ; 4000 ns
```

;; RAM Usage

```
CBLOCK 0x00C
```

```
_w ; ISR context storage
_status
bit_count ; bit shift counter
i2c_out ; output buffer
i2c_in ; input buffer
temp ; temporary storage
```

```
ENDC
```

;; Macro definitions

;; Receive bit from i2c master

```
This is a modified version of the macro published 11/9/97
on the PICList by Marc Heuler <marc@aargh.mayn.de>. Marc's
macro was intended for a 4-MHz PIC, but I'm using it at 10 MHz.
I've altered variable names & some of the comments and added
SCL clock stretching capability. I've also corrected Marc's
macro usage to reflect the proper bit reception order (i.e.,
MSB first).
```

```
rcv_bit MACRO BITNUM ; read SDA bit into W.0 during T_high
bsf W_SCL ; Stop stretching SCL
bcf STATUS, RP0 ; (Ports in Bank0)
rrf PORTA, w ; wait for & read next bit
; W.0 = SDA, C = SCL
btfss STATUS, C ; SCL was high when sampling?
goto $-2 ;
andlw 1 ; isolate SDA in W.0
btfsc R_SCL ;
goto $-1 ;
```

```
btfss STATUS, Z ; store SDA in proper bit
bsf i2c_in, BITNUM
bsf STATUS, RP0 ; (Tris in Bank1)
bcf W_SCL ; Start stretching SCL
```

;>>* Insert enable, disable interrupt sequence here?

```
ENDM
```

;; Transmit bit to i2c master

```
xmt_bit MACRO BITNUM ; Send the bit
btfss i2c_out, BITNUM
bcf W_SDA ; Stop stretching SCL
bsf W_SCL ; (Ports in Bank0)
bcf STATUS, RP0 ; Wait for SCL to go high
btfss R_SCL ; Now wait for SCL to drop
goto $-1 ;
btfsc R_SCL ;
goto $-1 ;
bsf STATUS, RP0 ; (Tris in Bank1)
bcf W_SCL ; Start stretching SCL
```

;>>* Insert enable, disable interrupt sequence here?

```
bsf W_SDA ; Clean up
ENDM
```

```
PAGE
```

```
org 0
```

```
i2c_init
bsf STATUS, RP0 ; (Tris in Bank1)
movlw i2c_set ; Set up PA0, PA1 as inputs
andwf TRISA ;
bcf STATUS, RP0 ; (Ports in Bank0)
movlw i2c_clr ; Set up active low zeros
andwf PORTA ; in PORTA
```

```
stop_rcvd
clrf i2c_in
clrf i2c_out
```

```
i2c_wait
bsf STATUS, RP0 ; (Tris in Bank1)
movf TRISA ; Get I2C bits
andlw i2c_clr ;
iorlw idle_out ; SCL=1, SDA=1
movwf TRISA ; Output bus pin values
bcf STATUS, RP0 ; (Ports in Bank0)
nop ; Let bus settle 1.2 usec to
; meet I2C 1 usec max rise time
```

```
wait2
movlw idle_out ; SCL=1, SDA=1
xorwf PORTA, w ; Check bus state
andlw i2c_set ;
btfss STATUS, Z ; I2C bus idle?
goto wait2 ; No, go wait for bus idle
movlw idle_out ; Yes, continue
xorwf PORTA, w ; Check I2C bus state 2nd time
andlw i2c_set ;
btfss STATUS, Z ; Bus still idle?
goto wait2 ; No, go wait for bus idle
movlw idle_out ; Yes, continue
xorwf PORTA, w ; Check I2C bus state 3rd time
andlw i2c_set ;
btfss STATUS, Z ; Bus still idle?
goto wait2 ; No, go wait for bus idle
```

```
idle
btfss R_SDA ; detects start condition when it lasts
goto start_rcvd ; for at least 4 cycles
btfss R_SCL ;
goto wait2 ;
btfsc R_SDA ;
goto idle ;
```

```
start_rcvd
btfsc R_SCL ; start cond. occurred <=5 cycles ago
goto $-1 ; wait for bit 0
; clk must be low at least 3 cycles
```

```
rcv_bit 7
rcv_bit 6
rcv_bit 5
rcv_bit 4
rcv_bit 3
rcv_bit 2
rcv_bit 1
rcv_bit 0
```

Listing 2

NOTEBOOK

then waits for SCL to cycle high, then low. It then pulls SCL low and releases SDA on exit. Releasing SDA allows the master to perform an ACK during a read cycle. This could be removed from the macro if more speed is desired, but an explicit release would need to follow the last invocation of the "xmt_bit" macro to ensure the SDA line is high for the ACK bit.

In both macros, notice the comment at the end about enabling and disabling interrupts. This is the wedge that will allow the slave to do work other than scanning the I2C bus. By combining clock stretching and interrupts, I believe a software-only slave can do useful work while processing an I2C datagram.

It would go something like this: Every time the slave detects that SCL has gone low, it can stretch out the SCL low time. While the slave pulls its SCL line low, it can safely enable interrupts. If the slave then gets an interrupt, or if there had been an interrupt pending, SCL will stay low

while the slave services the interrupt.

On entry into the next invocation of the macro, the slave would disable interrupts immediately before releasing SCL. The master goes into a wait state as long as the slave holds SCL low, so no data would be lost.

The only places where this scheme would fail are when the slave is waiting for bus idle or when polling for a START condition. I'll show what can be done in these areas next time.

Testing the Slave

To test both read and write functionality, I simply have the slave read the address from the master then echo it back as data. If the slave receives the address properly, the first byte should equal the second.

The first time I tried my slave code, everything seemed to be working except the data the slave echoed appeared to be backwards, with bit 0 first and bit 7 last. I pored over this

```
ack_address
bsf    STATUS, RP0    ; (Tris in Bank1)
bcf    W_SDA          ; Send ACK bit
bsf    W_SCL          ; Stop stretching SCL
bcf    STATUS, RP0    ; (Ports in Bank0)
btfss  R_SCL          ; Wait for SCL to go high
goto   $-1
btfsc  R_SCL          ; Now wait for SCL to drop
goto   $-1
bsf    STATUS, RP0    ; (Tris in Bank1)
bcf    W_SCL          ; Start stretching SCL
```

>>> Insert enable, disable interrupt sequence here?

```
bsf    W_SDA          ; Clean up
```

>>> Echo address received to test master/slave interaction

```
movf   i2c_in, w      ; get value received...
movwf  i2c_out         ; ...and echo it back
```

```
xmt_bit 7
xmt_bit 6
xmt_bit 5
xmt_bit 4
xmt_bit 3
xmt_bit 2
xmt_bit 1
xmt_bit 0
```

Listing 2 continued

>>> Get ACK pulse from master - (ignores ACK/NACK status for testing)

```
get_master_ack
bsf    W_SCL          ; Stop stretching SCL
bcf    STATUS, RP0    ; (Ports in Bank0)
btfss  R_SCL          ; Wait for SCL to go high
goto   $-1
btfsc  R_SCL          ; Now wait for SCL to drop
goto   $-1
bsf    STATUS, RP0    ; (Tris in Bank1)
bcf    W_SCL          ; Start stretching SCL
```

>>> Insert enable, disable interrupt sequence here?

```
bsf    W_SDA          ; Clean up
```

```
wait_stop
bcf    STATUS, RP0    ; (Ports in Bank0)
btfss  R_SCL          ; Wait for SCL to go high
goto   $-1
btfss  R_SDA          ; Wait for SDA to go high
goto   $-1
bsf    STATUS, RP0    ; (Tris in Bank1)
goto   stop_rcvd

end
```

Metric
Equipment Sales, Inc.

800-432-3424

Fax: 510-264-0886

www.metricsales.com

RENT • BUY • SELL

Yes, we will buy your surplus equipment!

**Scopes, Meters, Analyzers, Power Supplies, Signal
Generators, Counters, Recorders and more**

Hewlett-Packard, Tektronix, Fluke, Dranetz, TTC, Anritsu,
Wavetek, Keithley, and more

Test & Measurement Instruments

Over 7000 Models • 6-Month Warranty

Save 30-90% • 5-Day Free Trial

Write in 65 on Reader Service Card.

Celebrating our 17th Year Of Service !!

COLLIMATING LENS

This economical collimating lens assembly consists of a black anodized aluminum barrel that acts as a heat sink, and a glass lens with a focal point of 7.5mm. Designed to fit standard 9mm laser diodes. Simply place diode in the lens assembly, adjust beam to desired focus, then set with adhesive.

STOCK#	1-4	10-24	25+
LSLENS Lens Assembly	24.99	23.74	21.37

DIODE/TRANSISTOR TESTER KIT

This dynamic tester allows checking of transistors & diodes in circuit. Identifies NPN or PNP transistors. Checks all types, small or large power. Identifies anode or cathode of diodes.

STOCK#	1-4	10-24	25+
DT100K	24.99	23.74	21.37

ANTI-STATIC FOAM CLEANER

A thick, foaming cleaner for use in static sensitive applications. Safe for plastics and fiberglass. Use on computer cases and all office equipment. Also cleans soft fabrics. 5 oz. aerosol can.

STOCK#	1-4	10-24	25+
S81102	1.99	1.89	1.70

EPROMS

STOCK#	1-4	25-99	100+
2716	2.99	2.84	2.56
2732	4.49	4.27	3.84
2732A-20	5.49	5.22	4.70
2764-20	5.39	5.12	4.61
2764-25	4.49	4.27	3.84
2764A-20	3.49	3.32	2.99
2764A-25	2.99	2.84	2.56
27C64-15	2.99	2.84	2.56
27256-15	4.79	4.55	4.10
27C256-15	2.99	2.84	2.56
27512-25	3.09	2.94	2.65
27C512-25	2.99	2.84	2.56
27C010-15	2.79	2.65	2.39
27C020-15	3.49	3.32	2.99
27C040-12	5.49	5.22	4.70
27C080-12	10.99	10.44	9.40

Popular I.C.'s

STOCK#	1-24	25-99	100+
7400	.39	.37	.33
74LS00	.19	.18	.16
4017	.29	.28	.25
7805T	.33	.31	.28
7812T	.33	.31	.28
LM317T	.49	.47	.42
LM386N-1	.33	.31	.28
NE555N	.24	.23	.21
LM741N	.24	.23	.21
NE5532N	.55	.52	.47
68HC705C8P	8.99	8.54	7.69
8749	17.99	17.09	15.38
62256LP-10	2.79	2.65	2.39
2816	2.79	2.65	2.39

FM MICROPHONE KIT

Transmit your voice on any FM radio. Range up to 1000'. Case included.

STOCK#	1-4	10-24	25+
K30	15.99	15.19	13.67

What Do We Have ?

- I.C.'s
- Oscillators
- Crystals
- Diodes
- Tools
- Laser Diodes
- Vices
- Resistors
- Capacitors
- Connectors
- Trimpots
- Kits
- Vices
- Transistors
- And more!

GADGETEER'S GOLDMINE

This exciting collection of electronic projects features experiments ranging from magnetic levitation and lasers to high-tech surveillance and digital communications.

• By Gordon McComb

STOCK#	1-4	10-24	25+
TB3360	24.99	23.74	21.37




• Order Line — (800) 824-3432 • International — (724) 495-1230 • Fax Orders — (724) 495-7882
• Technical Support — (724) 495-1231 • No Minimum Order — (Orders under \$20 subject to \$5 charge)
• UPS 3 day, Blue, Red, & Fed. Ex. Shipping Available (Call for charges) • PA Res. Add 7% Sales Tax • Open Mon-Fri 9:00 AM - 5:00 PM (EST) • Corporate Accounts / Quantity Discounts Available • We accept M/C, VISA, Discover & American Express with no surcharge • Call For FREE Catalog (\$2.00 Outside U.S.)
• We Carry A Complete Line Of Electronic Components • Email - unielect@aol.com
Visit us on the web ! www.unielectronics.com

FREE SHIPPING!! on pre-paid orders

Unicorn Electronics
1142 State Route 18
Aliquippa, PA 15001

Write in 64 on Reader Service Card.

Nuts & Volts Magazine/NOVEMBER 1999 71

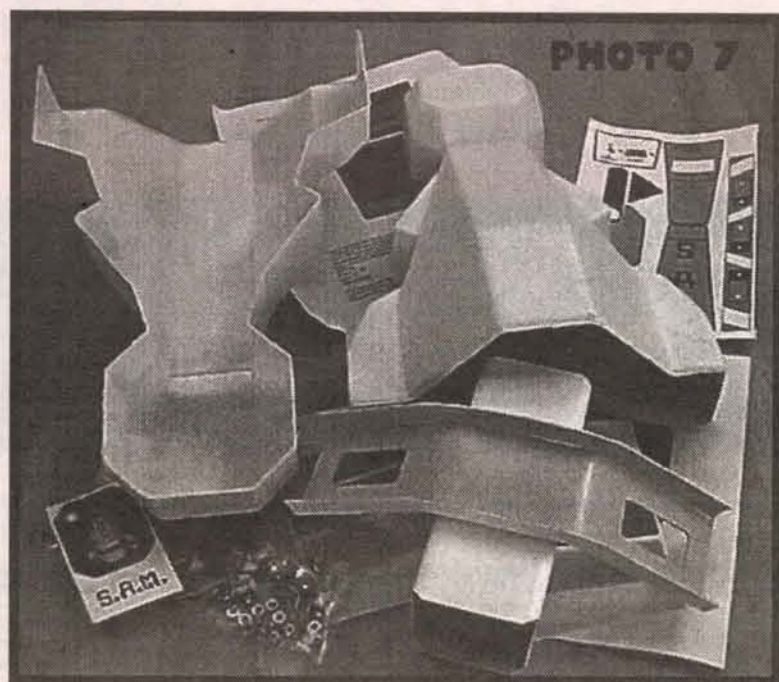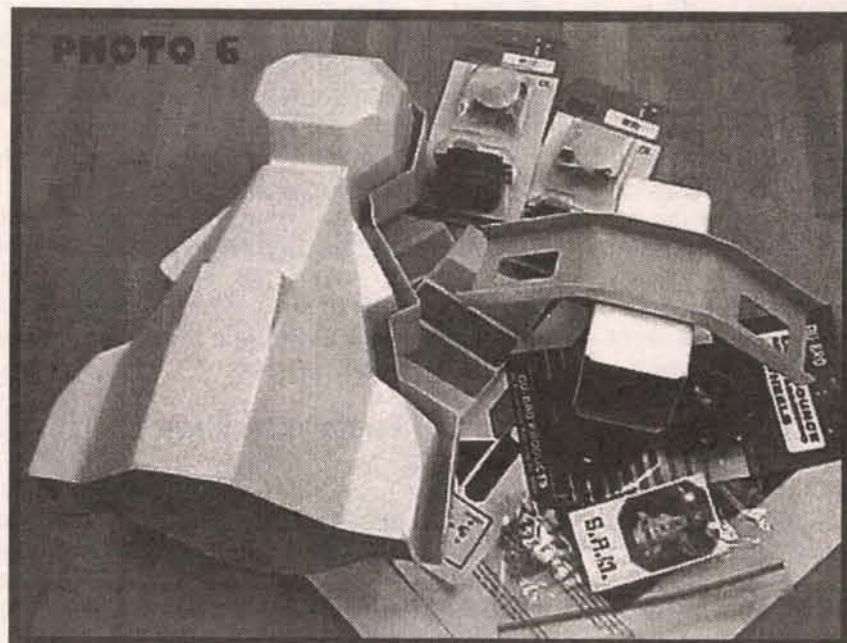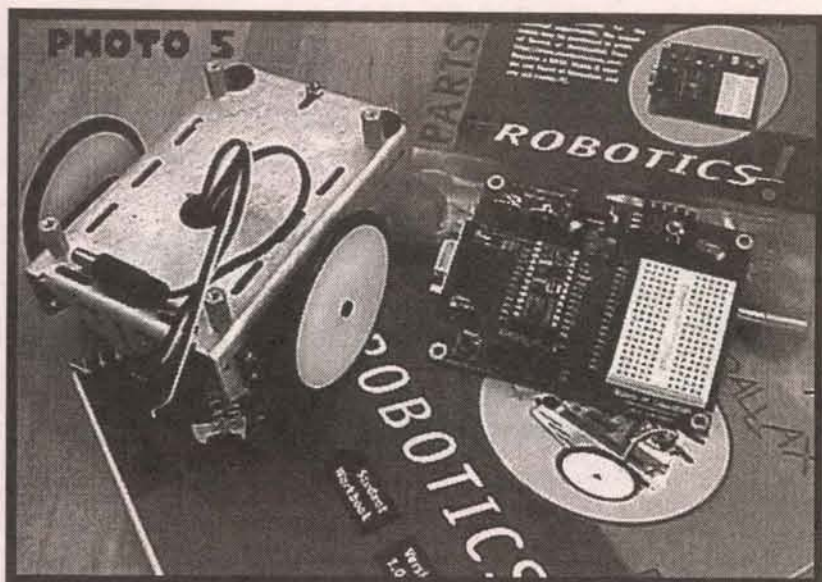

bug for about an hour, added a snippet of code to write the data the slave received to Port B to check that it was indeed backwards.

The more observant among you may already have figured out what the problem was. The address + R/W bit came out of the master as 01110001 — I could see it on my 'scope! No matter what I did, though, the slave always echoed it as 10001110, which does indeed look as if the bits were being reversed. But 10001110 is also the one's complement of the first byte, and this is where my decision to make the master output the "correct" value for the R/W bit came back to bite me. If I'd left it zero for the first test, I'd immediately have seen that the data was logically inverted, not reversed at all.

The bug? I'd put "btfs STATUS, Z" into the rcv_bit macro instead of "btfs STATUS, Z," thus inverting the received data. The lesson here: choose test data with care.

Boe-Bot

Just two days before this column deadline, I received a package from Parallax (www.parallaxinc.com), and in it was their newest low-cost robot kit, "Boe-Bot." "Boe" stands for "Board Of Education," one of their BASIC Stamp 2 experiment boards intended for the education market (hence the name). I'd seen a couple magazine ads for Boe-Bot in the last month, so I was eager to get my hands on one (Photos 1-5).

Unlike Parallax's GrowBot, Boe-Bot has a CNC-machined aluminum chassis with lots of holes and slots for mounting components. This makes for a more solid, precise, and versatile mechanical base.

Boe-Bot and GrowBot use the same servos, drive wheels, and tail roller. The wheelbase is about the same, but Boe-Bot has an inch wider tracking width, making it more stable. It would make a great robot fire fighter for the contest in Hartford.

Boe-Bot is simple to build and requires no soldering. The full kit (Photo 5) includes a manual and parts for experiments for \$199.00. For \$99.00, there's a mechanical-parts-only kit (no B.O.E.) for folks who want to use Botboards, SIMMSticks, Handiboards, etc., and, for you GrowBot owners out there, you can buy an upgrade (the aluminum chassis and some hardware) for \$49.00. The GrowBot board mounts nicely on the center slots.

More on Boe-Bot when I've had time to play with it.

S.A.M.

The second kit has been on my shelf for <mumble> months waiting

BOB SAVED THE WORLD TODAY...



Bob, Super-Tech extrodinaire, has a secret weapon. This amazing device allowed him to locate and replace all 34 bad electrolytic capacitors in this TV in less than 30 minutes. So instead of throwing this TV into the local landfill and adding more pollution, Bob's secret weapon enabled him to give the World a brighter future. Impressed his manager and his customer too. Bob's secret weapon? The world's best in-circuit cap checker, the *CapAnalyzer 88A* by EDS.

Smart techs know that to be productive you need to find

defective components quickly and accurately. That's why General Motors, Matsushita Industrial, Sears Service, Pioneer Electronics, Panasonic Authorized Service, NASA/Kennedy Space Center, Time/Warner Communications, NBC TV and thousands more independent service technicians have chosen the *CapAnalyzer 88A* over all of the other capacitor checkers. Check www.eds-inc.com/88users.html for actual *CapAnalyzer* users' comments as they compare their *CapAnalyzer* to the "wizards" and "z-meters" they already own. They all prefer the *CapAnalyzer* because it checks electrolytic capacitors, *in-circuit*, with 100% accuracy. No unsoldering to check out-of-circuit, no mistaking a shorted or leaky cap as good, as other "ESR" meters do, no guessing about whether a value is good or bad. With our exclusive three-color comparison chart right on the front panel, auto-discharge, multi-beep alert, and one-handed tweezer test probe, even your pet monkey could find defective caps in that problem PWM power supply, TV, monitor or VCR in a few seconds.

...NOW IT'S YOUR TURN.

So get your own *CapAnalyzer 88A*. It's only \$179. With our exclusive 60-day satisfaction-or-money-back guarantee, you risk nothing. Prepare to be amazed: your only problem will be running out of work as you take care of all of those "dogs" that you've been sitting on. We're Electronic Design Specialists. We make test equipment designed to make you money. Available at your distributor now, or call 561-487-6103. Check out www.eds-inc.com for the details.

Power Quality Inc. 800-255-5545
Fax: 520-344-8847

Heavy Duty Surge Suppressor
Plug Strips, 6 outlet, circuit breaker,
Case of 25 in individual boxes...\$50/case

HP Power Supplies, HP6260B
current is 0-50A,\$100

UPS, 250va to 3 kva, functional and
nonfunctional.....Please call

Power Conditioners, Oneac, TLC,
Teal, Sola, various sizes.....Please call

BMI, Dranetz, and RPM
Power Quality Monitors.....Please call

www.powerqualityinc.com

SURPLUS SALE

1,000,000 WALL TRANSFORMERS



3VDC/100MA CX099 \$0.75
6VDC/100MA CS039 \$1.45
9VDC/100MA CR314 \$1.45
12VDC/200MA CS033 \$0.99
13.5VAC/400MA.. CR574 \$1.29
24VDC/500MA CR174 \$3.40

Min 1000/type -- Call for other types

SURPLUS TRADERS

PO Box 276,
Albany, VT 05440
Tel: (01) 514-739-9328
Fax: (01) 514-345-8303
<http://www.73.com/w>

FREE CATALOG!

IC PROGRAMMERS

ADVANTECH EETOOLS NEEDHAM DATA IO BP MICRO
XELTEK SYSTEM GENERAL ICE TECHNOLOGY CHROMA

1295 Advantech Labtool-48
895 Needham EMP-30
869 EETool Topmax
650 Xeltek SuperPro III
629 ICE Tech Micromaster LV
469 Xeltek SuperPro F
419 Needham EMP-20
419 EETool Megamax
379 Xeltek SuperPro LX
299 EETool ChipMax
279 Xeltek Rommaster II
209 Needham EMP-10



Gang Programmers 4 TO 8 Sockets
CALL Advantech Labtool-848 8XGang
1085 EETool TopMax W/8XGang
689 Needham SA-20 8X Gang
529 EETool MegaMax4G 4XGang

General Device Instruments

Sales 916-393-1655 Fax 916-392-4949
Order Only Toll Free 800-760-3820

WWW.GENERALDEVICE.COM
WWW.LABTOOL.COM

COMPUTER I/O

Model CRD155B

- ISA bus interface
- 24 digital I/O lines (inputs or outputs)
- DB25 connector
- User Manual
- Software API

Price: \$45

Please visit our web site for more information and our complete product line.

Winford Engineering

4169 Four Mile, Bay City, MI 48706

Toll free: 1-877-634-2673

www.winfordeng.com

CUSTOM PLASTIC PARTS

- MODELS (WOOD AND RESIN), TO EVALUATE YOUR PARTS BEFORE COMMITTING TO MANUFACTURE A MOLD.
- MOLD DESIGN AND BUILDING.



- PRODUCTION OF INJECTION MOLDED PARTS. NO ORDER TO SMALL OR TO BIG.
- VERY COMPETITIVE ON HIGH LABOR PARTS.

We also have manual low pressure machines for injection molding of very small runs or prototypes of parts up to 2 oz. At a surprisingly low price.

USA. Office: V&V Mach. & Equip Inc.
Tel (281) 397-8101, Fax (281) 397-6220.
Please send blue prints or samples to:
Marketing Tech. S.A. *Alamo 93, 4.Piso *Sta. Monica,
Tlat. *Edo. de Mexico 54040 *Tel. 011 (525) 361-3351.
Fax 011(525) 361-5996. ATTN: VICTOR M.MENDOZA
e-mail: marktech@infosel.net.mx

PLEASE VISIT OUR SITE
WWW.VANDVMANCHY.COM

JUNE SPECIAL SAVE \$10.00

SHIELDED LOOP RECEIVER

30M, 40M KITS W/ ANTENNA.
VERY SENSITIVE. HAS HIGH
IMMUNITY TO QRN & LOCAL
AM BROADCAST. \$92.50 PP

12/14V PULSE BATTERY TESTER

(LEAD ACID). ATTACH THE BATTERY &
PUSH THE BUTTON TO DETERMINE IF THE
BATTERY NEEDS RECHARGING. A MUST
FOR THE GLIDDER SET, BOATERS, ETC.
BASIC KIT \$55.50 PP
ASSEMBLED WITH ENCLOSURE \$106.50 PP

MARCONI ANTENNA 700W 50 Ω

THE BEST "LITTLE" LOW BAND ANTENNA

80M: 67' OVERALL \$47.45 PP

160M: 130' OVERALL \$54.45 PP

CODE PRACTICE OSCILLATOR... \$23.45 PP

SEND FOR FREE CATALOG

1-800 JADE PRO (523-3776)

www.jadeprod.com/

email: jadeprod@jadeprod.com

JADE PRODUCTS E. HAMPSTEAD NH 03826-0368

CABLE SECRETS!!!

This ad has been

CENSORED!

Want to know why?

Visit us at <http://www.worldwyde.com>

- Find out how "Test" Devices work
- Installation of "Test" Devices
- Descrambling Methods Explained
- Detailed Construction of "Test" Devices

Includes plans and source code

Complete source code \$79.95

Code for individual boxes \$29.95

DSS SECRETS — Vol. 2

Instructions on programming DSS access

cards. This is the most current information

on the market! Includes software, plans, and

hardware sources. Book & CD-ROM.

Get this before they censor it too!!!

DSS Secrets Vol. 2 \$49.95

VISA • MasterCard • American Express

To order, call Worldwyde • 1-800-773-6698

21365 Randall Street • Farmington Hills, MI 48336

Visit us on the web at www.worldwyde.com

Sensors and Real Time Clocks



AT6 Digital Inclinometer kit

▲ 2-axis measure of variation

from the level position

▲ For robots, vehicles, more!

▲ \$59.95+ ship/handling

RHT7 kit

▲ Relative Humidity &

Temperature Sensor

▲ Sends data over 100 feet

▲ \$64.95+ ship/handling

Visit our Webpage for more! See

the MicroClock II kit!

www.technologykit.com

Technology Electronics, Ltd.

Phone: 937-438-4683 Fax: 937-438-5934

www.technologykit.com kits@technologykit.com

for me to find time to build it. It's called S.A.M., Small Android Model (Photos 6 and 7). Those of you who remember Topo and B.O.B. will instantly recognize S.A.M.'s lineage.

For those of you who aren't familiar with ancient amateur robotics history, Topo was a three-foot-tall hobbyist robot from the early 80s, and B.O.B. ("Brains On Board") was Topo's smarter brother. Topo was unique in that it used only two drive wheels with no casters or skids.

The trick was that the wheels were tilted fairly steeply so that Topo didn't run on the rims of its wheel so much as the sides. This tilt, along with a low center of mass, made Topo inherently stable (mostly). Actually, the old Topos wobbled like Weebles. And, like Weebles, they didn't fall down (mostly).

S.A.M. is a smaller, lighter version of the Topo idea from Norland Research (www.smallrobot.com). The basic kit, without wheels or servos, costs \$29.95. For that you get two vacu-formed ABS body shells, a preformed vinyl servo mounting bracket, and a square-tube chassis with cutout for a four AA-cell battery holder.

For another \$29.95 you get servos, Dubro rubber wheels, and mounting hardware. You can fit most popular robot controllers

inside, including a solderless breadboard. S.A.M. is about 14 inches tall and the body shell and chassis weighs just 12 oz.

The workmanship of the parts is pretty good, but this is definitely not a snap-together kit. You'll need to do some cutting, drilling, filing, and gluing to fit everything together.

Decorative stickers come with the kit to jazz S.A.M. up, or you can do your own custom paint job. But, for under \$60.00, you'll have the coolest-looking robot on the block. You'll be hearing more about S.A.M. in the future.

Lonely Gearhead Contest

Over the years, I've gotten tons of letters and E-Mail from folks who are convinced they are the only robot builders in their area. Sometimes, these people live in places where there are vibrant amateur robotics groups, such as Seattle, San Francisco, or Hartford.

Others come from isolated places in third-world nations. The two things they have in common are the burning desire to build robots and the need to get together with other robot builders.

I try to connect these people up with any local robotics groups I'm

TV 85 PJ & TV 86 CABLE CONVERTERS VOLUME & NON-VOLUME CONTROL

SALES/SERVICE
VOICE 1-800-473-0506
FAX 1-800-488-0525

FOSS WAREHOUSE DISTRIBUTORS

285 Schenck St.
N. Tonawanda, NY 14120
www.fossw.com

aware of, because there is no substitute for sitting down with another gearhead to compare notes and 'bots.

To help our lonely brothers and sisters, I propose that anybody anywhere who wants to find a local club or get one going should send me a letter or E-Mail. Also, anybody who has a club going should give me contact information. Those listings I receive by December 1, 1999 will make it into my January 2000 column.

Send me contact names, addresses, URLs, E-Mail addresses,

UHF Wireless Telephone Recorder

Easy to install Superb sound quality



ONLY \$299.00

The UX-200 is a UHF telephone transmitter with combined Receiver & Recorder, which works with battery or mains. It will record up to 7 Hours and has a range of more than 100 meters.

Bitz Technology
E-mail: Bitztechnology@compuserve.com

phone numbers, etc., whatever way you would wish other robot builders to get in touch with you. If you have a club you want folks to know about, drop me a line. Likewise, if you are looking for a club.

To sweeten the deal, all who respond by December 1st will get their names thrown in a hat; I will randomly select one person to receive a complete Parallax GrowBot kit, free of charge. Real names and addresses only, please, and no names of my relatives or friends will go in the hat.

So, let's hear from you. **NV**



GPS Design Kit — \$379

The design kit SGM5600KS is a complete and immediately usable means of evaluating the SiGEM GPS receiver module and high performance GPS antenna, which are included in the kit. Software running on the GPS receiver module communicates to a user supplied computer via NMEA 0183 formatted messages. Advanced PC software provides map integration and a demonstration of tracking. Provision has been made for DGPS inputs.

SiGEM Inc.
50 Hines Road
Kanata, Ontario
Canada K2K 2M5
Tel: (613) 271-1601 (Can)
(541) 923-3733 (USA)
Fax: (613) 271-1896

SiGEM

Web: www.sigem.ca
Email: info@sigem.ca

SINGLE SIDED PCBs

9¢

9 C PER SQIN, \$100 SET UP,
SMOBC, ONE OUNCE COPPER, PC75, 1/16",
ONE SOLDER MASK AND ONE SILK SCREEN.
PHOTO PLOT \$ 50

DOUBLE SIDED PCBs

14¢

14 C PER SQIN, \$150 SET UP,
PTH, ONE OUNCE COPPER,
FR4, 1/16", TWO SOLDER MASKS AND ONE
SILK SCREEN. PHOTO PLOT \$ 75.


PLEASE VISIT OUR WEB SITE FOR MORE INFORMATION

WWW.VANDVMACHY.COM

V&V MACHY & EQUIP. INC. (HOUSTON TX OFFICE)
PH. (281) 397 6220
MARKETING TECH. S.A. (MEXICO CITY)
PH. 011 525 361 3351, FAX. 011 525 361 5996

SBC2000-074

RS-232

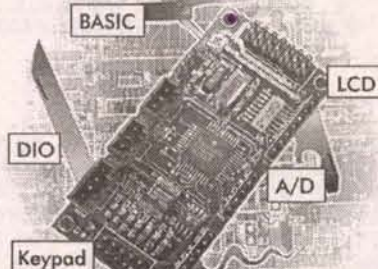


Versatility starting at \$64 each.

Voice: 303.422.8088 Fax: 303.422.9800

www.sbc2000.com

Vesta Technology, Inc.

2.4 GHz Wireless Transmitter & Receiver

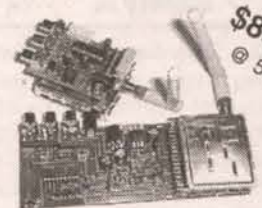

\$89/pair
@ 50 pcs

2.4 GHz - 2.48 GHz User Selectable
Over 700' Range and 4 Chl Auto-scan
NTSC, PAL, Composite video B/W or Color
2 Audio Inputs may be used for digital data
Customizations including battery packs
and Special Frequencies

Matco Inc.

(800)440-0299 or (800)719-9605
www.mat-co.com

Telecom Hardware/Software Developers

STOP using your phone lines to test and demonstrate your telecom devices. Our affordable telephone line simulators offer authentic USA dial tone, busy signals, ringing, and exceptional speech quality.



RING-IT! TELCO SIMULATOR

- Single Line (two RJ-11 Jacks)
- LED Display
- DTMF Operation
- Automatic Ring-up Mode
- \$325 (\$149 kit available)

PARTY-LINE TELCO SIMULATOR

- Six Extensions
- Caller-ID (Name/Nbr)
- Distinctive Ringing
- \$425 (\$199.95 kit avail)



Digital Products
COMPANY

134 Windstar Circle
Folsom, CA 95630 USA
Tel: 916-985-7219
Fax: 916-985-8460

<http://www.digitalproductsco.com>

LCD Terminal \$99



Re-Programmable
LCD 240 x 64 EL Backlit
RS-232 Port
1200 Baud Modem
8051 Compatible Microcontroller
192k Low Power Static Memory
Infrared Transmitter
Nicad Battery Pack
QWERTY Keyboard
FM SCA Data Receiver

Junkware.com

<http://www.junkware.com>

PC BOARD SERVICES

PCB Design Layout

Thru Hole

SMT

Multilayer

PCB FABRICATION

In-house Prototypes

Single and Double Side

Plate Thru Hole

ASSEMBLY

Thru Hole

Small Project Specialists

Serving Engineers and Hobbyists
for 16 Years

MIDLAND TECHNOLOGIES

800-726-8871 Voice

406-586-0300 FAX

Press-n-Peel Transfer Film

PC Boards in Minutes

8.5" x 11" Shts.
* Or Photocopy
** Use standard
household iron

1. LaserPrint*
2. Press On**
3. Peel Off
4. Etch



Use Standard Copper Clad Board
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100
Visa/MC/PO/Ck/MO \$4 S&H/Foreign Add \$7

Techniks Inc.

P.O. Box 463, Ringoes NJ 08551
ph. 908.788.8249 fax 908.788.8837
www.techniks.com

Visit Our E-Store On-Line!

Serial Port Problems ???

No heavy, aging serial protocol analyzer available? Use **Serial** to turn your PC into a test tool for asynchronous serial communications. **Serial** uses your PC serial ports to capture data, control and time stamps to give you what's needed to develop or debug your serial communications.

- Captures Data & Control lines
- Contextual Help
- Autobaud Detect
- Block Transmit
- Millisecond Timing
- Trigger Strings
- Extensive Manual
- Full Duplex Monitoring

Serial with manual US\$99.00
Full Duplex monitor cable US\$40.00

Allison Technology Corporation

2006 Finney Valley Rd., Rosenberg, TX 77471
800-980-9806 or 281-239-8500, Fax: 281-239-8006
<http://www.atcweb.com> atc@accesscomm.net

New!

ActiveWire™USB Simple USB Interface



- Internet Browser Scriptable
- 24 MHz CPU core with USB
- Firmware downloadable via USB
- 16 bit parallel I/O
- Expandable add-on boards
- New firmware and scripts available from website

\$59 plus shipping

ActiveWire, Inc.

www.activewireinc.com

ph(650) 493-8700 fx(650) 493-2200

QUALITY KITS

#1 Source for Electronic Kits

Great selection of Hi-Fi AUDIO Kits,
PSUs, Transmitters, Oscilloscopes,
PIC Programmers, and much more.

Toll Free Order Line:

1-888-464-5487

Secure On-Line Ordering

www.qkits.com


Call 613-544-6333 for free catalog

North American Kit Distributor

49 McMichael St., Kingston, ON
K7M 1M8, CANADA

Convert RS-232 to RS-485
or TTL/CMOS for Only \$49.00

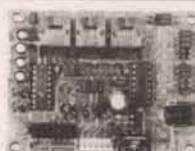Communicate up to
1,000 feet, at up to
1 MEGA-BPS, full
or half duplex, up to
32 units on one serial
link, with 31 jumper
options for flexible
configuration, LED
indicators.



COMMUNICATIONS CONVERTER

- FULL SCHEMATIC AND DOCUMENTATION
- FULL FAMILY OF MODULAR DESIGNS
- RS-485/RS-422 REMOTE I/O MODULE KITS
- NETWORK SOFTWARE AND SOURCE CODE
- AUTOMATIC OR RTS UNITS AVAILABLE
- RJ-11/12 CONNECTORS OR TERMINAL STRIP
- TURN YOUR PC INTO A DISTRIBUTED DATA ACQUISITION AND CONTROL SYSTEM

R.E. SMITH

(513) 874-4796

4311 TYLERSVILLE RD. ■ HAMILTON, OHIO 45011
www.rs485.com

Program PICs in Basic

Complete kits to get started!



Includes: PIC Basic Compiler, EPIC
Programmer, 16F84 PIC, Cable & Batteries

ORDER



Electronic Products
www.elproducts.com

PRINT toVIDEO!

Tiny BOB-II module superimposes up to 308 characters on NTSC/PAL video or generates video automatically. Fast 2.4-19.2kbps RS-232 serial interface. Simple to control; like a printer. Many powerful applications:

Home Automation - MATV
Video Inspection & Testing
Surveillance - CCTV - ATV
Remotely Piloted Vehicles
Gaming - Racing - Sports
Process/Experiment Monitor
Robotics - Electronic Signs

BOB-II-NTSC only \$79.95

Information & Ordering: www.decadenet.com

DECADE ENGINEERING

5504 ValView Dr. SE, Turner, OR 97392
Tel: 503.743.3194 - Fax: 503.743.2095

Globaltech Distributors

THE ULTIMATE ELECTRONIC SAVING STORE

Wholesale Prices Available—Don't Miss-Out

Call Today!---1-(800)582-5116

- | | |
|-----------------------|--------------------|
| Computer Acc. | Recordable CD's |
| Remote Controls | Alkaline Batteries |
| Semiconductors | 4 Wire Harness |
| IC's & Microprocessor | Anti-Virus Prog. |
| Radios & Amplifiers | Soldering Stations |
| Satellite Acc. | Cellular Chargers |
| Telephone Acc. | Hearing Aids |
| Anti-Tapping Devices | Laser Pointers |
| 2-Way Radios | Power Supplies |


*Free Internet Service - Free Color Catalog

Buy Direct

Buy Today

& Save

Order@globaltechdistributors.com

 

GREAT
FOR TEST FIXTURE
BUILDING



LAB-1
(1.5" x 2.0" x 0.75")

FREE!
PHONE, FAX, WRITE
OR E-MAIL WITH YOUR
MAILING ADDRESS
MUST MENTION
OFFER "LAB199"

PRE-PUNCHED END PANELS
ALSO AVAILABLE
9 BOX SIZES
25 PRE-PUNCHED
END PANELS

ALSO IN STOCK AT:
JENSEN TOOLS: 800-436-1194
MCM ELECTRONICS: 800-543-4339
TECH AMERICA: 800-442-7271

ALL ALUMINUM CONSTRUCTION LOW COST
OFFER GOOD ONLY IN THE 48 STATES. ENDS DECEMBER 30, 1999. LIMIT ONE
REQUEST PER CUSTOMER. MAILED 1ST CLASS, ALLOW 1-2 WEEKS FOR DELIVERY

ORDERS 800-634-3457 • FAX 800-551-2749

OFFICE 702-565-3400 • FAX 702-565-4828

www.sescom.com • info@sescom.com

SES.COM, INC. 2100 WARD DR., HENDERSON, NV 89015

SES.COM, INC. is not responsible for inadvertent typographical errors
and prices and specifications are subject to change without notice.

PCB EXPRESS, INC.

PROTOTYPE TO PRODUCTION

S/SIDED: 5-days, 10 Pcs.	\$275.00
D/SIDED: 5-days, 5 Pcs.	\$300.00
D/SIDED: 5-days, 10 Pcs.	\$350.00
4-LAYERS: 5-days, 5 Pcs.	\$750.00
4-LAYERS: 7-days, 10 Pcs.	\$850.00
6-LAYERS: 5-days, 5 Pcs.	\$950.00
6-LAYERS: 7-days, 10 Pcs.	\$1,175.00
(Up to 30 sq. inch each, includes Tooling)	

SERVICES — UL Approved


SMOBC, LP1 mask & Legend
Photoplotting, Electrical Testing
Thru hole/SMT, Gold/Nickel Plating
Routing and Scored Panel, Instant Quotes

PH: (888) 427-2920, Fax (847) 427-1949

E-Mail: cir1920@aol.com

LOWEST COST & FAST DELIVERY

VIDEO PRODUCTS

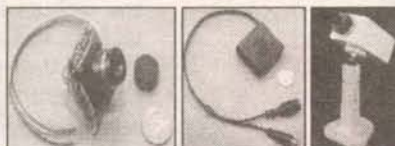

CNL-100 **BX-120-P** **SX-800**
\$49 **\$59** **\$79**

- 430 TV Lines Resolution
- 9-14 VDC Operation
- Infrared Sensitive
- SX-800 has Audio Output
- A-300 Camera Enclosure also available

MATCO, INC.

Schaumburg, IL

1-800-719-9605 • 1-847-619-0852 FAX

E-Mail: info@matco.com

Website: www.matco.com

10&14 Hour Telephone

Recorders Starting at \$69

Times based on a 180 tape
14 Hour \$89+S/H



120 Tape included!

Automatically starts recording when the phone is picked up and stops when you hang up. Records both sides of the conversation! Printed catalog \$3 (free with order)

Visit our Online Catalog
www.mscelectronics.com

MSC Electronics

PO BOX 461 Jessup, MD 20794

(301) 497-1600

FAX (301) 497-1925

No Checks • US & Canada Only



EPS

EPROMS AS LOW AS 25¢

27C256	27C040	27C1024	87C51
27C512	27C400	28F010	8751
2732A	27C4096	28F020	8755
27C32	574000	28F040	MC68HC70
27C128	574200	8749H	5C8A
27C64	27C402	8748H	PIC16C56
2716	27C020	8741	PIC16C54
2708	27C210	8742	PIC16C62
27C512-90	27C010	8744	GAL16V8
			GAL22V10
			MEMORY
			D-RAMS
			SRAM

STATIC RAM

HM628128
62256
6264
6116

PROCESSOR

8255
8254
80C31

- Many more parts in stock
- All major brands
- All guaranteed

E-Mail: eproms@aol.com

TEL: (818) 774-9444 • FAX: (818) 774-0822

WE BUY EXCESS INVENTORY



**FREE
SAMPLE COPY!**

ANTIQUE RADIO CLASSIFIED

*Antique Radio's Leading
Monthly Magazine*

Articles — Classifieds — Ads for Parts & Services. Also: Ham Equip. — Books — Telegraph — 40's, 50's & 60's Radios — Early TV — Auction Reports & more...

1-Year: \$39.49 (\$57.95 by 1st Class)

6-Month Trial - \$19.95. Foreign - Write.

A.R.C., P.O. Box 802-G23
Carlisle, MA 01741
Call: 978-371-0512 — Fax: 978-371-7129
Web: www.antiqueradio.com

TOGGLE SWITCHES — All sizes and types Commercial Quality

TYPE	MODEL	RATING	LEAD	PRICE 100-1000
SPST	D125	6A/125V	6" wire	.77 .67
SPST	D128	4A/125V	Solder	.57 .47
DPDT	D126	5A/125V	Solder	.77 .67
DPDT	D127	10A/125V	Solder	1.17 1.06
on-off-on		5A/250V	Screw	

MINIATURE TOGGLE SWITCHES 1/4" DIA.

SPST	D131	6A/125V	Solder	.57 .47
SPST	D132	6A/125V	Solder	.61 .51
SPDT	D129	6A/125V	Solder	.77 .67
mom-off-mom		3A/250V	Solder	
SPDT	D134	6A/125V	Solder	.77 .67
on-off-on		3A/250V	Solder	
DPDT	D133	6A/125V	Solder	.77 .67
DPDT	D135	6A/125V	Solder	.92 .82
on-off-on		3A/250V	Solder	
DPDT	D130	6A/125V	Solder	.92 .82
mom-off-mom		3A/250V	Solder	

MOMENTARY PUSHBUTTON SWITCHES 1/4" DIA.

SPST Nor Open DM1	3A/125V	Solder	.32 .27
SPST Nor Close DM2	3A/125V	Solder	.32 .27

ANY ORDERS LESS THAN 100, ADD 20¢ EACH

LEDs Red, Yellow, Green — \$12.00/100 \$10.00/1,000

DEMARC ELECTRONICS

P.O. Box 7215, Algonquin, IL 60102

Toll Free 877-655-6433

Fax 847-854-4434

CABLE BOXES

CUT MANUFACTURING COST!
WE ACCEPT SMALL ORDERS TOO.


SHEET METAL

20 GAUGE

SILK SCREEN

PRINTED

WITH YOUR CO. NAME

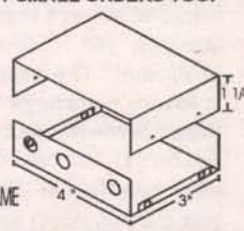

ALSO PCB, SMT, PROTOTYPES, ASSEMBLY,
PLASTIC MOLDS, INJECTION MOLDING

USA Office: V&V Mach. & Equipment, Inc.

Ph: (281) 397-8101, Fax: (281) 397-6220.

Mexico Plant: Marketing Tech.

Ph: 011 (525) 361-3351, Fax: 011 (525) 361-5996.

PLEASE VISIT OUR SITE

WWW.VANDVMACHY.COM

COVERT CATALOG 2000

BRAND NEW!

*The Latest, Up-to-date, Hands-on
Supplier and Source Guide for:*

- Electronic surveillance equipment
- Covert video cameras and transmitters
- Counter measures gear
- Entry supplies
- Electronic tracking systems
- Computer surveillance and remote viewing

Equipment, exact addresses and ordering info from 15 countries!! 220 pages — \$39.95

II 3555 S El Camino Real, San Mateo, CA 94403
Phone 650-513-5549 ■ fax 650-728-0525 or
www.intelligence.to (no ".dot com")

ASSEMBLY & ENGINEERING

Producible designs since 1970

Contract Engineering

Embedded Microprocessors
PCB Layout and Packaging Design
Analog Including RF to 1 GHz
Instrumentation
A/D and D/A

Contract Assembly

High-Speed Fuji Surface Mount
Through hole
Turn-key or Kit
Run sizes one through thousands
Test and burn-in available

Bilocon Corp.

800-736-5927

425-353-2276

www.bilocon.com

Stereo Microscopes for Large PC boards



9 in. arm for
Large boards
-10X & 30X
-Dust cover
-Eye guards
-5 year warranty
ST 231P — \$395.00



jlittle@netwizards.


3580 Haven Ave. Redwood City, CA 94063

650/367-8320 Fax 365-5845

CONTROL • MEASURE • INPUT

MODEL 40—\$109

- RS-232 interface
- 28 lines digital I/O
- Eight analog inputs
- PWM output
- Three stepper ports

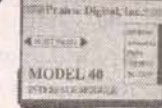

MODEL 100—\$279

- 12-bit 100KHz A/D • Four analog outputs
- Three timer counters • 24 digital I/O



PRAIRIE DIGITAL, INC.

920 SEVENTEENTH ST., INDUSTRIAL PARK

PRAIRIE DU SAC, WI 53578

TEL: (608) 643-8599 • FAX: (608) 643-6754

dmdsystems.com

- [electronic test & mfg]
- [test]
- [measurement]
- [rf/microwave]
- [specialized equipment]
- [computers]



DMD SYSTEMS RECOVERY, INC.
602 305-8485
fax 602 305 8490 • email info@dmdsystems.com

ASTRO TOO

Surplus/Electronics Equipment

Web Site: AstroToo.Com

E-Mail: Astro@AstroToo.Com

2854 Sarno Road
Melbourne, FL 32935

(407) 253-3371
Fax: (407) 727-1546

When visiting Central Florida,
come see us!
I-95, Exit 72

GRADE "A" CD RECORDABLE DISKS DIAMONDBACK CD-R

DISK TYPE	QTY	EA	SPINDLE
74 Min. 650MB (on spindle)	100	.79	Silver/Silver
80 Min. 700MB (on spindle)	100	\$1.29	Silver/Blue

- Excellent for Music and Data Integrity
- Reliable OEM Quality

Call Toll Free 1-(888) 967-8400

RISK FREE DISKS, INC.

— OUR 20TH YEAR —

www.riskfreedisks.com



softwarecloseouts.com

DOS - Windows - Win95
UNIX - MAC - Upgrades
Secure on-line ordering

softwarecloseouts.com

Corel Office 7 \$29
Norton Anti-Virus 2 \$5
Windows WGP 3.11 \$39
Office 4.2upg \$39

Up to 85% off titles by Symantec!

softwarecloseouts.com

New Arrivals Weekly!
Hard-to-find a specialty ...
We buy your surplus software.

softwarecloseouts.com

Doctor GB card / Xchanger

for Professional Game Developers

Doctor GB card is a Gameboy compatible ROM emulator FlashROM cartridge. It has built-in SRAM and supports MBC1 and MBC2 standards.



The advanced design of the Doctor GB card and Doctor GB Xchanger makes it easy for programmers and coders to burn a ROM file to the Doctor GB card. To transfer data into the Doctor GB card, the only requirements are the Doctor GB Xchanger, PC and our customized software. No need for expensive and difficult to use EEPROM burners.

www.UpstateGames.com

E-mail: sales@upstategames.com Fax: (716) 442-7223

P.O. Box 40184 Rochester, NY 14604 U.S.A.

ELECTRONICS

Q & A

With TJ Byers

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist.

Feel free to participate with your questions, as well as comments and suggestions.

You can reach me at:

TJBYERS@aol.com

TJBYERS@juno.com

*or by snail mail at
Nuts & Volts Magazine,
430 Princeland Ct.,
Corona, CA 92879.*

What's Up:

How about some **vintage car electrical fixes and upgrades** — two to be exact. How to get that buzzing bee out of your bonnet, or put a **neon lamp** in one. Don't understand my **schematics**? I'll tell you how to read them. Finally, let's **put Y2K fears to rest** — lots of suggestions and testing info.

Ready for the Holidays?

Check out these Web sites; I already have and I like them a lot.

Modem Tester Still Alive And Well

Q - In your Jan. '99 column, you referred to a Web page that had a modem speed test. That page is no longer there. Any idea where to find it or another modem speed test?

Jim WODIA
via Internet

A - This Web site (<http://homepage.tinet.ie/~leslie/testpage.htm>) is still valid, but AOL and other Internet servers stumble on it. Sometimes you get the message "file ... GIF could not be found" or "404 file not found." The best way to access this modem testing software is through Lycos. Simply bring up Lycos (<http://www.lycos.com>), type in "modem speed test" in the Search for box, and press Enter. The modem software specified in the column will be your first option. If you encounter an error message, either say OK or Cancel the error message and continue. If worse comes to worse, bail out and try again at a different hour. This is a very busy web site. It's strange that when I went searching for the perfect modem tester I had to really ferret out this software, which at the time was obscure. Since then, it's become the preferred choice and is highly recommended by computer specialists.

Vintage Car Low Fuel Lamp


Q - I am restoring a vintage car and I want to add a circuit to monitor the fuel level. The gas tank sender to the fuel gauge is about 250 ohms when empty and goes down to about 50 ohms when full. Obviously, the 12 volts goes through the meter and then to the variable resistor in the tank. Low ohms (full tank) gives a high reading and high ohms (empty) makes the meter read on the low or empty scale. I'm looking for a circuit that will turn on a light when the voltage drops to a certain point and stay on until the voltage rises (tank refills). I want to hook the monitor circuit across the meter and when the voltage drops down to whatever the 1/4 tank reading is, a light comes on as a reminder.

Frank Schwartz
via Internet

A - Your vintage gas gauge uses what's called a "hot wire" meter. The way it works is that there's a needle connected to a resistive wire — probably NiCr. As the wire heats up, it stretches in length which, in turn, causes the gas gauge needle to point towards FULL. As the fuel level drops, the current through the wire decreases and its length decreases — which causes the pointer to tend toward the EMPTY mark. The gas gauge and fuel tank resistance are balanced so that the needle spans the desired range. Now you know why the fuel gauge takes time to "warm" up to the right reading. Actually, this was intentional: A heated wire takes time to respond to level changes, which minimizes sloshing fluid levels in the tank.

What you need is a comparator circuit that triggers when the voltage across the level tank resistor reaches a certain level. As the tank empties, this voltage will increase, not decrease. When the trigger point is reached, the output of the comparator goes high and turns on the 2N2222 transistor — and the lamp. I don't know where you want the EMPTY light to trigger,

so you'll have to do that by rotating R1 to the desired spot. My guess is 7 volts, but that's only a guess. Run the tank down to the point where you want the lamp to light, and adjust R1 so that the lamp just goes on. R2 adjusts the hysteresis of the comparator. Hysteresis provides a dead-band where the voltage has to exceed a high voltage and low voltage to change the logic state of the comparator's output. This is needed to keep the lamp from winking on and off around the trigger point. Don't make the hysteresis too wide, or you'll have trouble turning the light off when the tank is filled. Again, you'll just have to experiment until you find the right setting. What's nice about this design is that these two adjustments aren't interactive like most comparator adjustments are, so the setting of one won't affect the other.

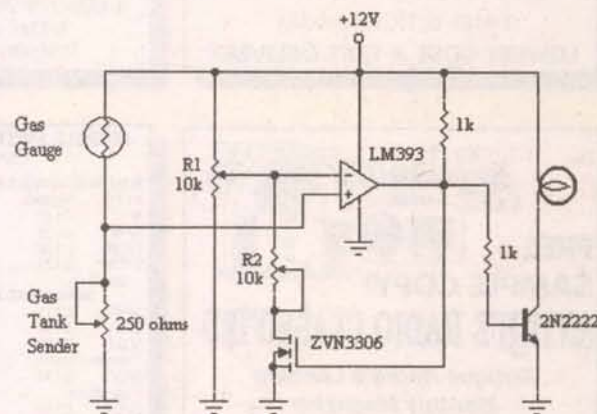


Neon Lamp High-Voltage Sensor

Q - I just read your column in the Aug. '99 issue. Your response to the question titled "Auto Tune-Up" came dangerously close to answering my question. I need some sort of inductive pick-up to detect the spark from a racing go-cart, that will provide a countable input to an Atmel microcontroller. I'm testing a circuit that uses a 100uH coil and op amp, but the coil is too large for the application. You mentioned using an "NE2H neon lamp coupled to a homemade optical sensor." Can you elaborate? Pointers? Web site? Any other inexpensive ideas?

Joe Knight
via Internet

A - Oddly enough, neon lamps don't need a direct connection to a voltage to light. Like fluorescent lamps, the presence of a high-energy field can cause them to glow. That's the idea behind this design. Place one lead close to a high-voltage source and ground the other, and you have light that can illuminate a photocell which, in turn, can trigger a logic circuit. The trick is in the light-to-photocell coupling, which is best done using white (not black) shrink tubing. Here's how the assembly looks.

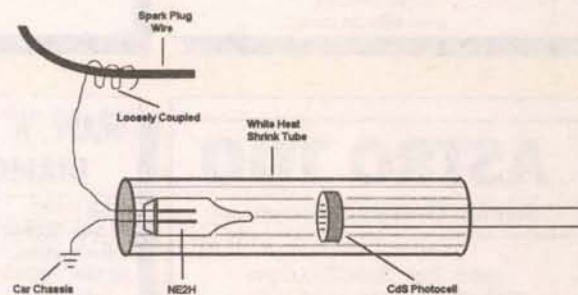


Place the NE2H and CdS photocell as close together as you can inside the shrink tube, crowding is allowed, then apply heat. This part of the operation is the most critical. Once done, wrap a couple turns of wire from one lead of the NE2 lead around the spark plug wire and return the other to ground. On the other end of this assembly, you're on your own. When the lamp lights, the resistance drops. As to how much depends on the CdS photocell. I've always used CdS photocells, but I don't see why a phototransistor won't work given the proper electrostatic precautions.

Ho Hummm ...

Q I recently bought a Leviton DHC X-10 Inductive Dimmer Switch module. The ad says it's designed for fans and other inductive loads. But when I tried it on my ceiling fan, it caused a loud, annoying hum. The hum is coming from the motor, and is loudest at high speeds. SmartHome's tech support said it's common in some fans, and offered to refund my money. But that leaves me without a speed controller. I'm considering replacing the triac inside the switch module with a Teccor "Alternistor." The description for this part says it has "been specifically designed for applications which are required to switch highly inductive loads, and has better turn-off characteristics than a triac." Would this improve the hum?

Randy Gamage
Rocklin, CA

A Most quality ceiling fans are operated by capacitors, which create distinct speed "steps" like high, medium, and low. Solid-state variable speed controllers use pulse-width modulation to create a speed control range from low to high. Capacitor and solid-state electronics are not completely compatible, which leads to the hum that you hear. For quiet fan operation, capacitor type fan controllers are required, which means upgrading to an Alternistor won't change a thing. The fan will still buzz. Fortunately, I was able to find this circuit, which was conceived and designed by Ed Cheung PhD, that uses an X-10 controller to switch the fan's speed with NO HUM!

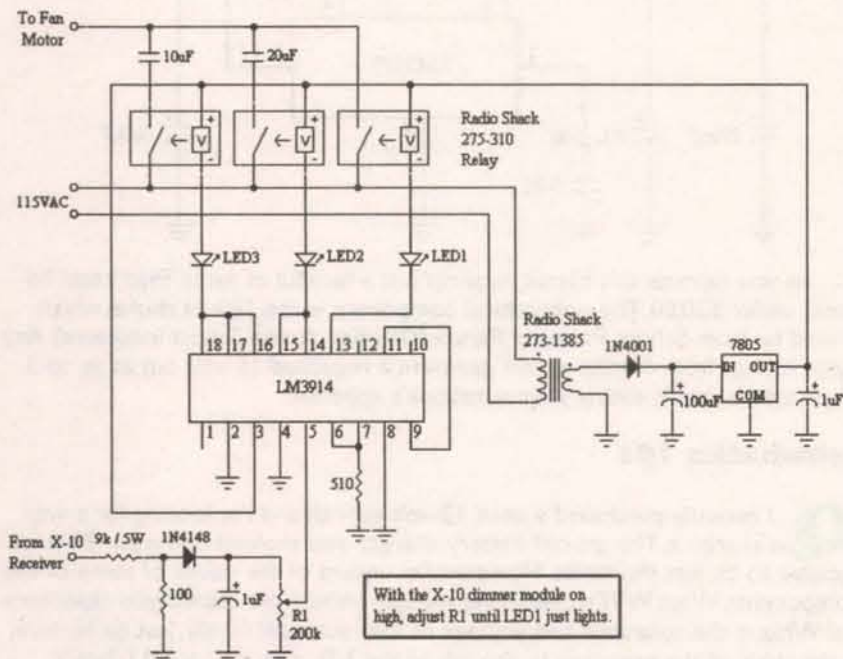

I've taken the liberty of streamlining the circuit just slightly, but essentially it's Dr. Cheung's design. (The original circuit can be found at http://www.mindspring.com/~dr_ed/automa/nohum.htm.) Basically, the circuit works by switching different-value capacitors in series with the motor winding — just like the pull-chain does. The opening and closing of the solid-state relays is controlled by an LM3914 dot display generator, the same kind used to indicate volume levels on audio equipment. As the voltage across the input (pin 5) increases the LEDs move up a linear scale. This voltage is derived from the output of an X-10 receiver, which doesn't have to be an inductive dimmer. A less expensive

lamp dimmer will work. There are 10 outputs from the LM3914 that can light up to 10 LEDs. What Dr. Cheung has done is wire the outputs to the "coil" of the relay, turning it on. The LEDs are used to indicate which relay is on at the time. To calibrate this circuit, turn on the dimmer to high, then adjust R1 so that LED1 just lights. Dimming the X-10 controller will cause LED1 to drop out and LED2 to light, indicating that a 20uF capacitor is now in series with the fan motor. The smaller the cap, which has to be 250V non-polarized mylar, the slower the fan spins. Don't attempt to use electrolytics in this circuit even if you place them back-to-back because the current draw may be too much for them and they will eventually pop like fire crackers. What I'd do is buy replacement caps from the manufacturer or (if you know what you're doing) remove the original caps from the fan and use them in this circuit.

Keep That Cool


Q I ask your pardon for taking advantage of you again, but when I sent you the last E-Mail asking questions about my vintage car project, I neglected to include an important one. Here's the problem: I am using two 12-volt automotive relays with SPDT contacts to activate two radiator fans that come on when the sensor in the radiator is closed (to ground). Each fan draws 7 amps and rather than have both come on at the same time, I was wondering what kind of circuit you could suggest that delays the second fan from coming on until two seconds later so that the total 14 amps isn't placed on the electrical system at the same time. First 7 amps, a two-second delay, and then the next 7 amps. Do you have a simple solution?

Frank Schwartz
via Internet

A Sorry, one question per customer ... just kiddin'. Actually, you have a legitimate concern here because what you're seeing isn't 14 amps when the fans kick on, but more like 140 amps of in-rush current. Have you ever noticed that when your refrigerator or dishwasher starts up, the lights dim slightly (actually, in my 1909 apartment, they go dark!). That's because everything from motors to lamps draw more current when they start than they do when humming along. There are two ways to curb this problem.

My first suggestion is to use an NTC (negative temperature coefficient) thermistor that's specifically designed to prevent high-current inrush. These devices, often called an inrush current limiter (ICL), have a high resistance when cold, and a lower resistance as they warm up. This characteristic limits the initial input current, but allows full current to flow after the thermistor warms up. Here's how it looks graphically.

Inrush Current

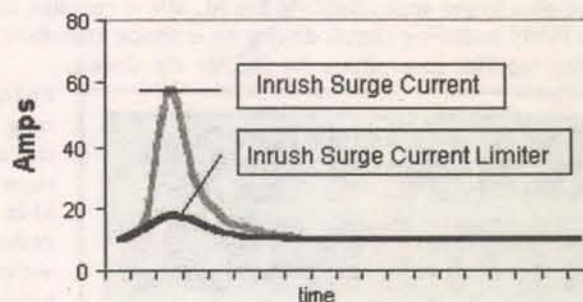

This solution is very cost-effective and available from many sources, including Digi-Key (1-800-344-4539; <http://www.digkey.com>), Mouser Electronics (1-800-346-6873; <http://www.mouser.com>), and even your

Catch The Bus

USB Relay Module

Control 8 to 16 "form C", 1 Amp relays

USB Opto Module

8 to 32 opto-isolated Inputs and Outputs

USB Digital Module

Industry standard 50 pin interface

USB Temperature Module

Measures temperature over multiple remote sensors

J-Works, Inc

12328 Gladstone St., Unit 4
Sylmar, CA 91342
(818) 361-0787 Voice
(818) 270-2413 Fax

Visit our Web site for free
information on all our products
<http://www.j-works.com>
E-mail sales@j-works.com

Write in 68 on Reader Service Card.

LASERS & ACCESSORIES

HELIUM NEON LASERS

- ☒ Complete Systems
- ☒ Plasma Tubes
- ☒ Power Supplies

ACCESSORIES

- ☒ Optics
- ☒ Electro-Optics
- ☒ IR Viewers
- ☒ Books & More


DIODE LASERS

- ☒ Visible / IR
- ☒ Complete Modules
- ☒ Collimating Optics
- ☒ Drive Circuits

FREE CATALOG

WEB SITE:

www.mi-lasers.com

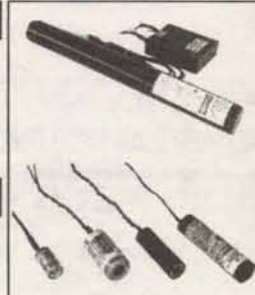

MEREDITH
INSTRUMENTS


Phone: 602-934-9387 • Fax: 602-934-9482

Write in 69 on Reader Service Card.

Nuts & Volts Magazine/NOVEMBER 1999 77

local appliance repair shop. All you have to do is match your 7-amp requirement to the steady-state current of the ICL.

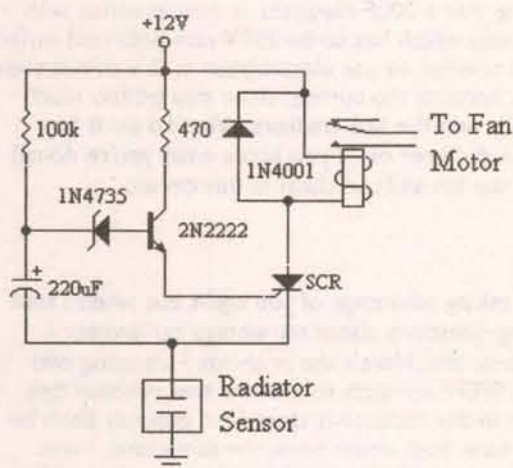However, if you still insist on sequencing the relays, the simplest solution I can come up with is an SCR in series with the second relay coil. Here's how it looks.



What I initially intended to do was a simple RC time constant to trigger the SCR's gates, until I looked at the specs. Guess what? Most SCRs need 20 mA of gate current to trigger. (Surprise, Surprise!) Using Ohm's Law, R1 has to be 550 ohms or less, which means we're going to have a humongous capacitor. Which is the reason I inserted the 2N2222. Even at its worse, it provides 100 hFE of gain — typically 300 hFE. (hFE is DC voltage gain as opposed to hfe, which is AC

voltage gain. Two different parameters.) That means we can scale down our calculations by a factor of 100, which I've kinda stabbed at. If you insert this circuit in line with the relay coil, it should provide a two-second delay, but don't quote me on that. At least I've put you in the ballpark, so experiment to find the optimum setting. Personally, I'd go with the ICLs.

A Real Sound Blaster Needs Power

Q My latest project is a 1kW audio power amp, but the only one I can find that's simple enough to build calls for a ± 85 -volt dual power supply. Can I just rectify the AC mains to obtain this voltage and, if so, how do I derive a common ground? I suppose I can use an isolation transformer to get these voltages, but these things weigh 31 pounds and cost nearly \$200.00. Is there any other means to power this beast?

Garry J. Iman
via Internet

A How about a dozen gel-cell batteries in series — or not? According to my calculations, the power supply must be capable of providing 6 amps at 170 volts — which is a very tall order. Fortunately, there is a simple solution called an off-line power supply — exactly the same kind used to power your desktop PC, but on a larger scale. Basically, the AC line is rectified and then processed by a PWM switching circuit driving an isolation transformer. The secondary is then rectified to produce the DC for the device.

Instead of running at 60 Hz, the switcher runs at 100 kHz, which reduces the weight and heat of the power supply. Because of the currents and voltages involved (the input power is equivalent to that used by a clothes iron), this isn't a project you want to take on without prior experience in winding large power transformers. I suggest you contact one of the following vendors. You might discover that it's cheaper to buy than build.

PRINTED CIRCUIT BOARDS

Since 1969

Prototype to Production
Quick • Quality • Service • Price

- Single Sided
- Double Sided
- Multi-Layer
- Surface Mount
- Punch Press Capability
- LPI

QUICK TURN AROUND
COMPLETE IN-HOUSE CAPABILITY

CIRCUIT ETCHING TECHNIQUES

Since 1969

700 Lee Street Phone: 847-228-1722
Elk Grove Village Fax: 847-228-1816
Illinois 60007 Modem: 847-228-6549
Toll Free: 888-657-3827

E-MAIL — CET@MET-NET.COM
WEB ADDRESS —
WWW.MET-NET.COM/USERS/CET

Astec America

1-888-412-7832

http://www.astec.com/

PowerQuotes

http://www.powerquotes.com/

Opt Industries

908-454-2600


http://www.optind.com/SinglePhase10_84.html

On The Road Again

Q I was wondering how difficult it is to make a DC adapter that converts 12 volts to 15 volts at 3 amps? It's for mobile use of a laptop, and I thought I could make one cheaper than buying (about \$100.00). What do you think? Obviously, I'm a rookie.

John D. McGuire
via Internet

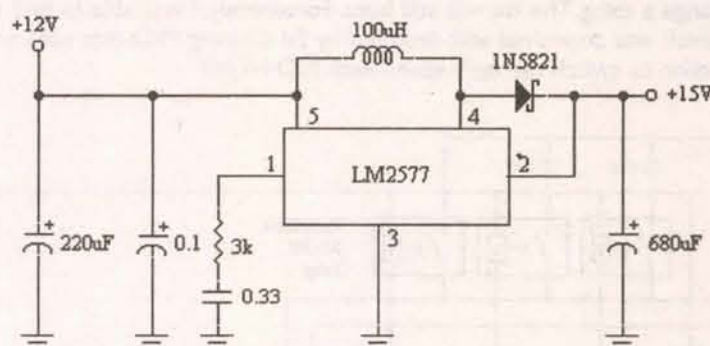A Missed my "Switching Voltage Regulator Basics" series (May & Jun. '99), eh? Check it out, because it has a wealth of information on voltage conversion regulators for "rookie" users like you, plus plenty of tips for the pros. Back issues are available. Meanwhile, I can show you how to do this cheaply using an LM2577-15.




As you can see, this circuit requires but a handful of parts. Total cost? I'd guess under \$20.00. The only critical component is the 100uH choke, which should be from Schott, Pulse, or Renco (Digi-Key stocks Schott inductors). Any input voltage from 5 volts up will generate a regulated 15 volt out at up to 3 amps, which should satisfy your notebook's appetite.

Schematics 101

Q I recently purchased a used 12-volt gel-cell and I'm looking for a way to charge it. The gel-cell battery charger you showed in the Jul. '99 issue appears to be just the ticket. However, I'm unsure of the values of some of the components. What WVDC (working voltage) should the electrolytic capacitors be? What is the tolerance and wattage of the resistors? Finally, just to be sure, is the value of the capacitor to the left of the 3.3k ohm resistor 0.1 farad?

John Crawford, Jr.
Hamburg, NY

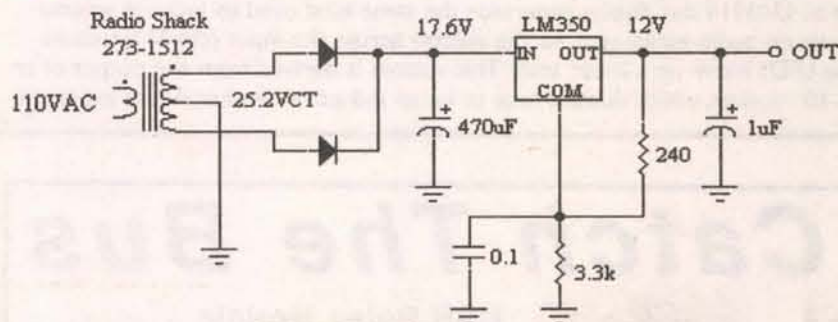A Okay, here's a quick lesson in reading schematics. Let's use the simple circuit below for this discussion.



This is a simplified version of the front end of the gel-cell charger shown in the Jul. '99 issue. First, the transformer, which reads 25.2VCT. That means 25.2 volts center tapped. The center tap is returned to ground, so there's 12.6 volts ($V = 25.2/2 = 12.6$) across each winding. The two diodes form a full-wave rectifier, the output voltage of which is 1.4 times that of the AC input voltage, or 17.6 volts ($V = 12.6 \times 1.4 = 17.6$). So the working voltage of the 470 uF capacitor has to exceed 17.6 volts. You absolutely want the WVDC of an electrolytic capacitor to be higher than the circuit voltage, but not excessively higher for reasons that go beyond this discussion. For this circuit, I'd choose a 35V capacitor, not the 50V or 100V version. This voltage is then input to the LM350 voltage regulator, where it's reduced to 12 volts. This means that a 1 uF, 16V electrolytic would be the perfect choice. Now about the capacitor to the left of the 3.3k resistor: It's a ceramic disk, which are typically rated at 50V. Unlike

electrolytics, any voltage above the working voltage is acceptable, which means the 100V version is perfectly okay. However, the physical size of the cap grows larger as the WVDC increases. As for the value, it's 0.1 uF — microfarad not farad. Capacitors with a schematic decimal value of 0.99 and lower are expressed in microfarads (uF). Values of 1.0 and beyond mean pF or uF, and are identified as such on the schematic. For example, the 470 uF cap on the above schematic; a smaller value cap would have said 470 pF.

About the resistors. Wattage is equal to voltage times current. Here you can use math to calculate the power dissipation ($P = E^2/R = 122 / 3300 = 144/3300 = .04$ watts). Unless indicated otherwise on the drawing, a 1/4-watt (0.25W) resistor will work. In many cases, so will a 1/8-watt (0.125W) resistor, but do your math first. If the value of the resistor is below 1k (1000 ohms), the nomenclature on the schematic is in ohms — like the 240-ohm resistor shown on our example. This normally includes values down to 0.1 ohms and below. Above 999.999k, the nomenclature reverts to 1M (one million ohms). The next step is 1B (1000M), one billion ohms. Beyond that, the only values you'll find higher (trillions of units) are the input impedance of an op amp and the national budget. In all but a few cases, resistor tolerance isn't an issue. Whatever RadioShack has on the shelf (typically 5%) is just fine. If tolerance is a critical factor, it will say so on the schematic. Now get off your duff and build that charger!

Y2K Woes

Q I'm worried about the Y2K syndrome. A while back you gave the Web site of a Y2K test program, but I've misplaced that issue. Can I have that address again?

Ruth McDougall
via Internet

A As the Millennium nears, I get more and more requests like this. Fortunately, the Internet is littered with Y2K test software, some better than others. Here are some of my favorites.

Microsoft: <http://www.microsoft.com/technet/year2k/pca/pca.htm>

PC Magazine: <http://www.zdnet.com/pcmag/special/y2k/>

PC World: http://www.pcworld.com/online_feature/1707/countdown2000/

ZD: <http://hotfiles.lycos.com/cgi-bin/texis/swlib/lycos/mlt.html?link=1&Utext=compliance+system+utilities+y2k+check+hardware+problem+file+application+program+&UTcat=utilities&UTsubcat=system+utilities>

Be Leery of Y2K Cassandra's

The following is directly from the pages of Microsoft's Web site.

TJ Byers
Q & A Editor

There is a hoax E-Mail in circulation on the Internet concerning the Y2K compliance of Windows 95, Windows 98, and Windows NT. There are various versions of this mail which resemble the text below:

"Every copy of Windows will fail on January 1st unless you fix it now, to fix it ..."

1. Click on "My Computer."
2. Click on "Control Panel."
3. Click on "Regional Settings."
4. Click on the "Date" tab. Where it says, "Short Date Sample" look and see if it shows a "two digit" year. Of course it does. That's the default setting for Windows 95, 98, and NT. This date RIGHT HERE is the date that feeds application software and WILL NOT rollover in the year 2000. It will rollover to 00.
5. Click on the button across from "Short Date Style" and select the option that shows mm/dd/yyyy. Be sure your selection has four Y's showing, not two.
6. Click "Apply" and then click on "OK" at the bottom. Easy enough to fix. However, every single installation of Windows worldwide is defaulted to fail Y2K rollover.

"Thanks and have a great day"

Facts about Windows 95, Windows 98, Windows NT, and Y2K ...

Microsoft Windows 95, Windows 98, and Windows NT are compliant assuming all recommended actions specified in the respective compliance documents have been taken. The steps above are not required actions and do not have to be performed in order to obtain compliance.

• The short date format style in Regional Settings is a display setting only.

• Dates are stored and processed by Windows in a four-digit format regardless of the short date format style selected in Regional settings.

AMAZING MICROVIDEO!

SUPERCIRCUITS.COM

America's #1 Microvideo Source

LIPSTICK VIDEO CAMERAS

**MICRO
COLOR
CAMERA
1" X 1"
350 TVL
\$89.95!!**

STEALTHY SUPER
PINHOLE
\$69.95

**FREE
CATALOG!
CALL US
TODAY
AND GET
YOURS!**

COLOR
\$149.95

WOW!

**FREE PLUG & PLAY CABLES
1 YEAR WARRANTY**

1 YEAR WARRANTY

STEALTHY SEE-IN-THE-DARK
WEATHERPROOF WITH 56
IR LED'S \$159.95

WIRELESS VIDEO

\$99.95

2.4 GHz AUDIO/VIDEO
TRANSMITTER, RECEIVER
W/ 700 FOOT RANGE
PART 15 FCC APPROVED

DIGITAL VIDEO RECORDER

480 HOURS RECORDING TIME, IBM
COMPATIBLE, 4 CAMERA SWITCHER

**COVERT CLOCK
RADIO CAM \$249.95**

**CCTV
VIDEO
CAMERA
\$79.95!**

SONY CHIPSET

1 YEAR WARRANTY

**WORLD'S SMALLEST!
LISTED IN 1999 GUINNESS
BOOK OF RECORDS**

AMAZING!

**MICRO
VIDEO
CAMERA
\$59.95!**

**WIRELESS
VIDEO**

**WORLD'S SMALLEST VIDEO
CAMERA & TRANSMITTER-
700 FOOT RANGE \$299.95
1 YEAR WARRANTY**

UNBEATABLE DEAL!

350 Lines of Resolution
**COLOR VIDEO
CAMERA-AUDIO,
PLUG & PLAY-
ONLY \$69.95!!**

CAP CAM \$149.95
GLASSES CAM
TIE CAM
BAG CAM
PAGER CAM

SONY GV-A500HI-8 VCR WITH
4" TFT MONITOR \$979.95

www.supercircuits.com

1-800-335-9777 ext. NV
Or fax us at 512-260-0444
www.supercircuits.com

Free Catalog- Call Us Today And Get Yours

1-800-335-9777

Write in 71 on Reader Service Card.

Nuts & Volts Magazine/NOVEMBER 1999 79

Customers can use the regional settings tab to adjust how the date is displayed (e.g., mm/dd/yy or mm/dd/yyyy).

In order to avoid ambiguous dates, Microsoft recommends using four digits when entering date data and expanding the date field in regional setting to four digits. However, this is not required to attain compliance.

Last Updated: Friday, August 20, 1999 - 11:30 a.m. Pacific Time
©1999 Microsoft Corporation. All rights reserved.

Holiday Helpers

The holidays will soon be upon us, and our thoughts turn to what else, feasts. However, if you're growing bored with the same old holiday fodder, check out these Web sites for fresh fare.

SOAR — <http://soar.berkeley.edu/recipes/>
Searchable database for recipes

ChefTalk — <http://www.chef-talk.com/>
Tips from the pros

FoodLines — <http://www.foodlines.com/>
For People Who Have A Passion For Food!

The Taste Of The Web — includes links to other sites (low air fare, etc.)
<http://www.epicurious.com/>

Mixed-Drink.com — <http://www.mixed-drink.com/>
Shaken or Stirred?

The Ultimate Undo

If you frequently install new software, change system settings, or delete a lot of files, Windows can easily become corrupted — a situation that often brings your system to its knees. Don't you wish you could turn the calendar back to just before this happened? Well now you can. Three Windows utilities claim to do just that.

WildFile's GoBack (1-888-945-3345; <http://www.goback.com>) monitors your operating system and records any changes to your hard drive. Should you find yourself in the Twilight Zone, you can get out of trouble by simply turning back the "clock" to a time before the problem occurred. GoBack also lets you restore a specific file instead of the whole system. Moreover, it can restore the system even when Windows won't boot.

PowerQuest's SecondChance (1-800-379-2566; <http://www.powerquest.com/usindex.html>) works by taking periodic (both automatic and manual) snapshots of your system. You can name each snapshot, then choose the one you think is best when the crash occurs. This is a great feature because not all problems are immediately noticeable, and the ability to select from more than one time frame is a big plus. The program prompts you when you run out of disk space, thus allowing you to delete old snapshots before it's too late. However, SecondChance cannot undo changes made in DOS like GoBack can.

Unlike GoBack and SecondChance, which monitor your system and record the changes on the hard drive, Duomark's 9Lives (310-493-7711; <http://www.duomark.com/9Lives>) works by creating a folder called C:\9LIVES. When new software is installed, the newly loaded software and system changes are saved in this folder. This allows you to inspect the new software to see if it works properly. If it does work as advertised, simply click on the 9Lives icon and reboot the PC; if it doesn't work or is causing problems, get rid of it using another 9Lives button.

You can download demo versions of all three programs by going to the Web sites listed above. The cost of GoBack and SecondChance is \$69.95, whereas 9Lives sells for \$49.95. All three companies also offer free Y2K system checking software.

TJ Byers
Q & A Editor

MAILBAG

I just read your reply to Jim Allen in the Oct. '99 issue and, as an "expert" (35 years in the satellite design field), I have several problems with your response.

First DSS (Digital Satellite System) is a trademark of Hughes; other systems are known as DBS (Direct Broadcast Systems). However, Jim Allen is using a 10-foot antenna that is neither of these systems but rather on a TVRO (TV Receive Only), which is either C or K band, and until recently was using exclusively analog TV signals. Neither of these systems use circular polarization, but use orthogonal linear polarization, H or V. Usually adjacent channels use different polarizations to prevent interference. The receive antenna is sent a signal from the receiver to select the proper polarization. A fine adjust is provided to compensate for polarization shift in the atmosphere. The only satellites now using CP are the Intersats. These were indeed spin stabilized satellites, but the spin has nothing to do with the polarization used. Using CP does allow for separation (LHCP and RHCP) and the receive antennas do not need fine polarization tracking. All of the present satellites are three-axis stabilized, and can indeed guarantee either horizontal or vertical polarization.

Incidentally, circular polarizations as generated by combining two linear polarizations in quadrature phase one-quarter wavelength apart in space. The "spin rate" is at the RF carrier frequency and has nothing to do with the satellite's spin.

Hope this clears up some more misconceptions you may have inadvertently perpetuated.

Virg Wall K6EVE
Los Angeles, CA

Response:

I thank you for finally capsulating what I've been trying to say over the last few months — a bite at a time. H and V polarization is not LHCP or RHCP, despite what most DSS and DBS retailers would have you believe (RadioShack frustration!). It's one of the those great myths of satellite TV. Furthermore, DSS is DBS, but neither are TVRO. Hooray, and thanks!

TJ Byers
Q & A Editor

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

Modern Communications • (405) 691-0594 TEL & FAX

Converters

Converters:	10	50	100
Panasonic: TZPC-175	\$49.00	\$45.00	\$39.00
Panasonic: TZPC-145	\$45.00	\$39.00	\$35.00
Centurion CF-3000 (NEW)			
True 99 Channel	\$65.00	\$60.00	\$55.00
Regal: CR-83	\$39.00	\$35.00	\$32.00
Remotes:			
Jerrold: 400, 450, 550	\$4.50	\$4.00	\$3.75
CFT: 2XXX	\$4.95	\$4.50	\$4.25
S/A: 175, 475	\$4.95	\$4.50	\$4.25
S/A: 8600 Display	\$4.95	\$4.50	\$4.25
Panasonic: 170, 175	\$4.95	\$4.50	\$4.25
Zenith (ALL)	\$4.95	\$4.50	\$4.25
Pioneer (ALL)	\$4.95	\$4.50	\$4.25
Tocom 5503-VIP	\$4.95	\$4.50	\$4.25
4-in-1 Universal	\$5.95	\$5.50	\$5.25



Parts, Parts, Parts

	10+	50+	100+
PIC16C622	\$3.15	\$2.95	\$2.75
PIC16C54RC/P	\$2.15	\$1.95	\$1.75
PIC16C56RC/P	\$2.15	\$1.95	\$1.75
Micro 68H705C8P	\$6.50	\$6.15	\$5.95
4 MHz (Resonator 2 pins)	\$0.45	\$0.40	\$0.35
4 MHz (3 pins)	\$0.45	\$0.40	\$0.35
Crystal: 117, 119	\$3.75	\$3.50	\$3.25
18 pin IC Socket	\$0.15	\$0.12	\$0.10
Toggle Switch on/on	\$0.95	\$0.85	\$0.75

Call for Larger Quantity Quotes

Remotes

Converters ★ Remotes ★ Converters ★ Remotes ★ Converters ★ Remotes

HOW TO PLACE A CLASSIFIED AD

TYPE or PRINT your **ELECTRONICALLY RELATED** ad copy **CLEARLY** (not all caps) on a separate piece of paper. Spell out words when submitting handwritten copy. Calculate the number of words and multiply it by the appropriate rate (see RATE PER WORD section). Include any charges for **bold** and/or **CAPPED** words, any artwork costs that would be applicable, and/or costs for boxing your ad (explained below). Choose the appropriate classification for your ad(s) to appear in (see below). If no classification is indicated, it will be placed in Misc. Electronics or wherever we deem most suitable. **Enclose your name, address, phone number, and Nuts & Volts account number from your mailing label** (if available) for identification purposes. Include full payment — **CLASSIFIEDS RUN ON A PRE-PAID BASIS ONLY** — and mail your completed order to:

NUTS & VOLTS MAGAZINE, 430 Princeland Ct., Corona, CA 92879.

RATE PER WORD

The ad rate for **current PAID subscribers** is **60¢** per word. All others pay **\$1.20** per word. There is a **\$9.00 minimum** charge per ad per insertion.

WORDS IN BOLD AND/OR ALL CAPS

Words to be set in **bold** or **CAPS** are each **10¢** extra PER WORD. **BOLD CAPS** are **20¢** extra per word. The first two words of each ad are bold capped at no charge. Indicate bold words by underlining. Words normally written in caps (e.g., IBM) and accepted abbreviations such as VAC or MHz are NOT charged as all cap words. Use a two-letter abbreviation for states.

PHOTOS, DRAWINGS, AND BOXES

A photo or drawing may be run at the top of your classified ad for an additional **\$10.00** (1" depth max.) for camera-ready art. No wording is allowed in this area. Add a one-time charge of **\$5.00** to enlarge, reduce, or duplicate line

art, or **\$8.00** for halftone of photographs. To **BOX** your ad, include an additional **\$50.00** for copy-only ads, or **\$75.00** for ads with art or photos.

FAXING IN AD COPY

You may fax in ad copy or changes before the closing date (5:00pm on the **5th**) at 909-371-3052 using MasterCard or Visa. Include credit card expiration date, the name that appears on the card, a daytime phone number, and your **Nuts & Volts** account number. Ads without credit card information will not be listed as received until payment is received in full. **WE DO NOT CALL OR FAX BACK VERIFICATION OR QUOTES OF FAXED-IN ADS.** For verification of faxed-in ads, please call 909-371-8497.

DEADLINE

Prepaid ads received by 5:00pm on the **closing date (5th of the month)** will appear in the following month's issue. Ads postmarked through the **5th**, but received after the closing date, will be placed in the next available issue. No cancellations or changes after the 5th. Cancellations and changes must be submitted in writing.

IMPORTANT INFORMATION

All classified ads are running copy only. No special positioning, centering, dot leaders, extra space, etc. is allowed. All advertising in **Nuts & Volts** is limited to **electronically related items ONLY**. All ads are subject to approval by the publisher. We reserve the right to reject or edit any ad submitted. We do not take ad copy or changes over the phone. We do not bill for classified ads. Repeat ads or ads run in multiple classifications within the same issue are allowed. Paid subscribers may run ads at the 60¢ rate only through their subscription expiration date. **NO REFUNDS.** Credit only. No credit for typesetting errors will be issued unless you **clearly** print or type your ad copy.

Choose a category for your ad from the classifications listed below.

10. Ham Gear For Sale	80. Test Equipment	120. Components	155. Manuals/Schematics Wanted
20. Ham Gear Wanted	85. Security	125. Microcontrollers	160. Misc. Electronics For Sale
30. CB/Scanners	90. Satellite Equipment	130. Antique Electronics	170. Misc. Electronics Wanted
40. Music & Accessories	95. Military Surplus Electronics	135. Aviation Electronics	175. BBS & Online Services
50. Computer Hardware	100. Audio/Video/Lasers	140. Publications	180. Education
60. Computer Software	110. Cable TV	145. Robotics	190. Business Opportunities
70. Computer Equipment Wanted	115. Telephone/Fax	150. Plans/Kits/Schematics	200. Repairs/Service

ADVERTISER'S INDEX

Abacom Technologies17	EDS72	M2L Electronics50	Saelig Company89
ABC Electronics61	E.H. Yost & Co.64	Matco, Inc.74-75	Sam's Electronics60
ACP Super Store58	Electro Mavin64	Meredith Instruments77	Scott Edwards Electronics, Inc.60
ActiveWire, Inc.74	Electro Science Applications, Inc.63	Metric Equipment Sales, Inc.71	Seabird Technical75
Alfa Electronics36	Electro Tool, Inc.39	microEngineering Labs19	Sescom, Inc.74
All Electronics Corporation38	Electronic Products74	Micromint69	Shreve Systems15
Allison Technology Corporation61, 74	EMAC, Inc.41	Midland Technologies74	SiGEM74
Alltech Electronics27	EPS75	Milestone Products68	Skycraft Parts & Surplus, Inc.59
Alltronics24	Equipment Management Technology53	Modern Communications80	softwarecloseouts.com75
Andromeda Research18	Excess Solutions61	Mouser Electronics22	Square 1 Electronics41
Antique Radio Classified75	ExpressPCB90	Mr. NiCd64	SuperCircuits79
AST Global Electronics16	Foss Warehouse Distributors73	MSC Electronics75	Surplus Traders73
Astro Too75	Fusion Electronic Security55	Netcom23	Techniks, Inc.74
Baylin Publications47	Gateway Electronics, Inc.31	Norcomm20	Technological Arts51
Bilocon Corp.75	General Device Instruments73	Optoelectronics4	Technology Electronics, Ltd.73
Bitz Technology73	Gibraltar Trade Center, Inc.37	OS Systems8	Telulex, Inc.14
Brigar Electronics50	Globaltech Distributors74	Parallax, Inc.Back Cover	Test Equipment Plus41
C & S Sales, Inc.62	Halted Specialties Co.3	PARAMAX, INC.59	The RF Connection22
C and H Sales Company37	H.T. Orr Computer Supplies56	Patco Service, Inc.8	Timeless Products56
Chicago Circuits Corporation17	Hyatt Electronics51	PCB Express, Inc.75	Timeline, Inc.55
Circuit Etching Technics78	Information Unlimited85	PCW, Inc.58	Unicorn Electronics71
Circuit Specialists, Inc.94	Inkjet Southwest57	Phelps Instruments53	Upstate Games75
Consumertronics36	Intek Electronic Systems42	Pioneer Hill Software60	USI Corp.39
Corby39	intelligence75	Polaris Industries11	V&V Mach. & Equipment, Inc.73-75
Corporate Systems Center2, 95	Intronics, Inc.58	Power Quality, Inc.73	Velleman67
Cunard Associates59	Jade Products, Inc.73	Prairie Digital, Inc.75	Vesta Technology, Inc.74
Davilyn Corp.42	Jameco Electronics9	Pulsar, Inc.47	Visitect, Inc.40
Decade Engineering74	Jam RF52	Quality Kits74	Weeder Technologies63
DeMar Electronics75	Junkware.com74	R & S Surplus21	Western Test Systems34-35
DesignNotes.com63	J-Works, Inc.77	Ramsey Electronics, Inc.33	Winford Engineering73
Digital Products Company74	La Paz Electronics Int'l.58	R.E. Smith74	Worldwyde73
Direct Factory Supply, Inc.69	Lemos International Co., Inc.27	Resources Un-Ltd.28-29	
DMD Systems Recovery, Inc.75	Linear Systems19	Risk Free Disks, Inc.75	
Earth Computer Technologies40	Lynxmotion, Inc.18	Roger's Systems Specialist32	

AMATEUR RADIO & TV

Alltronics	24
Astro Too	75
Gateway Electronics, Inc.	31
Jade Products, Inc.	73
Lemos International Co., Inc.	27
Matco, Inc.	74-75
Norcomm	20
Ramsey Electronics, Inc.	33
The RF Connection	22

ASSEMBLY SERVICES

Bilcon Corp.	75
--------------	----

BATTERIES/CHARGERS

Cunard Associates	59
E.H. Yost & Co.	64
Globaltech Distributors	74
Jade Products, Inc.	73
Mr. NiCd	64
Power Quality, Inc.	73

BUSINESS OPPORTUNITIES

Corby	39
Intek Electronic Systems	42

BUYING ELECTRONIC SURPLUS

ABC Electronics	61
Alltech Electronics	27
C and H Sales Company	37
Earth Computer Technologies	40
EPS	75
Equipment Management Technology	53
Excess Solutions	61
Intek Electronic Systems	42
Metric Equipment Sales, Inc.	71
Roger's Systems Specialist	32
Skycraft Parts & Surplus, Inc.	59
Timeline, Inc.	55

CABLE TV

Direct Factory Supply, Inc.	69
Foss Warehouse Distributors	73
Milestone Products	68
Modern Communications	80
PCW, Inc.	58
Sam's Electronics	60
Timeless Products	56
Worldwide	73

CB/SCANNERS

USI Corp.	39
-----------	----

CCD CAMERAS/VIDEO

Circuit Specialists, Inc.	94
Decade Engineering	74
Fusion Electronic Security	55
Matco, Inc.	74-75
MSC Electronics	75
Polaris Industries	11
Ramsey Electronics, Inc.	33
Resources Un-Ltd.	28-29
Seabird Technical	75
SuperCircuits	79
Timeline, Inc.	55
USI Corp.	39

COMPONENTS

Chicago Circuits Corporation	61
Circuit Etching Technics	78
Electronic Products	74
EPS	75
Excess Solutions	61
Hyatt Electronics	51
Jameco Electronics	9
La Paz Electronics Int'l.	58
Linear Systems	19
OS Systems	8
Pulsar, Inc.	47
SiGEM	74
Skycraft Parts & Surplus, Inc.	59
Unicom Electronics	71
Visitec, Inc.	40

COMPUTER

Hardware	
ACP Super Store	58
ActiveWire, Inc.	74
Allison Technology Corp.	61, 74
Alltech Electronics	27
Consumertronics	36
Corporate Systems Center	2, 95

DMD Systems Recovery, Inc.	75
Earth Computer Technologies	40
Electro Mavin	64
General Device Instruments	73
Gibraltar Trade Center, Inc.	37
Halted Specialties Co.	3
Jameco Electronics	9
La Paz Electronics Int'l.	58
Risk Free Disks, Inc.	75
Roger's Systems Specialist	32
Shreve Systems	15
Techniks, Inc.	74
Upstate Games	75

Software

Electro Science Applications, Inc.	63
Gibraltar Trade Center, Inc.	37
Globaltech Distributors	74
Pioneer Hill Software	60
softwarecloseouts.com	75
Winford Engineering	73

Microcontrollers / I/O Boards

EMAC, Inc.	41
Jameco Electronics	9
Junkware.com	74
La Paz Electronics Int'l.	58
Micromint	69
OS Systems	8
Parallax, Inc.	Back Cover
PARAMAX, INC.	59
Prairie Digital, Inc.	75
R.E. Smith	74
Scott Edwards Electronics, Inc.	60
Square 1 Electronics	41
Technological Arts	51
Vesta Technology, Inc.	74
Winford Engineering	73

Printers/Printer Supplies

H.T. Orr Computer Supplies	56
Inkjet Southwest	57

DESIGN/ENGINEERING SERVICES

Chicago Circuits Corporation	61
DesignNotes.com	63
Electro Science Applications, Inc.	63
ExpressPCB	90
Midland Technologies	74
Prairie Digital, Inc.	75
Pulsar, Inc.	47
V&V Mach. & Equipment, Inc.	73-75

EDUCATION

Electro Science Applications, Inc.	63
EMAC, Inc.	41

EVENTS/SHOWS

ACP Super Store	58
Gibraltar Trade Center, Inc.	37

KITS

Alltronics	24
C & S Sales, Inc.	62
Digital Products Company	74
Earth Computer Technologies	40
Electronic Products	74
EMAC, Inc.	41
Gateway Electronics, Inc.	31
Information Unlimited	85
Inkjet Southwest	57
Jade Products, Inc.	73
Quality Kits	74
Ramsey Electronics, Inc.	33
Scott Edwards Electronics, Inc.	60
SiGEM	74
Technology Electronics, Ltd.	73
USI Corp.	39
Velleman	67
Weeder Technologies	63

LASERS

Information Unlimited	85
Meredith Instruments	77
Resources Un-Ltd.	28-29
Unicom Electronics	71

MISC./SURPLUS

All Electronics Corporation	38
Alltech Electronics	27
Brigard Electronics	50
C and H Sales Company	37
Consumertronics	36
DeMar Electronics	75
EPS	75
Equipment Management Technology	53
Excess Solutions	61
Halted Specialties Co.	3
Hyatt Electronics	51
Jam RF	52
Linear Systems	19

FIND
what you need . . .
FAST
BY PRODUCT OR CATEGORY

PCB Express, Inc.	75
Power Quality, Inc.	73
Resources Un-Ltd.	28-29
Shreve Systems	15
Skycraft Parts & Surplus, Inc.	59
Surplus Traders	73
Timeline, Inc.	55
Unicom Electronics	71
Visitec, Inc.	40
Weeder Technologies	63

PROGRAMMERS

Andromeda Research	18
Electronic Products	74
General Device Instruments	73
Intronics, Inc.	58
M2L Electronics	50
microEngineering Labs	19
Upstate Games	75

PUBLICATIONS

Antique Radio Classified	75
Consumertronics	36
intelligence	75
Mouser Electronics	22
Netcom	23
Square 1 Electronics	41

RF TRANSMITTERS/RECEIVERS

Abacom Technologies	17
---------------------	----

ROBOTICS

Astro Too	75
Lemos International Co., Inc.	27
Lynxmotion, Inc.	18
OS Systems	8
PARAMAX, INC.	59
SuperCircuits	79

SATELLITE

Baylin Publications	47
Milestone Products	68
SiGEM	74
Worldwide	73

SECURITY

Bitz Technology	73
Fusion Electronic Security	55
Information Unlimited	85
intelligence	75
Lemos International Co., Inc.	27
Matco, Inc.	74-75
MSC Electronics	75
Norcomm	20
Polaris Industries	11
SuperCircuits	79
Visitec, Inc.	40

SOLAR EQUIPMENT

STEPPER MOTORS

Alltronics	24
PARAMAX, INC.	59

TELEPHONE

Digital Products Company	74
Globaltech Distributors	74
Telulex, Inc.	14
Weeder Technologies	63

TEST EQUIPMENT

ABC Electronics	61
Alfa Electronics	36
Allison Technology Corp.	61, 74
AST Global Electronics	16
Astro Too	75
C & S Sales, Inc.	62
C and H Sales Company	37
Circuit Specialists, Inc.	94
Davilyn Corp.	42
DesignNotes.com	63
Digital Products Company	74
DMD Systems Recovery, Inc.	75
EDS	72
Electro Tool, Inc.	39
Equipment Management Technology	53
Intronics, Inc.	58
J-Works, Inc.	77
Metric Equipment Sales, Inc.	71
Optoelectronics	4
Phelps Instruments	53
Pioneer Hill Software	60
Power Quality, Inc.	73
Prairie Digital, Inc.	75
R & S Surplus	21
Saelig Company	89
Seabird Technical	75
Sescom, Inc.	74
Telulex, Inc.	14
Test Equipment Plus	41
Western Test Systems	34-35

TOOLS

C & S Sales, Inc.	62
Electro Tool, Inc.	39
Hyatt Electronics	51
Patco Service, Inc.	8
The RF Connection	22

WIRE/CABLE & CONNECTORS

Roger's Systems Specialist	32
The RF Connection	22

Questions & Answers

TECH FORUM

This is a READER TO READER Column. All questions AND answers will be provided by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. All questions submitted are subject to editing and will be published on a space available basis if deemed suitable to the publisher. All answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

QUESTIONS

Does anyone know of a good reference book or where I might find any kind of information on troubleshooting strobe lights that work off of the 12-volt system in a vehicle?

11991 Charles
via Internet

I have a robotics project that has a 12-volt system. I need to reduce the voltage to 4.8 and 9.6 volts to run servos and accessories. Also, the main drive motors when activated, lurch forward and peel out.

I need a way to reduce the voltage to three volts, then gradually increase to 12 volts over five seconds. I would like the five seconds to be adjustable, if possible.

11992 Chad Giddings
Spokane, WA

I need hook-up schematics of E-Lab's serial-to-parallel interface (EDE 1400) and parallel/serial transceiver (EDE 300) to interface a three-wire serial input to parallel printer.

11993 Terry K. Laraway
Bremerton, WA

I need a source and supplier (company name or distributor address and fax number) for electronic radio tubes.

I repair and restore old radios and the tubes are difficult to find.

11994 Lloyd H. Berg
Ontario, Canada

I have a nice generator that I would love to get working again, if possible. This was given to me by a friend, who found the generator (taken apart) at a yard sale. I have since rebuilt the engine.

This generator is an AC/DC generator/starter. The generator is suppose to start the engine, then start generating power.

The manufacturer seems to be out of business.

The generator appears as if it was used in a motor home (RV) because it is an AC/DC type generator, used for giving light, as well as charging the motor home's battery (I think).

Here is all the information that is available.

Manufacturer's name: Ralph Electric Plants, Inc. Last known

Send all material to **Nuts & Volts Magazine**, 430 Princeland Court, Corona, CA 92879, OR fax to (909) 371-3052, OR E-Mail to forum@nutsvolts.com

address: Chula Vista, CA. Model# PKN, serial# 76091980U, spec.# 542510. Color: aqua, more a bluish metallic look. Ratings: AC 3KW at 110 volts; DC 12 volts at 3 amps, DC amps at starting mode unknown. Engine: Techumsie 7 HP tapered shaft, all cast iron block. Age: very old, possibly 20 years plus.

The armature/rotor is two in one. It has a serrated commutator and slip rings. The slip rings are the AC and the commutator is for the DC.

The field/stator has four leads coming out from the windings. Two leads are heavy gauge wire that I think are used for the DC, and the other two are thinner and used for the AC. (Maybe the heavy gauge wire is needed for the starting of the generator.)

I need some information on how to wire this back together to make it work again, or who was the manufacturer for this generator.

11995 Ray Samples
via Internet

Does anyone know of a product that can block Caller ID in Australia? When I make a call, I don't want the other party to see my phone number on their GSM digital cellular phone display. I have 30 analog lines.

11996 Joe Dooman
Australia

I need information and sources for the following components.

1. Volume control double 50K to mixer Gemini PMX2000.

2. SVI 3206 integrated circuit for amplifier (Technics).

11997 Rodrigo Paba
Holtville, NY

I want to experiment with varying light intensities using ordinary household light bulbs.

I need a circuit that will automatically and very slowly, cycle voltage up and down between 60 VAC (or so), and 120 VAC, taking as much as 20 minutes to go all the way up and as much as 30 minutes to go all the way down. This rate should be adjustable to as fast as eight minutes in each direction to cover the maximum voltage span.

The low-voltage limit must be

adjustable higher to establish preferred minimums.

Ideally, a variety of cycle and ramping patterns could be experimented with, where 1) the high limit and low limit would automatically shift each cycle; 2) the rate of change could stop and hold, for variable lengths of time, at various plateaus before continuing on. The more adjustability, the better.

11998 Edgar Montgomery
Los Angeles, CA

ANSWERS

ANSWER TO #109912 - OCT. 1999

I need program code numbers and instructions for extended transmit frequencies for my Dai AT-600 dual band transceiver.

To expand the frequency coverage of your ADI handheld, try the following: press function O, then enter the code 14623, the radio will beep, but the display will show no response; then enter 11289, the radio will beep and display "key ok ver ????"

This works on my HT 204 (not tried on at 600). It will still not transmit in the 800-900 range.

Anonymous
via Internet

ANSWER TO #109910 - OCT. 1999

Need pinouts for the Sony HVM-302 Watchman Camera?

It should be 6V DC positive, negative, audio, and video.

This first camera in the Watchcam series set a standard for quality performance and small size. It was the first of the now-common miniature, quality video cameras typically used for surveillance.

The HVM-302 was popular about 15 years ago when it came out, and thousands are still in use today. Believe it or not, this camera used a "tube," but still offered small size and low-current drain.

The camera has a 1/2" Saticon tube, with an 11mm F1.8 fixed focus, auto-iris lens. Sensitivity was 5 lux. The connector is a four pin, unique to this series — as far as I am aware.

If you look at the camera's connector (as opposed to the cable),

ANSWER INFO

- Include the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed.
- In most cases, only one answer per question will be printed.
- Your name, city, state, and E-Mail address, (if submitted by E-Mail), will be printed in the magazine, unless you notify us otherwise with your submission.
- Due to space limitations, we can not reprint the original questions with the answer. The question number and the issue it appeared in are printed above the answer.
- Unanswered questions from a past issue may still be responded to.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

QUESTION INFO

TO BE CONSIDERED FOR PUBLICATION

All questions should relate to one or more of the following:

- 1) Circuit Design
- 2) Electronic Theory
- 3) Problem Solving
- 4) Other Similar Topics

INFORMATION/RESTRICTIONS

- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions may be subject to editing.

HELPFUL HINTS

- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Write legibly (or type). If we can't read it, we'll throw it away.
- Include your Name, Address and Phone Number. Only your name will be published with the question, but we may need to contact you.

with the key up, you will have four pins as follows: straight up (under the key) pin 1, 6VDC in; pin at 3 o'clock, pin 2, video out; pin at 6 o'clock, pin 3, common ground (power and signal); pin at 9 o'clock, pin 4, audio out.

Video out is composite, 1V P-P into 75 ohms, negative sync. Audio out is -5 dB into 10K ohms, or 450 mV RMS.

The camera draws approximately one watt with the auto iris open.

If you happen to have the official Sony cable, and you cannibalize it, the internal wires correspond to the

above as follows:

White	DC in
Blue shielded	Audio out
Plain shield	Common ground
Red shielded	Video out

Note that the camera will run fine long term on 12 VDC, but the companion FDM-402 monitor must not be connected to greater than 6 volts.

Steve Uhrig
Street, MD

ANSWER TO #99912 - SEPT. 1999

I bought a Toshiba T4600C notebook computer at a local hamfest. How can I bypass the power-on password?

I had the same problem on my Toshiba Tecra 500CS. The trick is, when asked to specify the password, simply press the "Esc" key. This works on most systems operating on Windows 95.

Thomas Ng
San Jose, CA

ANSWER TO #10999 - OCT. 1999

Need schematic/parts list/parts placement list for a Gateway Monitor CS11572FS. Also identity to part number 3H 15DFB.

I have horizontal waves traveling up the screen.

The Gateway Monitor with the grey line moving up the screen every four seconds is poor power supply filtering.

You are seeing the result of the 60 Hz AC power line being allowed into the monitor power circuits. This beats with the 59-3/4 Hz vertical sync frequency, and causes the grey bar to scroll up the screen taking four seconds to complete the cycle.

60 Hz - 59 3/4 Hz = 1/4 Hz, or one complete cycle every four seconds. The first place I would check is the electrolytic capacitors in the power supply.

It is likely they are not doing an adequate job of removing the 60 or 120 Hz ripple (depending on whether it is halfwave 60 Hz ripple, or fullwave 12 Hz ripple) before it gets to the voltage regulating circuitry.

If the ripple minimum voltage i.e., the valleys of the DC voltage is too low, this ripple is passed onto the power bus in the monitor where it beats with the vertical sync frequency.

The filter capacitor on the primary rectified source can fail to maintain this voltage above the voltage regulating minimum voltage, and when the AC ripple on the DC lines drops below the regulating voltage of the voltage regulating devices, which occurs on each alternating cycle of the AC Power.

Replacing this filter capacitor will hold the voltage between cycles from dropping below the minimum regulat-

ANSWERS TO #109913 - OCT. 1999

I'm using a Bearcat BC235XLT "Trunk Tracker" portable scanner with a (BNC) rubber duck.

I would like to experiment with used/junked TV/FM antennas.

What antennas have omni directional reception, as well as the types used to aim at the signal source?

#1 The antennas you request for the various frequencies being a scrapped TV antenna will work. The main difference being the TV antenna is normally mounted horizontal, which provides horizontal polarization, and most public service use vertical polarization.

Mount the antenna vertical or rotated 90° from the normal mounting. Rabbit ears are omni-directional when mounted vertical, but typically are not tuned to the frequencies you might want to listen to.

The rods can be extended or compressed to approximately be at resonance. In most cases, this will not affect the operation. A log periodic-type antenna will provide a directional, antenna, and will typically be more closely resonant at multiple frequencies. It will, however, be directional, so some means of rotating the antenna would be desirable.

It also should be mounted with the elements vertical 90° from the original horizontal mounting. The boom will still be horizontal, only the elements are rotated to vertical. The direction of most gain is the smaller end of the antenna. Like an arrow pointing toward the desired direction.

You also mentioned using an "N" to "BNC" adapter. Typically, the RG 59, or RG 6 coax used with TV antennas, uses an "F" connector. I suspect this is the adapter you are using.

Ed Pruitt
via Internet

#2 This question deals with using TV/FM antennas with scanners. I also have a trunking scanner and for the past two years have enjoyed excellent reception using a RadioShack omni-directional FM antenna [part #15-2164, \$15.00].

You will also need an BNC to F connector [part #278-251, \$3.00] to connect your scanner to the FM coax.

I live in a valley where I get no TV reception [thank God for the Dish Network], but with my scanner, I catch calls 30 to 50 miles away. For \$18.00, it's hard to beat.

Randy Boettjer
Oak View, CA

#3 The basic design for a good TV antenna is to make them one directional so that they eliminate ghosts caused by signals reflected from secondary sources.

The VHF low signals are below the TV band, the VHF signals are mostly in the gap between channels 6 and 7 and the UHF signals are in the UHF TV band.

A second factor to consider, is that the TV signals are horizontally polarized while the radio bands you discussed are vertically polarized. [Rabbit ears being in a V are in between].

You can mount a TV antenna with the elements vertical, but you still have to point it for best reception.

The antenna I found best in the application you described is a Discone. It is vertically polarized and can have a response from 30-1200 MHz. They are \$59.90 from RadioShack, and are available elsewhere at ham radio sources (maybe cheaper). If that price is too steep, remove the elements from the TV antennas and make one.

Jim Schmidt
Deer Lodge, MT

ing voltage requirement.

You can carefully parallel a similar capacitor across the existing capacitor. If upon doing so, the grey band disappears, then replace the guilty capacitor. I said carefully, because the voltages present can be lethal.

If there is a transformer, then the voltages will be as much as 80-

100 volts, but probably lower. If it is a switcher, they rectify the AC power line coming in from the wall, and typical capacitor voltages can be 200 volts or more [120V x 1.414 for a simple half- or fullwave rectifier].

This, also coupled with the power line Ground/Neutral just touching one terminal of the capacitor, and anything grounded can produce a

nasty shock. So, as I said, parallel the suspected capacitor very carefully.

Best is to connect with the power off, unplugged, and allow time for charged capacitors to drain off. Then apply power while keeping both hands in your pocket (well at least one hand, you need one to plug it in, and turn it on). If this eliminates the grey band, replace the bad filter

AMAZING PRODUCTS!

BOX 716 AMHERST, N.H. 03031

Laser Window Listener

Access Internal Sounds Via A Beam Of Light!!

Remarkably simple concept uses a beam of laser light to illuminate a window acting as a microphone vibrating to the sounds and reflecting back to a sensitive filtered optical receiver that now reproduces this modulated light back into the actual sounds as heard thru a set of headphones

LWB9 Plans for Three Complete Systems.....\$20.00

LWB60 Demo System with 5mw VisRed Laser..\$159.95

Below Electronics for Two High Performance Infra Red Systems Shown Built From Above LWB9 Assembly Plans

LLR40 Optical Receiver/Processor.....\$199.95

CWL10 10 mw Infra Red Class IIIB Laser.....\$149.95

PLASMA FIRE SABERS

Duplicate the Effect Used in the SCI-FI Motion Picture Epic of the Century!!

Visit our web site at amazing1.com and see many Plasma Fire Saber Devices Ready to Use Sabers Parts and Accessories

Patented effect by Robert Iannini

Visual plasma field is controlled by grip pressure and adjusts saber length. No switches are used.

Active energy field produces weird and bizarre effects.

Specify available colors of Photon Blue, Neon Red, Starfire Purple, and Phaser Green.

PFS36K Kit of 36" Active Length....\$79.95

Please add \$20.00 for special handling of above

PFS26K Kit of 26" Active Length....\$59.95

Please add \$10.00 for special handling of above

PFS15K Kit of 15" Active Length....\$29.95

Kinetic Electric Gun

Pioneer A Futuristic Weapon

500 Joules Energy Storage
Constant Current Charging
Triggered Spark Switch
Ballistic Velocities
Handheld, Battery Operated
Labeled "Dangerous Product"

EGUN1 Plans.....\$20.00

All Parts are Individually Available

250 KV Tesla Coil

10-14" Explosive Bolts of Lightning!
Transmits Energy, Ion Motors Anti Gravity.

Size - 20"H x 8" Square
Weight - 25 Pounds
Input - 115 VAC/2Amps
See in "Action" on web www.amazing1.com

BTC3 Plans.....\$15.00

BTC3K Kit/Plans.....\$349.95

BTC30 Ready to Use.....\$449.95

BTC4 Plans 30" Sparks.....\$20.00

Attention

High Voltage Experimenters
Battery Powered Mini Sized Modules
For Research in: Hovercraft, Ion Guns, Force Fields, Shockers Etc.

MINIMAX4 4KV@10ma.....\$19.95

500,000 VOLTS!

SIZZLER Produces Explosive Stunning and Stopping Power
Intimidatingly Effective to 20'

SIZZ500 Complete \$79.95

Ion Ray Gun

Star Wars Technology Demonstrates Weapons Potential, Force Fields, IonMotors, Antigravity etc.

Projects electric shocks without contact!!
Conduct many weird and bizarre experiments

IOG7/9 Plans.....\$10.00

IOG7K Kit/Plans.....\$99.95

IOG70 Assembled/Tested.....\$149.95

Higher Powered Device

IOG9K Kit/Plans.....\$129.95

IOG90 Assembled/Tested.....\$199.95

Gravity Generator

Demonstrates a unique phenomena of electrical reactions that produce the effect of "anti-gravity". You build a small mock space ship from simple materials and use our power supply for energizing. Excellent demonstration of a fascinating method of levitation.

GRA3 Plans with Book.....\$20.00

GRA3K Pwr Sup Kit/Plans/Book.....\$99.95

GRA30 Assembled with Book.....\$149.95

Shock Force Field Vehicle

Object Electrifier
Hand shock balls, wands. Mini circuit is easily hidden
Great payback for those wise guys.

SHK1K Kit/plans.....\$19.95

FM Transmitter Kits

1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter

2 1 Mile+ Phone Transmitter

3 Line Powered Phone Transmitter Never Needs Batteries!

4 Tracking/Homing Beacon "Beeping Transmitter"

5 Video/Audio Rebroadcaster+1 Mile

6 TV/FM Radio Disrupter Neat Prank!!! Discretion Required

Includes Tricks Using Wireless Devices

COMBOX Above 6 Kits/Plans...\$59.95

COMBOP Above 6 Plans Only..\$10.00

1 800 221 1705 Orders Only! Fax 1 603 672 5406 Information 1 603 673 6493 Free Catalog on Request

Pay by MC,VISA,Cash, Check, MO, COD. Please Add \$5.00 S&H plus \$5.00 if COD. Overseas Please Contact for Proforma

capacitor with one of similar capacitance and, most of all, voltage rating. (It can be higher, but not lower.)

It is likely once you remove the faulty capacitor, you will see the seal blown, and electrolyte leakage under the capacitor or capacitors.

Often they use two or more in parallel to obtain the required capacitance, but staying within physical size constraints. So, if you find one defective, it is likely the parallel capacitors need to be replaced as well.

**Ed Pruitt
Keller, TX**

ANSWER TO #9993 - SEPT. 1999

Any suggestions on how to build a speech synthesis board for our BASIC II based robot? (It seems that the SPO256 chip is near extinct on the market right now.)

Please be advised that the SPO256A-017 voice processor and the SPRO16-117 expansion ROM are both available from **A & A Engineering**, 2521 W. LaPalma, Unit K, Anaheim, CA 92801. Cost is \$20.00 plus \$1.50 S&H to USA customers. Phone: 714-952-2114, fax: 714-952-3280.

**Anonymous
via Internet**

ANSWER TO #10993 - OCT. 1999

I am interested in programmable logic controllers (PLCs). Can anyone recommend good training hardware and textbooks?

PLC use has increased dramatically in the past few years. While common on the factory floor for years, their cost, power, and convenience have made them attractive for all kinds of applications.

The configuration of a PLC (Programmable Logic Controller) is also very flexible. From standard contacts and coils (inputs and outputs) to ADCs and DACs, thermocouple inputs, and motor controls, RS-232 and ethernet connections, intelligent user interfaces, etc.

The PLC is an important tool, monitoring all manner of inputs, and controlling all kinds of outputs.

Numerous books have been written, and a large number of vendors make an even larger variety of products. And, while each family is uniquely different, there are some important similarities.

The main programming language is called ladder logic, so called because of the appearance of the logic diagram. With its vertical and horizontal lines, it appears much like the rungs on a ladder. Each rung being a particular element of the control logic. And like any computer program, each rung is typically executed in order or its placement in the program.

Each PLC family will have its own options for programming, though

ANSWERS TO #10994 - OCT. 1999

I need to project the image from an 8mm camcorder tape onto a screen larger than a television screen, for a club with a number of people viewing it. Can anyone suggest a technique?

#1 Obviously, a projection TV is out of the question price wise, but a fairly good version would be to acquire a computer LCD projection frame, and place it on an overhead projector.

The device needed is an older version prior to current day standards of VGA. Preferably one in the CGA or composite video input. I found some of these maybe three years ago. They were about \$50.00 and slightly used.

Usually, the CGA also had a composite video input. Some manufacturers of these units were sharp, and in focus. They are probably out of production now, since the current standard is VGA. I have seen some adapters built that will convert composite to VGA so, if you find a VGA, then you must also find a composite to VGA adapter.

The colors are not as brilliant as they are with a TV, or even a projection TV, but they will produce a usable image.

If you have a composite version or a converter, simply connect the video output of the 8mm camcorder to the composite input of the projection screen. Place the screen on the overhead projector, and you have a large screen display.

**Ed Pruitt
Keller, TX**

#2 It's easy to project the image from any video source (like your 8mm camcorder, a TV tuner, etc.) or from a computer, on a large projection screen. You simply need to use a "video/data projector."

most include Windows-based graphical interfaces to ease programming. The software usually includes various utilities to show which addresses are used, what their signal types are, and what the addresses used might be.

Debugging usually allows a program to be stepped through sequentially, and the provide feedback on logic errors.

A good place to start is by requesting the free catalog (800 pages of info) from **PLC Direct** (now Automation Direct). They provide a number of system families, some of which are literally the same as units branded by other manufacturers, but

at a lower price. Their entry-level PLC, the DO-05 series features: eight inputs, six outputs, 2K for ladder logic storage, two RS-232 inputs, etc. They can be reached at <http://www.automationdirect.com> or by calling 1-800-633-0405. The programming software is reasonably priced, and many of their specifications and user's manuals can be downloaded from their web site. Check the section on Books as well.

**Rick Nelson
Newport News, VA**

ANSWER TO #99920 - SEPT. 1999

I need a keyboard for an old

These projectors were formerly in the "professional only" category for price and for ease of operation. Older projectors used three high-power CRTs, one for each primary color, and three lenses, optical convergence of the three images on the projection screen was painful, at best.

The high-voltage power supplies would sometimes self-destruct, and I have seen CRTs overheat and implode!

In the last few years, the technology has become simple and reliable, the images have gotten brighter and sharper, and the prices have come down. Most of the newer projectors use internal LCD panels, prisms, and mirrors, so just one projection lens is needed and setup is very simple. Some even include an audio amplifier and loudspeakers.

Some of the more popular manufacturers are Sharp, Eiki, Boxlite, and Sony, to name just a few. Prices for the smaller portables start around \$3,000.00. At the other end of the scale, you'll find machines over \$50,000, like the Hughes/JVC Light Valve projector, which can easily fill a 30' x 40' screen (yes, that's feet, not inches)!

I formerly worked at a Scanticon conference center, where we used one of these for football "tailgate" parties in our ballroom, seating around 800 people ... now that's a party!

You can find a few projectors at mail order retail dealers, such as **Midwest Micro (1-800-682-2511)**, or **J & R Computer World (1-800-221-8180)**.

Your local A-V dealer probably has a wide selection, and is likely to have some rental projectors available, if you need one only occasionally.

**Greg Miller
State College, PA
gemiller@commedge.com**

EPSON ActionNote 500C. The plastic foil PCB has broken traces, so the enter key and couple of keys around it don't work.

I need this dinosaur for work (modern compatibility reason).

If someone has this notebook with a broken screen and good keyboard, I'm willing to buy it.

The Epson 500C has a design flaw. There is a screw under the F8 key that ends breaking the film ribbon cable. Remove it and throw it away. If you still need spares, let me know.

**Miguel
via Internet**

ANSWERS TO #10995 - OCT. 1999

I am looking for a source of 434 MHz miniature TV transmitters.

#1 Miniature TV transmitters can be obtained from Ramsey Electronics, Inc., of Victor, NY. Order toll-free 1-800-446-2295. They have transmitters with video only, and video and audio.

Check out their ad in *Nuts & Volts*, Oct. '99 page 40.

**Joseph Kish
Clackamas, OR**

#2 If you are a licensed amateur (ham radio operator), PC Electronics, www.hamtv.com or 2522 Paxson Lane, Arcadia, CA 91007, tel: 818-447-4565 has several well-designed video transmitter boards suitable for all sorts of projects.

If you are not a licensed amateur, any use of 434 (or 420-450 megacycle) is illegal, as those are frequencies in the 70cm amateur band requiring a license.

One way transmissions, commercial transmissions, or use by any other than amateur two-way communications are illegal. Further, thousands of hams spend tens of thousands of hours searching for weak signals there as part of their amateur activities. And many areas have amateur video repeaters with inputs on that frequency.

Do you want your operations monitored by potentially

thousands of hams over hundreds of square miles if you inadvertently key up one of their repeaters? This has happened, many times.

Many spy shops peddle (illegal) 434 megacycle and similar video transmitters. Be aware the performance of these things always is extremely exaggerated.

What a dedicated, talented, equipped, and experienced ham with huge towers and antennas can achieve with hundreds of hours of piddling, does not equate to what a little board will do when hidden in a surveillance scenario by someone not experienced in the technology.

Wireless video is a long way from plug and play, regardless of what the ads may have you believe.

The amateur frequencies are popular for commercial wireless video surveillance because the equipment is cheaper and higher powered than legitimate FCC type accepted equipment. 434 in particular, is common because that is a popular remote control frequency in Germany, and inexpensive SAW (Surface Acoustic Wave) resonators on 434 are easy to find and easy to design around.

If you are an amateur, PC Electronics is an honest and competent manufacturer and would be pleased to assist you. If you are not an amateur, look towards legal FCC type accepted wireless video equipment on 900 or 2.4 gigs.

**Steve Uhrig
Street, MD**



by Evert Fruitman W7RXV

Robbi's Violin/Guitar Tuner

"Hint, hint Dad, only 10 more shopping days until my birthday, hint, hint, hint." "That new video will be out in a week, hint, hint, hint." I asked Robbi to quit dropping hints and just tell me what she wanted for her birthday. We laughed most of the way home from school that day. And yes, she still has the video. In fact, if we will get the chips and dips, we can watch it, too.

While still in high school, our youngest gave subtle hints like that. So, it came as no surprise when a few years later, she asked me to make her a tuner. Of course, the music stores had tuners, but then they had metronomes too and she could still hear her sister Joy's Loud Enough Metronome echoing around here. It got written up under that title elsewhere. Some of the commercial tuners have LEDs, LCD displays, analog meters, or some combination of those indicators. They are almost automatic tuners. They start at \$20.00 and go up. A musician told me that with Robbi's tuner, instead of watching a dial or a light, you get to use your ear. He said that that helps keep your ear trained.

At the ripe old age of 10, Robbi decided to take up violin. Fifteen years later, she still fiddles around with it. Since our piano usually needed tuning and she wanted something a bit more portable, she



Photo A.
Robbi's Tuner
Four-note tuner
features simple,
single-switch control.
Turning the knob past
either endnote turns
off the tuner.

asked for the tuner. That couldn't be any harder to make than the metronome, or an 80 meter transmitter, or a light meter, or a ... could it?

The Tuner

She had a good point, and I need only a gentle hint to start working in the playroom. Photo A



Photo B. Robbi's Tuner II
Nine-note Violin/Guitar Tuner
This tuner covers the ranges of both
the guitar and the violin. Since it
has a 12-position switch, you could
expand it even more.

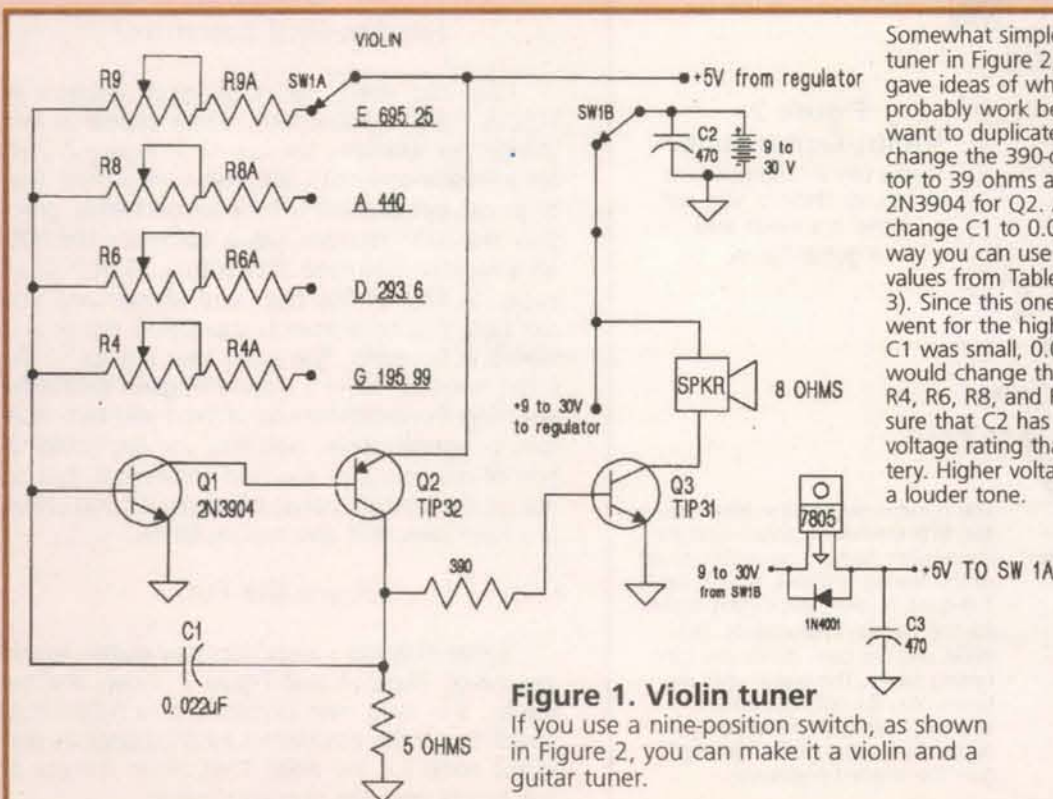


Figure 1. Violin tuner
If you use a nine-position switch, as shown
in Figure 2, you can make it a violin and a
guitar tuner.

Somewhat simpler than the tuner in Figure 2, this tuner gave ideas of what would probably work better. If you want to duplicate this one, change the 390-ohm resistor to 39 ohms and use a 2N3904 for Q2. Also change C1 to 0.068uF. That way you can use the resistor values from Table 1 (Figure 3). Since this one originally went for the higher notes, C1 was small, 0.022. That would change the values of R4, R6, R8, and R9. Make sure that C2 has a higher voltage rating than the battery. Higher voltage will give a louder tone.

and Figure 1 show the results of that logic. At first, all that was needed was a simple violin tuner. It had to give the four notes G, D, A, and E. Simple enough, one pole of a two pole, six-position switch supplies power to one of the tone-select resistors. The other pole supplies power to the regulator. Move the switch to an empty position and you have turned off the tuner.

How and Why

Q1, Q2, and the 0.022 uF capacitor in Figure 1 with the five-ohm resistor and one of the tone-select resistors make a complimentary-pair oscillator. The 390-ohm resistor couples the direct-current squarewave from Q2 to Q3 which drives the speaker.

When the oscillator first gets power, C1 starts charging through one of the tone-select resistors. When it reaches about 0.55 volts, Q1 turns on. That turns on Q2 through its emitter-base junction and the collector-emitter path of Q1. When Q2 turns on, that connects the top of the five-ohm resistor to the five volts from the regulator. That action discharges C1. That turns off Q1, which

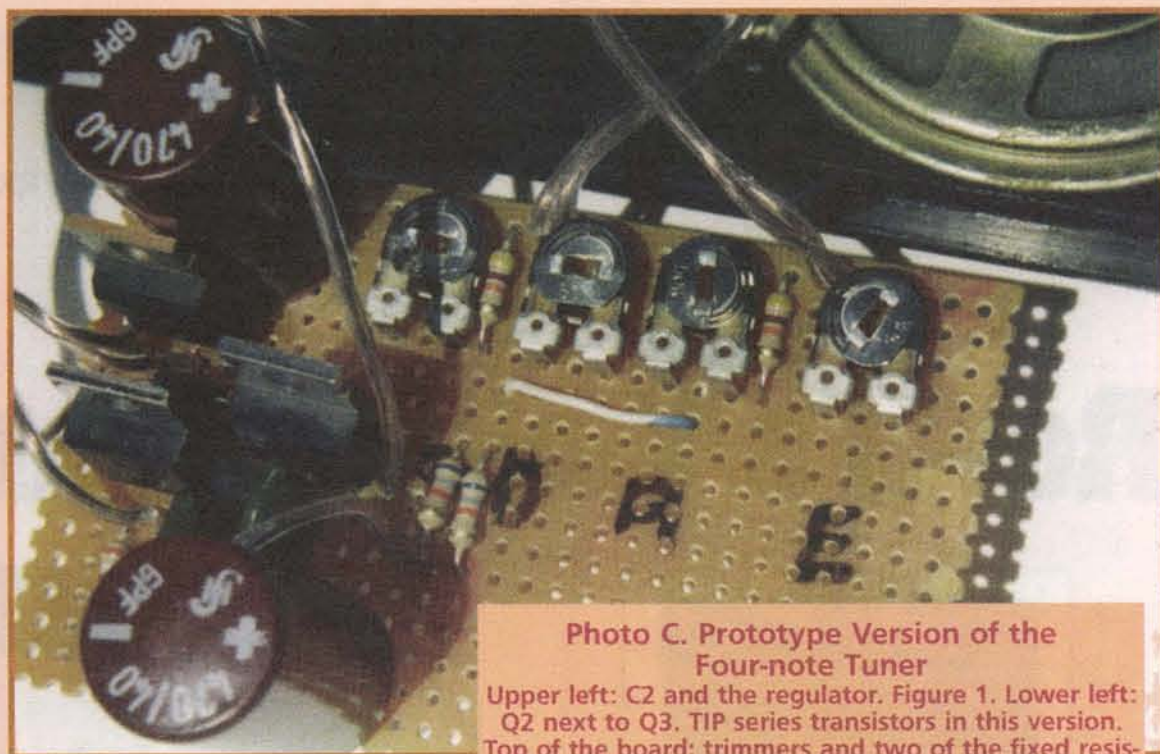


Photo C. Prototype Version of the Four-note Tuner
Upper left: C2 and the regulator. Figure 1. Lower left: Q2 next to Q3. TIP series transistors in this version. Top of the board: trimmers and two of the fixed resistors. Speaker held in with fast-setting epoxy.

turns off Q2. Then C1 starts charging again, which starts another cycle.

All of this action takes place in a period of time determined mostly by the size of C1 and the tone-select resistor. In essence, the collector of Q2 and the top of the five-ohm resistor switch from zero volts to plus five volts many times per second. Couple that signal to a speaker amplifier and you have an almost instant tuner. The speaker amplifier, Q3, draws power only when its base, through

the 390-ohm resistor, goes above about 0.6 volts. This drives current pulses through Q3. The current pulses in the collector of Q3 drive the speaker.

High Current

Even though it is for but a short time, both the five-ohm resistor and the speaker do draw a

fair bit of current. Five volts divided by five ohms equals about one amp. The current builds up and decays as opposed to a sudden, full on and full off state. So, one amp is close enough for our arithmetic. The same idea applies to the speaker, nine volts, eight ohms. Other things happen there because of the small but measurable amount of inductance in the speaker and the relatively sudden changes in current. That happens because the basic oscillator, Q1, and Q2 turn on and turn off at the same time. This delivers a squarewave to the speaker amplifier.

All of this means that you want a capacitor to store the current needed for the short but high current pulses to the two sections of the tuner. Capacitor C3 supplies the current to the oscillator section while C2 does the same for the speaker section. You may get away without C2 while the battery is still fresh. DO NOT even think about leaving out C3. Because of the short, high current demands of Q2, leaving off C3 can cause some strange, even unpleasant results. If you plan on the louder sound given by three nine-volt batteries, use a 35-volt capacitor for C2 as shown in the parts list.

Regulator Protection

Because, under some conditions, C3 could discharge through the regulator, put in the diode across the regulator. A cheap, one amp diode such as the 1N4001 gives the regulator good protection. Keep this in mind anytime that you have a relatively large capacitor across the output of a three-terminal regulator. The prototype model has the diode in it, from habit. However, by oversight on

my part, it got left off of the final version. After extensive tests, the regulator survived. It looks like, in this case, the tuner bleeds off the cap without letting it hurt the regulator.

You need the regulator since voltage changes cause some change in pitch. While I do not regard this as a precision instrument, a regulator helps stabilize the tones. That gives the instrument the ability to ignore the normal changes in

battery voltage over the useful life of the battery. That makes this a practical instrument.

TABLE 1. TUNING NOTES AND TONES

Note	E	F	G	A	B	C	D	E	F	G	A	B	C	D	E	F	G	A	B	C	D	E	F	G	A	B	C	D	E
Violin																195.99				293.6					440				659.25
Mandolin																													
Guitar							82.4			110			146.8			195.99		246.94			329.6								
Bass Guitar	42.20			55			73.41			97.99																			

Figure 3

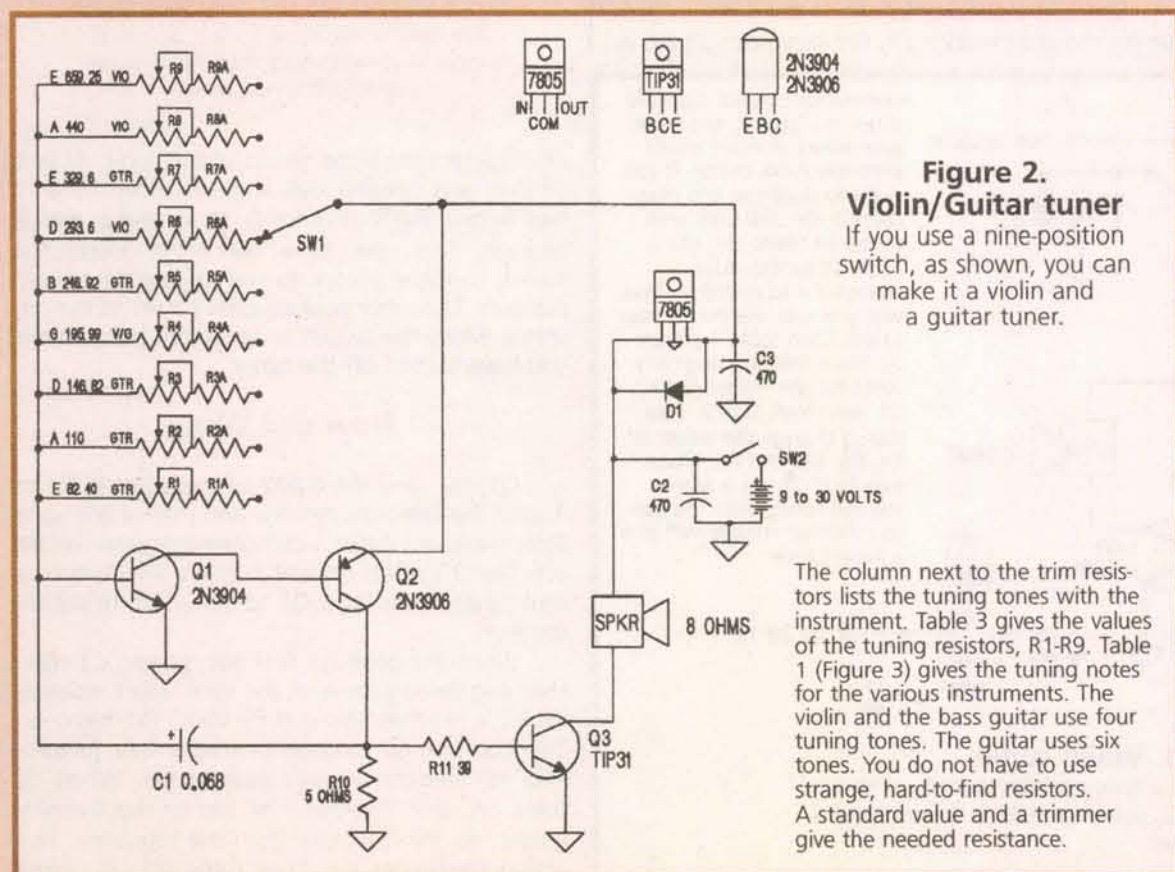


Figure 2. Violin/Guitar tuner
If you use a nine-position switch, as shown, you can make it a violin and a guitar tuner.

The column next to the trim resistors lists the tuning tones with the instrument. Table 3 gives the values of the tuning resistors, R1-R9. Table 1 (Figure 3) gives the tuning notes for the various instruments. The violin and the bass guitar use four tuning tones. The guitar uses six tones. You do not have to use strange, hard-to-find resistors. A standard value and a trimmer give the needed resistance.

Hard-to-Find Resistors?

You can make the tone-select resistors in Figures 1 and 2 easier than it may appear at first glance. For example, the low G, in Figure 2, calls for a resistance of 115,500 ohms: measured. Few of us can get or want to look for odd-value, precision resistors. You can get a common 100,000-ohm resistor. Combine that with a 25,000 or an easier to find 47,000-ohm trim resistor and you can tune that tone from G sharp to G flat or anywhere in between. The same idea applies to the other resistors. Table 3 (Figure 6) gives details for selecting the combinations of fixed and trim resistors for specific tones. You may use any combination of resistors that you find convenient, but do not let the total resistance fall under 27,000 ohms, as I have seen that give real problems.

Share the Fun

Some of Robbi's associates play guitar. Need I say more? Photo B and Figure 2 shows the net results. We used nine positions of a 12-position switch to get the extra notes for the guitar, as well as the notes for the violin. That allows the use of one box to tune the two instruments.

Photo D. Printed Circuit Board with Silkscreening

Following the writing on the board lets you put most of the tuner together without having to look at a diagram. Q1 is at the top just to the left of the first trim resistor. C1, which consists of two capacitors in parallel, sits in front of Q1, the 2N3904. R10, the two 10-ohm resistors, sit in front of C1. Q2 is hidden in back of Q3. Q3, the TIP31, is in back of the 7805 regulator. C2 and C3 sit in front of the regulator. The ceramic capacitor in back of and to the left of the regulator is more habit than necessity. It does not show up in the diagram. With C2 and C3 so close to the regulator, you could leave out the 0.1uF ceramic caps. In fact, you could put D1, the protection diode, there instead. It got left off of the layout. However, despite the potential danger to the regulator mentioned in the text, the tuner seems to bleed off the charge without letting it bother the regulator. The photo was made before cluttering up the board with the wires to the speaker, the switches, and the battery.

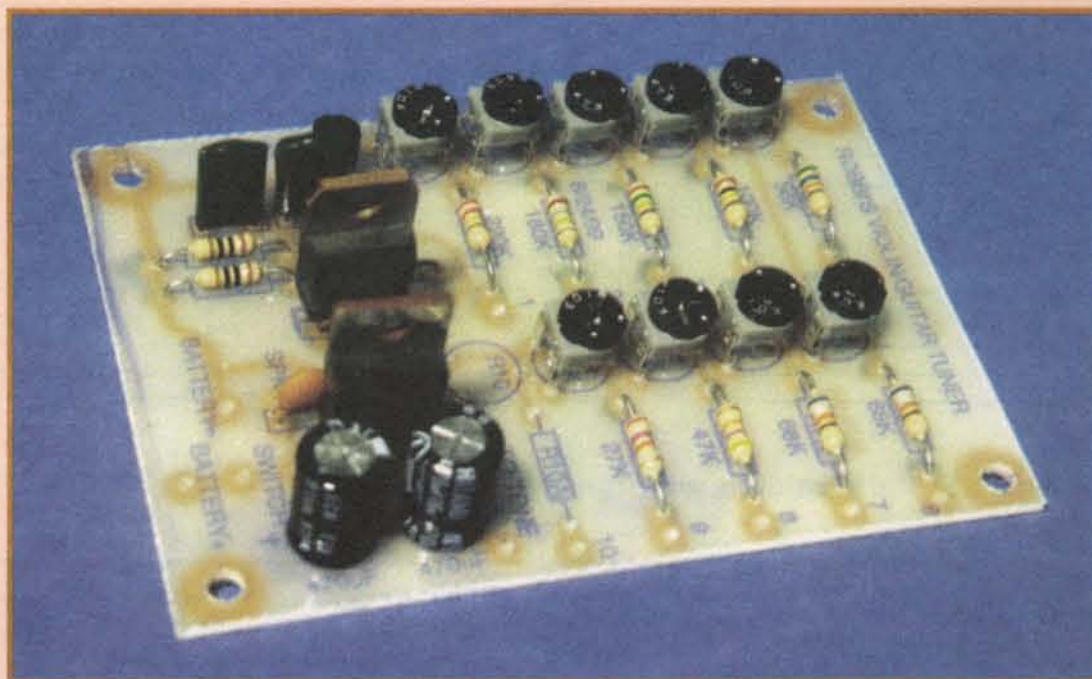


Table 1 (Figure 3) lists tuner notes and tones for violin, mandolin, guitar, and bass guitar. For reference, Table 2 (Figure 4) lists notes and their tones from low E on the bass guitar, to high G above E on the violin. Figure 5 puts the nine notes for the tuner on the staff. Additionally, it gives the four notes of the bass guitar. It shows the tones for all of those notes.

Stability

I would not classify Robbi's Tuner as a precision instrument. It stays within about 1% of where I set it. The complimentary oscillator, Q1-Q2, gives good temperature compensation. The inexpensive, green, polyester capacitors show a low temperature coefficient. From a practical standpoint, a hot soldering iron applied to one lead of the capacitor C1 caused about a one or two Hz change at 440. That figures out as less than one-half of one percent.

Following removal of the heat, the tone quickly returned to normal as indicated by a counter. I did not wait for the mounting wire to melt out of the capacitor. While this is not an environmental-chamber test, it gives an idea of what to expect. I have been known to put some of my 'toys' in the refrigerator for several hours and then take measurements. If this tuner is going on tour in your guitar case, I doubt that it will see extreme temperatures.

The voltage regulator stabilizes the voltage applied to the tuning components. You can get some idea of how much that stabilized the tone when you turn off the tuner. As the voltage from capacitors C2 and C3 falls to the point where the regulator drops out of regulation, the pitch changes enough to get your attention. If you use a couple of nine-volt batteries, the tuner will give loud tuning tones for a long time.

Sound Level

A sound-level meter shows 61-62 dB SPL (Sound Pressure Level) with a nine-volt power supply and about 72dB with 18 volts. At 18v, it draws 24mA. At nine volts it draws about 20mA. I could not get a reading above 21 volts as my tuner has only 16-volt capacitors in it. The

TABLE 2. PARTICULAR NOTES OF INTEREST AND THEIR TONES

Figure 4

A	A#	B	C	C#	D	D#	E	F	F#	G	G#
55	58.27	61.73	65.40	69.29	73.41	77.78	82.40	87.30	92.49	97.99	103.82
110	116.54	123.47	130.81	138.59	146.83	155.56	164.81	174.61	184.99	195.99	207.65
220	233.08	246.94	261.62	277.18	293.66	311.12	329.62	349.22	369.99	391.99	415.30
440	466.16	493.88	523.25	554.36	587.32	622.54	659.25	698.45	739.98	783.99	830.60

For reference, notes and their tones from low E on the bass guitar, to high G above the violin. To get the next higher note in the chromatic scale, multiply a note by 1.0594631. To get the next lower note, divide by the same. For example: D# below low E, divide 41.20 by 1.0594631 to get 38.89, D sharp or E flat.

NOTE	FREQUENCY	TRIMMER	FIXED
E	82.4	R1 100K	R1A 220K
A	110	R2 47K	R2A 180K
D	146.8	R3 47K	R3A 150K
G	195.99	R4 47K	R4A 100K
B	246.94	R5 100K	R5A 56K
D	293.6	R6 10K	R6A 68K
E	329.6	R7 10K	R7A 68K
A	440	R8 10K	R8A 47K
E	659.25	R9 10K	R9A 27K

TABLE 3. NOTES, FREQUENCIES, AND RESISTORS

Figure 6

This table may help you select the resistors you want for the desired tuning range for Photo B (Figure 2). G, D, A, and the last E are used for the violin. See Table 1 for more information.

Use your PC as a scope and datalogger!

Parallel Port Scope

spectrum analyzer, and digital multimeter



\$79 - \$799

ADC Virtual Instruments turn your PC or laptop into a sophisticated storage scope AND spectrum analyzer AND multimeter. Display simultaneously on large screen! 100MS/s 8-bit or 1.2MS/s 12-bit or 333KS/s versions. Great for schools, test depts, etc. Input to Excel! LabView/NT drivers included.

Environmental Logging

record temperature, humidity, etc.



\$129 - \$645

ENVIROMON - temperature (thermistor), humidity & light sensors, door position, etc. Record for 365/24 without a PC even if power fails. Monitor 30 sensors 400 yds away. With cables and easy software. Remote audio alarm. Use TC-08 for most thermocouples.

osziFOX

20MS/s handheld scope



\$129

osziFOX - handheld storage scope and DVM - stand-alone or plugs into your PC for display, store-to-disk, printing in color. Inputs to 100V, trigger, backlit LCD.

Download FREE demo software. Sales only: 1-888-7SAELIG

www.saelig.com 716-425-3753 • -3835 (fax) saelig@aol.com

pico
Technology Limited

Stocked in NY by Saelig Company: Virtual Instruments, I2C and embedded controllers, BITlink 2-wire networks, RS232/422/485, frame grabbers, etc. See www.saelig.com for Product of the Month!

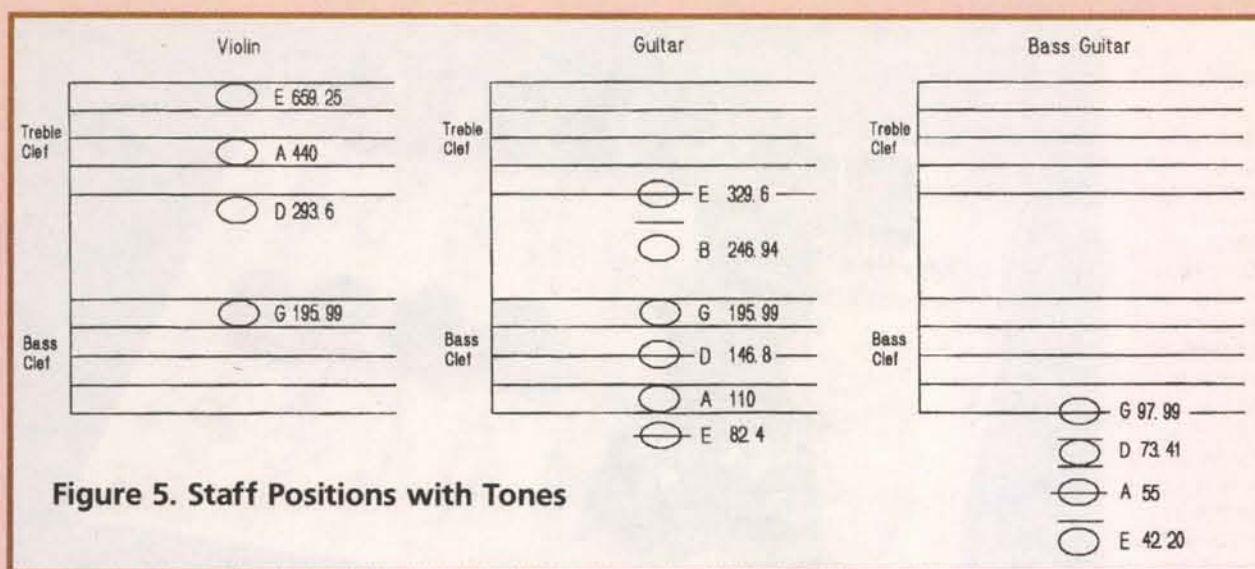


Figure 5. Staff Positions with Tones

Figure 7. 1:1 of the top of the board; which way and where the parts go.

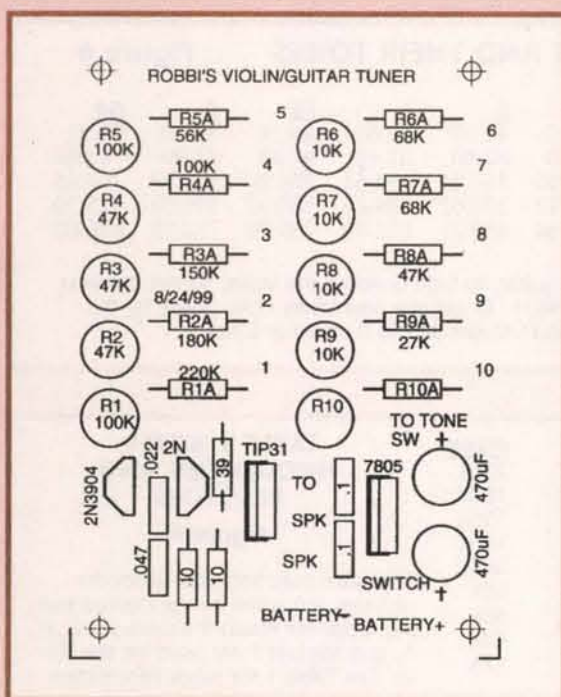


Figure 8. X-ray view from the top showing parts placement, as well as the foil on the under side of the board.


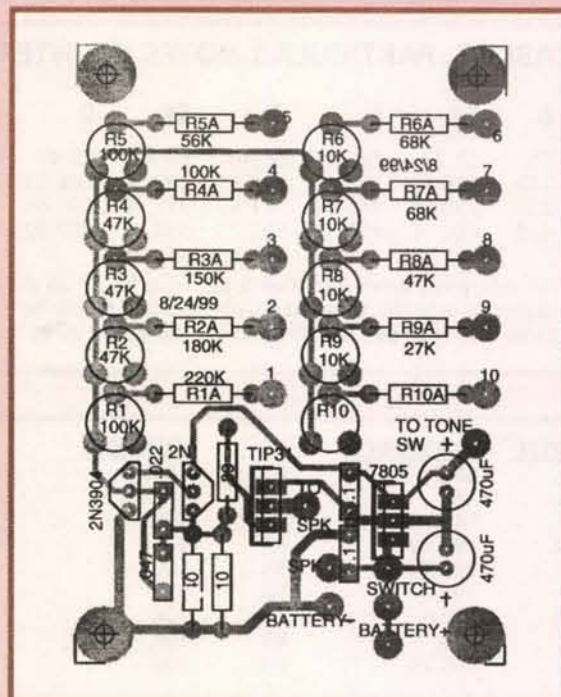


Figure 9. 1:1, shows the foil side of the tuner board.

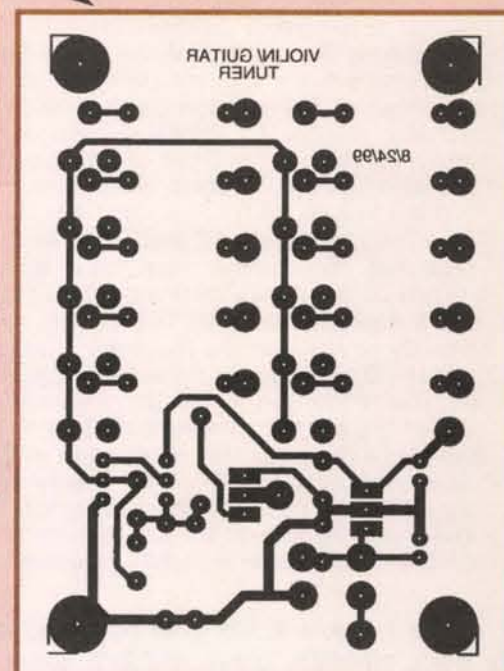

leave it to your imagination and ingenuity to make the tuner into a 'keyboard.'

If you use a larger capacitor, about 10uF, and larger tone-select resistors, you could make a metronome. This circuit lends itself to many uses.

Construction

If your interest extends no further than the simple, four-note tuner, you could start with Figure 1 and Photo C. That suggests one layout. It put C2 next to the regulator on the rear of the board. C3, the timing capacitors, with Q1 and Q2 went on the front of the board.

A Simpler Solution

Photo D shows what may be a simpler way to make the tuner. One of the high quality printed boards from Far Circuits can make the construction easier for you. If all you need is the four note tuner, just follow the silkscreening on the top of the board and install the resistors for the four violin tones. Use Table 1 and Table 3 to help you pick resistors. The same idea applies if all you want is the six-note guitar tuner. Just put the resistors on the board as indicated by the tables. Then put the six wires on the switch next to each other. Add the rest of the resistors, the transistors, and the capacitors.

Board Layouts

Fred, of Far Circuits, kindly allowed me to include the layouts for those who like to do their own boards from etch, or is that, from scratch? Figure 7 shows a 1:1 of the top of the board: which way and where the parts go. Figure 8 is an x-ray view from the top. Figure 9, also 1:1, shows the foil side of the tuner board. Figure 10 gives you a 2:1 x-ray view of the board.

Once you have decided on your board, lay out the box and make the mounting holes for the speaker and the controls. Mount the speaker last. Some speakers have mounting clips with them. Mine did not. I used a fast setting epoxy. Run the wires from the board to the switches, to the speaker, and to the battery.

Tune-up Time

Double check to see that the plus (+) sign on the electrolytic capacitors, C2 and C3, goes next to the plus sign on the board. Be sure that the NPN

sound level went up, but the higher voltage stressed capacitor C2 enough to show on the current meter in the power supply. The rest of the system will work with as much as 27 volts.

Battery Life

With a nominal 580mA-hour capacity, look for about 20-25 hours battery life from a nine-volt alkaline battery. If you want to use a bigger box and larger batteries, you can extend the run time. A set of six AA batteries should give about 45 hours of use. That is a lot of tuning.

Other Uses


As you change the tone-select switch, you will hear familiar intervals. If you connected a push-button switch between the regulator and SW1, you could play simple tunes by pressing the button and manipulating SW1. Since that is a bit crude, you could replace SW1 with as many momentary-contact buttons as you want and make an "instant toy organ." Just connect one side of each of the buttons to the regulator and the other side to one of the tone-select resistors. Follow Table 2 for the tones.

If that thought appeals to you, I will

PCB LAYOUT


Software For Windows - FREE

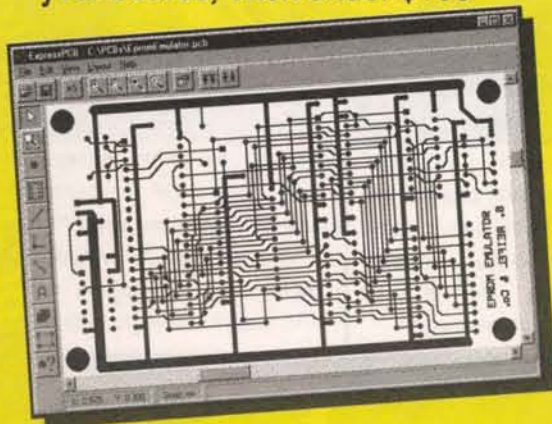- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



www.expresspcb.com

Figure 10. A 2:1 x-ray view of the board.

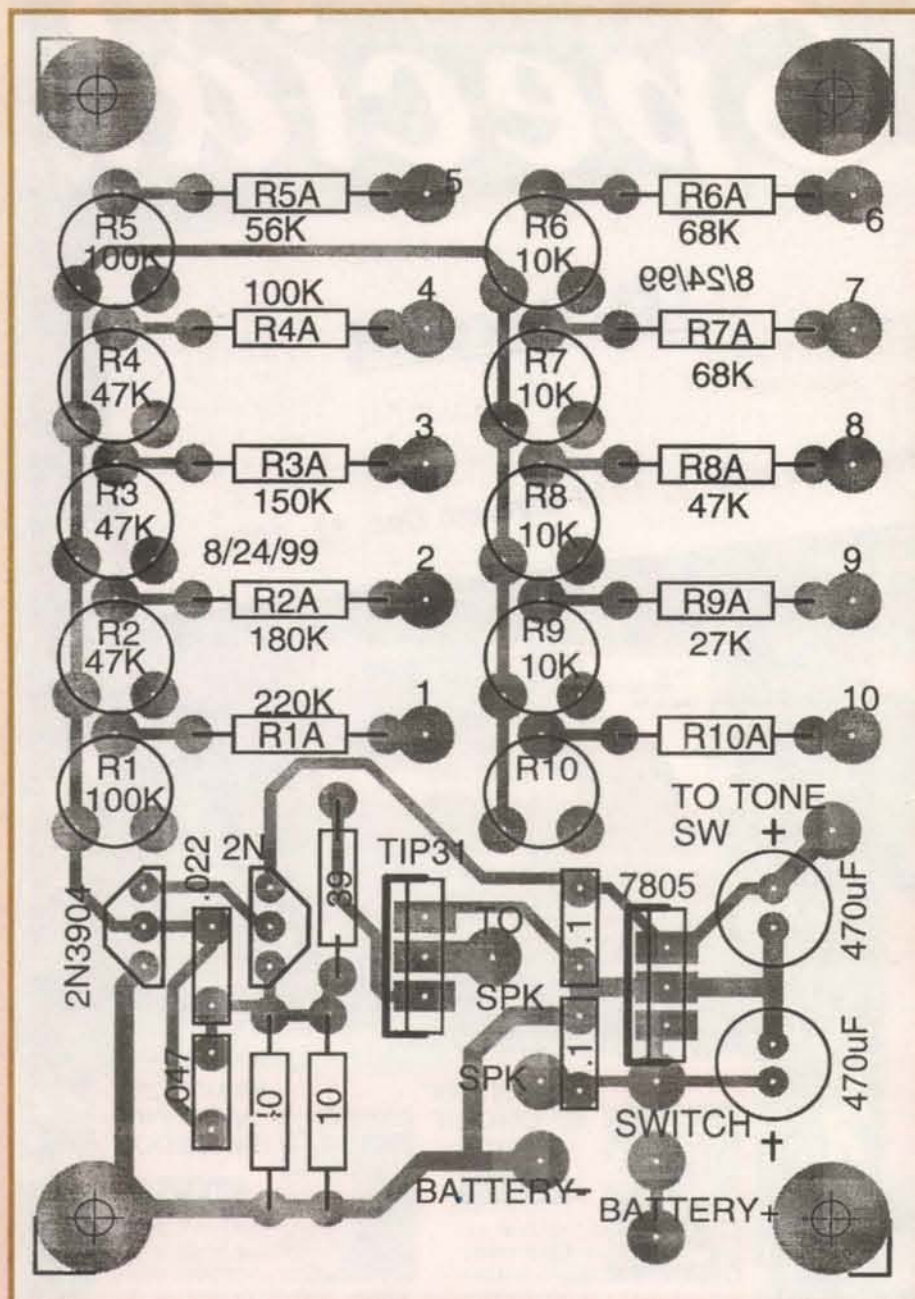

(2N3904) and the PNP (2N3906) transistors went into the correct places. Make sure that the battery plus goes to the assigned place. When all looks right, turn on the power switch. Run the tone-select switch through its range. You should hear the various tones. Most likely they will not be on pitch, but we will take care of that now.

Counter Measures

If you have, or can get a counter for a little while, connect it to R10 in Figure 2. BE SURE to follow the manufacturer's thoughts on input signal level for the counter. The indicated point will deliver a solid five-volt peak signal. Connecting the counter from the collector of Q3 to battery minus may work. However, the signal from that point may confuse the counter. The signal at that point rings due to the inductance in the speaker and the sudden change in current from the squarewave pulses.

Additionally, if you went for a louder sound and used a higher voltage battery, you will have to consider the larger signal that would send to the counter. Some counters will read the signal directly across the speaker. But the signal across the speaker does have a strange waveform.

Once you find a suitable signal source — and some counters are not as fussy as mine — select a tone. Compare the reading on the counter with the specified frequency shown on the drawing or in one of the tables. Adjust the trim resistor as needed. You will not need to readjust the trim-

mers as they do not interact with each other. Simply 'tweek' the trimmers as needed and then double check them. A dot of finger-nail polish or cement should secure the adjustment.

Hear! Hear!

If you wish to tune it by ear, find a good, stable tone source and adjust the trimmers as needed. If you have an accurately calibrated signal generator, that could help. Connect it to a suitable amplifier and a loudspeaker.

Perhaps you could run the signal generator through one of the auxiliary inputs on a hi-fi system. That would give you a steady tone for tuning. If needed, 'Zero' the signal generator against a well-tuned piano or other instrument. Once you have your comparison signal-source, adjust the trimmers as needed.

If All Else Fails

Lacking any of the above, counter, signal generator, a friend with a good ear, sit down at the piano and tune the trimmers. The tuner gives a non-sinewave tone. It contains many harmonics. You will have to listen carefully, but you will certainly be able to tell when the tuner and the tuning note agree. Once you have it tuned, put the cover on and you can start tuning your violin, guitar, or both.

I hope that Robbi's Violin/Guitar Tuner helps you to stay in tune. **NV**

PARTS LIST / FIGURE 2 / PHOTO B

TRIMMER			FIXED		NOTE/INSTRUMENT
R1	100K	271-284	R1A	220K	(E GTR)
R2	47K	271-283	R2A	180K	(A GTR)
R3	47K	271-283	R3A	150K	(D GTR)
R4	47K	271-283	R4A	100K	(G GTR/VIO)
R5	100K	271-284	R5A	56K	(B GTR)
R6	10K	271-282	R6A	68K	(D VIO)
R7	10K	271-282	R7A	68K	(E GTR)
R8	10K	271-282	R8A	47K	(A VIO)
R9	10K	271-282	R9A	27K	(E VIO)
R10	5 ohms two each 10 ohm resistors in parallel or a single 4.7 ohm resistor is okay. Generally, it is easier to find the 10s. The board from Far Circuits will accommodate the two resistors.				
R11	39	33-47 okay			
C1	0.068uF one ea. 0.022 and 0.047 in parallel. 272-1066 and 272-1068 (That adds up to 0.069, 0.068 is a standard value, which you may be able to find.)				
C2	470/16 272-957 If you use two nine-volt batteries, use the 272-1030, rated at 35V.				
C3	470/16 272-957 This cap never sees more than five volts				
Q1	2N3904 NPN 276-1603 (15 to a package, watch the pin connections)				
Q2	2N3906 PNP 276-1604 (15 to a package, watch the pin connections)				
Q3	TIP31 276-2017				
D1	1N4001 or other one-amp power diode, optional in this case.				
7805	276-1770 Five-volt Regulator				
SW1 ON/OFF	SPST 275-406				
SW2 TONE-SELECT	1 pole 12 position 275-1385				

Speaker two-inch replacement type 40-250 or a 273-092 eight-ohm (4-16 ohms okay). The speaker may be as large as you like: one inch to an on-sale 5x7 oval. It will just take a bigger box.

Box About 5x2x2 1/4 see what they have in stock when you get there.

Circuit board Perf board, or an easy-to-wire printed circuit board from Far Circuits, 18 N. 640 Field Court, Dundee, IL 60118

They always give the project a nice look and they shorten construction time.

Layouts: Figures 7-10.

If you have a neighborhood wholesale electronics store, feel free to take the parts list there. Except for the printed circuit board, they will have equivalent parts that will work just as well as the ones listed above.

A word to the wise

Fact of the matter is, it may be necessary to get transistors from some place other than the ones listed above. Unless you have a way to verify that they are 2N3904s or equal, that is probably the safest thing to do. Of the last four packages of 276-1617 transistors, a good percentage of the transistors had the emitter and the collector leads switched. Their package ALWAYS shows the collector on one end, NEVER in the middle. I found out that a number of them had the collector in the middle. I have enough electronics background to figure it out and correct it. Many readers may lack the 40+ years practice that I have had which helps with that kind of problem.

The second problem that came to light, or should I say lack of light resulted from them putting DARLINGTON-PAIR transistors in that package. I put together one of the bike lights (*Nuts & Volts* Oct. '99) and spent a frustrating 30 minutes trying to figure out why one of the LEDs lit, and I needed a flashlight to see the other one. It blinked, but oh, such a feeble light.

Again, careful testing with an analog ohmmeter on the RX1 scale showed that the transistors for that LED, had too much voltage drop from the emitter-base to pass as a simple NPN transistor. I took back 10 or so and gave them to the clerk. He will talk to their purchasing/QC next week. I took my ohmmeter in and tested the next 30 transistors before buying them. Several of them had the collector base leads reversed.

In the last 20-25 years, I have found an occasional questionable transistor once in 200 or so transistors in those packages. I have no problem with that. But switching the leads or putting a Darlington-pair in the package could cause a lot of frustration to those who want to build these, or other projects with the left-overs.

Winter Special

BOOKS PUBLISHED BY MCGRAW HILL

ATTENTION PAID SUBSCRIBERS:
Receive a **15% discount** off the listed price shown here instead of the usual 10% discount!!
Offer valid Nov. 1, 1999 through Dec. 31, 1999.




\$39.95
"Encyclopedia of Electronic Circuits"
Vol. 7
by R. Graff

An extensive library of 1,000 circuits from the bestselling, seven-volume "Encyclopedia of Electronic Circuits."



\$34.95
"Programming and Customizing the BASIC Stamp Computer"
by S. Edwards

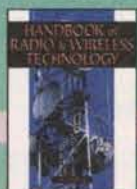Build smart electronics projects with the inexpensive, simple-to-use, surprisingly powerful BASIC Stamp.




\$44.95
"Handbook of Radio and Wireless Technology"
by S. Gibilisco

A comprehensive compendium on the entire field of radio and wireless technology.



\$39.95
"Circuit Troubleshooting Handbook"
by J. Lenk

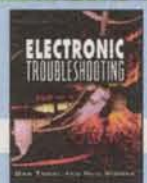This handbook gives full descriptions of the operation of important circuits, and how each circuit's characteristics may figure in its failure or poor performance.



\$34.95
"Electronic Troubleshooting"
by D. Tomal and N. Widmer

Troubleshoot and repair any type of electronics with this comprehensive guide.



\$54.95
"Handbook of Microcontrollers"
by M. Predko

This much-needed reference is the first to cover all the most common types of eight-bit microcontrollers.

by Joseph J. Carr



\$39.95
"Programming and Customizing the 8051 Microcontroller"
by M. Predko

This tutorial/disk package details the features of the 8051 and demonstrates how to use these embedded chips to access and control many different devices.



\$24.95
"How Electronic Things Work ... and What to Do When They Don't"
by R. Goodman

Never again be flummoxed, flustered, or taken for a ride by a piece of electronic equipment with this fully illustrated, simple-to-use guide.



SECRETS OF RF CIRCUIT DESIGN
\$29.95

From one of today's most respected electronics authors comes this pragmatic, intermediate-level guide to designing, building, and testing all types of radio frequency circuits. Filled with functional projects that demonstrate the principles of RF circuits, this revision of a bestseller also provides a handy parts list and sources of components.



PRACTICAL ANTENNA HANDBOOK
\$49.95

The most popular book on antennas ever written, widely known as "the antenna builder's bible." This Third Edition is a work for anyone with an interest in antennas, from the newest of novices to the most experienced engineer. This empowering book gives you all kinds of projects and material that explains why what you did works.

"The Illustrated Dictionary of Electronics"
by S. Gibilisco **\$39.95**

"The Robot Builder's Bonanza"
by G. McComb **\$18.95**

"Programming and Customizing the PIC Microcontroller"
by M. Predko **\$34.95**

"How Radio Signals Work"
by J. Sinclair **\$24.95**

"Making Printed Circuit Boards"
by J.L. Axelson **\$22.95**

"TAB Encyclopedia of Electronics for Technicians and Hobbyists"
by S. Gibilisco **\$69.50 (Hard Cover)**

"How to Read Electronic Circuit Diagrams"
by R.M. & Lawrence Brown **\$19.95**

"Build Your Own Test Equipment"
by H.L. Davidson **\$22.95**

"Radio Receiver Projects You Can Build"
by H.L. Davidson **\$21.95**

"Basic Electronics Theory"
by D.T. Horn **\$26.95**

"Troubleshooting and Repairing Consumer Electronics Without a Schematic"
by H.L. Davidson **\$24.95**

"Amateur Radio Encyclopedia"
by S. Gibilisco **\$50.00 (Hardcover Only)**

"Ready-to-Build Telephone Enhancements"
by D.T. Horn **\$17.95**

"The Benchtop Electronics Handbook: 260 Most Common Popular Electronics"
by V. Veley **\$65.00 (Cloth Cover)**

OTHER AVAILABLE TITLES ...

OTHER AVAILABLE TITLES ...

Send check or money order to Nuts & Volts, 430 Princeland Court, Corona, CA 92879. Include a complete shipping address (no P.O. Boxes, please). Shipping & handling \$4.50. CA residents add 7.75% sales tax. Or, call our toll-free order-only line at 1-800-783-4624 and use your MasterCard or Visa. **ALL ORDERS MUST BE PREPAID.**

Call 1-800-783-4624 today!
WE ACCEPT VISA AND MASTERCARD

New Product News

RF BUG

The RF Bug is a receiver that detects both incoming and outgoing calls. When a call is detected, six chasing LEDs are set in motion.

Sensitive enough to detect calls from about 12" of digital phones, and 40" of cell phones. Use the provided strap to attach it to the phone's antenna or wrist strap or the outside of a purse, bag, carry case, etc. Whether the ringer is off or you simply can't hear it, the lights alert you of incoming calls. Especially useful in theatres, restaurants, business meetings, classrooms, or anywhere a ringing phone is inappropriate.

Wireless Internet users will never miss a message again. The RF Bug detects the PC/laptop's reply to the sender, setting the lights in motion.



The RF Bug will sniff out and expose hidden transmitters. Place it within a few inches of the suspected item and it activates when it senses a transmission from a hidden camera or audio transmitter.

Due to its sensitive nature, the RF produced by microwave ovens will encourage the RF Bug to display its visual antics, as well as two-way and amateur radios, some remote controls, cordless phones, and virtually any other transmitter.

Suggested list price is \$15.95.

For more information, contact:

NCG COMPANY
1275 N. GROVE ST., DEPT. NV
ANAHEIM, CA 92806-2114
714-630-4541 FAX: 714-630-7024
1-800-962-2611
E-MAIL: micks@rffbug.com



PERSONALSCOPE™ HP55

Velleman introduces the PersonalScope™, a complete portable oscilloscope at the size and the cost of a good multimeter.

Its high sensitivity — down to 5mV/div — and extended scope functions make this unit ideal for hobby, service, automotive, and development purposes. Because of its extreme value for money, the PersonalScope is well-suited for educational use, too.

Some applications are: Measurements on audio equipment, AC power lines, digital signals, all kinds of sensors, signal analysis in automotive applications, car stereo, etc.


Its ultra fast full auto setup function makes measuring waveforms very easy.

Dimensions are 4.13" x 7.95" x 1.38".

The PersonalScope comes with a protective case and test leads with alligator clips.

For more information, contact:

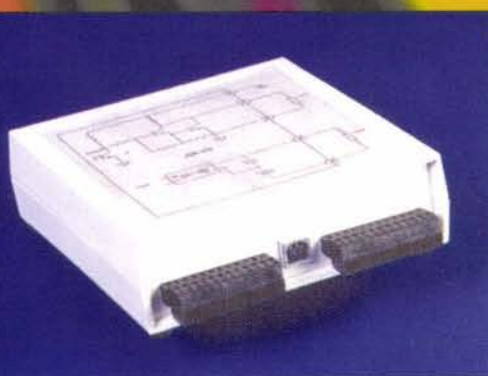VELLEMAN
7415 WHITEHALL ST. STE. 119
DEPT. NV
FORT WORTH, TX 76118
817-284-7785 FAX: 817-284-7712
E-MAIL: velleman@earthlink.net
WEB: www.velleman.be



USB OPTO I/O MODULE MODEL JSB-320

J-Works, Inc., announces that it has begun production shipments of the Model JSB-320 USB Opto I/O Module.

The Model JSB-320 provides opto-isolated input and outputs that plugs 'n plays into the standard USB. Several configurations of output and input up to 32 points are available. The user

controls the input and output from any programming language that supports USB communications.

Plug-in style terminal block connectors allow quick hook-up. Output is rated at 1 amp @ 7-30VDC and input range is 10V to 30V.

The module replaces internal PC-based plug-in cards in various test, control, and measurement applications.

Complete data is available on J-Works web site at www.j-works.com

Single unit price for the Model JSB-320 range \$205.00 to \$299.00. Delivery is from stock.

For more information, contact:

J-WORKS, INC.
12328 GLADSTONE AVE., UNIT 4, DEPT. NV
SYLMAR, CA 91342
818-361-0787 FAX: 818-270-2413
E-MAIL: sales@j-works.com
WEB: <http://www.j-works.com>



NHRC-4/M2 REPEATER CONTROLLER

NHRC LLC announced the introduction of the NHRC-4/M2 repeater controller. Now available to the public, the NHRC-4/M2 is a integrated repeater controller that installs inside General Electric™ MASTR II™ mobile radios and stations. It provides complete repeater operation and control with a remote base port.

Installation of the NHRC-4/M2 repeater controller into the GE radio is quick and easy. In the

mobile radio, two wires must be added, and one trace severed on the radio's system board and the controller is simply plugged in.

In station applications, installation consists of adding three wires and then the controller is plugged in. Per request, application notes for station or mobile radio modifications can be provided by NHRC.

The NHRC-4/M2 repeater controller provides CW ID, ID timer, individual timeout timers for the main and remote base ports, and a hang timer. Five different distinctive courtesy tones indicate channel activity and remote base status. A digital output is included for control applications. Or the digital output can be configured to control a fan to run

while the transmitter is on and for a programmable amount of time afterward.

The CW ID, timer setting, fan control, and distinctive courtesy tones are programmable over-the-air with DTMF command sequences. The programming is protected from unauthorized access with an access code which cannot be changed without physical access to the controller.

The NHRC-4/M2 repeater controller is priced at \$189.00.

For more information, contact:

NHRC LLC
444 MICOL RD., DEPT. NV
PEMBROKE, NH 03275
603-485-2248
E-MAIL: info@nhrc.net
WEB: www.nhrc.net

Showcase your New Products here! Send all press releases or information/photos to:

Nuts & Volts Magazine
New Product News

430 Princeland Court,
Corona, CA 92879
or E-Mail to

newproducts@nutsvolts.com

Fantastic DMM Offer!

Don't let this price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch. **Rubber Boot Included!**
Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity
Overrange Indication: 3 Least Significant Digits Blank
Temperature for Guaranteed Accuracy: 23°C ±5°C RH<75%
Temperature Ranges:
Operating: 0°C to 40°C (32°F to 104°F)
Storage: -10°C to 50°C (14°F to 122°F)
Power: 9V Alkaline or Carbon-Zinc Battery (NEDA 1604)
Low Battery Indication: BAT on Left of LCD Display
Dimensions: 188mm(L) x 87mm(W) x 33mm thick
Net Weight: 400g



ONLY \$19
#9300G

2GHz RF Field Strength Analyzer

Protek

- Frequency Range: 100KHz to 2.060MHz
- Narrow Band FM (NFM), Wide Band FM (WFM), AM and Single Side Band (SSB) Modulated Signals May Be Measured
- PLL Tuning System for Precise Frequency Measurement and Tuning
- LED Backlight LCD (192x192 dots)
- Built-In Frequency Counter
- Hand-Held and Battery Operated
- All Functions are Menu Selected
- RS232C for PC Interface and Printer



ONLY \$1589
#3201

Removable Hard Drive Rack

For IDE/Ultra DMA Hard Drives

This product can be used with any 3-1/2 IDE hard drive up to 1" high. It includes an electronic keylock for safe removal and insertion. Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI). **Other Models are Available.**



ONLY \$1495
any qty.

RH-10C-IDE

new!

- Auto door on the outer frame
- ABS material of outer frame, High efficiency cooling fan
- Worldwide patent pulling function handle
- CE Approved
- Coating iron bottom cover
- For IDE interface
- For 1" high 3.5" HDD
- Not compatible with our RH10 & RH20 series. Compatible with our RH17-IDE model.



ONLY \$1895
any qty.

#MR-27

Auto-Temp Solder Station with Ceramic Element

- With Ceramic Heating Element for More Accurate Temp Adjustment
- 3 Conductor Grounded Power Cord
- 250°C-480°C (470°F-900°F)
- Fast Heating Feature



ONLY \$39
SR-976

CTRL - D to bookmark this site

www.web-tronics.com
Don't forget the dash
Circuit Specialists Inc.

- Easy to Navigate
- Includes a Search Engine That Really Works
- New Items Added Constantly

For More Info See www.web-tronics.com

- ASIC CCD Area Image Sensor
- Extremely Low Power Consumption
- 0.5 Lux Min Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation



VM1030PA-B
30mmx30mmx25mm, Pinhole lens with audio, 12V
\$49.00 any qty.



VMCB21
44mmx38.5mmx28mm with 6 infra-red LEDs, 12V
\$49.00 any qty.



VM1030A
30mmx30mmx26mm Standard lens with audio, 12V
\$49.00 any qty.



VM1035A
42mmx42mmx25mm Standard lens with audio, 12V with back light compensation
\$59.00 any qty.



VM1036A
32mmx32mmx25mm Standard lens with audio, 12V, reverse mirror image feature
\$59.00 any qty.

COLOR

- Low Power Consumption
- 1 Lux Illumination
- Built-In Electronic Auto Iris for Auto Light Compensation
- Internal Synchronization
- 12Vols
- 400 TV Lines



VM3011-A
45mmx40mmx24mm Standard lens with audio, single board
\$99.00 any qty.



VM3010PA
33mmx33mmx18mm Pinhole lens with audio
\$129.00 any qty.



VM3010-A
33mmx33mmx32mm Standard lens with audio
\$129.00 any qty.

B&W and Color

- Smart Rugged Metal Housing
- Extremely Low Power Consumption
- 12 Volt
- CCD Area Image Sensor for Long Camera Life
- Built-In Electronic Auto Iris for Auto Light Compensation
- No Blooming, No Burning
- 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)



VMBLT3025W
Digital Color, Weatherproof 20mm(D)x83mm(L)
\$189.00 any qty.



VMBLT1020W
B&W Weatherproof 21mm(D)x58.5mm(L)
\$79.00 any qty.



VMBLT1020A
B&W with audio 21mm(D)x55mm(L)
\$69.00 any qty.

new!

Sensational NEW Design for Small Observation Cameras. Smaller and Better!

- Ultra Miniature Design
- Black & White Versions Only 25mm x 25mm
- Color Versions Only 32mm x 32mm
- Available in Standard Lens or Pinhole Lens
- All Include Audio
- All Include Pre-Wired Cable Harness for Audio, Video & Power
- 12V Regulated Power Supply Required (120mA typical power consumption)
- 0.1 LUX Rating (B/W), 1 LUX (color)
- CCD Area Image Sensor for Long Camera Life
- Back Light Compensation Circuit
- Built-In Electronic Auto Iris Lens



VMPS-718A
25mmx25mmx30mm, B/W CCD with standard lens, pre-wired cabling for video/audio, 12V DC Power Input
\$69.00 \$59.00 5 or more



VMCW-H11A
32mmx32mmx30mm Color CCD with standard lens, pre-wired cabling for video/audio, 12V DC Power
\$149.00 \$139.00 5 or more



VMCW-H12A
32mmx32mmx19mm, Color CCD with pinhole lens, pre-wired cabling for video/audio, 12V DC Power Input
\$149.00 \$139.00 5 or more



VMPS-250A
25mmx25mmx15mm, B/W CCD with pinhole lens, pre-wired cabling for video/audio, 12V DC Power Input
\$69.00 \$59.00 5 or more

Protek

Series 6500 Deluxe 20MHz/40MHz/60MHz/100MHz Dual-Trace Oscilloscopes

- Alternate Trigger
- Internal Sync Separator Circuit
- Alt-Mag Sweep
- Delay Sweep (6510)



Part No.	6510	6506	6504	6502
Bandwidth	100MHz	60MHz	40MHz	20MHz
Vert. Sensitivity	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV	1mV/DIV to 5V/DIV
Max Sweep Rate	2nS/DIV to 0.2S/DIV	0.1µS/DIV to 0.2S/DIV	0.1µS/DIV to 0.2S/DIV	0.2µS/DIV to 0.5S/DIV
Delay Sweep	YES	YES	YES	YES
Vert. Mode Trig.	YES	YES	YES	YES
Cursor Readout	NO	NO	NO	NO
CRT Volts	12KV	10KV	10KV	2KV

new!

3000 Series Digital R/O Bench Power Supplies

- Low Cost Single Output
- High Performance Triple Output

High stability digital read-out bench power supplies featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. The dual output versions can be used in both serial voltage and parallel current configurations to double maximum outputs. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.

Line Regulation: $2 \times 10^{-4} + 1 \text{ma}$
LED Accuracy: Voltage $\pm 1\%$ +2 digits
Current $\pm 1.5\%$ +2 digits
Wave Line Noise: $\leq 1 \text{mVrms}$
Dimensions: 291mm x 158mm x 136mm (CSI3003 & CSI3010)
365mm x 265mm x 164mm (CSI3003-3 & 3005-53)



CSI3003: 0-30v/0-3amp Digital R/O Bench PS, $1 \times 10^{-4} + 5 \text{mV}$ Load Regulation	\$99.00 5/\$89.00
CSI3010: 0-30v/0-10amp Digital R/O Bench PS, $1 \times 10^{-4} + 30 \text{mV}$ Load Regulation	\$149.00 5/\$139.00
CSI3003-3: Triple Output 2x(0-30v/0-3amp)+5v, 3amp Fixed, $1 \times 10^{-4} + 5 \text{mV}$ Load Regulation	\$239.00 5/\$219.00
CSI3005-3: Triple Output, 2x(0-30v/0-5amp) +5v, 3amp Fixed, $1 \times 10^{-4} + 25 \text{mV}$ Load Regulation	\$269.00 5/\$249.00

We Sold Over 700 Last Year!
with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bargraph

- True RMS Mode
- 10MHz Frequency Counter
- Time Mode with Alarm, Clock, and Stop Watch
- Dual Display
- 10 Location Memory
- Min, Max, Avg and Relative Mode
- Decibel Measurement
- Cap and Ind. Measurement
- Temperature Mode (C/F)
- K Type Temperature Probe Included
- Pulse Signal for Logic & Audible Test
- Continuity/Diode Test
- Logic Test
- Auto Power OFF/"Keep ON" Mode
- Fused 20A Input with Warning Buzzer
- Back Light
- Data Hold/Run Mode
- Safety Design UL1244 & VDE-0411
- Protective Holster
- Silicon Test Leads



NOW ONLY \$129
Reg. \$169

PROTEK 506



CLONE, TEST OR REPAIR ANY HARD DRIVE

"THE MOST COMPLETE HARD DRIVE WORKSTATION WE'VE SEEN!" BOB ROSENBLOOM, DIGITAL VIDEO, INC.

DRIVE SERVICE STATION

Copy entire hard drives with ease. Drive duplicators are essential tools for dealers and system builders. Don't spend hours installing and formatting drives. Do it instantly with the Pro. Set up any SCSI or IDE drive with your original software. Connect blank drives to the Pro and press start. You'll copy entire drives faster and more accurately than is possible on any PC. With our combination IDE and SCSI model, you can even copy data between different interfaces. All models include both 2.5" and 3.5" interface adapters. The Pro also supports SCA and Wide SCSI drives.

Choose the Pro, and you'll also have an entire factory drive test and repair system for under \$1000. The Pro gives

BUY MANUFACTURER DIRECT: \$995

408 330-5525

you the ability to copy, reformat, repair, translate, and test any hard drive. Use the Pro to put any hard drive through its paces. A full factory final test and performance analysis is performed. Complete test and repair reports are sent to any standard printer.

The Pro will also reassign and eliminate drive defects. Here's how it works: First, a precise media analysis system scans the disk for errors. Defects are mapped out, and effectively "erased." The error correcting system then "trains" the drive to permanently avoid defective areas. Data is stored only on the safe

areas of the disk. Capacity is reduced by an insignificant amount, and the drive works flawlessly once again. Get the technology used by major repair shops and data recovery centers. The Pro repairs all disk defects caused by normal wear. Drives with mechanical damage may not be repairable.



CORPORATE SYSTEMS CENTER

3310 WOODWARD AVE., SANTA CLARA, CA 95054
WWW.DRIVEDUPLICATORS.COM

Call today for high volume multi-drive copiers and CD Duplicators
Sold and intended for backup purposes only. Copyright laws must be observed.

MORE MEMORY! MORE SPEED!

With the new Al Williams BS2SX-IC Starter Bundle!

Al Williams BS2SX-IC Starter Bundle!

The new Al Williams BS2SX-IC Starter Bundle is a promotional BS2SX-IC package. The bundle includes the new Al Williams "BASIC Stamp Microcontroller Projects" book, a BS2SX-IC module, the Board of Education and jumper wires, and Al's Pak-I Math Coprocessor. Priced at \$159, this bundle has a \$30 savings over purchasing the parts individually.

The BS2SX-IC has a 16KB EEPROM (8x larger than the BS2-IC) and executes 10,000 PBASIC instructions per second (2.5x faster than the BS2-IC) from a Scenix Semiconductor SX28AC/SS.

This bundle is ideal for:

- Customers who want to use a BASIC Stamp as a data logger;
- BS2-IC users who need faster program execution speed and code space; or
- Somebody simply getting started with the BS2SX-IC

Microcontroller Projects with the BASIC Stamp

This book is for you if you want to solve problems with a microcontroller, learn how to automate a manufacturing process, or simply learn about the BASIC Stamp. Book contents include motors, analog input, serial I/O, LCDs and keypads - along with new PBASIC commands and examples specifically for the BS2SX-IC.


Projects include the Reaction Game, Logic Probe, PocketWatch, Morse Code IDer, and a Morse Code Keyer. A CD-ROM in the back of the book includes Parallax Stamp manuals and software.

Pak-I Math Coprocessor

Al's Pak-I is a 32-bit IEEE floating-point math coprocessor for your BASIC Stamp IISX. Using the SHIFTIN and SHIFTOU commands with a two-wire interface to the Pak-I, you'll learn serial communication with the benefit of easy floating point math.



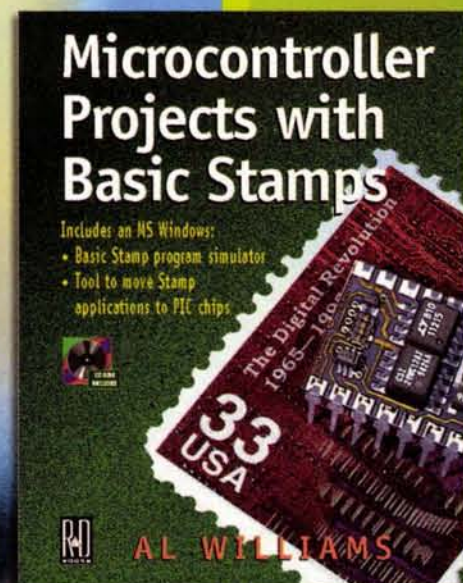BASIC Stamp II SX module
(alone #BS2SX-IC, \$59.00)



Al Williams book
(alone #27952, \$44.95)

Order the Al Williams BS2SX Bundle (#27208)
for \$159 (save \$30) through December 31, 1999
(price does not include shipping charges or international fees)

PARALLAX


To order call toll free 888.512.1024
(8 a.m. to 5 p.m. Monday-Friday PST)
in the United States; elsewhere call 916.624.8333

For more information visit www.parallaxinc.com

BASIC Stamp and the Parallax logo are registered trademarks of Parallax, Inc.



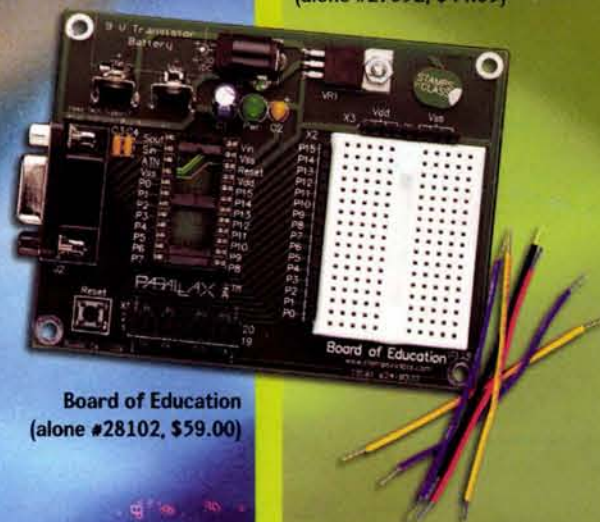PAK-I Math
coprocessor
(to order alone
#553-00004, \$25)



Board of Education
(alone #28102, \$59.00)

Write in 194 on Reader Service Card.

NUTS & VOLTS MAGAZINE
430 PRINCELAND COURT
CORONA, CA 92879-1300

